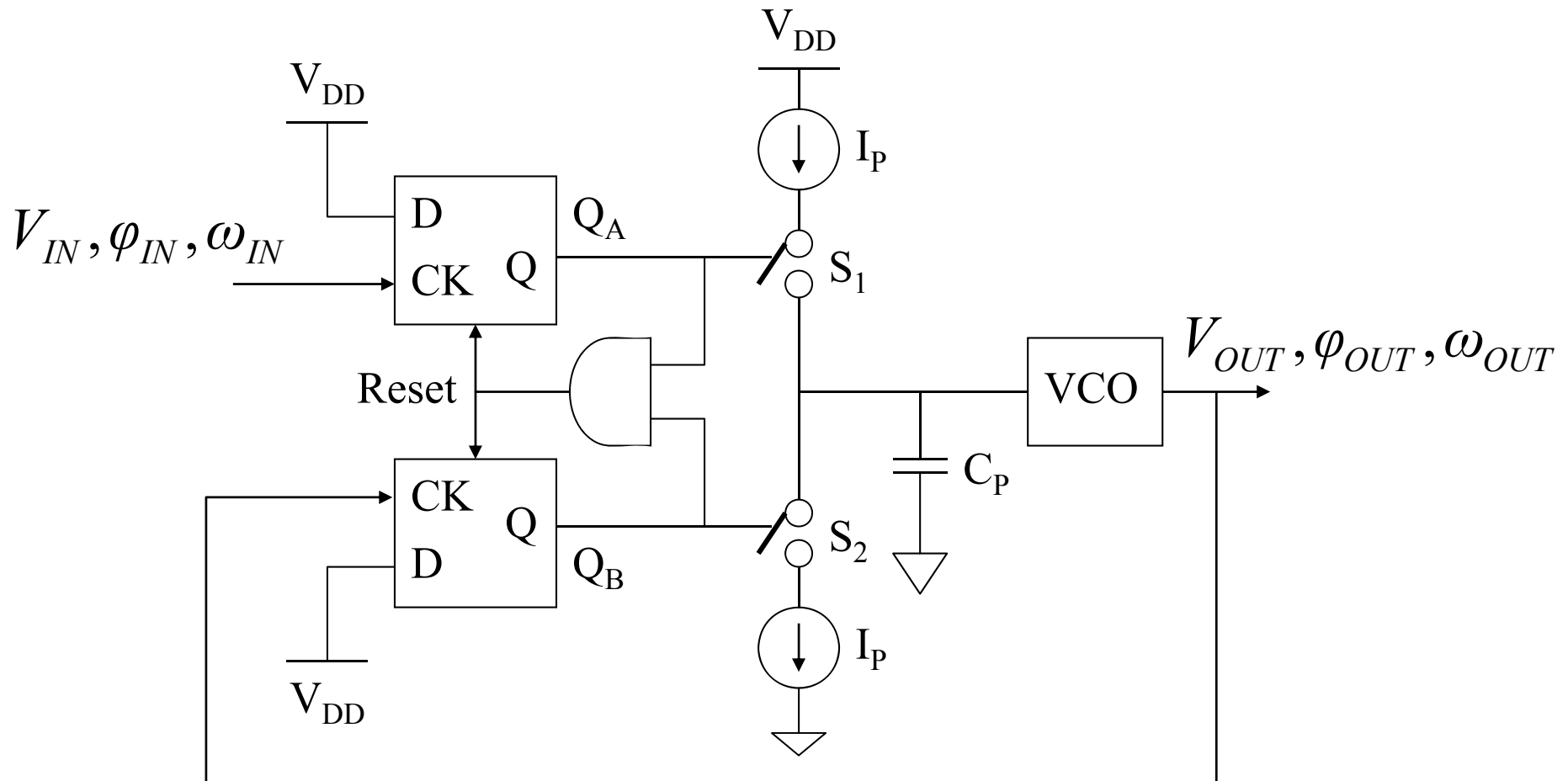


EE4011: RF IC Design

Type II PLLs and Charge Pump Phase Detectors

Type II PLLs


An architecture which overcomes some of the limitations of the Type I PLL is the Phase-Frequency-Detector (PFD)/Charge-Pump PLL (CPPLL):




Operation of PFD for same i/p Frequency

The PFD based on two D-type flip flops and an AND gate generate outputs whose mark/space ratio depends on the difference in frequency and phase of the two input signals.

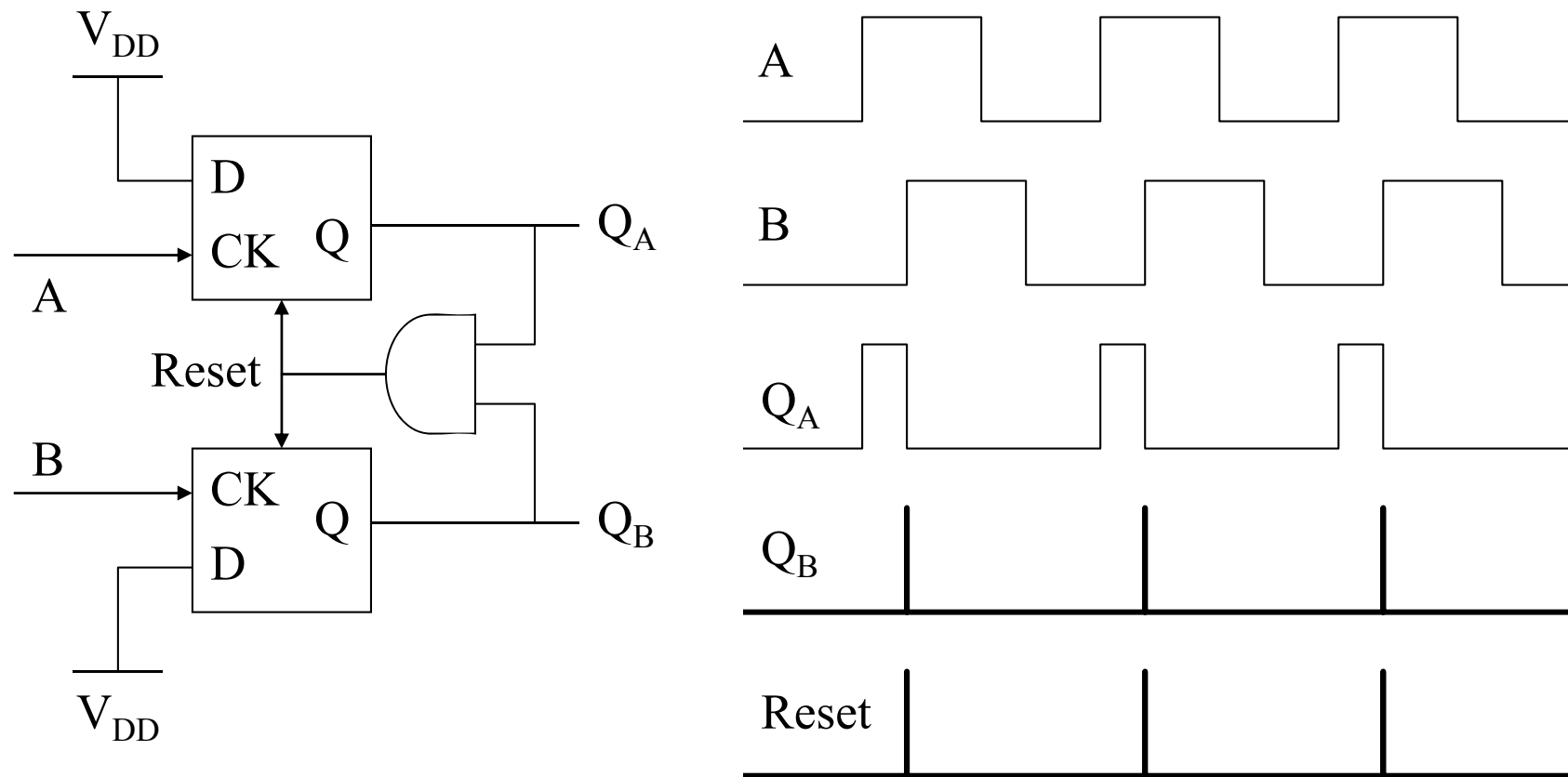Example where the inputs at A and B are the same frequency but A *leads* B:




Zoom-in to show pulse timing - 1

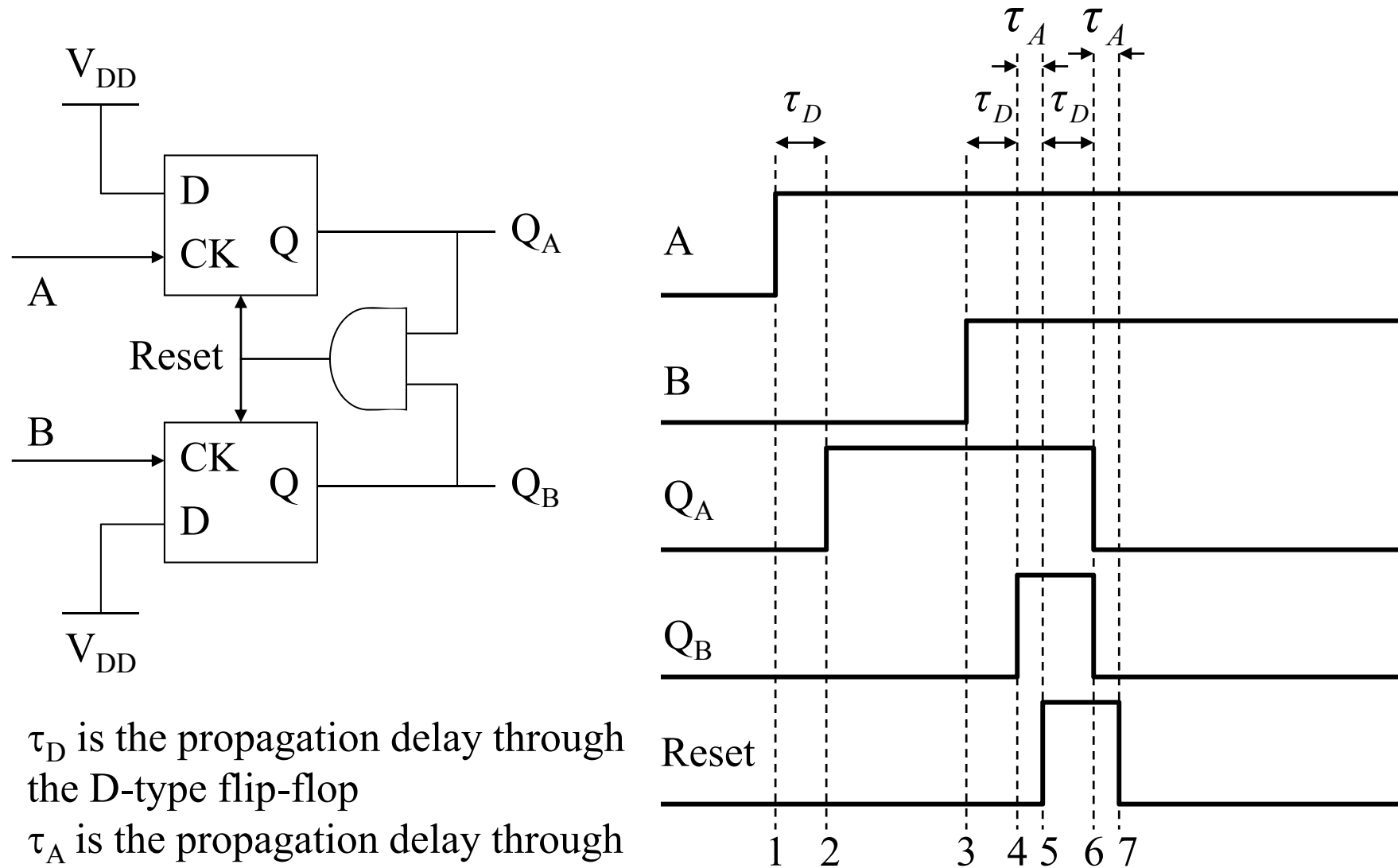

τ_D is the propagation delay through the D-type flip-flop

τ_A is the propagation delay through the AND gate

Zoom-in to show pulse timing - 2

 


1. Input A goes high.
2. Signal A propagates through the D latch and the output Q_A goes high.
3. Input B goes high.
4. Signal B propagates through the D latch and the output Q_B goes high.
5. As Q_A is already high, Q_B propagates through the AND gate causing its output (Reset) to go high.
6. The reset signal propagates through both latches and Q_A and Q_B go low.
7. Q_A and Q_B propagate through the AND gate so its output (Reset) goes low.


Q_A is a wide pulse determined by the phase difference between A and B. Q_B and Reset are narrow pulses determined by the propagation delays through the gates.

Operation of PFD for same i/p Frequency

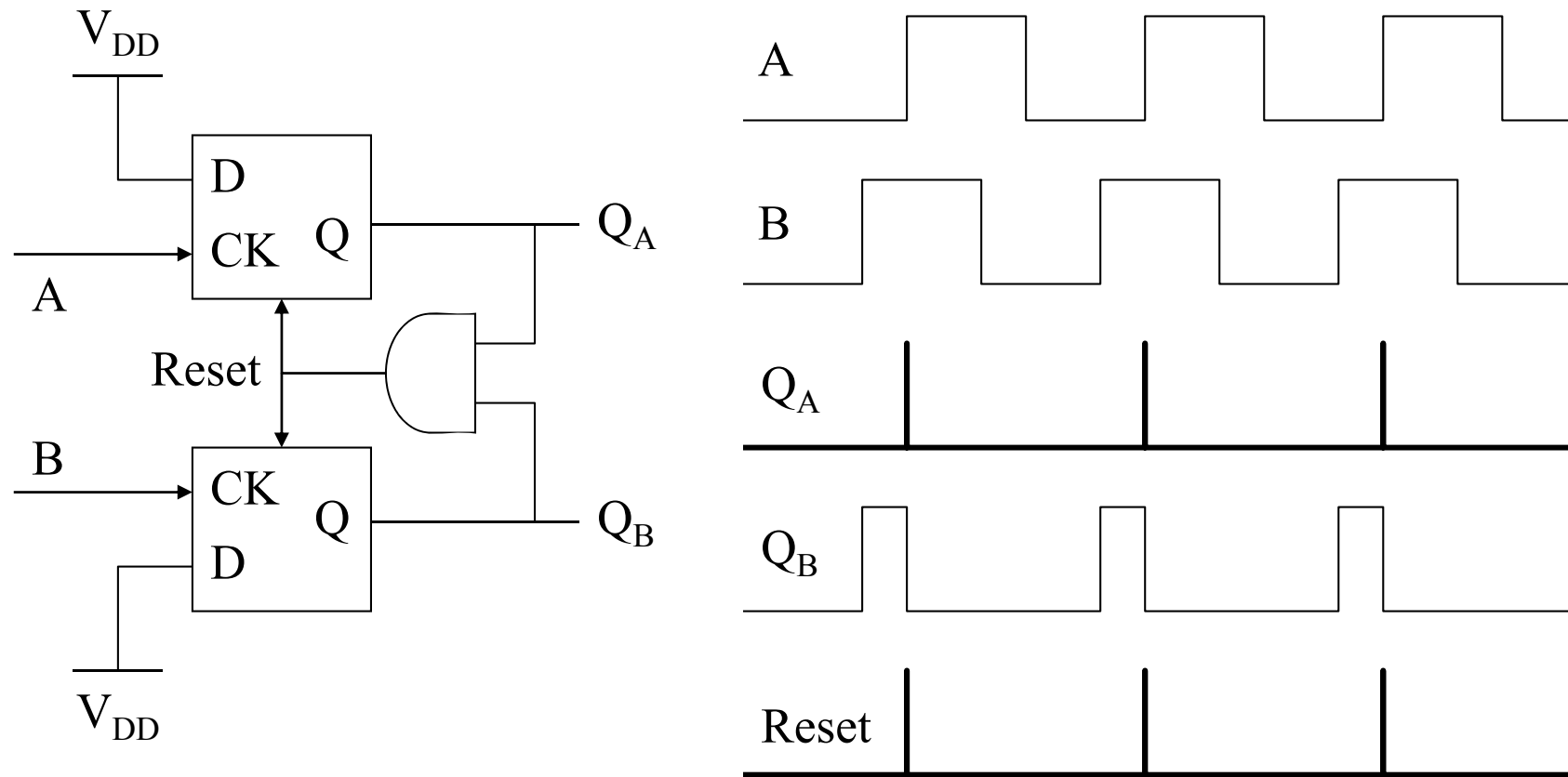Case where the inputs at A and B are the same frequencies but B *leads* A.



Zoom-in to show pulse timing - 3

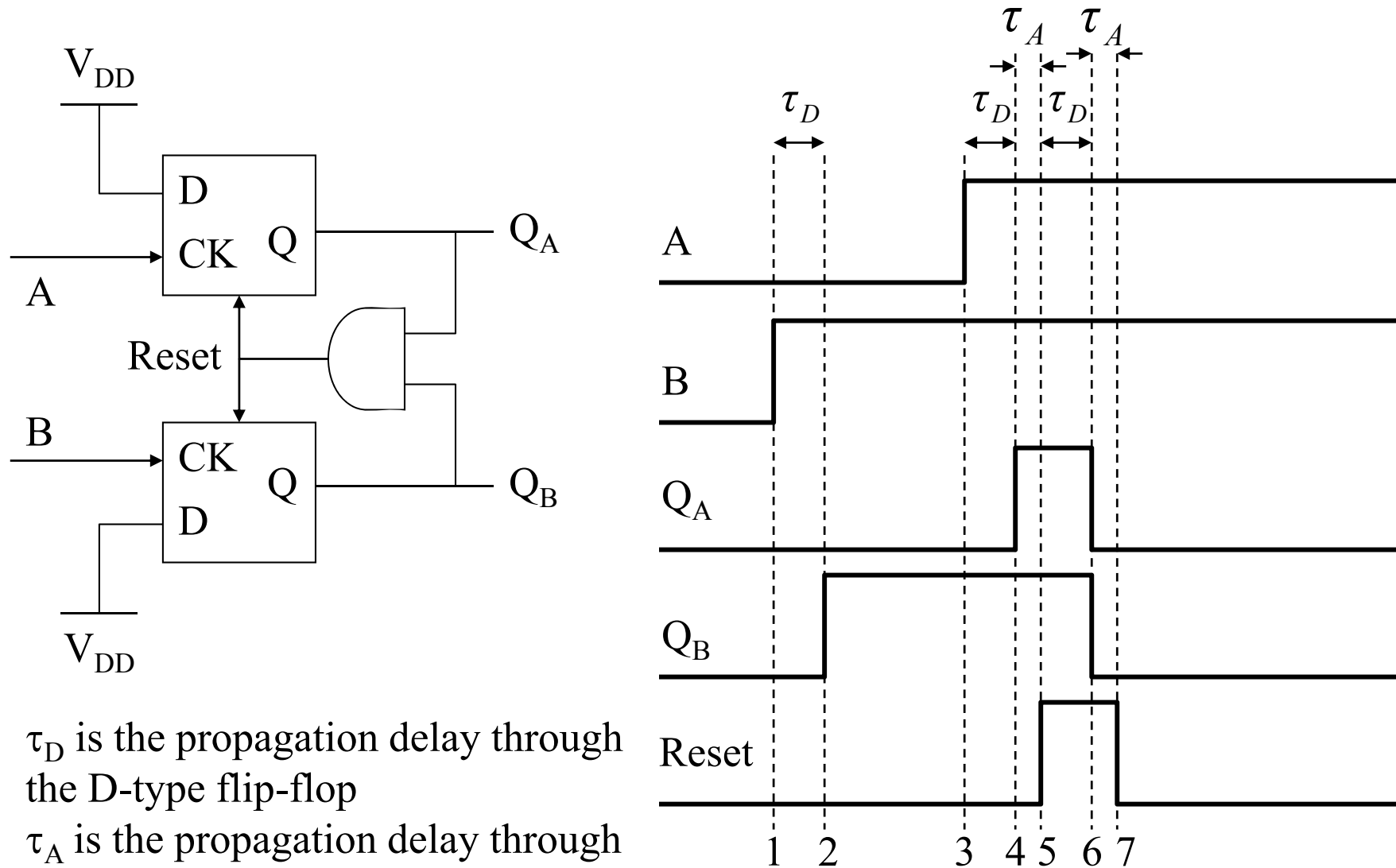


τ_D is the propagation delay through the D-type flip-flop



τ_A is the propagation delay through the AND gate

Operation of PFD for different i/p frequencies

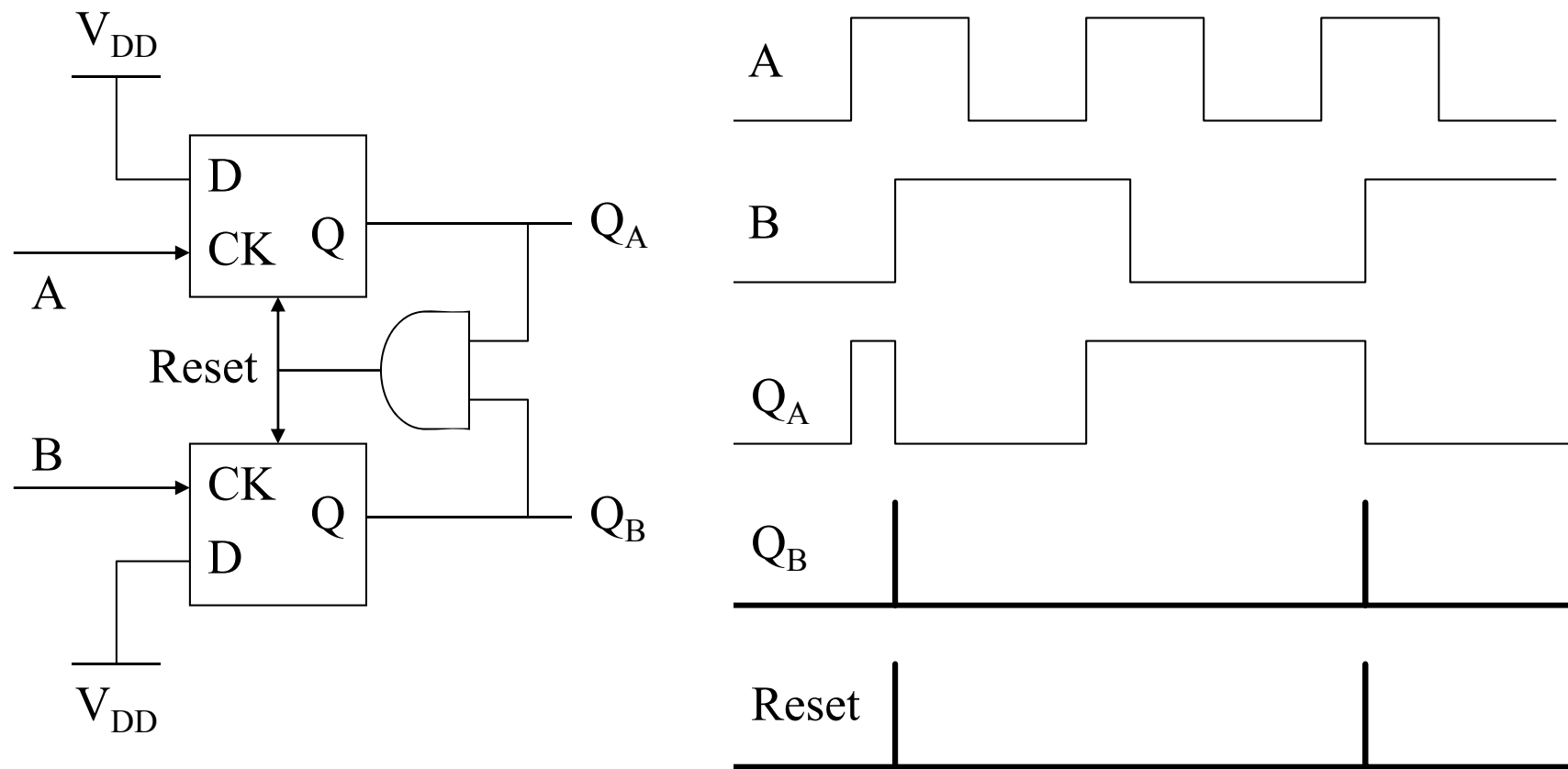Case where input A is twice the frequency of B. There are very wide pulses on Q_A which will cause the charge pump capacitor to charge quickly.





The Charge Pump

 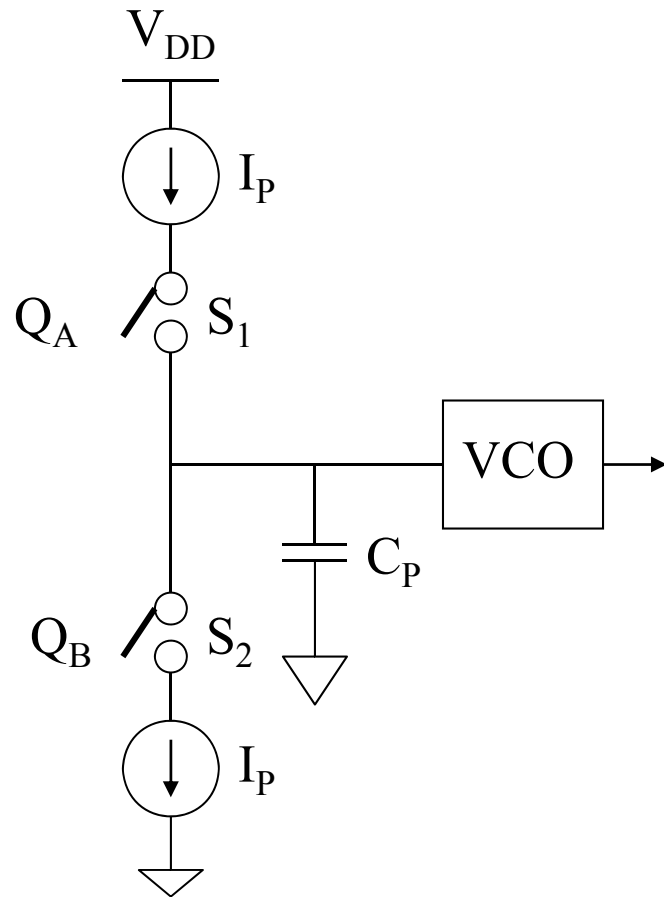


S_1 and S_2 are CMOS switches (or just single MOSFETs) driven by the logic signals Q_A and Q_B . When Q_A is high S_1 is closed and the capacitor is charged with current I_P causing its voltage to rise and thus the VCO frequency to increase. When Q_B is high, S_2 is closed and the capacitor is discharged with current I_P causing its voltage to drop and the VCO frequency to decrease.

Model of Simplest PFD/CP - 1

  

If signals A and B have the same frequency but a phase difference $\Delta\phi$ then the time between their rising edges is $\Delta t = (\Delta\phi/2\pi)T$. During this time interval switch S_1 is on and the capacitor is charged with current I_P .

Model of Simplest PFD/CP - 2

 

During the interval Δt the capacitor is charged with current I_P giving a voltage rise rate of I_P/C_P V/s. The total voltage rise in this interval is:

$$\Delta V_C = \frac{I_P}{C_P} \Delta t = \frac{I_P}{C_P} \frac{\Delta \phi}{2\pi} T$$

During the remainder of the period of A the switches are turned off and the voltage on the capacitor remains constant. Thus on average, the voltage rises by ΔV_C in one period, T . The behaviour can be approximated by a straight line:


$$\text{slope} = \frac{dV_C}{dt} \approx \frac{\Delta V_C}{T} = \frac{I_P}{C_P} \frac{\Delta \phi}{2\pi} T \frac{1}{T} = \frac{I_P}{2\pi C_P} \Delta \phi$$

$$\Rightarrow \frac{dV_C}{dt} = \frac{I_P}{2\pi C_P} \Delta \phi \Rightarrow V_C = \frac{I_P}{2\pi C_P} \int \Delta \phi$$

$$\Rightarrow V_C(s) = \frac{I_P}{2\pi C_P} \frac{1}{s} \Delta \phi(s)$$


Simplest Type II PLL

 The configuration seen so far can be represented by the following blocks:




Unfortunately, the closed-loop transfer function of this system has two imaginary poles and can be unstable. To avoid stability problems, a zero is added to the open loop transfer function by placing a resistor in series with the charge pump capacitor. An extra smoothing capacitor is often used to smooth out the rapid voltage steps which would occur from a capacitor being charged through a resistor by means of a switch which is opening and closing. All this makes the analysis of the system more difficult but a linear model can be created by using an “average current” approach.

Type II PLL with added zero

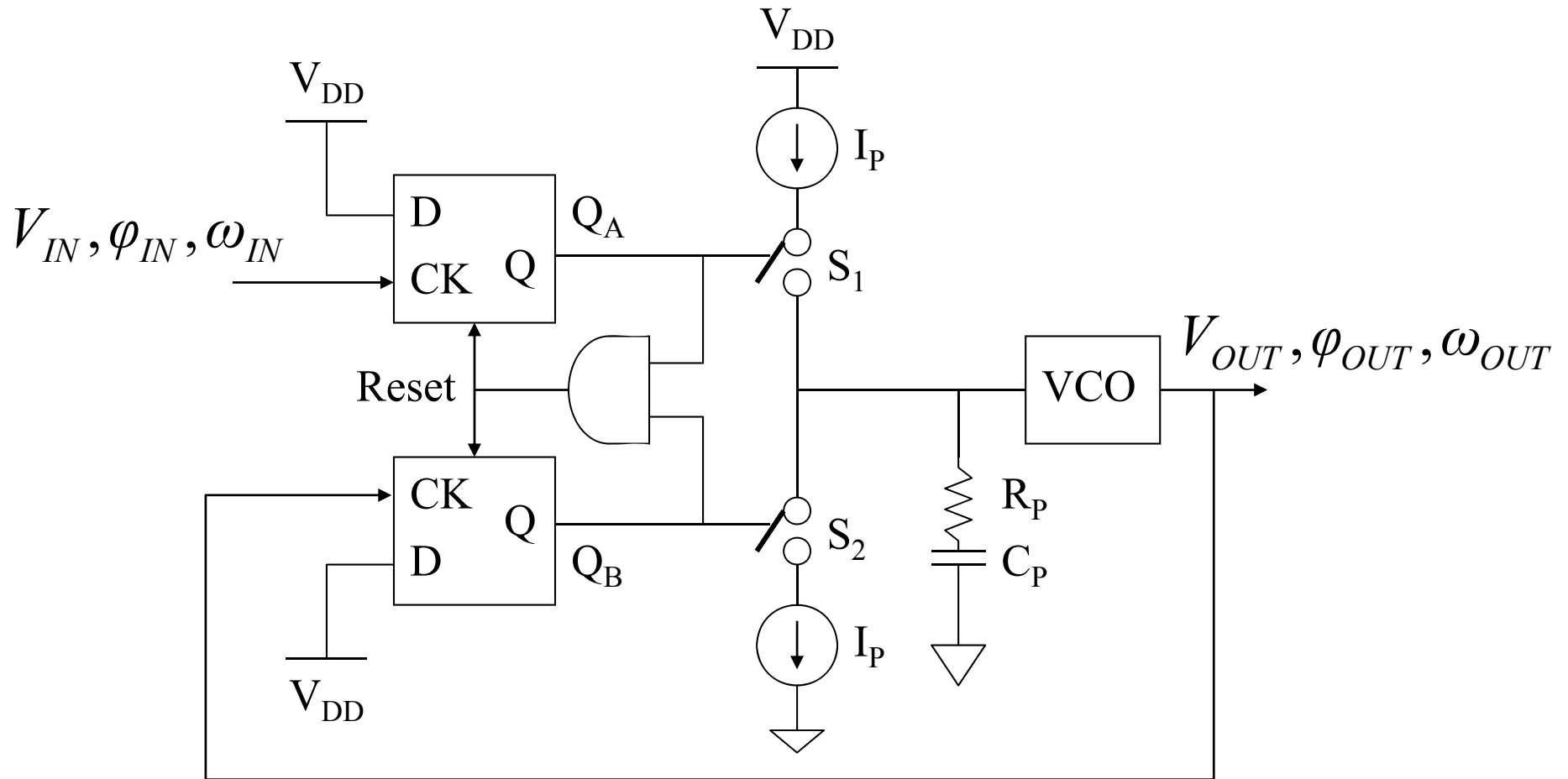

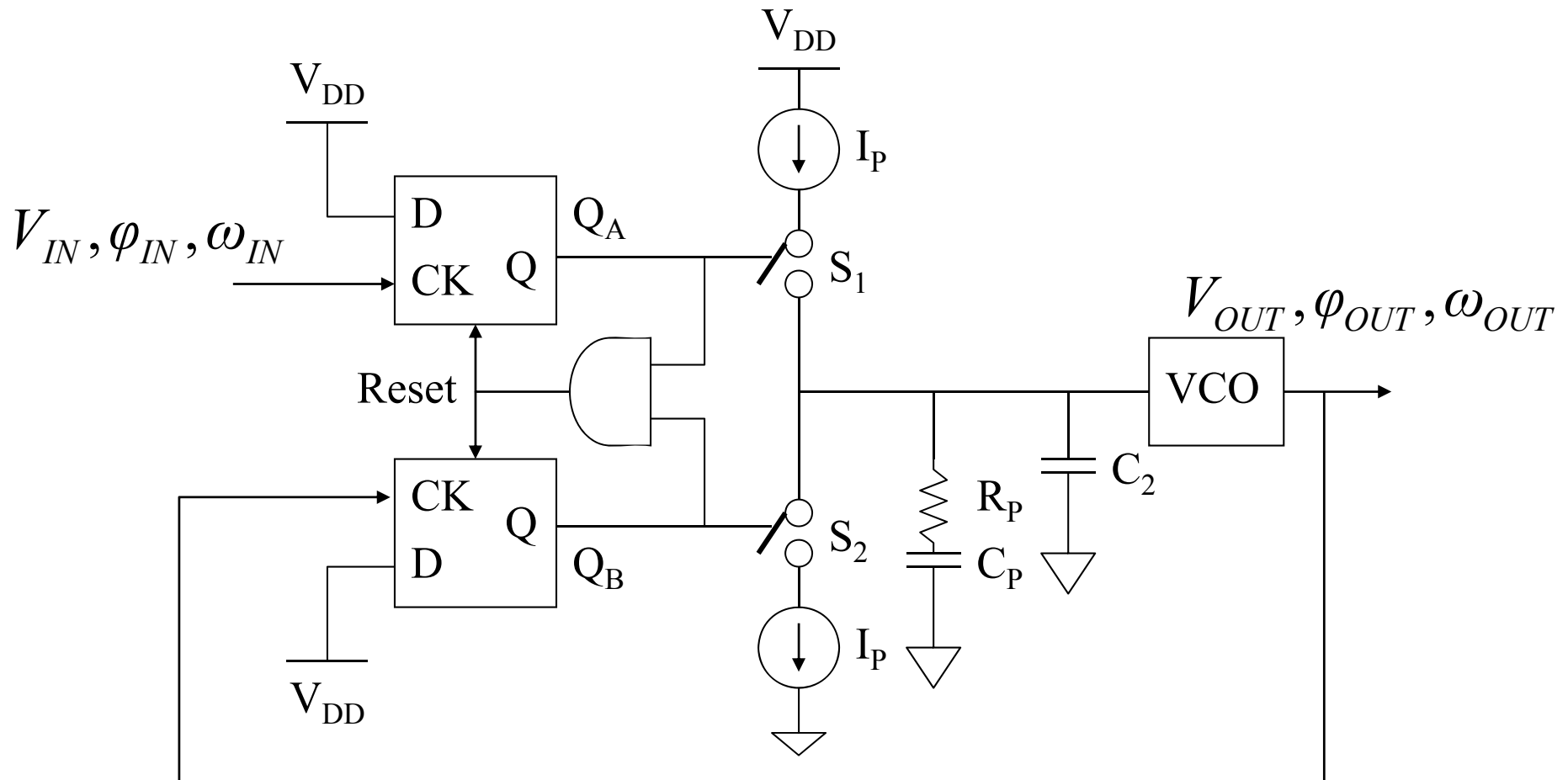
Type II PLL with added zero and smoothing capacitor



A Linear Model of the CPPLL


Linear modelling of more complicated charge pump filter arrangements is possible by:

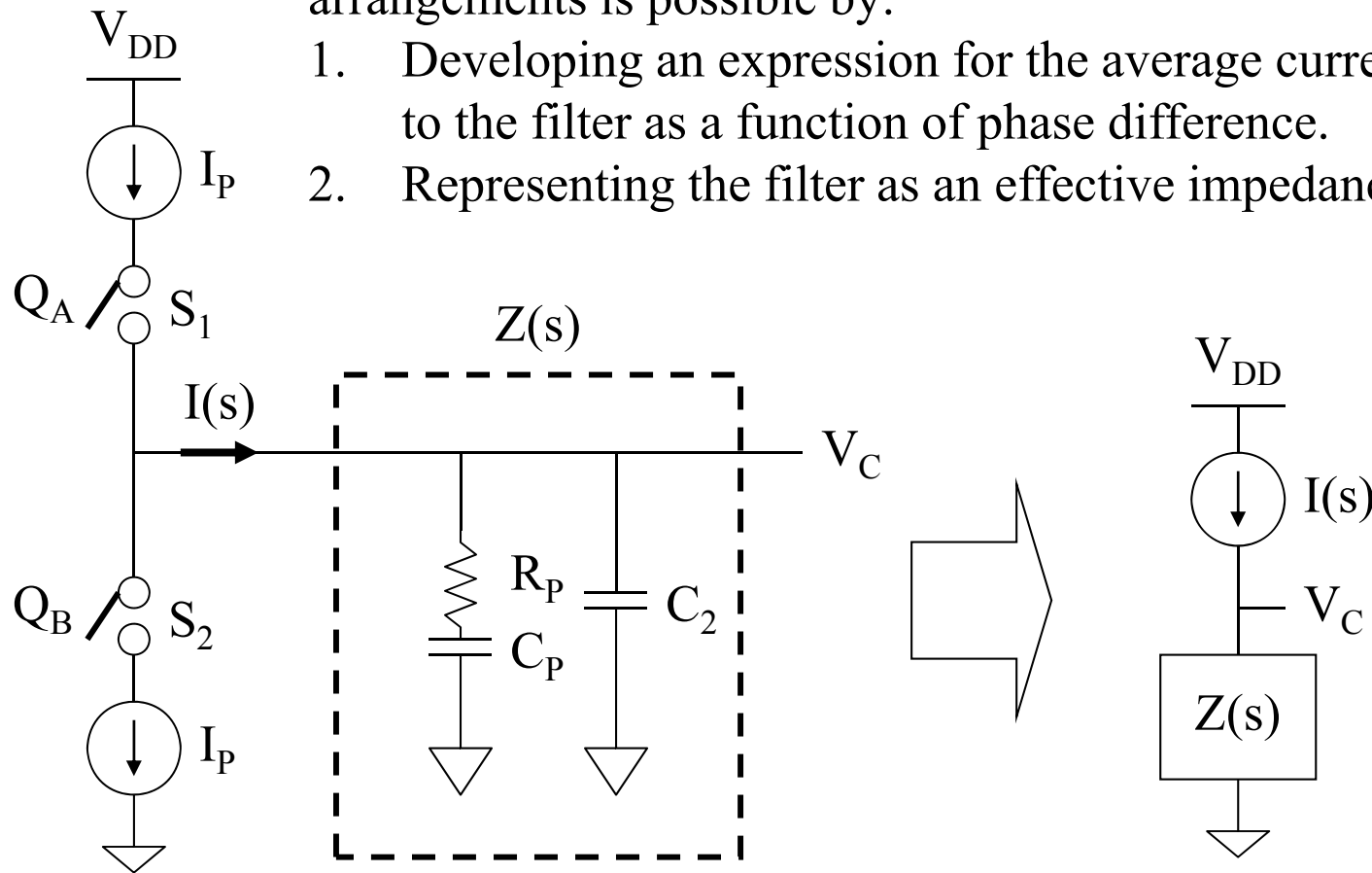1. Developing an expression for the average current supplied to the filter as a function of phase difference.
2. Representing the filter as an effective impedance.



Treating the capacitor/filter as an impedance

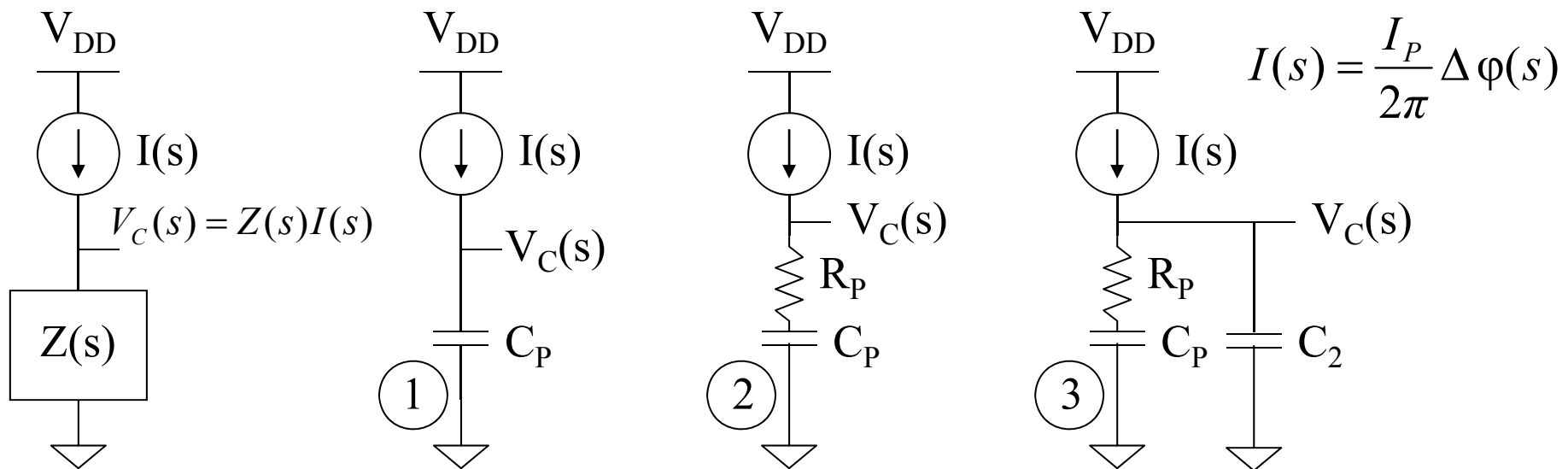With the average current $I(s)$ known, the capacitor/resistor combination can be treated as an impedance and the voltage determined from Ohm's law.




$$\textcircled{1} \quad Z(s) = \frac{1}{sC_P} \Rightarrow V_C(s) = \frac{1}{sC_P} I(s) = \frac{I_P}{2\pi C_P} \frac{\Delta \phi(s)}{s}$$

$$\textcircled{2} \quad Z(s) = R_P + \frac{1}{sC_P} \Rightarrow V_C(s) = \left(R_P + \frac{1}{sC_P} \right) I(s) = \frac{I_P}{2\pi} \left(R_P + \frac{1}{sC_P} \right) \Delta \phi(s)$$

$$\textcircled{3} \quad Z(s) = \left(R_P + \frac{1}{sC_P} \right) \parallel \left(\frac{1}{sC_2} \right) \Rightarrow V_C(s) = \frac{I_P}{2\pi} \left(\frac{R_P C_P s + 1}{(R_P C_P C_2 s + C_P + C_2)s} \right) \Delta \phi(s)$$

PFD/CP PLL with C_p/R_p - 1

 

Open loop transfer function:

$$H(s) = \frac{\varphi_{OUT}(s)}{\varphi_{IN}(s)} = \frac{I_P K_{VCO}}{2\pi s} \left(R_P + \frac{1}{C_P s} \right)$$

Closed loop:

$$H_{Closed}(s) = \frac{H(s)}{1 + H(s)}$$

$$= \frac{\frac{I_P K_{VCO}}{2\pi s} \left(R_P + \frac{1}{C_P s} \right)}{1 + \frac{I_P K_{VCO}}{2\pi s} \left(R_P + \frac{1}{C_P s} \right)} = \frac{\frac{I_P K_{VCO}}{2\pi C_P} (R_P C_P s + 1)}{s^2 + \frac{I_P K_{VCO}}{2\pi} R_P s + \frac{I_P K_{VCO}}{2\pi C_P}}$$

PFD/CP PLL with C_p/R_p - 2


$$H_{Closed}(s) = \frac{\frac{I_P K_{VCO}}{2\pi C_P} (R_P C_P s + 1)}{s^2 + \frac{I_P K_{VCO}}{2\pi} R_P s + \frac{I_P K_{VCO}}{2\pi C_P}} = \frac{\frac{I_P K_{VCO}}{2\pi C_P} (R_P C_P s + 1)}{s^2 + 2\zeta \omega_n s + \omega_n^2}$$

$$\Rightarrow \omega_n = \sqrt{\frac{I_P K_{VCO}}{2\pi C_P}} \quad \zeta = \frac{R_P}{2} \sqrt{\frac{I_P C_P K_{VCO}}{2\pi}} \quad \tau = \frac{1}{\zeta \omega_n} = \frac{4\pi}{I_P R_P K_{VCO}}$$

The denominator has been arranged to show up the 2nd-order system characteristics such as the natural frequency, the damping factor and the time-constant.

If R_p is zero then the damping factor is zero and the time constant is infinity i.e. the system will not converge to a steady-state solution in response to a step input.

PFD/CP PLL with Feedback Divider - 1

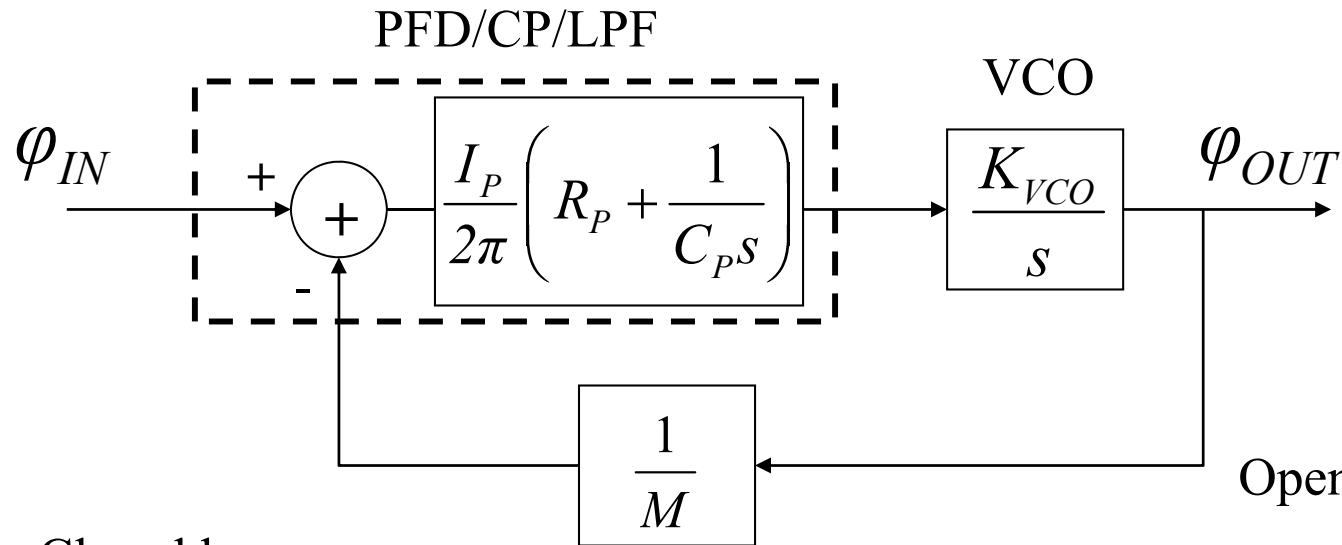

Closed loop:

$$\varphi_{OUT}(s) = \left(\varphi_{IN}(s) - \frac{\varphi_{OUT}(s)}{M} \right) H(s)$$

Open loop:

$$H(s) = \frac{I_P K_{VCO}}{2\pi s} \left(R_P + \frac{1}{C_P s} \right)$$

$$\Rightarrow H_{closed}(s) = \frac{H(s)}{1 + \frac{H(s)}{M}} = \frac{\frac{I_P K_{VCO}}{2\pi s} \left(R_P + \frac{1}{C_P s} \right)}{1 + \frac{I_P K_{VCO}}{2\pi M s} \left(R_P + \frac{1}{C_P s} \right)}$$

PFD/CP PLL with Feedback Divider - 2

After some manipulation:

$$H_{Closed}(s) = \frac{\frac{I_P K_{VCO}}{2\pi C_P} (R_P C_P s + 1)}{s^2 + \frac{I_P K_{VCO}}{2\pi M} R_P s + \frac{I_P K_{VCO}}{2\pi C_P M}} = \frac{\frac{I_P K_{VCO}}{2\pi C_P} (R_P C_P s + 1)}{s^2 + 2\zeta \omega_n s + \omega_n^2}$$

$$\Rightarrow \omega_n = \sqrt{\frac{I_P K_{VCO}}{2\pi C_P M}} \quad \zeta = \frac{R_P}{2} \sqrt{\frac{I_P C_P K_{VCO}}{2\pi M}} \quad \tau = \frac{1}{\zeta \omega_n} = \frac{4\pi M}{I_P R_P K_{VCO}}$$

Placing a divider, M, in the feedback loop decreases the natural frequency and the damping factor and increases the settling time. To maintain the same stability as a PLL without a divider, the other loop parameter such as K_{VCO} or I_P have to be increased. In terms of the step response, the CPPLL with a divider behaves like a PLL with a VCO whose gain constant is K_{VCO}/M .