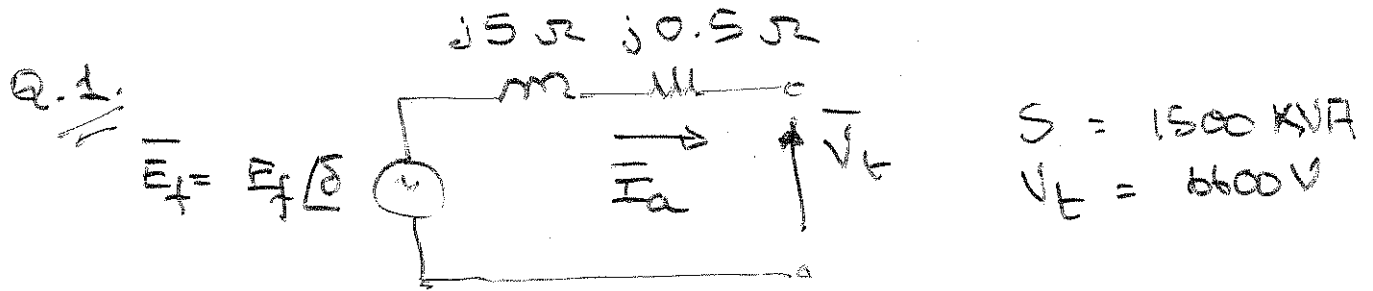


SYNCHRONOUS MACHINE PROBLEMS

①



$$S = \sqrt{3} V_t I_a$$

$$\Rightarrow I_a = \frac{1500 \times 10^3}{\sqrt{3} \times 6600}$$

$$= 131.22 \text{ A}$$

THEN, FOR RATED POWER OPERATION AT 0.8 p.f LAGGING,

$$\begin{aligned} \bar{I}_a &= 131.22 \angle -\cos^{-1} 0.8 \text{ A} \\ &= 131.22 \angle -36.87^\circ \text{ A} \end{aligned}$$

THE REQUIRED EXCITATION VOLTAGE IS THEN

$$\bar{E}_f = E_f \angle \delta = V_t + \bar{Z}_s \bar{I}_a$$

$$\begin{aligned} \Rightarrow E_f \angle \delta &= \frac{6600}{\sqrt{3}} + (0.5 + j5) 131.22 \angle -36.87^\circ \\ &= 3810.5 + 659 \angle 47.42^\circ \\ &= 4284.3 \angle 6.51^\circ \end{aligned}$$

(2)

$$\begin{aligned}
 \text{Regulation} &= \frac{E_f - V_t}{V_t} \\
 &= \left(\frac{4284.3 - 3810.5}{3810.5} \right) 100\% \\
 &= 12.43\%
 \end{aligned}$$

CHECK :-

$$\begin{aligned}
 P_o &= \sqrt{3} V_t I_a \cos \phi \\
 &= \sqrt{3} 6600 \times 131.22 \times 0.8 \\
 &= 1200 \text{ kW}
 \end{aligned}$$

AS EXPECTED.

$$\begin{aligned}
 P_o &= S_{\text{RATED}} \text{ Pf} \\
 &= 1500 \times 0.8 = 1200 \text{ kW}
 \end{aligned}$$

ALSO


$$\begin{aligned}
 P_o &\doteq \frac{3 E_f V_t \sin \delta}{X_s} \quad (\text{NEGLECT } R_a) \\
 &\doteq \frac{3 \times 4284.3 \times 3810.5 \sin(6.51^\circ)}{5} \\
 &\doteq 1110.5 \text{ kW}
 \end{aligned}$$

EXERCISE :- CALCULATE $3I_a^2 R_a$ AND $\bar{S} = 3\bar{E}_f \bar{I}_a^*$

EE4010
SYNCHRONOUS MACHINES

①

Q.2.

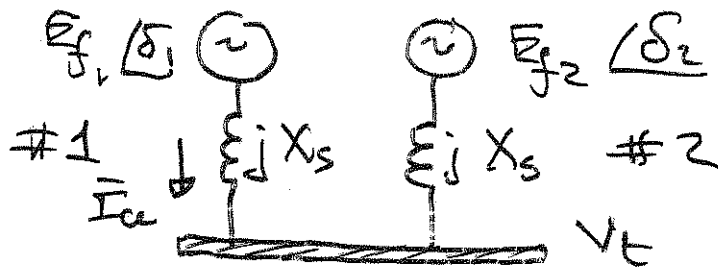

$$X_s = 4.5 \Omega$$

$$E_{f1} = E_{f2} = 1910 \text{ V/phase.}$$

$$\delta_1 - \delta_2 = 30^\circ$$

HENCE,

$$\bar{I}_a = \frac{E_{f1} \angle \delta_1 - E_{f2} \angle \delta_2}{2jX_s}$$

TAKING δ_2 AS THE REFERENCE PHASOR,

$$\begin{aligned} \bar{I}_a &= \frac{1910 \angle 30^\circ - 1910 \angle 0^\circ}{2j4.5} \\ &= 109.8 \angle 15^\circ \text{ A} \end{aligned}$$

THE PER-PHASE TERMINAL VOLTAGE IS

$$\begin{aligned} \bar{V}_t &= E_{f2} \angle \delta_2 + jX_s \bar{I}_a \\ &= 1910 + (j4.5)(109.8 \angle 15^\circ) \\ &= 1845 \angle 15^\circ \text{ V/phase} \end{aligned}$$

CHECK :-

$$\begin{aligned}\bar{V}_t &= E_{f1} \angle \delta_1 - jX_s \bar{I}_a \\ &= 1910 \angle 30^\circ - j4.5(109.8 \angle 30^\circ) \\ &= 1845 \angle 15^\circ \text{ V/phase}\end{aligned}$$


THE POWER TRANSFER IS

$$\begin{aligned}P &= \frac{3 E_{f1} E_{f2} \sin(\delta_1 - \delta_2)}{2X_s} \\ &= 3 \frac{1910^2}{9} \sin(30^\circ) \\ &= 608 \text{ kW.}\end{aligned}$$

CHECK :-

$$\begin{aligned}P &= \operatorname{Re} [3 \bar{E}_{f2} \bar{I}_a^*] \\ &= \operatorname{Re} [3 \times 1910 \times 109.8 \angle 15^\circ] \\ &= 608 \text{ kW.}\end{aligned}$$

EXERCISE :- CONSTRUCT THE PHASOR DIAGRAM.

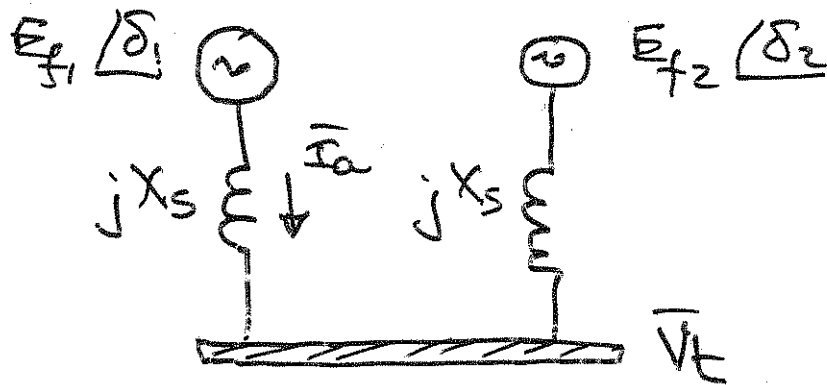Q. 3

$$X_s = 4.5 \Omega$$

$$E_{f1} = 2240 \text{ V / phase}$$

$$E_{f2} = 1600 \text{ V / phase}$$

THE EMF'S ARE IN PHASE OPPOSITION.

HENCE

$$\begin{aligned} \bar{I}_a &= \frac{\bar{E}_{f1} - \bar{E}_{f2}}{2jX_s} \\ &= \frac{2240 - 1600}{2j4.5} \\ &= 71.1 \angle -90^\circ \text{ A} \end{aligned}$$

THE TERMINAL VOLTAGE IS


$$\bar{V}_t = \bar{E}_{f2} + jX_s \bar{I}_a$$

SYNC M/C Q.3.

(2)


$$\Rightarrow V_t = 1600 + (j4.5)(71.1 \angle -90^\circ) \\ = 1920 \angle 0^\circ \text{ V/phase}$$

EXERCISE:-

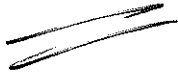

CONSTRUCT THE CORRESPONDING
PHASOR DIAGRAM.

Q.4.

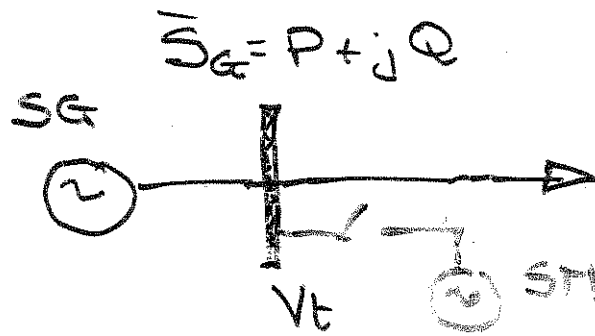

$$\begin{aligned} S_G &= 2.8 \text{ MW AT } 0.7 \text{ pf LAGGING} \\ &= \frac{2.8}{0.7} \angle \cos^{-1} 0.7 \\ &= 4.0 \angle 45.6^\circ \text{ MVA} \end{aligned}$$

HENCE, THE GENERATOR RATING IS 4.0 MW

INCREASE THE GENERATOR POWER FACTOR TO UNITY AND STILL OPERATE AT RATED CONDITIONS TO GIVE A REAL POWER INCREASE OF

$$\begin{aligned} \Delta P &= 4 \text{ MW} - 2.8 \text{ MW} \\ &= 1.2 \text{ MW} \end{aligned}$$

THE SYNCHRONOUS MOTOR MUST PRODUCE $4.0 \sin(45.6^\circ) = 2.85 \text{ MVA}$ OF REACTIVE POWER AND SO ITS OPERATING COMPLEX POWER IS

$$\begin{aligned} \bar{S}_M &= P - jQ \\ &= 1.2 - j2.85 \text{ MVA} \end{aligned}$$

SYNC M/C Q. 4.

(2)


$$\Rightarrow \bar{S}_M = 3.09 \angle -67.2^\circ \text{ MVA}$$

THUS, THE RATED CAPACITY OF THE GENERATOR MUST BE 3.1 MVA
AND ITS OPERATING POWER FACTOR IS

$$\begin{aligned} \text{PF}_M &= \cos(-67.2^\circ) \\ &= 0.387 \text{ LEADING.} \end{aligned}$$

Q.5.

(1)

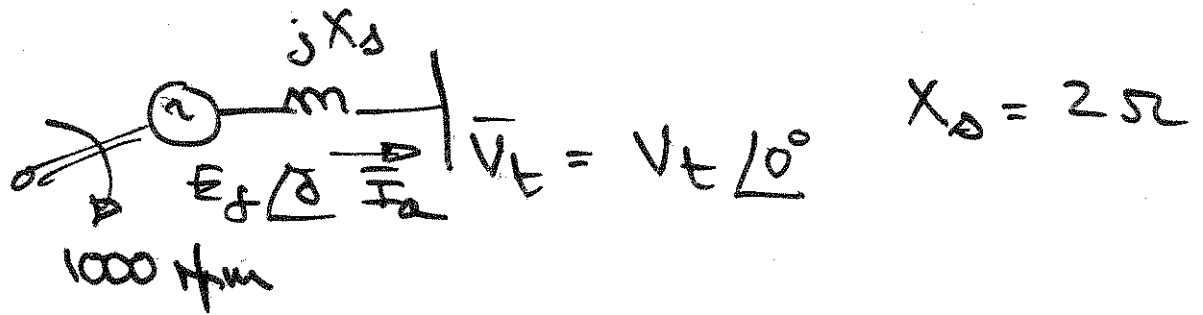

$$I_f = 16 \text{ A}$$

$$E_f = 460 \text{ V LINE}$$

$$\Rightarrow E_f = \frac{460}{\sqrt{3}} = 265.6 \text{ V.}$$

$$\bar{I}_a = 50 \text{ A @ } 0.8 \text{ pf LAGGING}$$

BY KVL,

$$\bar{E}_f = \bar{V}_t + jX_d \bar{I}_a$$

$$\Rightarrow E_f (\cos \delta + j \sin \delta) = V_t \angle 0 + jX_d I_a (\cos \phi - j \sin \phi) \quad (1)$$

WHERE $\phi = \cos^{-1}(0.8) = 36.87^\circ$.

HENCE, EXPANDING EQ.(1) INTO REAL AND IMAGINARY PARTS,

$$E_f \cos \delta = V_t + X_d I_a \sin \phi \quad (2)$$

$$E_f \sin \delta = X_d I_a \cos \phi \quad (3)$$

FROM (3)

$$\delta = \sin^{-1} \left[\frac{X_d I_a \cos \phi}{E_f} \right]$$

Q.5.

(2)

$$\Rightarrow \delta = \sin^{-1} \left[\frac{2 \times 50 \times 0.8}{265.6} \right]$$
$$= 17.53^\circ$$

HENCE

$$V_t = E_f \cos \delta - X_d I_a \sin \phi$$
$$= 265.6 \cos(17.53^\circ) - 2 \times 50 \times 0.6$$
$$= 193.3 \text{ V.}$$

NOW, SINCE

$$P = \frac{3 E_f V_t \sin \delta}{X_d}$$

THEN


$$P = \frac{3 \times 265.6 \times 193.3 \sin(17.53^\circ)}{2}$$
$$= 23.19 \text{ kW}$$

BUT THE SHAFT SPEED IS 1000 RPM
SO THAT

$$T_e = \frac{P}{\omega_m} = \frac{23.19 \times 10^3}{2\pi \times 1000/60}$$
$$= 221.5 \text{ Nm.}$$

Q.6.

①

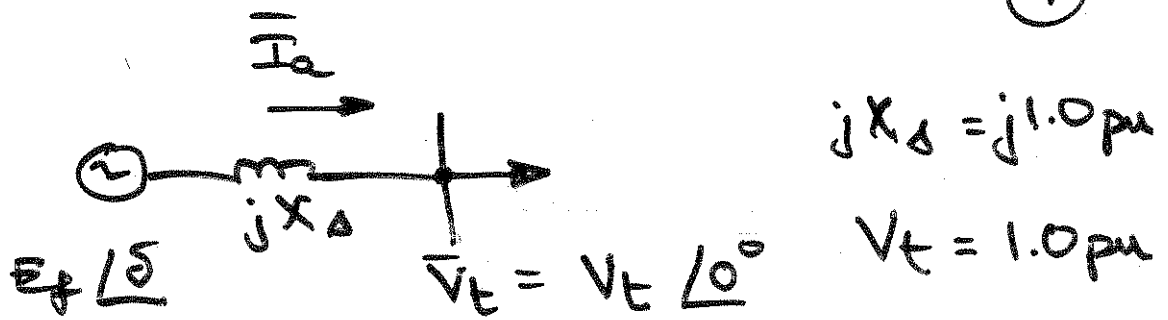

$$\bar{I}_a = 1.0 \angle -\cos^{-1} 0.8$$

$$\bar{I}_a = 0.8 - j0.6$$

$$(i) \quad \bar{E}_f = \bar{V}_t + jX_d \bar{I}_a$$

$$\Rightarrow \bar{E}_f = 1.0 \angle 0^\circ + j1.0(0.8 - j0.6)$$

$$= 1.0 + j0.8 + 0.6$$

$$= 1.6 + j0.8$$

$$= 1.789 \angle 26.57^\circ \text{ pu}$$

ALSO

$$\bar{S}_1 = \bar{V}_t \bar{I}_a^*$$

$$= 1.0 (0.8 - j0.6)^*$$

$$= 0.8 - j0.6$$

\Rightarrow

$$P_1 = 0.8$$

$$Q_1 = 0.6$$

(ii) SINCE THE REAL POWER REMAINS THE SAME

$$P_1 = \frac{E_f' V_t \sin \delta'}{X_d}$$

$$\begin{aligned} \Rightarrow \delta' &= \sin^{-1} \left[\frac{P_1 X_d}{E_f'} \right] \\ &= \sin^{-1} \left[\frac{0.8 \times 1}{1.2 \times 1.789} \right] \\ &= 21.88^\circ \end{aligned}$$

THUS

$$\bar{I}_a' = \frac{\bar{E}_f - \bar{V}_t}{jX_d}$$

$$= \frac{1.2 \times 1.789 \angle 21.88^\circ - 1 \angle 0^\circ}{j1}$$

$$= 1.275 \angle -51.12^\circ \text{ pu}$$

$$\cos \phi' = \cos(51.12^\circ) = 0.627$$

$$\bar{S}' = V_t \bar{I}_a'^*$$

$$\begin{aligned} &= 1.0 \times (1.275 \angle -51.12^\circ)^* \\ &= 0.8 + j0.992 \end{aligned}$$

(iii) P IS INCREASED BY 20%

HENCE

$$P'' = \frac{E_f V_t \sin \delta''}{X_d}$$

$$\Rightarrow \delta'' = \sin^{-1} \left[\frac{P'' X_d}{E_f V_t} \right]$$

$$= \sin^{-1} \left[\frac{1.2 \times 0.8 \times 1.0}{1.789 \times 1.0} \right]$$

$$\delta'' = 32.45^\circ$$

THUS

$$\begin{aligned} \bar{I}_a'' &= \frac{E_f \angle \delta'' - \bar{V}_t}{j X_d} \\ &= \frac{1.789 \angle 32.45^\circ - 1.0}{j 1} \end{aligned}$$


$$= 1.087 \angle -27.97^\circ \text{ pu}$$

$$\Rightarrow \cos \phi'' = \cos(27.97) = 0.883$$

$$\begin{aligned} \bar{S}'' &= \bar{V}_t \bar{I}_a''^* \\ &= 1.0 (1.087 \angle -27.97^\circ) \\ &= 0.96 + j 0.509 \text{ pu} \end{aligned}$$

Q.8

⑦

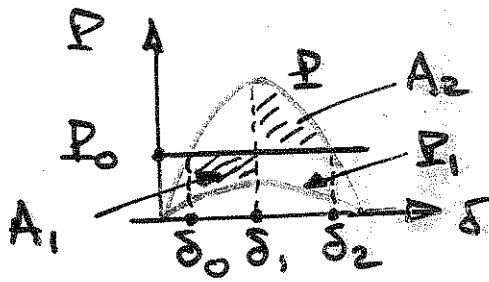

$$P_0 = 0.6 \text{ pu.}$$

$$P = 1.3 \text{ pu}$$

$$P_1 = 0.1 \text{ pu}$$

$$\delta_0 = \sin^{-1}\left(\frac{0.6}{1.3}\right) = 27.5^\circ = 0.48 \text{ rad.}$$

$$\delta_2 = 180^\circ - \sin^{-1}\left(\frac{0.6}{1.3}\right) = 152.5^\circ$$

$$= 2.66 \text{ rad.}$$

THE EQUAL AREA CRITERION REQUIRES THAT

$$A_1 = A_2$$

$$\Rightarrow \int_{\delta_0}^{\delta_1} (P_0 - P_1 \sin \delta) d\delta + \int_{\delta_1}^{\delta_2} (P_0 - P \sin \delta) d\delta = 0$$

$$\Rightarrow \left[P_0 \delta + P_1 \cos \delta \right]_{\delta_0}^{\delta_1} + \left[P_0 \delta + P \cos \delta \right]_{\delta_1}^{\delta_2} = 0$$

$$\Rightarrow \{ P_0 \delta_1 + P_1 \cos \delta_1 - P_0 \delta_0 - P_1 \cos \delta_0 \} + \{ P_0 \delta_2 + P \cos \delta_2 - P_0 \delta_1 - P \cos \delta_1 \} = 0$$

$$\Rightarrow \cos \delta_1 = \frac{P_0(\delta_0 - \delta_2) + P_1 \cos \delta_0 - P \cos \delta_2}{(P_1 - P)}$$

$$\Rightarrow \cos \delta_1 = \frac{0.6(0.48 - 2.66) + 0.1 \cos(27.5^\circ) - 1.3 \cos(152.5^\circ)}{0.1 - 1.3}$$


Q.8.

②

$$\Rightarrow \cos \delta_1 = \frac{-1.308 + 0.0887 + 1.153}{-1.2}$$
$$= 0.055$$

$$\Rightarrow \delta_1 = \cos^{-1}(0.055)$$
$$= 86.8^\circ.$$

Q.9.

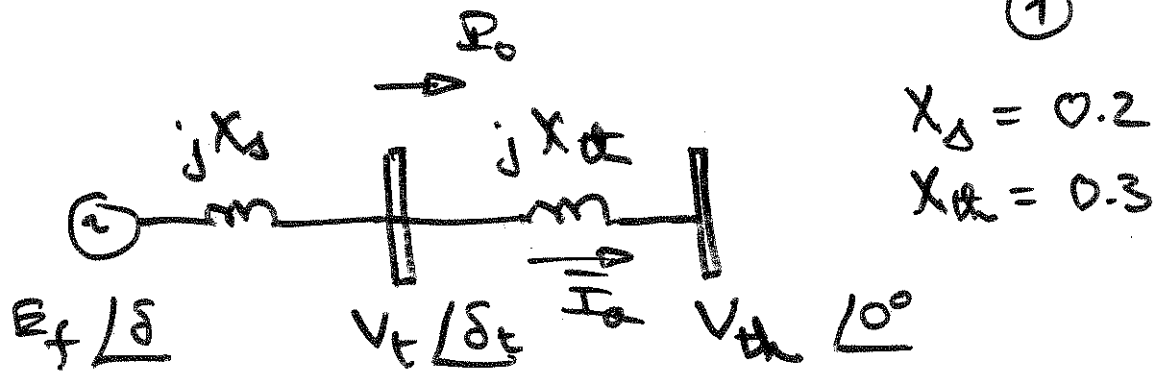

$$P_o = 450 \text{ MW} \quad S_{\text{base}} = 500 \text{ MVA}$$

$$\Rightarrow P_o = \frac{450}{500} = 0.9 \text{ pu.}$$

INITIALLY

$$V_t = V_{th} = 1.0 \text{ pu.}$$

ALSO,

$$P_o = \frac{V_t V_{th} \sin \delta_t}{X_{th}}$$

$$\Rightarrow \delta_t = \sin^{-1} \left[\frac{P_o X_{th}}{V_t V_{th}} \right]$$

$$\delta_t = 15.66^\circ$$

HENCE

$$\vec{I}_a = \frac{V_t \angle \delta_t - V_{th} \angle 0^\circ}{jX_{th}}$$

$$= \frac{1 \angle 15.66^\circ - 1.0 \angle 0^\circ}{j0.3}$$

$$= 0.908 \angle 7.83^\circ \text{ pu}$$

(2)

$$\Rightarrow E_f \angle \delta = \bar{V}_{th} + j(X_d + X_{th}) \bar{I}_a$$

$$\begin{aligned} \Rightarrow E_f \angle \delta &= 1.0 + j0.5(0.908 \angle 7.83^\circ) \\ &= 1.04 \angle 25.62^\circ \text{ pu.} \end{aligned}$$

THE INITIAL POWER/LOAD ANGLE CURVE IS

$$\begin{aligned} P &= \frac{E_f V_{th} \sin \delta}{X_d + X_{th}} \\ &= \frac{1.04 \times 1.0}{0.2 + 0.3} \sin \delta \\ &= 2.08 \sin \delta \end{aligned}$$

SINCE THE TERMINALS OF THE GENERATOR ARE DIRECTLY SHORTED, THE FAULTED POWER CURVE IS

$$P_1 = 0.0 \sin \delta$$

USING THE NOTATION OF PROBLEM 8,

$$\cos \delta_1 = \frac{P_0(\delta_0 - \delta_2) + P_1 \cos \delta_0 - P \cos \delta_2}{P_1 - P}$$

$$\begin{aligned} \text{WHERE } \delta_0 &= \sin^{-1} \left[\frac{0.9}{2.08} \right] = 25.63^\circ \\ &= 0.447 \text{ rad} \end{aligned}$$

(3)

ALSO $\delta_2 = \pi - \delta_0 = 154.3^\circ$
 $= 2.694 \text{ rad.}$

$$P_0 = 0.9, P_1 = 0.0, P = 2.08$$

HENCE,

$$\cos \delta_1 = \frac{0.9(0.447 - 2.694) + 0 - 2.08 \cos(154.3^\circ)}{0 - 2.08}$$

$$= \frac{-2.022 + 1.874}{-2.08}$$

$$= 0.071$$

$$\Rightarrow \delta_1 = \cos^{-1}(0.071)$$

$$\delta_1 = 85.9^\circ.$$

