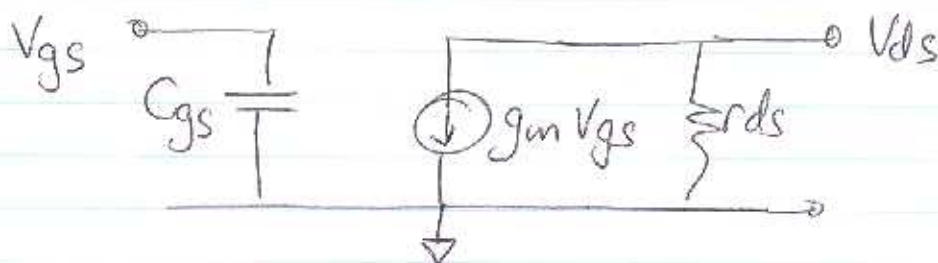


Q1

(a) Directly from the notes



$$I_{DS} = \frac{1}{2} \frac{W}{L} \mu C_{ox} (V_{gs} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$I_{DS} \approx \frac{1}{2} \frac{W}{L} \mu C_{ox} (V_{gs} - V_{TH})^2$$

$$\Rightarrow g_m = \frac{dI_{DS}}{dV_{gs}} = \frac{W}{L} \mu C_{ox} (V_{gs} - V_{TH})$$

$$g_{ds} = \frac{dI_{DS}}{dV_{DS}} = \lambda \frac{1}{2} \frac{W}{L} \mu C_{ox} (V_{gs} - V_{TH})^2 \approx \lambda I_{DS}$$

$$r_{ds} = \frac{1}{g_{ds}}$$

Cut off frequency (following derivation in notes):

$$f_T = \frac{g_m}{2\pi C_{gs}}$$

Note: Q7 not answered as it's straight out of the notes.

$$(b) \mu = 400 \text{ cm}^2/\text{Vs} = 400 \times 10^{-4} = 0.04 \text{ m}^2/\text{Vs}$$

$$C_{ox} = \frac{\epsilon_{ox}}{T_{ox}} = \frac{(\epsilon_r)_{ox} \epsilon_0}{T_{ox}} = \frac{3.9 \times 8.854 \times 10^{-12}}{4 \times 10^{-9}}$$

$$V_{GS} - V_{TH} = 2.5 - 0.5 = 2 \text{ V} \quad = 0.0086 \text{ F/m}^2$$

~~$I_{DS}$~~  Not given  $V_{DS}$  so ignore  $\lambda$  factor for  $I_{DS}$  calculation

$$I_{DS} = \frac{1}{2} \frac{10 \times 10^{-6}}{0.25 \times 10^{-6}} \times 0.04 \times 0.0086 \times 2^2$$

$$= 0.0275 \text{ A}$$

$$= 27.5 \text{ mA}$$

$$g_m = \frac{10 \times 10^{-6}}{0.25 \times 10^{-6}} \times 0.04 \times 0.0086 \times 2$$

$$= 0.0275 \text{ A/V}$$

$$= 27.5 \text{ mA/V} \quad (\text{just a coincidence that } g_m \text{ and } I_{DS} \text{ worked out the same for this bias voltage).)$$

The total gate oxide capacitance is

$$C_{GS} = C_{ox \text{ TOTAL}} = C_{ox} \cdot WL$$

$$= (0.0086) (10 \times 10^{-6}) (0.25 \times 10^{-6})$$

$$= 2.15 \times 10^{-14} \text{ F}$$

$$= 21.5 \text{ fF}$$


$$f_T = \frac{g_m}{2\pi C_{GS}} = \frac{27.5 \times 10^{-3}}{2\pi \times 21.5 \times 10^{-15}} = 200 \text{ GHz}$$

(~~bit~~ <sup>very</sup> unrealistic for this dimension)
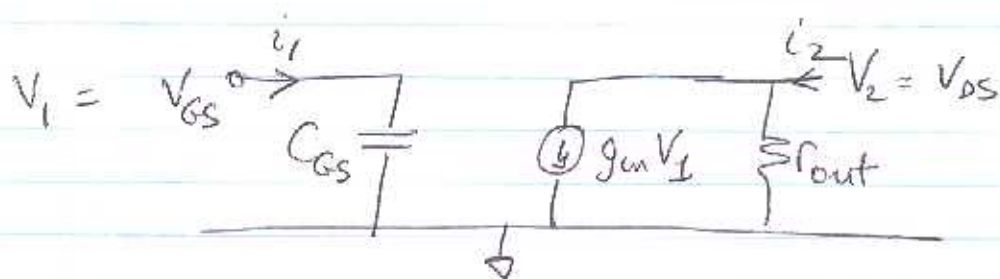
## Q1(b) Continued

$$\begin{aligned}
 g_{ds} &= \lambda I_{DS} \\
 &= 0.01 \times 0.0275 \\
 &= 0.00275 \\
 &= 2.75 \text{ mA/V}
 \end{aligned}$$

$$r_{ds} = \frac{1}{g_{ds}} = 364 \Omega$$



$y$ -parameters

$$y_{11} = \frac{i_1}{V_1} \Big|_{V_2=0} = \frac{j\omega C_{GS} V_1}{V_1} = j\omega C_{GS}$$

$$y_{12} = \frac{i_1}{V_2} \Big|_{V_1=0} = \frac{0}{V_2} = 0$$

$$y_{21} = \frac{i_2}{V_1} \Big|_{V_2=0} = \frac{g_m V_1}{V_1} = g_m = 0.0275$$

$$y_{22} = \frac{i_2}{V_2} \Big|_{V_1=0} = \frac{V_2 / r_{out}}{V_2} = \frac{1}{r_{out}} = g_{ds} = 0.00275$$

The only frequency-dependent term is  $y_{11}$

$$\begin{aligned}
 \text{At } 1 \text{ GHz, } y_{11} &= j\omega C_{GS} = j 2\pi \times 10^9 \times 2.15 \times 10^{-14} \\
 &= j 1.35 \times 10^{-4}
 \end{aligned}$$

$$|y_{11}| = 1.35 \times 10^{-4} \text{ A/V}$$



## Question 2

2(a) Derivation from notes i.e. full derivation is expected leading to:

$$F = 1 + \frac{(V_n + R_s i_n)^2}{4kTR_s} \quad \text{for } 1\text{Hz} \quad \Delta F =$$

2(b) Use the "normal" small signal circuit to calculate the small signal quantities and the formulas given to calculate  $V_n$  and  $i_n$  and then do the calculation for the 3 source impedances given.

$$g_m = \frac{q}{kT} I_c = 0.0387 \text{ A/V}$$

$$\beta = 100 \text{ given}$$

Using given  $T$ ,  $r_b$ ,  $\beta$  for a 1 Hz bandwidth

$$V_n = 1.02 \times 10^{-9}$$


$$i_n = 1.79 \times 10^{-12}$$

(i)  $R_s = 10, f = 7.51$

(ii)  $R_s = 100, f = 1.89$

(iii)  $R_s = 1000, f = 1.48$

(iv)  $R_s = 10,000, f = 3.16$

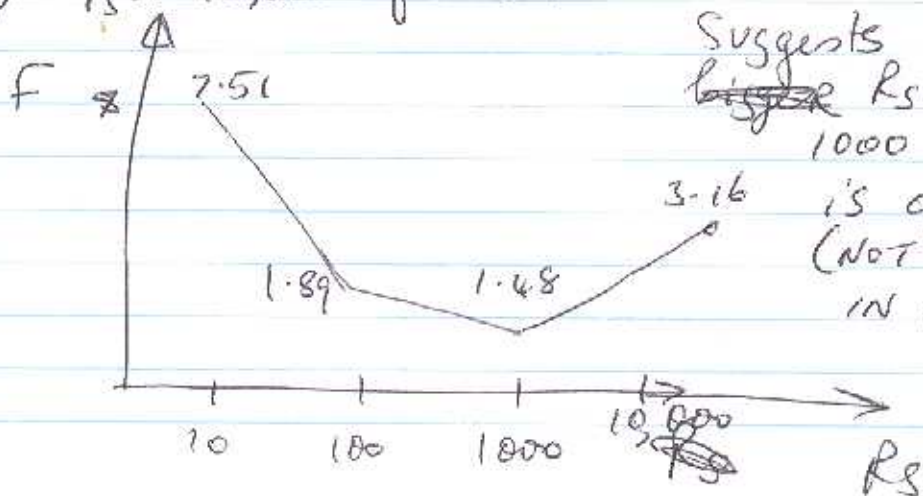

Suggests that the ~~best~~  $R_s$  between 1000 and 10000 is optimum. (NOT VERY LIKELY IN PRACTICE!)


### Question 3

- (a) From notes <sup>i.e. have to go through derivation similar to the notes leading to the final formula</sup> (except easier because can set  $\alpha_0 = 0, \alpha_2 = 0$  from beginning)

$$A_{dB} = \sqrt{0.145 \left| \frac{\alpha_1}{\alpha_3} \right|}$$

(b)

$$A_{dB} = 3.81 \text{ V}$$

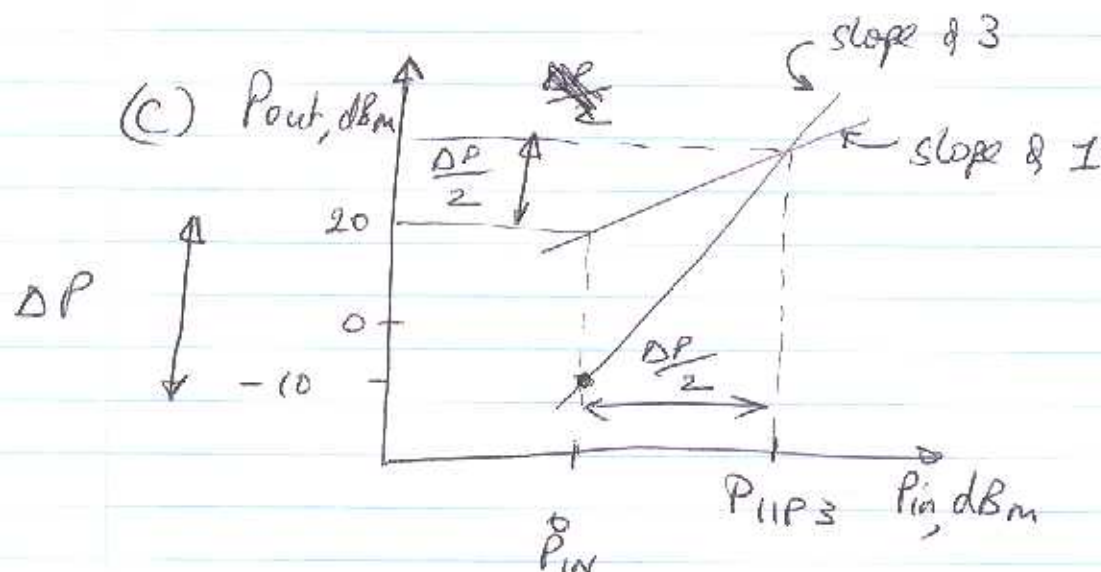

$$\Delta P = 30 \text{ dBm} \Rightarrow$$

$$P_{IIP3} = P_{in} + \frac{\Delta P}{2} = 0 + \frac{30}{2} = 15 \text{ dBm}$$

(mainly a test of remembering the graphical rule)

A slight typo in question - "third harmonic" should have read "third order IM products".

Q6(c) - Derivation from notes and "picture" of hyperabundant diode

### Question 6

6(a) Pick a topology from the notes and draw the circuit diagram.

(b)  $f = \frac{1}{2\pi\sqrt{LC}} \Rightarrow C = \frac{1}{L} \cdot \frac{1}{(2\pi f)^2}$

$$L = 1 \text{ nH}$$

~~f~~  $f = 1.8 \text{ GHz} \Rightarrow C = 2.6 \text{ pF}$

$$f = 2.0 \text{ GHz} \Rightarrow C = 2.11 \text{ pF}$$

This is the total capacitance i.e.

$$C = C_{\text{Diode}} + C_{\text{PAR}} \Rightarrow C_{\text{DIODE}} = C - C_{\text{PAR}}$$

$$f = 1.8 \text{ GHz} \therefore C_{\text{Diode}} = 2.6 - 1 = 1.6 \text{ pF}$$

$$f = 2 \text{ GHz} \therefore C_{\text{DIODE}} = 2.11 - 1 = 1.11 \text{ pF}$$

$\therefore$  Zero bias capacitance  $C_{J0} = 1.6 \text{ pF}$

With Reverse bias:

$$C = \frac{C_{J0}}{\left(1 - \frac{V_D}{V_J}\right)^M}$$

here  $M_J = 0.5$ ,  $V_J = 0.8$

$$C = \frac{C_{J0}}{\sqrt{1 - \frac{V_D}{0.8}}} \Rightarrow \left(\frac{C}{C_{J0}}\right)^2 = \frac{1}{\left(1 - \frac{V_D}{0.8}\right)}$$

$$\Rightarrow 1 - \frac{V_D}{0.8} = \left(\frac{C_{J0}}{C}\right)^2 \Rightarrow V_D = 0.8 \left(1 - \left(\frac{C_{J0}}{C}\right)^2\right)$$

$$V_D = 0.8 \left(1 - \left(\frac{1.6}{1.11}\right)^2\right) = -0.86 \text{ V}$$