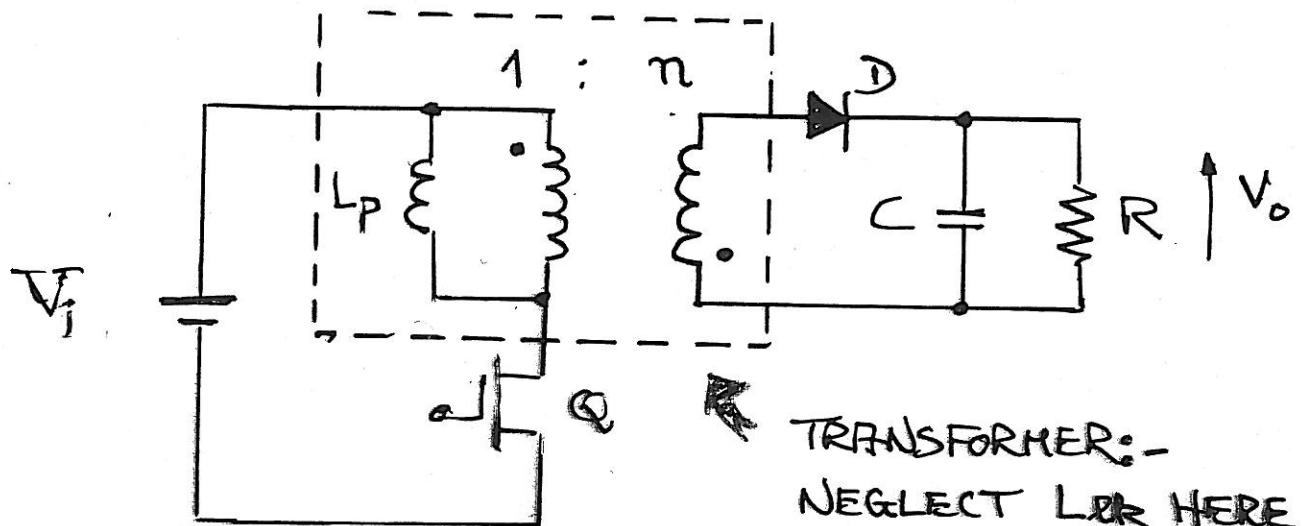





FLYBACK DC/DC CONVERTER.

(1)



Q ON


Q OFF

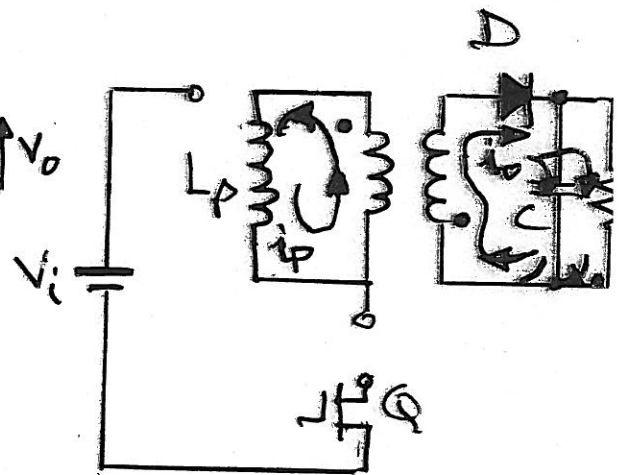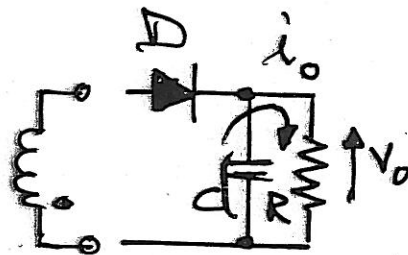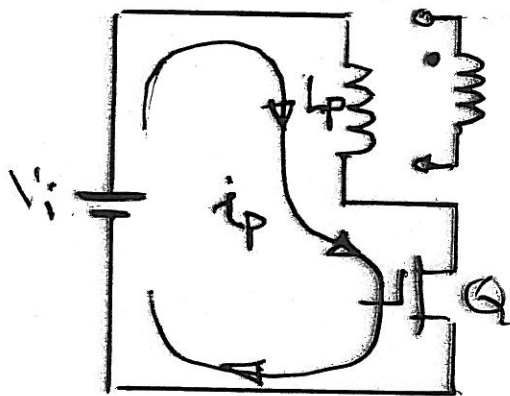

EQUATING AREAS

$$\frac{V_o}{n} (T - t_{on}) = V_i t_{on}$$
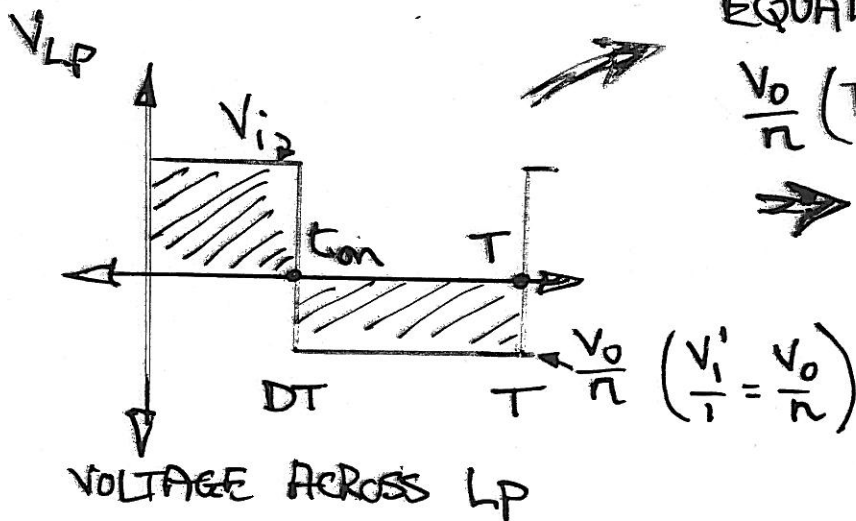
$$\Rightarrow \frac{V_o}{V_i} = n \left(\frac{D}{1-D} \right)$$



* AS BEFORE

(2)

$$I_{pmax} - I_{pmin} = \frac{V_i DT}{L_p}$$

* INPUT POWER = OUTPUT POWER

$$P_o = V_o^2 / R = P_i = V_i I_{i(avg)} = V_i \left(\frac{I_{pmax} + I_{pmin}}{2} \right) D$$

* SOLVE FOR I_{pmax} AND I_{pmin}

* FOR CONTINUOUS CONDUCTION

$$I_{pmin} \geq 0$$

$$\Rightarrow L_p \geq \frac{(1-D)^2 T}{2} \left(\frac{R}{n^2} \right)$$

* SAME AS NON-ISOLATED BUCK-BOOST WITH REFLECTED LOAD RESISTANCE (R/n^2) AS EXPECTED

* BE CAREFUL WITH THE MAXIMUM SWITCH BLOCKING VOLTAGE DURING THE OFF-TIME

$$\begin{aligned} V_Q &= V_i + \frac{V_o}{n} = V_i + \frac{1}{n} \left(\frac{n D}{1-D} \right) V_i \\ &= V_i \left[1 + \frac{D}{1-D} \right] \end{aligned}$$

$$V_Q = \frac{V_i}{1-D}$$

EG. $V_o = 2V_i$ FOR $D = 1/2$!

①

FLYBACK CONVERTER DESIGN

EXERCISE P.15.

CONTINUOUS MODE FLYBACK CONVERTER

$$P_o = 150 \text{ W @ } 5.0 \text{ V}_{dc}$$

$$V_{in} = 300 \text{ V}$$

$$f = 100 \text{ kHz}$$

$$\frac{N_1}{N_2} = 60$$

$$I_o = \text{AVERAGE O/P CURRENT} = P_o / V_o = \frac{150}{5} = 30 \text{ A}$$

$$\text{RATED LOAD RESISTANCE} = \frac{V_o}{I_o} = \frac{5}{30} = 0.167 \Omega$$

FOR CONTINUOUS MODE OPERATION

$$\frac{V_o}{V_{in}} = \frac{nD}{1-D}, \quad n = \frac{N_2}{N_1}$$

$$\Rightarrow D = \frac{1}{\left[1 + \frac{nV_{in}}{V_o}\right]}$$

$$\Rightarrow D = \frac{1}{\left[1 + \frac{300}{60 \times 5}\right]} = \frac{1}{2} \quad (*)$$

THE REFLECTED CORE VOLTAGE DURING THE OFF-TIME IS V_o/n SO THAT THE SWITCH VOLTAGE IS $V_{sw} = [V_{in} + V_o/n]$

(2)

HENCE

$$V_{sw} = \frac{V_{in}}{1-D}$$

SO THAT

$$V_{sw} = \frac{300}{1-1/2} = 600V \text{ (**)}$$

WHICH IS THE MINIMUM SWITCH BLOCKING VOLTAGE
THE MAGNETISING INDUCTANCE FOR CONTINUOUS
CURRENT OPERATION IS


$$L_m \geq \left(\frac{R}{n^2} \right) (1-D)^2 \frac{T_s}{2}$$

HENCE


$$L_m \geq \frac{0.167}{(1/60)^2} (1-1/2)^2 \frac{10 \times 10^{-6}}{2} H$$

$$\Rightarrow L_m \geq 751 \mu H \quad (***)$$

ISOLATED BUCK OR FORWARD CONVERTER

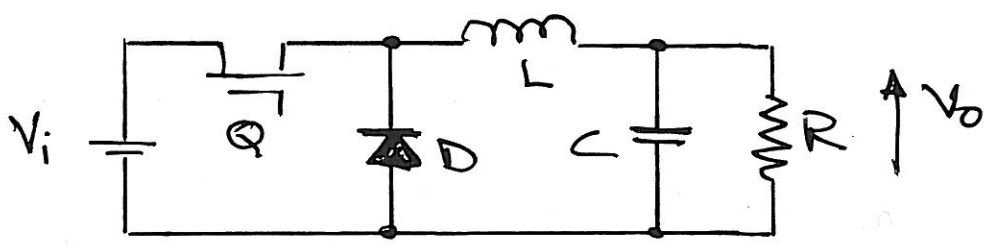


BUCK CONVERTER

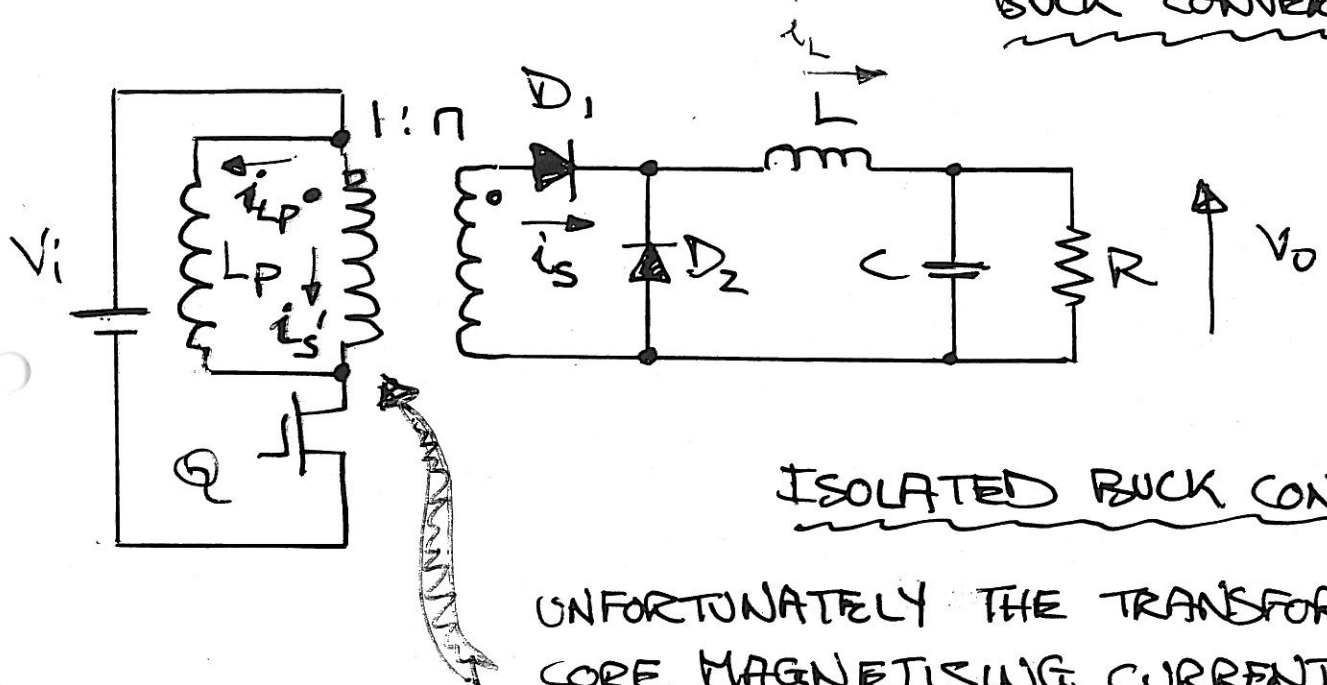


ISOLATED BUCK CONVERTER

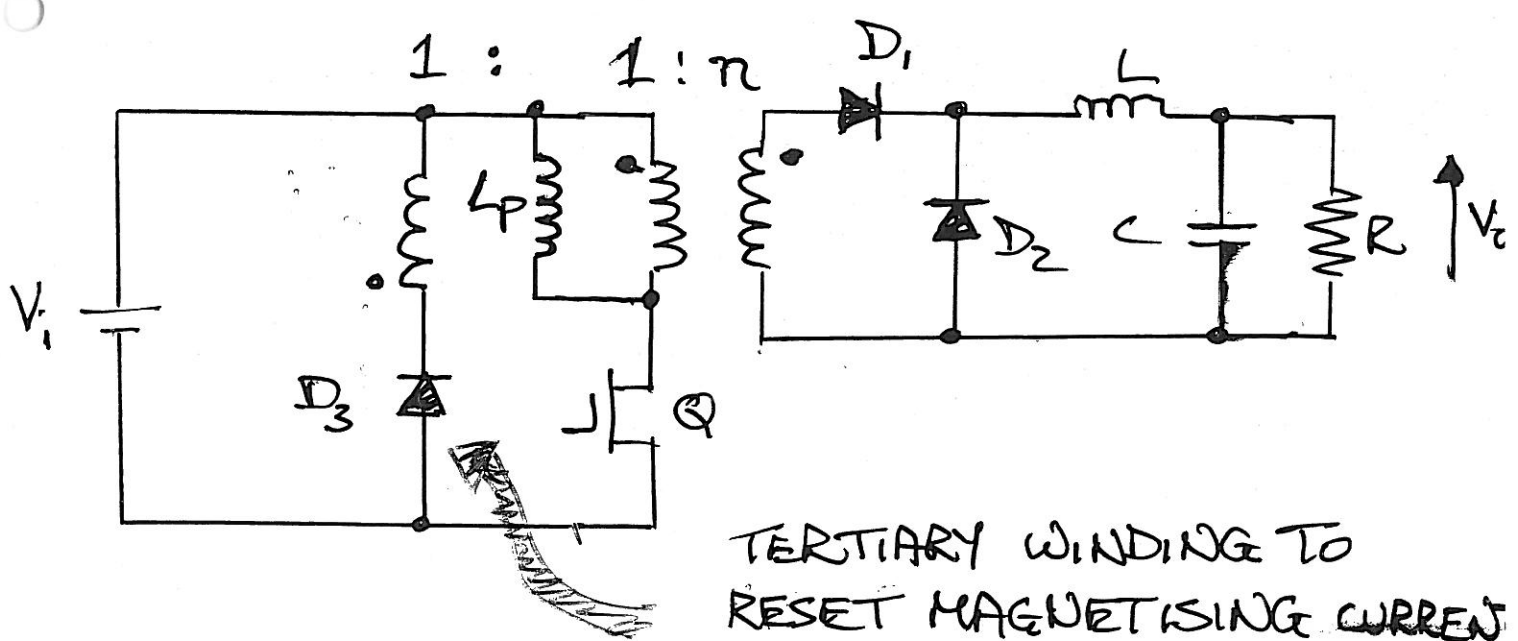UNFORTUNATELY THE TRANSFORMER CORE MAGNETISING CURRENT HAS NO PATH TO FLOW WHEN Q TURNS OFF / CORE SEES NETT AVERAGE VOLTAGE / CORE SATURATES




TERTIARY WINDING TO RESET MAGNETISING CURRENT TO ZERO DURING OFF TIME.

(2)

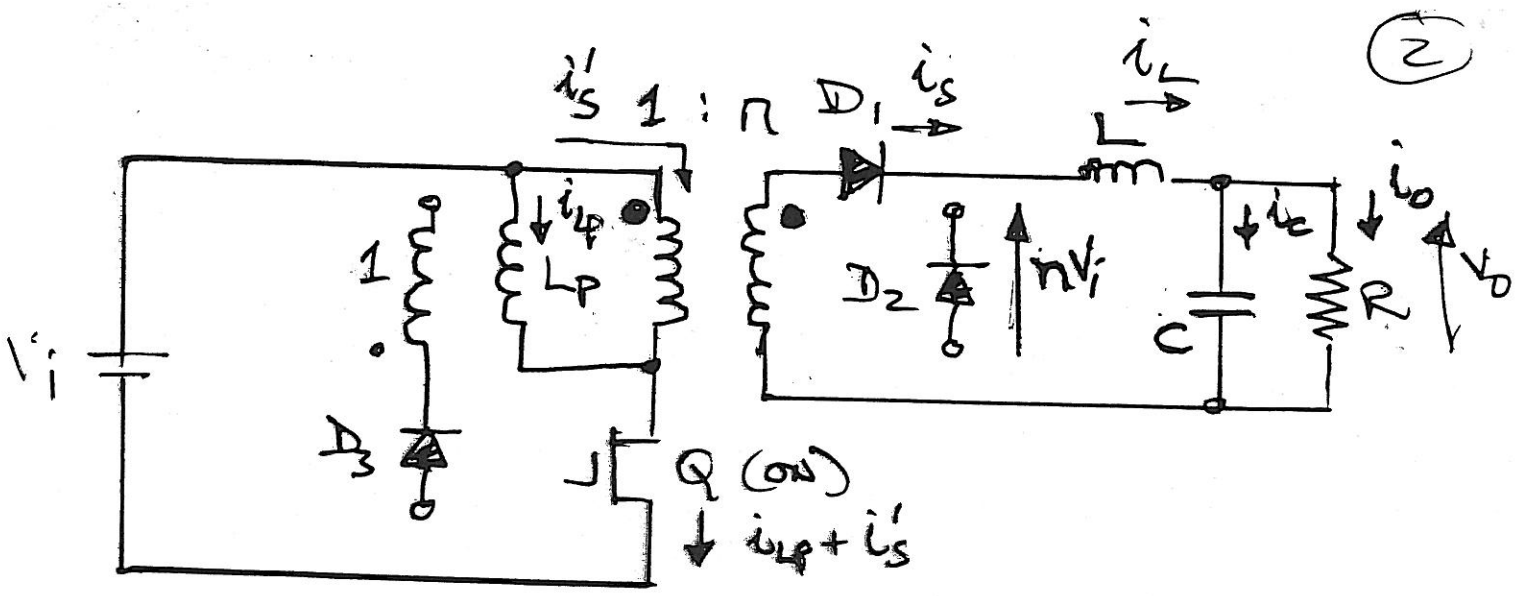


CURRENTS AND VOLTAGES DURING ON-TIME

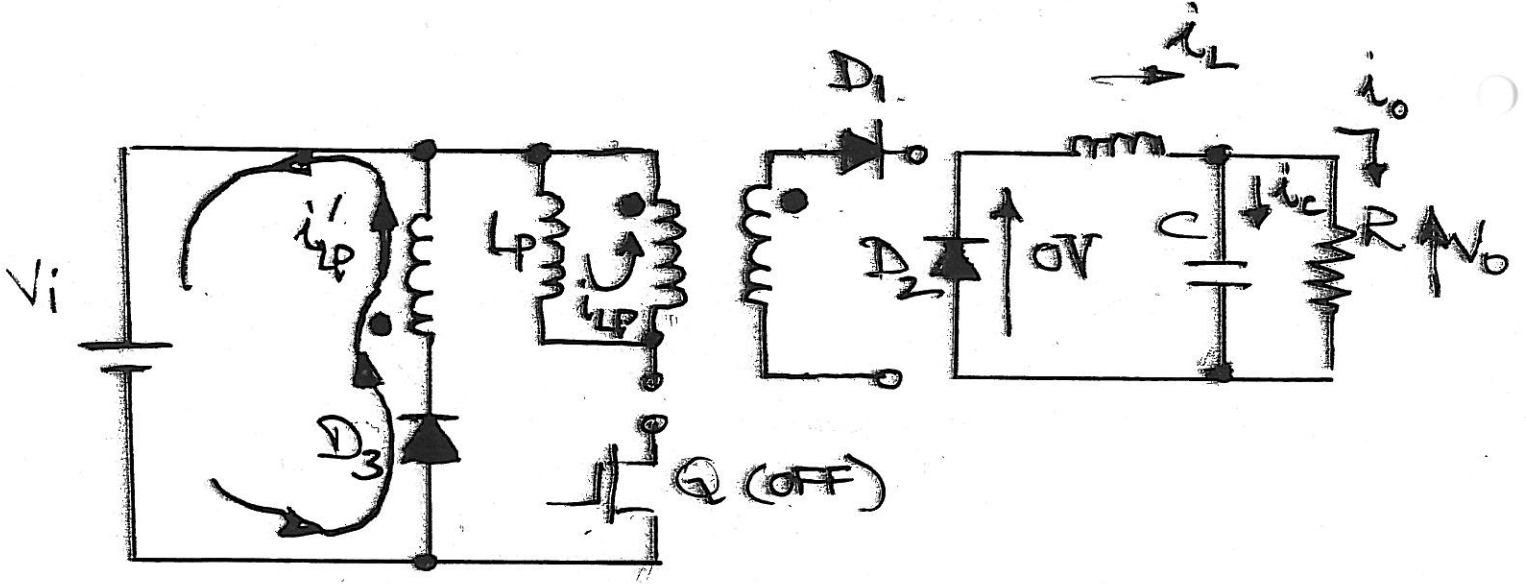

CURRENTS AND VOLTAGES DURING OFF-TIME

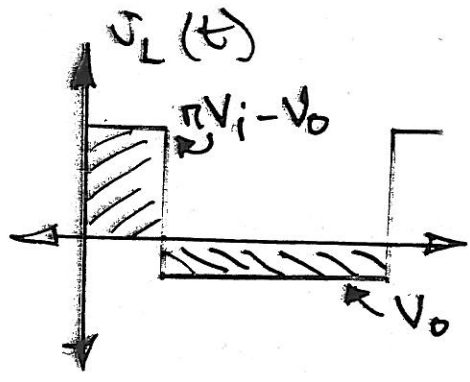* NOTE LIMIT ON D TO ALLOW ENOUGH TIME TO RESET i_L



* EQUATE OUTPUT INDUCTOR VOLT-SECONDS

$$(nV_i - V_0) t_{on} = V_0 (T - t_{on})$$

$$\Rightarrow \frac{V_0}{V_i} = nD$$

$$* I_{Lmax} - I_{Lmin} = \frac{V_0}{L} (1-D)T$$

* EQUATE INPUT AND OUTPUT POWERS (3)

$$P_i = P_o = r V_i \left(\frac{I_{Lmax} + I_{Lmin}}{2} \right) D$$
$$= V_o^2 / R$$

* HENCE SOLVE FOR I_{Lmax} AND I_{Lmin} .
FOR CONTINUOUS CONDUCTION

$$I_{Lmin} \geq 0$$

$$\Rightarrow L \geq \left(\frac{1-D}{2} \right) T R$$

BE CAREFUL WITH SWITCH VOLTAGE
DURING OFF TIME.

E.G. FOR EQUAL TURNS RATIO

$$V_Q = 2V_i$$

