

University College Cork  
Department of Electrical and Electronic Engineering

Module UE4002 – Analog IC Design  
Op-Amp Design Assignment

Student Name: Cian O'Mahony

Student No.: 108444897

16/04/2012

## 1 Introduction

This assignment required the design of an op-amp circuit with the following specifications:

**Table 1.1: Op-Amp Specifications**


<b>DC Loop Gain</b>	> 80dB
<b>Phase Margin</b>	> 60°
<b>Gain Bandwidth Product</b>	> 15MHz
<b>Power Dissipation</b>	< 1mW

The external conditions under which the op-amp was to be simulated are as follows:

**Table 1.2: Op-Amp External Conditions**

<b>Supply Voltage</b>	3.3V
<b>Input Bias Current</b>	100μA
<b>Common-mode Voltage Reference</b>	1.5V
<b>Capacitive Load</b>	10pF
<b>Process</b>	c35b4

The top-level schematic of the design is thus as shown in the figure below:

 

**Figure 1.1: Top-level Amplifier Schematic**

## 2 Op-Amp Architecture Description

The open-loop architecture chosen for this design is a two stage operational amplifier shown below in Figure 2.1. A differential amplifier with a diode load (M1-4 and M7) is the first stage, the output of which feeds into a PMOS common source stage (M5 and M6). The bias currents relative to the input bias current  $2I_B$  in both stages are determined by the (W/L) ratios of M7 and M6 to the (W/L) ratio of M8.

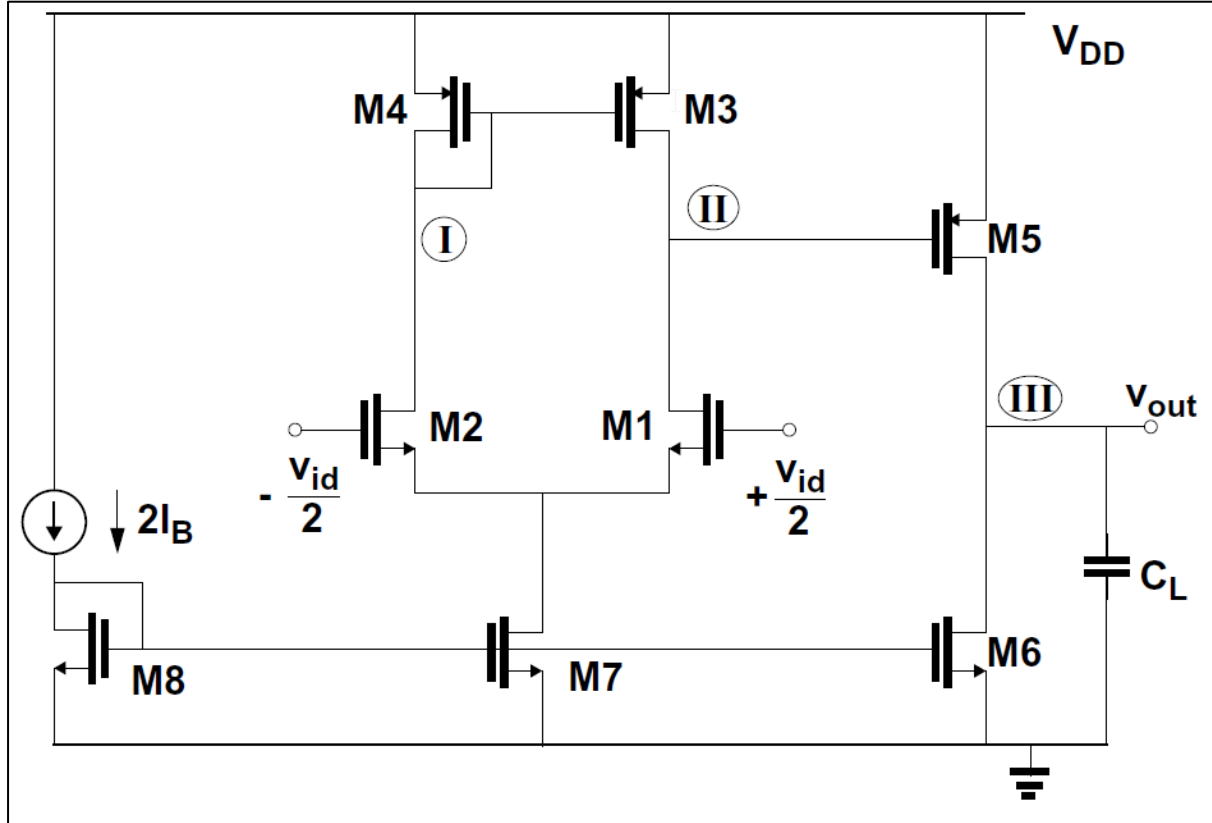


Figure 2.1: Two-stage Op-Amp Architecture

The gain of the first stage in terms of the small-signal parameters (assuming all transistors are operating in saturation) is given by:

$$Gain_1 = \frac{g_{m1}}{g_{ds1} + g_{ds3}}$$


The gain of the common source stage (again assuming both transistors are biased in saturation) is given by:

$$Gain_2 = \frac{g_{m5}}{g_{ds5} + g_{ds6}}$$

Therefore, the total open-loop gain of the op-amp is given by the product of both these terms:

$$Gain_{tot} = Gain_1 * Gain_2 = \frac{g_{m1}}{g_{ds1} + g_{ds3}} \cdot \frac{g_{m5}}{g_{ds5} + g_{ds6}}$$

A frequency compensation element is also added to the circuit by placing a resistor and capacitor in series between the gate and drain of M5 as shown in Figure 2.2 below.

 

**Figure 2.2: Frequency Compensation Components**

The capacitor has the effect of splitting the poles of the circuit by reducing the frequency of the first-stage pole and increasing the frequency of the second-stage pole, and so the first pole becomes dominant and the second can be neglected in some of the terms of the transfer function. Just adding a capacitor would however also introduce a zero to the transfer function which ruins the stability of the op-amp. This effect is negated by the addition of the resistor in series which can theoretically push the zero frequency to infinity.

### 3 Op-Amp Design and Specifications

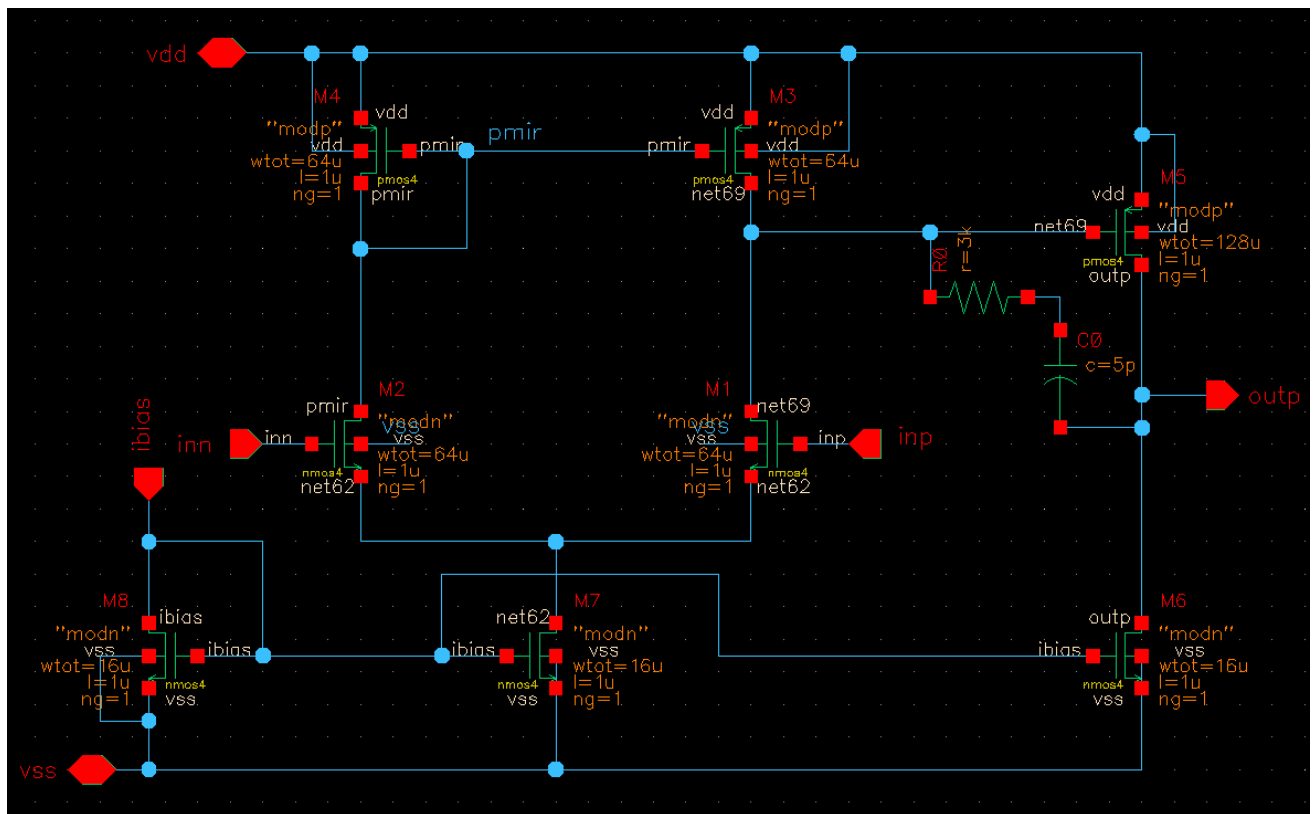


Figure 3.1: Finalised Op-Amp Design

The finalised design for the op-amp is shown above. The external bias current input to the op-amp is specified in the assignment as being  $100\mu\text{A}$ . With a  $3.3\text{V}$  supply voltage also specified along with a maximum power of  $1\text{mW}$ , this limits the total current allowed to flow in the circuit to  $\sim 300\mu\text{A}$ . Hence, the (W/L) values of both M7 and M6 were set to be the same as M8 ( $16/1$ ) to ensure that  $100\mu\text{A}$  flowed in each of the three branches of the circuit.

By experimenting with the values of the compensation resistor and capacitor, the best results were observed with  $R=3\text{k}\Omega$  and  $C=5\text{pF}$ .

The final specifications of the op-amp are recorded in Table 3.1 below:

Table 3.1: Op-Amp Design Characteristics

Power	1mW
DC Gain	90.94dB
Phase Margin	72.05°
Gain Bandwidth Product	24.23MHz
3dB Frequency	687.2Hz
Overshoot	0.78%

An interesting observation from the design is that a power saving of approximately 33% can be obtained from the design if the (W/L) ratios of M7 and M6 are halved, while the other

device specifications are still acceptable, with only the Gain Bandwidth product (marginally) failing to meet the requirements. This would be useful in such applications where minimising the power dissipation is more important than maximising specifications. When this is done for the above design the following specifications result:

<b>Power</b>	0.66mW
<b>DC Gain</b>	93.88dB
<b>Phase Margin</b>	60.94°
<b>Gain Bandwidth Product</b>	14.57MHz
<b>3dB Frequency</b>	249.9Hz
<b>Overshoot</b>	2.792%

## 4 Testbenches

The testbenches used to simulate the op-amp design are shown below. The frequency plots and step response of the system are shown on the following page.

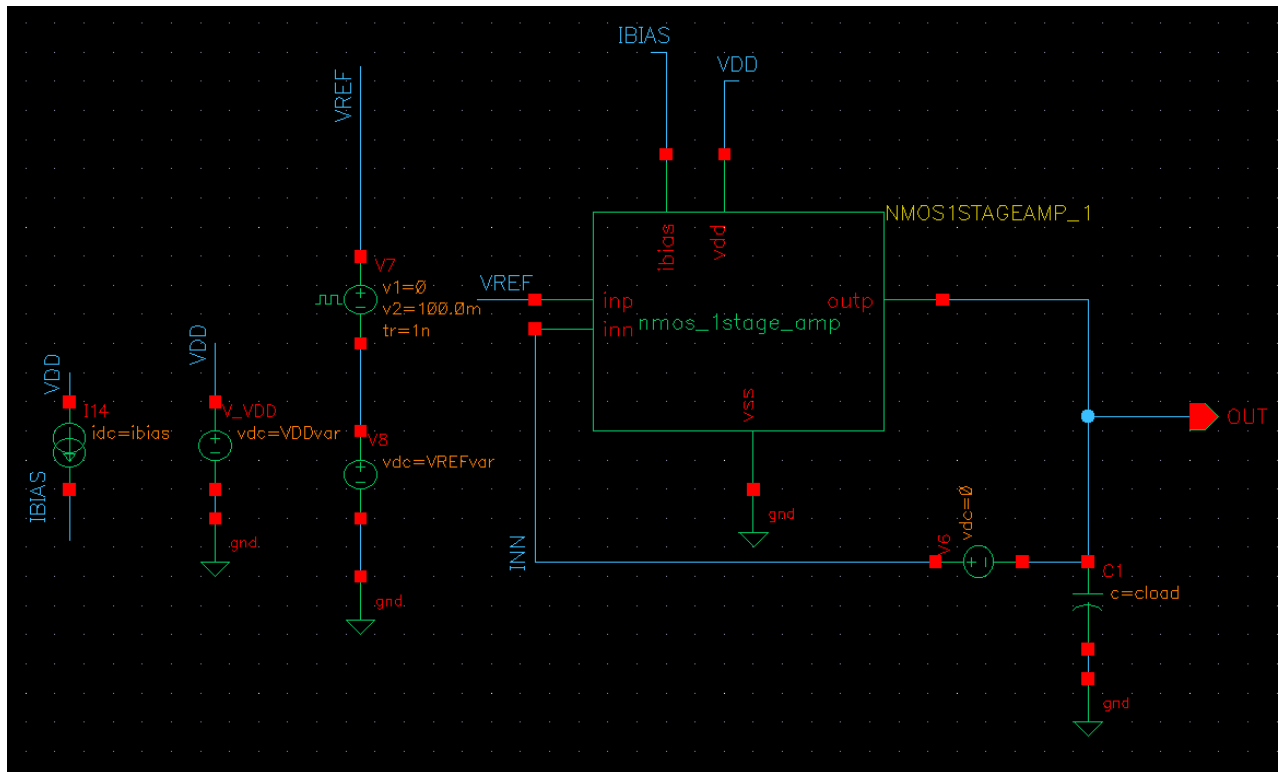


Figure 4.1: AC Simulation Testbench

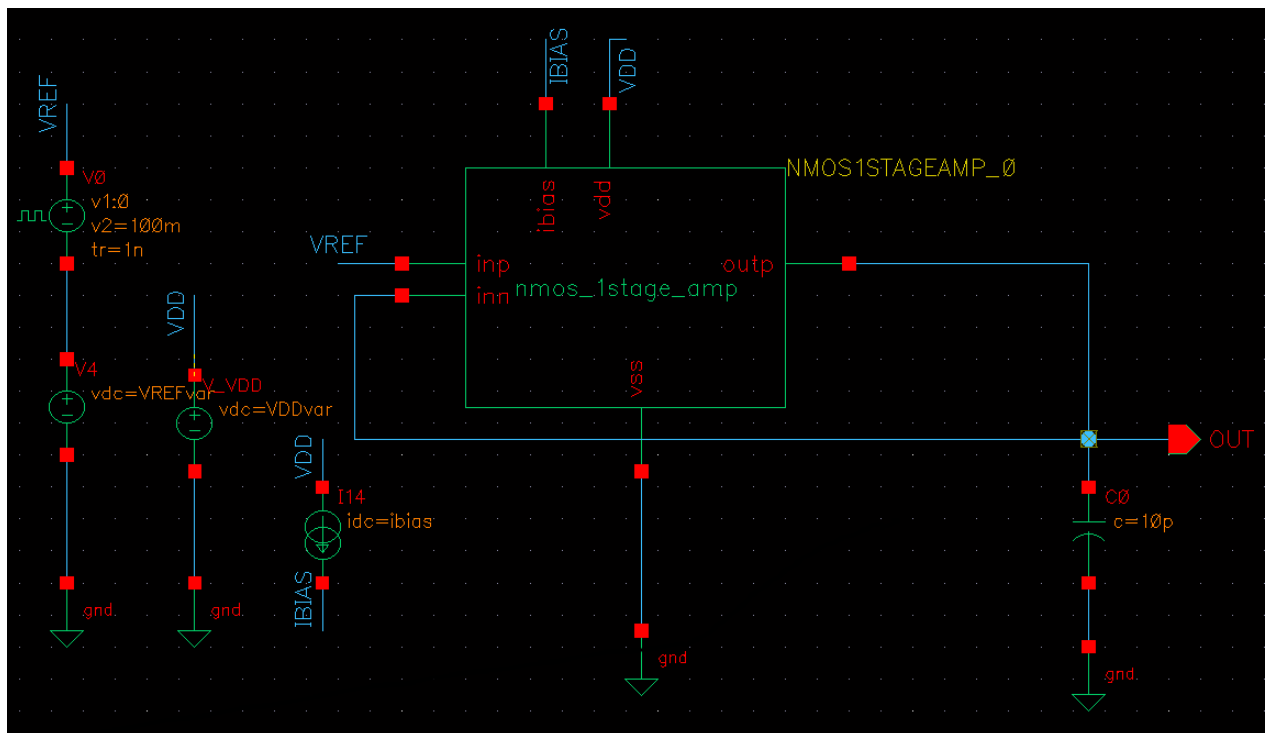


Figure 4.2: Transient Stability Testbench

 


Figure 4.3: Phase Margin and Gain vs. Frequency Plots

 


Figure 4.4: Op-Amp Step Response



## 5 Conclusion

A two-stage operational amplifier has been designed exceeding each of the minimum specified criteria in the assignment. The design was simulated in Cadence with frequency and step responses plotted and included in this report. The use of a capacitor and resistor for frequency compensation to control the placement of the dominant pole was also included in the design to improve the basic performance of the two-stage amplifier.