ED Chapter 10 Peoblem 1 1=100 Nm VR= 300 Vac essp=0.9 a= 2007 rad/s mm = 0.9 i) Vph = M 2-12 = 106.1 U Vpn = Vph cast + jVph sint = Eph + Iph Rs + j XLs Iph = 95.46 + 146.23 B= 62.831 KW Pi = 69.813 kW = 3Uph Iph COSP jii) Ipu = 243.7A Eph = 88.15 V IV) Iph X2s = 46.23 V 27 fe Ls Iph = 46.23 fe = 2 fr Ls = 46.23 Iph 4007 = 15 Jul V) $K = T = 136.8 \times 10^{-3}$ PL= Pi-Po= 6.981 kW Par = 3 Ipn R = 5.345 kW VII) PCFW = 1.636KW

```
ED Chapter 10
    Problem 2
2a) T=20Nm
                                    VB = 42 Vac
     Wm = 6,000 Rpm = 200 TT rad/s nmotor = 0.9
                                   cosp = 0.9
                                  sin 0 = 0.436
     i) V_{ph} = m \frac{V_s}{2\sqrt{3}} \Rightarrow m = 1
        Von = 14.85 V
    ii) Uph = Vph cost + j Uph sint
            = Eph + j XLs Iph + Rs Iph
        Vpn cos $ = 13.365 V = Eph + Iph Rs
        Von sin 0 = 6.473
         Po = 12.566 kW
         Pi = 13-962 kW = 3 Uph Iph cosp
    111) -> Iph = 348.24A
        Eph = 13.365 - (348-24 x 0.0015)
     ii) -> Eph = 12.84
            Iph XLS = 6.473 V
    IV)
               XLS = 0.018588 1 = 2 Tfel= = = Coe
               4-pde machine => we = 2 cm
              Ls = 0.018588
                  = 14.79uH
         K = \frac{T}{3Tph} = 0.01914
           = Eph = 0.0204
    VI) Ross = R-Po = 1,396W Vn) Perw = PLOSS - PLCU
          Pren = 3I2Rs = 545.72W
                                          = 85028W
```

```
ED Chapter 10
Problem 3
  Po = 13.92 kW
 10 = 13.92 kW

ω= 173.99 rad/s => T = 80 Nm
K- = 3.05 Nm/Arms
\Rightarrow K = \frac{KT}{3} = 1.016 \text{ Nm/Arms}
=> Eph = kw
 > Eph = 176.89 V
   R_{ph} = \frac{R_{w}}{2} = \frac{1.06}{2} = 0.531
L_{s} = \frac{L_{w}}{2} = \frac{6.58}{2} = 3.29 \text{ m H}
   n = 88%
→ Pi = Po = 15.818 kW
   Ross = 1,898W
-> Iph = 3k = 26.23A
     Pi= 3 Upt Iph cost
     Vph cos 0 = 31ph = Eph + Iph Rph = 226. 9766
    Vph = Eph + Iph Rph + j ωe Ls Iph
= 176.89 + (26.23×0.53)+j (6×ωm×Ls×Iph)
           = (190.7919 + j90.09)V
           = 210.99 (25.2760
    cost = 0.904
        Pau = 3Ipn Rpn = 1093.94W
          PCFW = 804W
```