

## Chapter 4

# DESIGNING FEEDBACK CONTROLLERS IN SWITCH-MODE DC POWER SUPPLIES

- 4-1 Objectives of Feedback Control
- 4-2 Review of the Linear Control Theory
- 4-3 Linearization of Various Transfer Function Blocks
- 4-4 Feedback Controller Design in Voltage-Mode Control
- 4-5 Peak-Current Mode Control
- 4-6 Feedback Controller Design in DCM
- References
- Problems

# OBJECTIVES OF FEEDBACK CONTROL

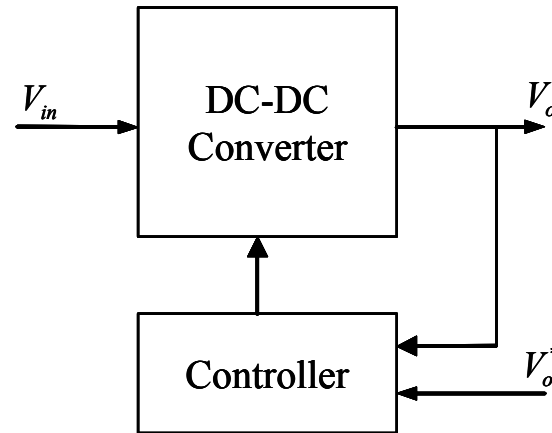


Figure 4-1 Regulated dc power supply.

- zero steady state error
- fast response
- low overshoot
- low noise susceptibility.

## The steps in designing the feedback controller:

- Linearize the system for small changes around the dc steady state operating point
- Design the feedback controller using linear control theory
- Confirm and evaluate the system response by simulations for large disturbances

# REVIEW OF LINEAR CONTROL THEORY

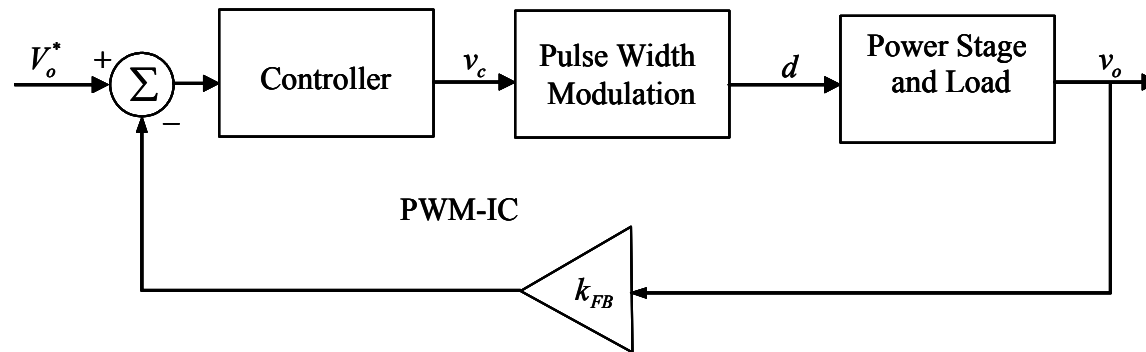


Figure 4-2 Feedback control.

Small signal representation:

$$\bar{v}_o(t) = V_o + \tilde{v}_o(t)$$

$$d(t) = D + \tilde{d}(t)$$

$$v_c(t) = V_c + \tilde{v}_c(t)$$

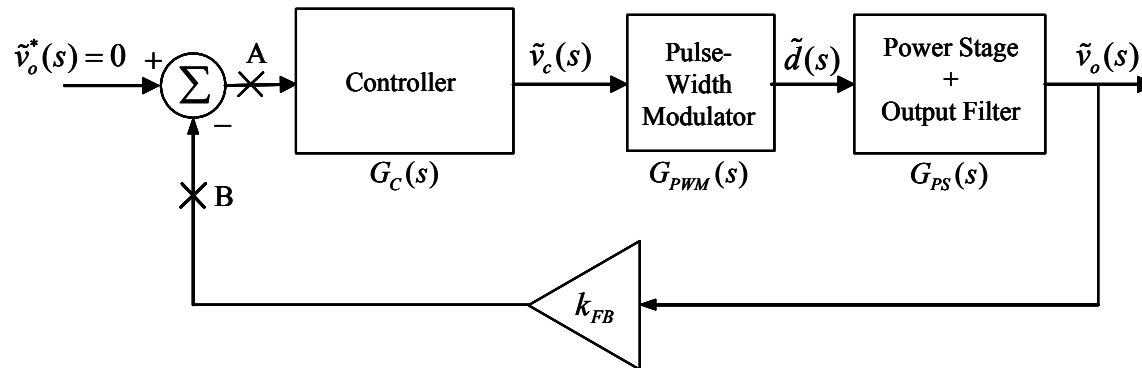


Figure 4-3 Small signal control system representation.

Loop Transfer Function:

$$G_L(s) = G_C(s)G_{PWM}(s)G_{PS}(s)k_{FB}$$

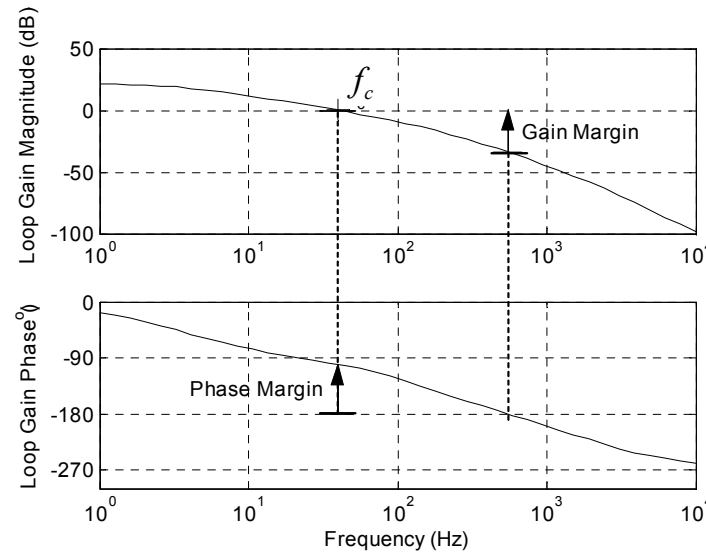


Figure 4-4 Definitions of crossover frequency, gain margin and phase margin.

Phase Margin:

$$\phi_{PM} = \phi_L|_{f_c} - (-180^\circ) = \phi_L|_{f_c} + 180^\circ$$

# LINEARIZATION OF VARIOUS TRANSFER FUNCTION BLOCKS

## Linearizing the PWM Controller IC

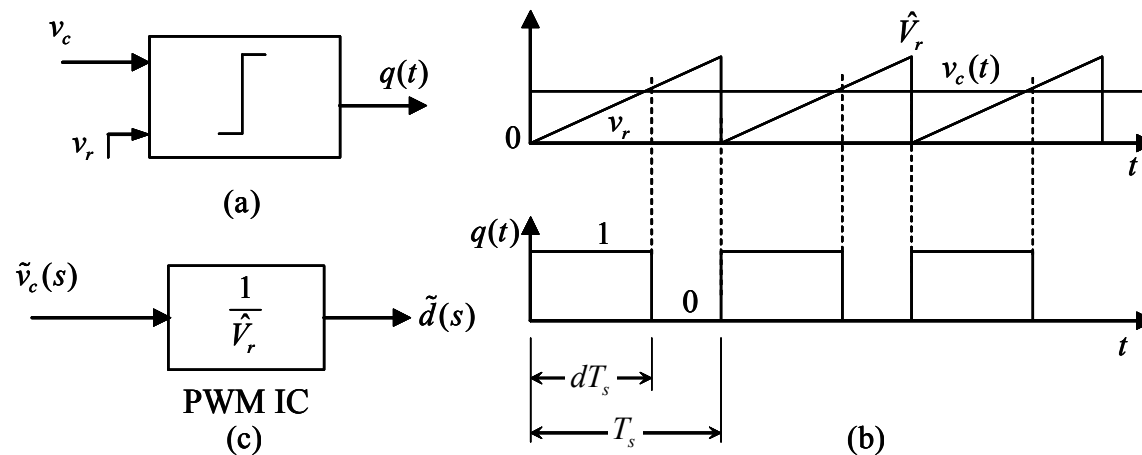


Figure 4-5 PWM waveforms.

$$d(t) = \frac{v_c(t)}{\hat{V}_r}$$

$$v_c(t) = V_c + \tilde{v}_c(t)$$

$$d(t) = \underbrace{\frac{V_c(t)}{\hat{V}_r}}_D + \underbrace{\frac{\tilde{v}_c(t)}{\hat{V}_r}}_{\tilde{d}(t)}$$

$$G_{PWM}(s) = \frac{\tilde{d}(s)}{\tilde{v}_c(s)} = \frac{1}{\hat{V}_r}$$

## Linearizing the Power Stage of DC-DC Converters in CCM

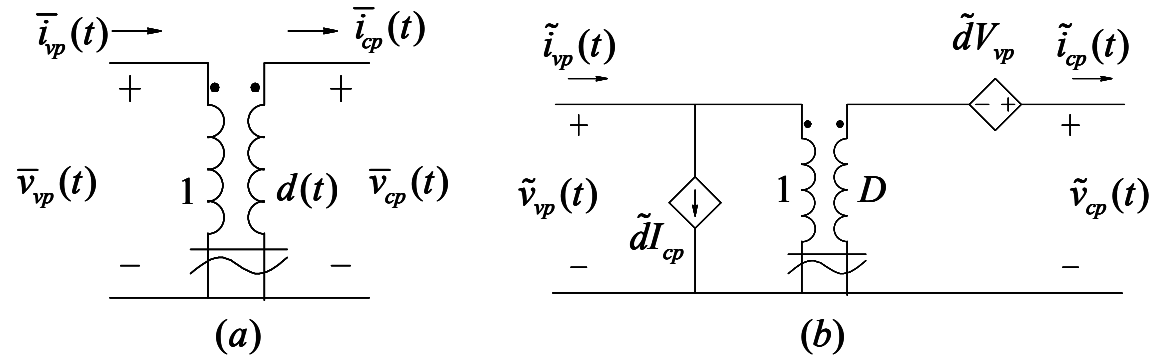


Figure 4-6 Linearizing the switching power-pole.

$$d(t) = D + \tilde{d}(t)$$

$$\bar{v}_{vp}(t) = V_{vp} + \tilde{v}_{vp}(t)$$

$$\bar{v}_{cp}(t) = V_{cp} + \tilde{v}_{cp}(t)$$

$$\bar{i}_{vp}(t) = I_{vp} + \tilde{i}_{vp}(t)$$

$$\bar{i}_{cp}(t) = I_{cp} + \tilde{i}_{cp}(t)$$

# Linearizing single-switch converters


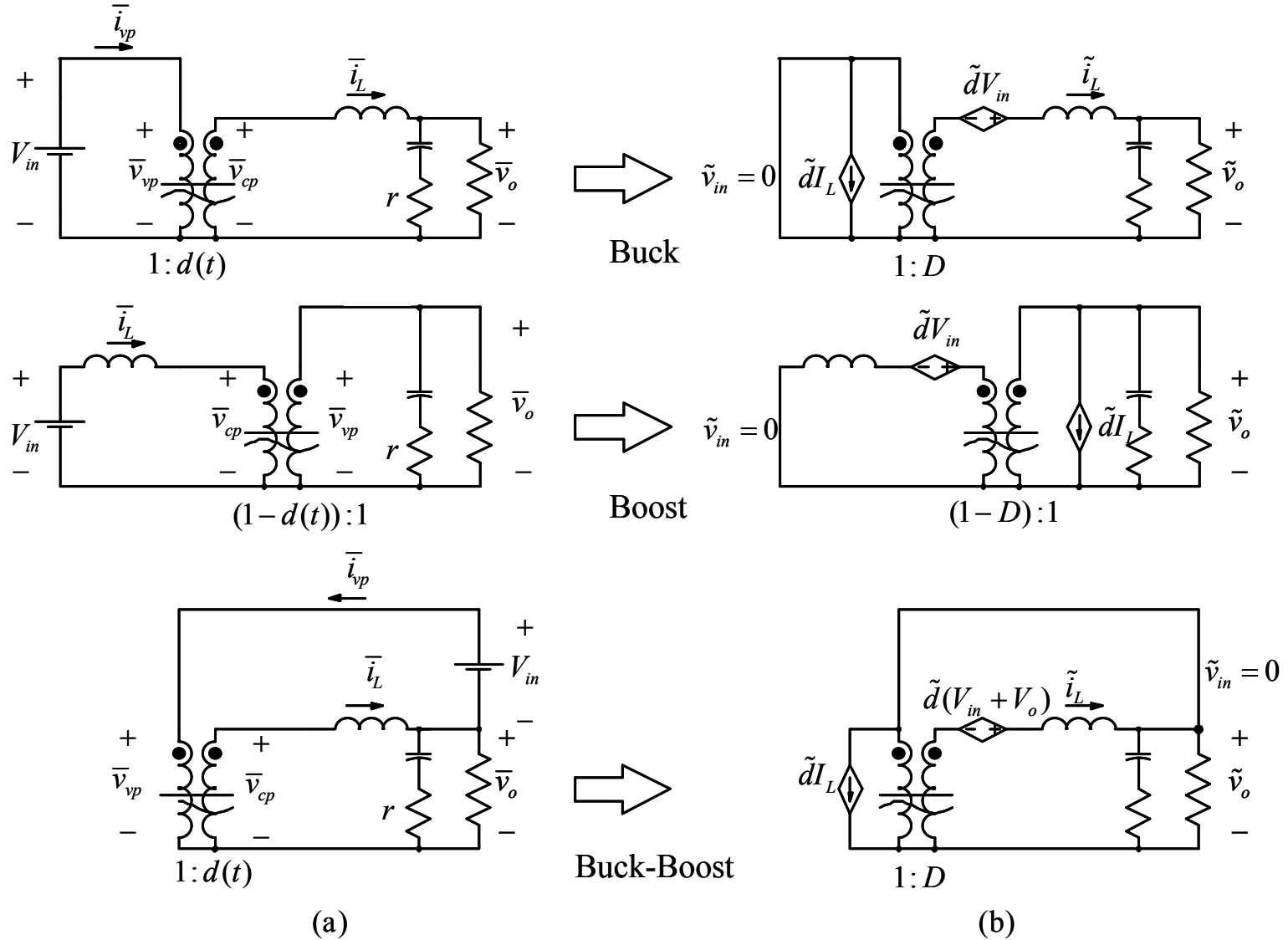


Figure 4-7 Linearizing single-switch converters in CCM.

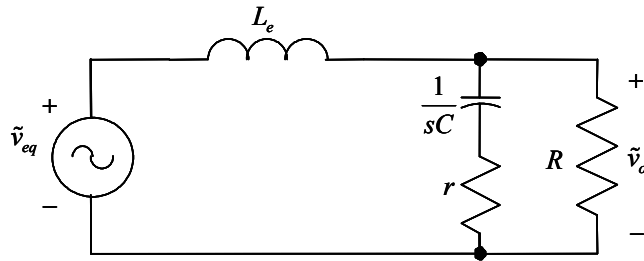

# Small signal equivalent circuit for Buck, Boost and Buck-Boost converters



$$L_e = L \quad (\text{Buck})$$

$$L_e = \frac{L}{(1-D)^2} \quad (\text{Boost and Buck-Boost})$$

Figure 4-8 Small signal equivalent circuit for Buck, Boost and Buck-Boost converters.

$$\frac{\tilde{v}_o}{\tilde{d}} = \frac{V_{in}}{LC} \frac{1 + srC}{s^2 + s\left(\frac{1}{RC} + \frac{r}{L}\right) + \frac{1}{LC}} \quad (\text{Buck})$$

$$\frac{\tilde{v}_o}{\tilde{d}} = \frac{V_{in}}{(1-D)^2} \left(1 - s \frac{L_e}{R}\right) \frac{1 + srC}{L_e C \left(s^2 + s\left(\frac{1}{RC} + \frac{r}{L_e}\right) + \frac{1}{L_e C}\right)} \quad (\text{Boost})$$

$$\frac{\tilde{v}_o}{\tilde{d}} = \frac{V_{in}}{(1-D)^2} \left(1 - s \frac{DL_e}{R}\right) \frac{1 + srC}{L_e C \left(s^2 + s\left(\frac{1}{RC} + \frac{r}{L_e}\right) + \frac{1}{L_e C}\right)} \quad (\text{Buck-Boost})$$

## Using Computer Simulation to Obtain the transfer function Bode Plots

▲ **Example 4-2** A Buck converter has the following parameters and is operating in CCM:  $L = 100 \mu H$ ,  $C = 697 \mu F$ ,  $r = 0.1 \Omega$ ,  $f_s = 100 kHz$ ,  $V_{in} = 30V$ , and  $P_o = 36W$ . The duty-ratio  $D$  is adjusted to regulate the output voltage  $V_o = 12V$ . Obtain both the gain and the phase of the power stage  $G_{PS}(s)$  for the frequencies ranging from 1 Hz to 100 kHz.



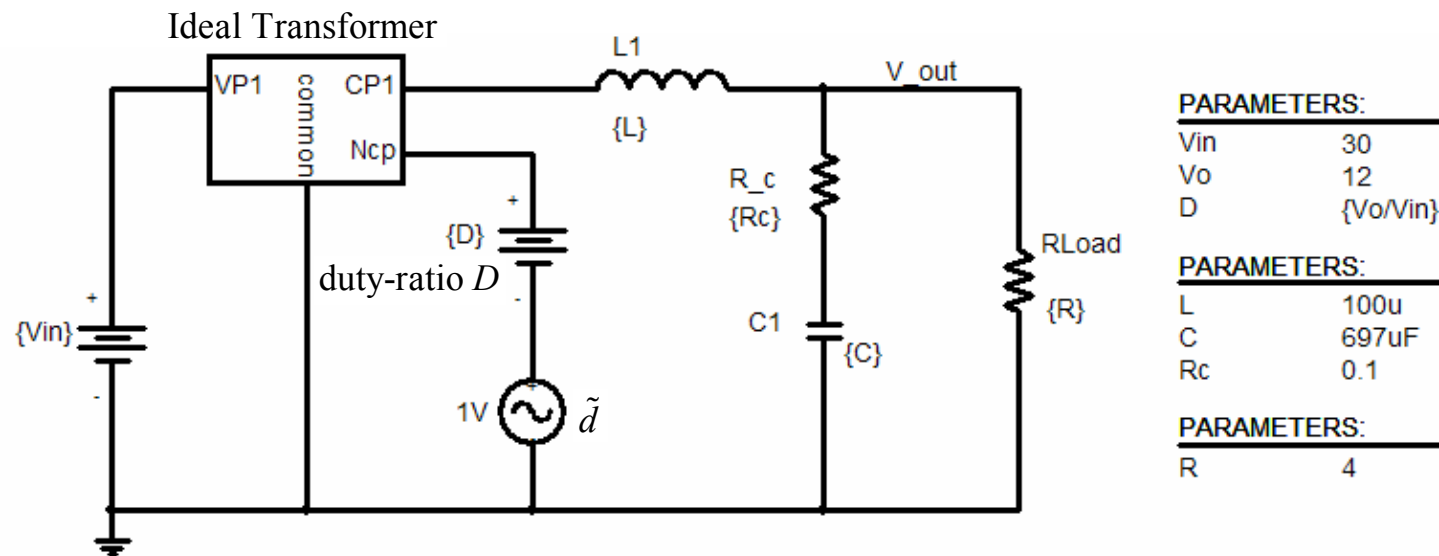


Figure 4-9 PSpice Circuit model for a Buck converter.
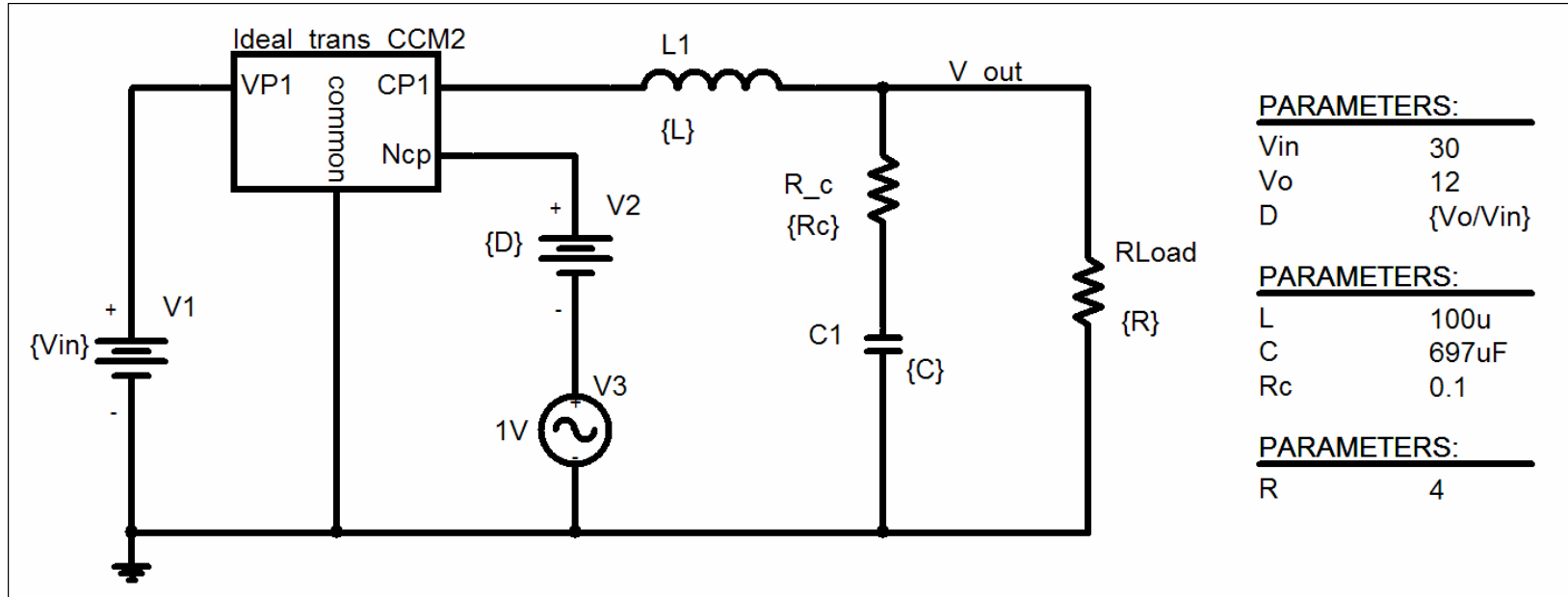
# PSpice Modeling: C:\FirstCourse\_PE\_Book03\buck\_conv\_avg.sch



# Simulation Results

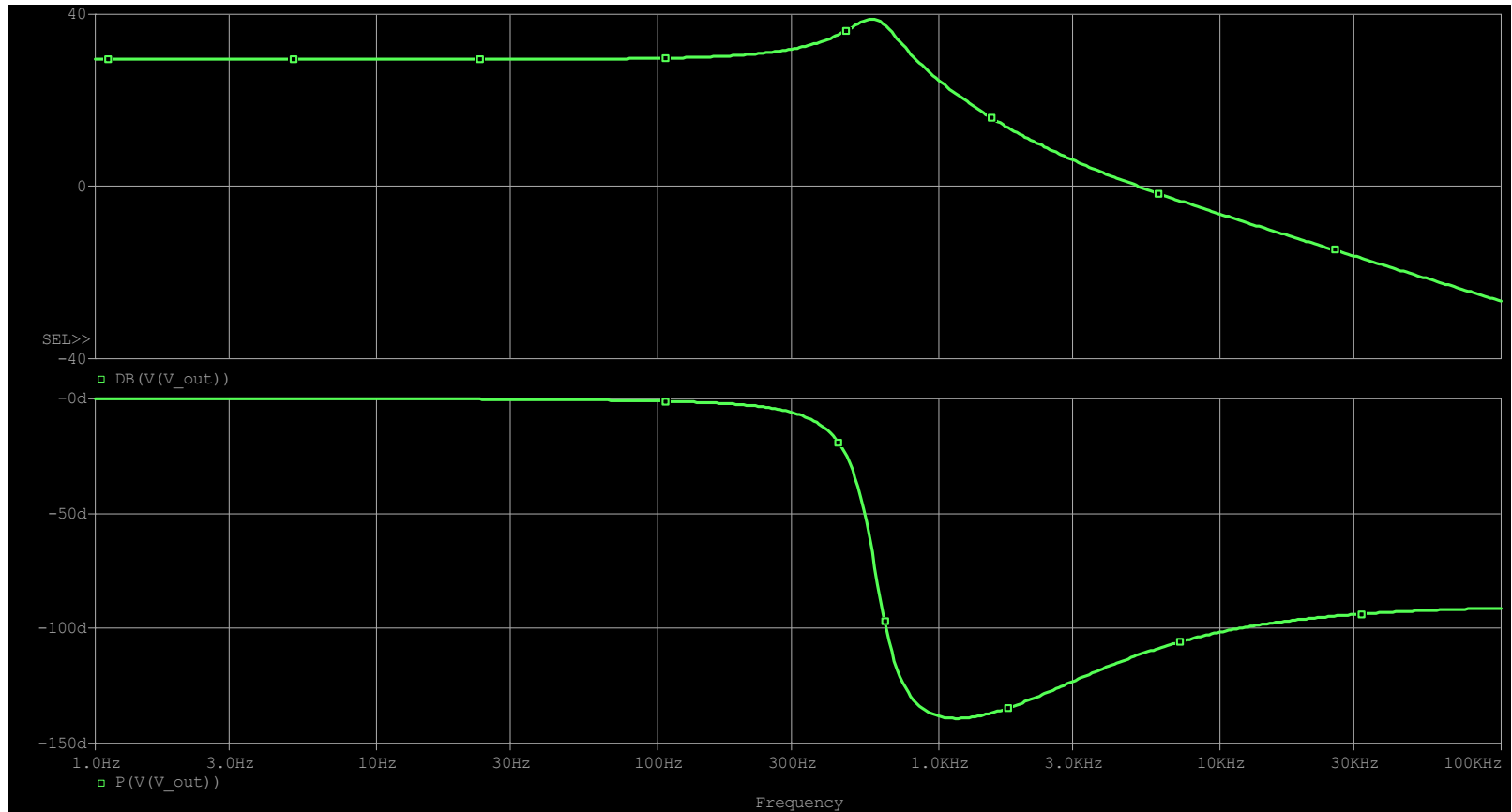

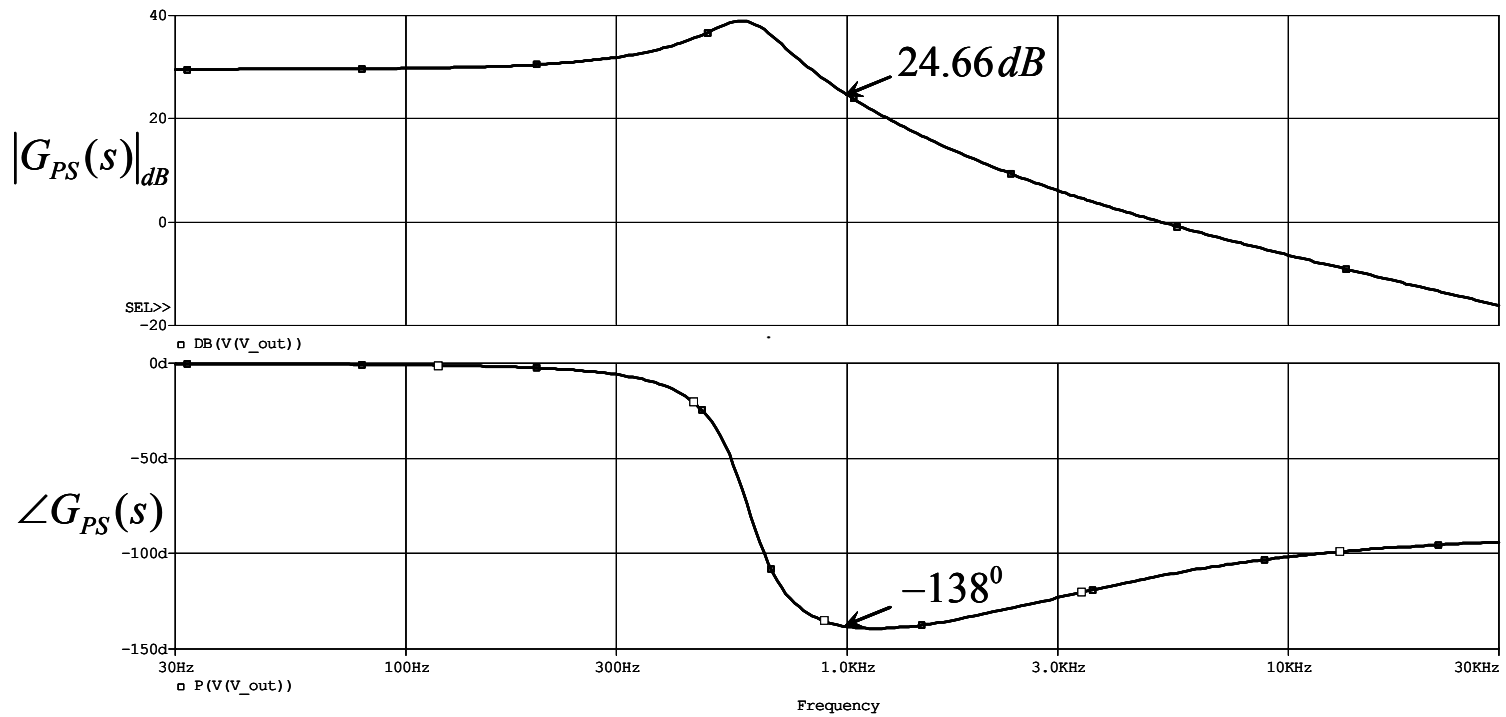


Figure 4-10 The gain and the phase of the power stage

# FEEDBACK CONTROLLER DESIGN IN VOLTAGE-MODE CONTROL

▲ **Example 4-3** Design the feedback controller for the Buck converter described in Example 4-2. The PWM-IC is as described in Example 4-1. The output voltage-sensing network in the feedback path has a gain  $k_{FB} = 0.2$ . The steady state error is required to be zero and the phase margin of the loop transfer function should be  $60^\circ$  at as high a crossover frequency as possible.

1. The crossover frequency  $f_c$  of the open-loop gain is as high as possible to result in a fast response of the closed-loop system.
2. The phase angle of the open-loop transfer function has the specified phase margin, typically  $60^\circ$  at the crossover frequency so that the response in the closed-loop system settles quickly without oscillations.
3. The phase angle of the open-loop transfer function should not drop below  $-180^\circ$  at frequencies below the crossover frequency.

$$G_c(s) = \frac{k_c}{s} \underbrace{\frac{(1 + s/\omega_z)^2}{(1 + s/\omega_p)^2}}_{\text{phase-boost}}$$

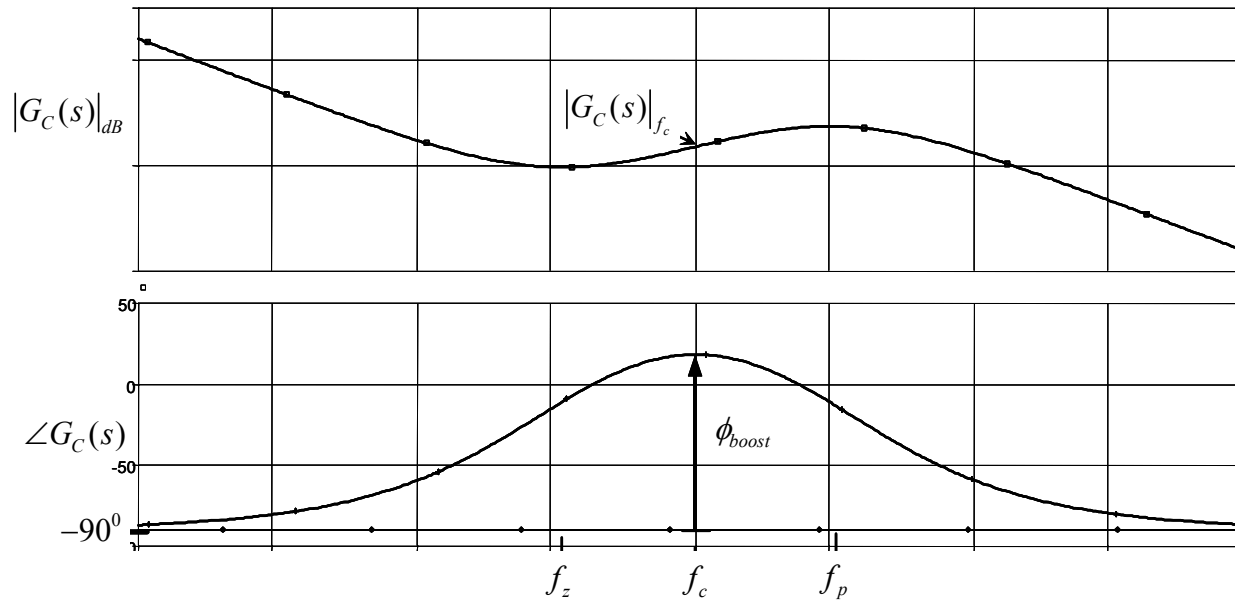


Figure 4-11 Bode plot of  $G_C(s)$  in Eq. 4-18.

Step 1: Choose the Crossover Frequency. Choose  $f_c$  to be *slightly* beyond the  $L$ - $C$  resonance frequency  $1/(2\pi\sqrt{LC})$ , which in this example is approximately 600 Hz. Therefore, we will choose  $f_c = 1$  kHz. This ensures that the phase angle of the loop remains greater than  $-180^\circ$  at all frequencies.



Step 2: Calculate the needed Phase Boost. The desired phase margin is specified as  $\phi_{PM} = 60^\circ$ . The required phase boost  $\phi_{boost}$  at the crossover frequency is calculated as follows, noting that  $G_{PWM}$  and  $k_{FB}$  produce zero phase shift:

$$\angle G_L(s)|_{f_c} = \angle G_{PS}(s)|_{f_c} + \angle G_C(s)|_{f_c} \quad (\text{from Eq. 4-2}) \quad (4-19)$$

$$\angle G_L(s)|_{f_c} = -180^\circ + \phi_{PM} \quad (\text{from Eq. 4-3}) \quad (4-20)$$

$$\angle G_C(s)|_{f_c} = -90^\circ + \phi_{boost} \quad (\text{from Fig. 4-11}) \quad (4-21)$$

Substituting Eqs. 4-20 and 4-21 into Eq. 4-19,

$$\phi_{boost} = -90^\circ + \phi_{PM} - \angle G_{PS}(s)|_{f_c} \quad (4-22)$$

In Fig. 4-10,  $\angle G_{PS}(s)|_{f_c} \simeq -138^\circ$ , substituting which in Eq. 4-22 yields the required phase boost  $\phi_{boost} = 108^\circ$ .

Step 3: Calculate the Controller Gain at the Crossover Frequency. From Eq. 4-2 at the crossover frequency  $f_c$

$$|G_L(s)|_{f_c} = |G_C(s)|_{f_c} \times |G_{PWM}(s)|_{f_c} \times |G_{PS}(s)|_{f_c} \times k_{FB} = 1 \quad (4-23)$$

In Fig. 4-10, at  $f_c = 1kHz$ ,  $|G_{PS}(s)|_{f_c=1kHz} = 24.66dB = 17.1$ . Therefore in Eq. 4-23, using the gain of the PWM block calculated in Example 4-1,

$$|G_C(s)|_{f_c} \times \underbrace{0.556}_{|G_{PWM}(s)|_{f_c}} \times \underbrace{17.1}_{|G_{PS}(s)|_{f_c}} \times \underbrace{0.2}_{k_{FB}} = 1 \quad (4-24)$$

or

$$|G_C(s)|_{f_c} = 0.5263 \quad (4-25)$$

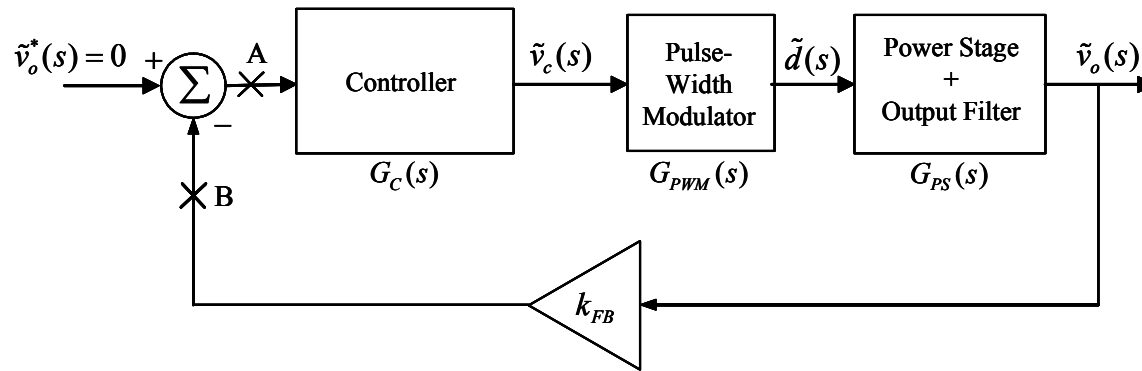


Figure 4-3 Small signal control system representation.

$$G_c(s) = \frac{k_c}{s} \underbrace{\frac{(1 + s/\omega_z)^2}{(1 + s/\omega_p)^2}}_{\text{phase-boost}}$$

$$K_{boost} = \sqrt{\frac{\omega_p}{\omega_z}}$$

$$K_{boost} = \tan\left(45^\circ + \frac{\phi_{boost}}{4}\right)$$

$$f_z = \frac{f_c}{K_{boost}}$$

$$f_p = K_{boost} f_c$$

$$k_c = |G_c(s)|_{f_c} \frac{\omega_z}{K_{boost}}$$

## Implementation of the controller by an op-amp

$$G_c(s) = \frac{k_c}{s} \underbrace{\frac{(1 + s/\omega_z)^2}{(1 + s/\omega_p)^2}}_{\text{phase-boost}}$$

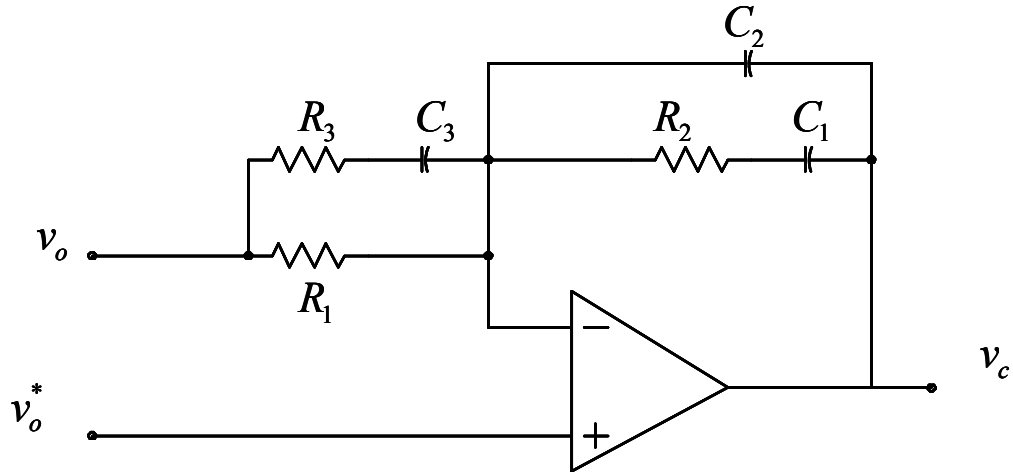


Figure 4-12 Implementation of the controller by an op-amp.

$$C_2 = \omega_z / (k_c \omega_p R_1)$$

$$C_1 = C_2 (\omega_p / \omega_z - 1)$$

$$R_2 = 1 / (\omega_z C_1)$$

$$R_3 = R_1 / (\omega_p / \omega_z - 1)$$

$$C_3 = 1 / (\omega_p R_3)$$

In this numerical example with  $f_c = 1 \text{ kHz}$ ,  $\phi_{boost} = 108^\circ$ , and  $|G_C(s)|_{f_c} = 0.5263$ , we can calculate  $K_{boost} = 3.078$  in Eq. 4-27. Using Eqs. 4-27 through 4-30,  $f_z = 324.9 \text{ Hz}$ ,  $f_p = 3078 \text{ Hz}$ , and  $k_c = 349.1$ . For the op-amp implementation, we will select  $R_1 = 100 \text{ k}\Omega$ . From Eq. 4-30,  $C_2 = 3.0 \text{ nF}$ ,  $C_1 = 25.6 \text{ nF}$ ,  $R_2 = 19.1 \text{ k}\Omega$ ,  $R_3 = 11.8 \text{ k}\Omega$ , and  $C_3 = 4.4 \text{ nF}$ .

# PSpice model of the Buck converter with voltage-mode control

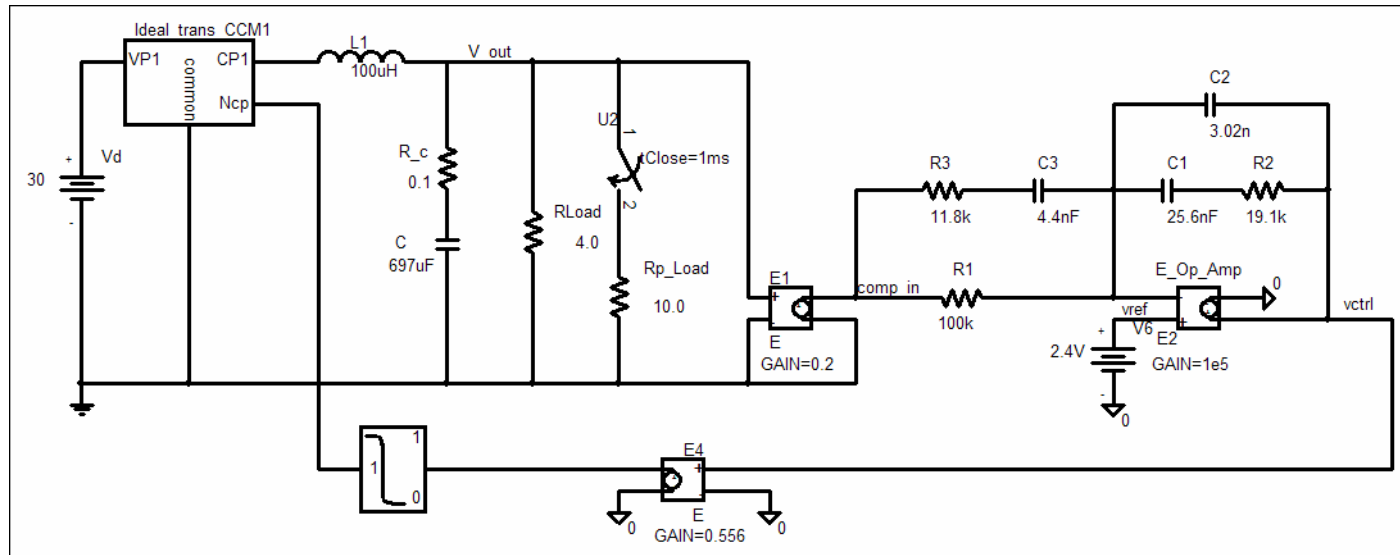


Figure 4-13 PSpice average model of the Buck converter with voltage-mode control.



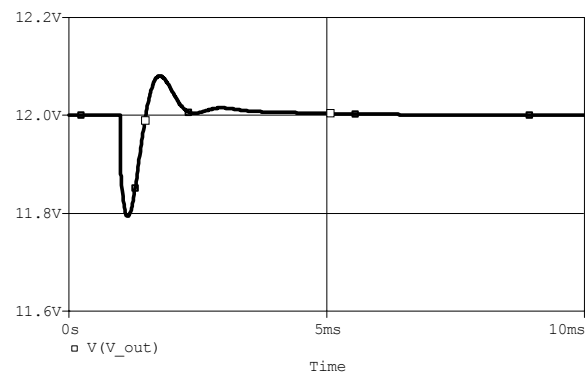


Figure 4-14 Response to a step-change in load.
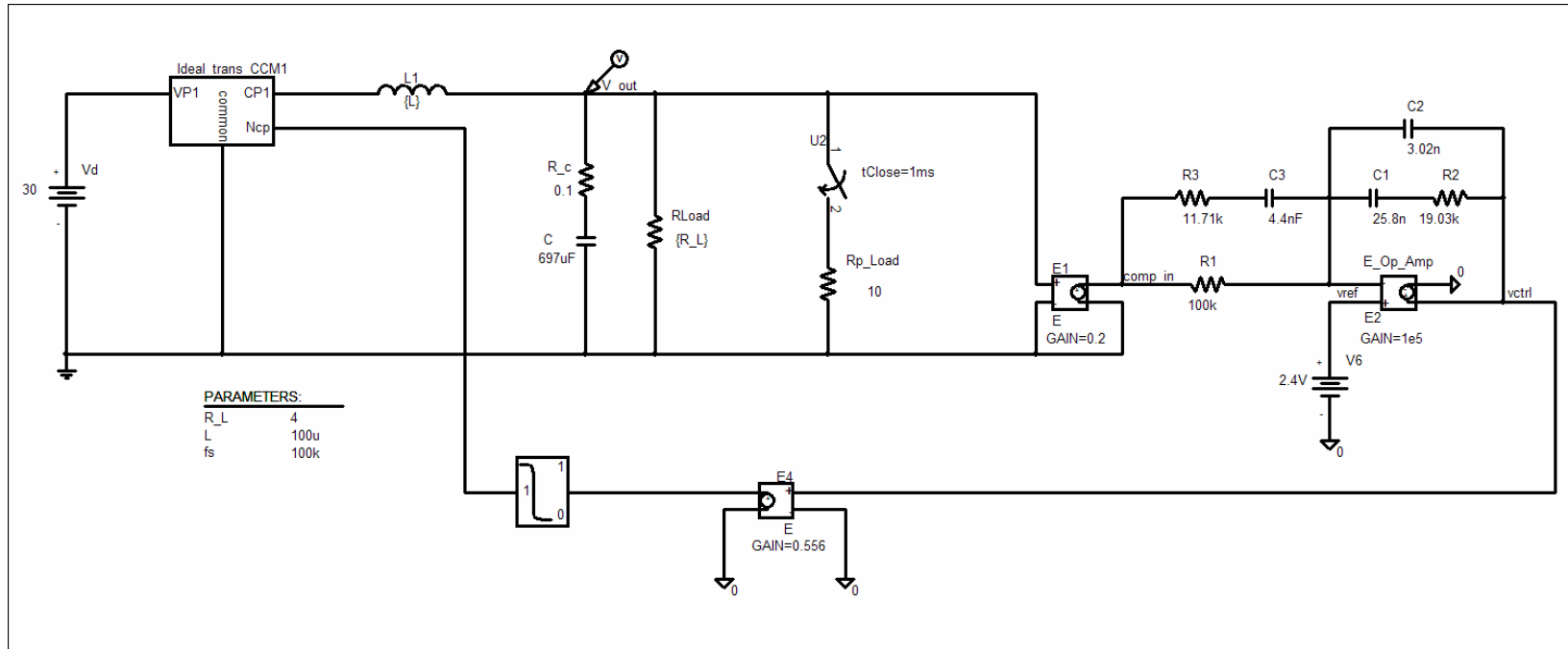
# PSpice Modeling: C:\FirstCourse\_PE\_Book03\buck\_conv\_avg\_fb\_ctrl\_op.sch



## Simulation Results

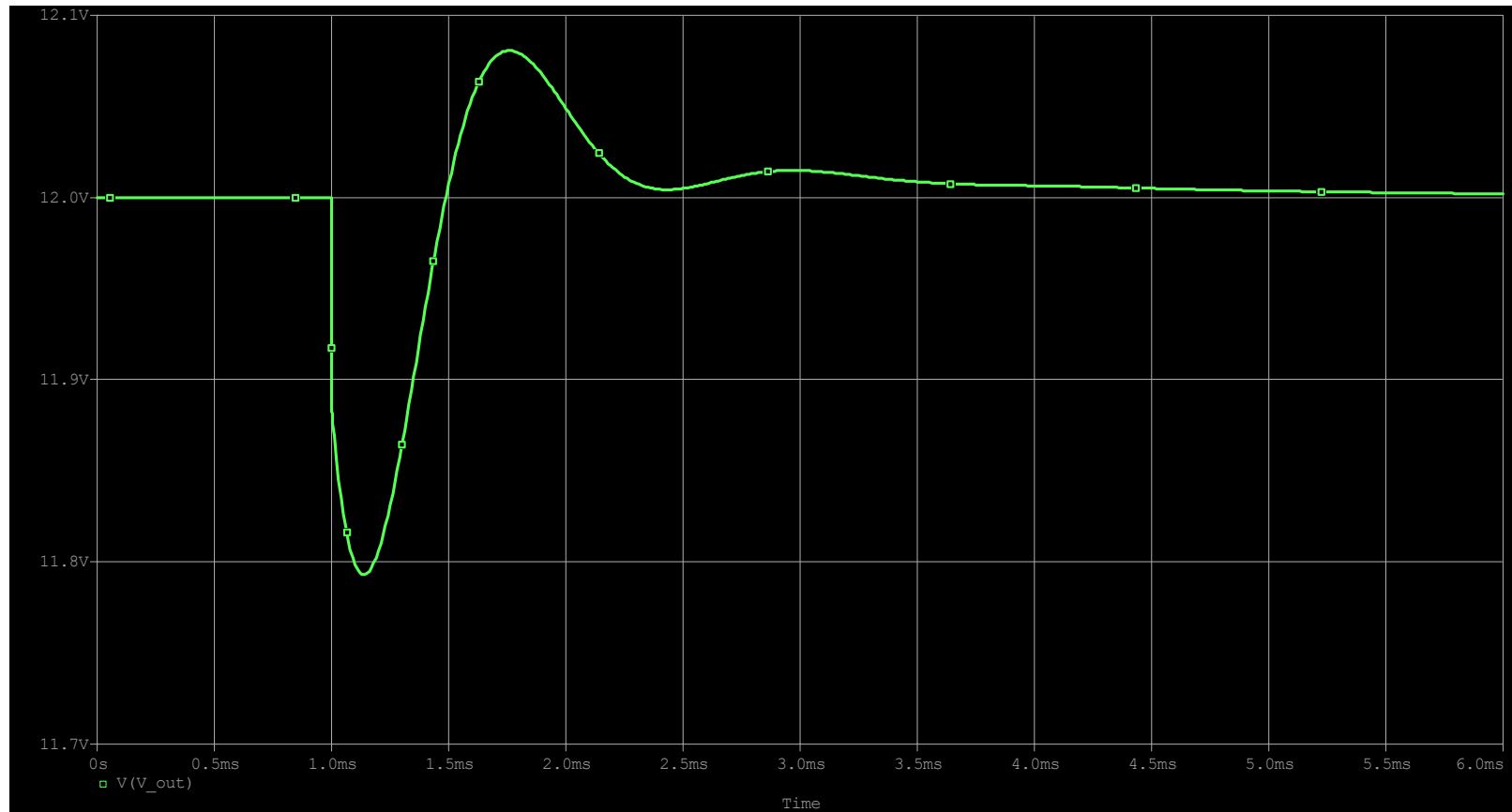



# PEAK-CURRENT MODE CONTROL

- Peak-Current-Mode Control, and
- Average-Current-Mode Control.

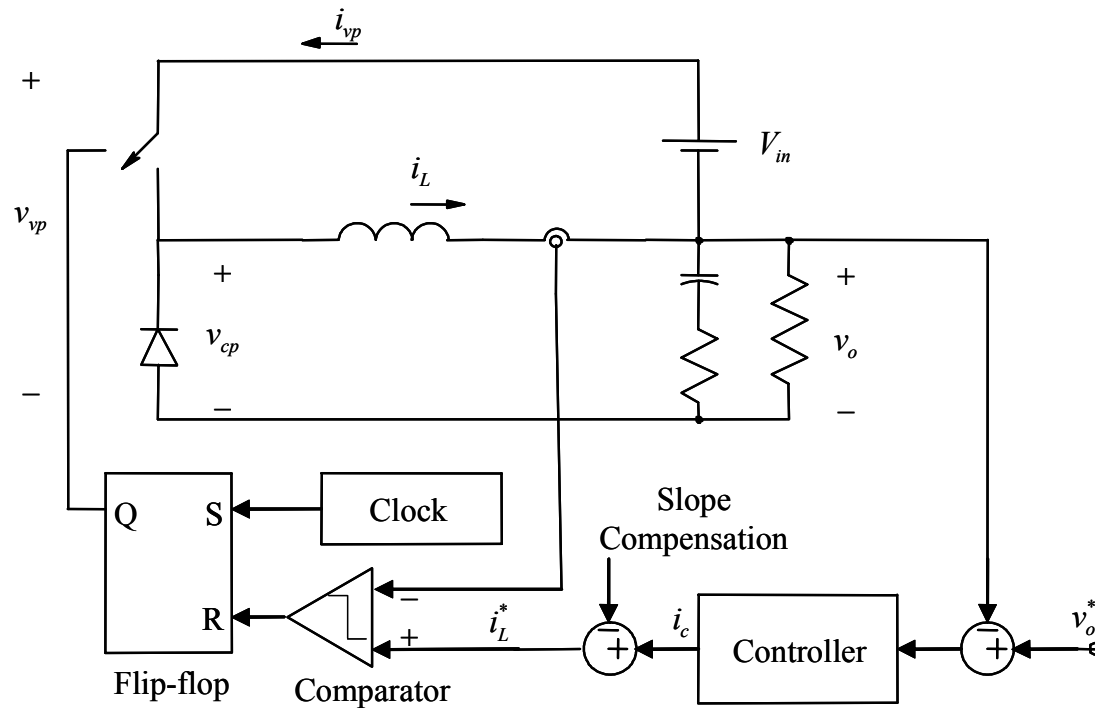


Figure 4-15 Peak current mode control.

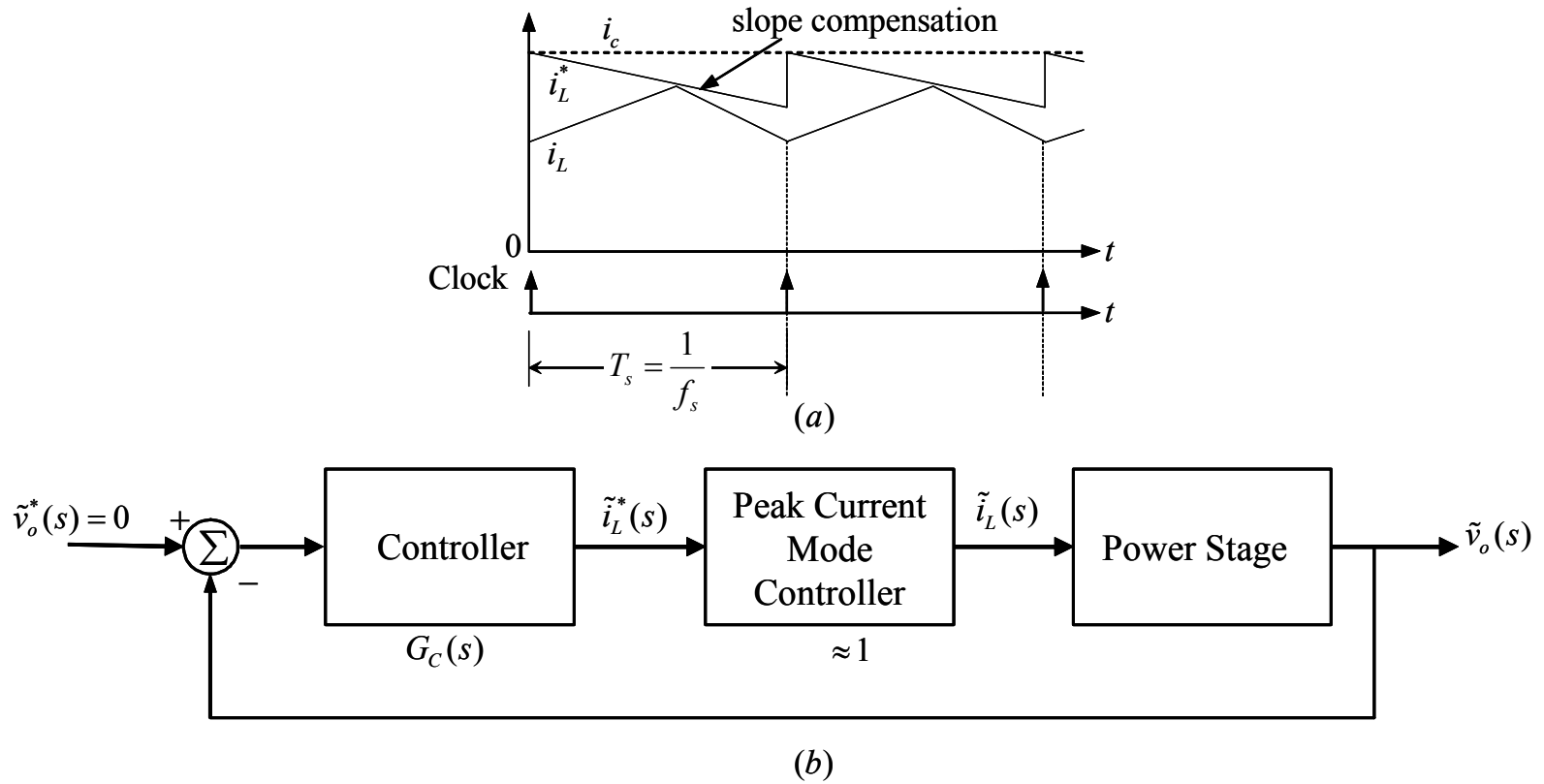


Figure 4-16 Peak-current-mode control with slope compensation.

▲ **Example 4-4** In this example, we will design a peak-current-mode controller for a Buck-Boost converter that has the following parameters and operating conditions:  $L = 100 \mu\text{H}$ ,  $C = 697 \mu\text{F}$ ,  $r = 0.01 \Omega$ ,  $f_s = 100 \text{ kHz}$ ,  $V_{in} = 30 \text{ V}$ . The output power  $P_o = 18 \text{ W}$  in CCM and the duty-ratio  $D$  is adjusted to regulate the output voltage  $V_o = 12 \text{ V}$ . The phase margin required for the voltage loop is  $60^\circ$ . Assume that in the voltage feedback network,  $k_{FB} = 1$ .

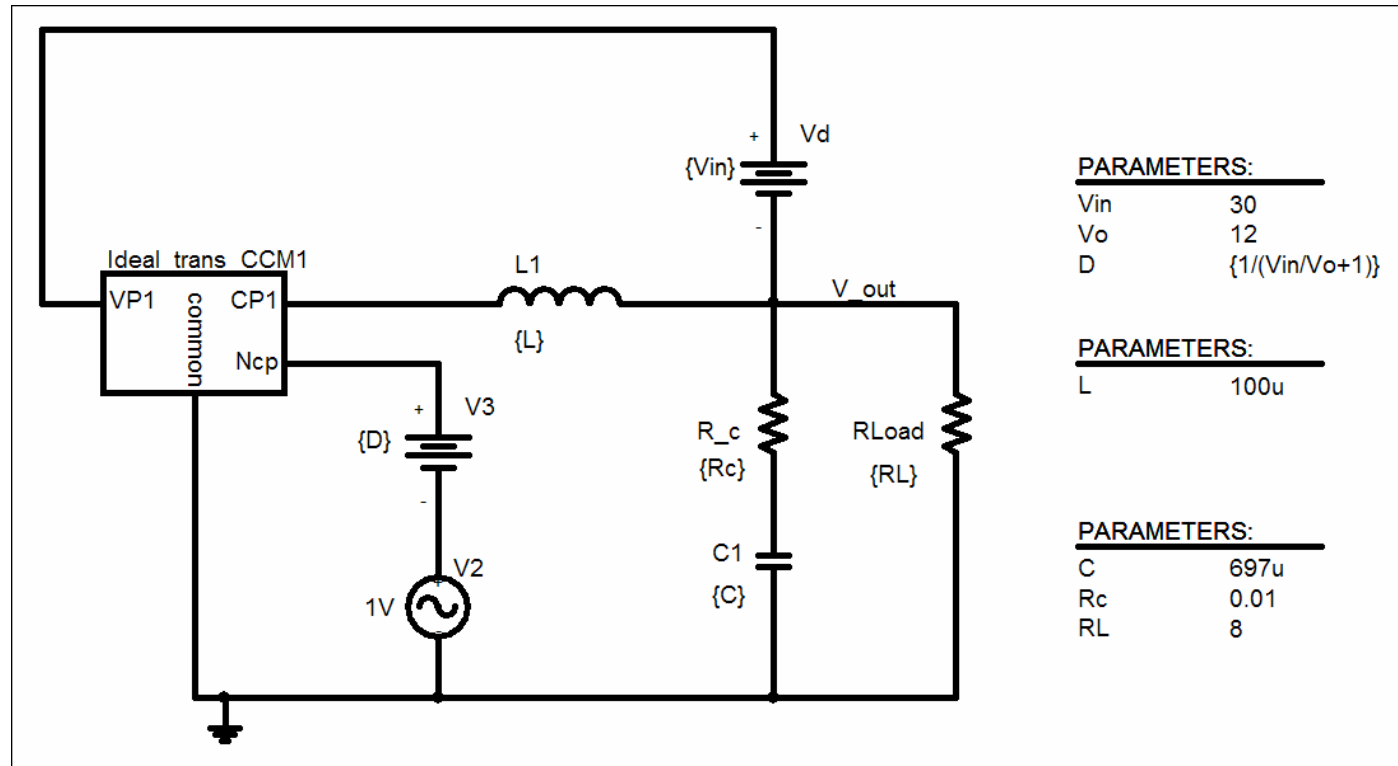


Figure 4-17 PSpice circuit for the Buck-Boost converter.


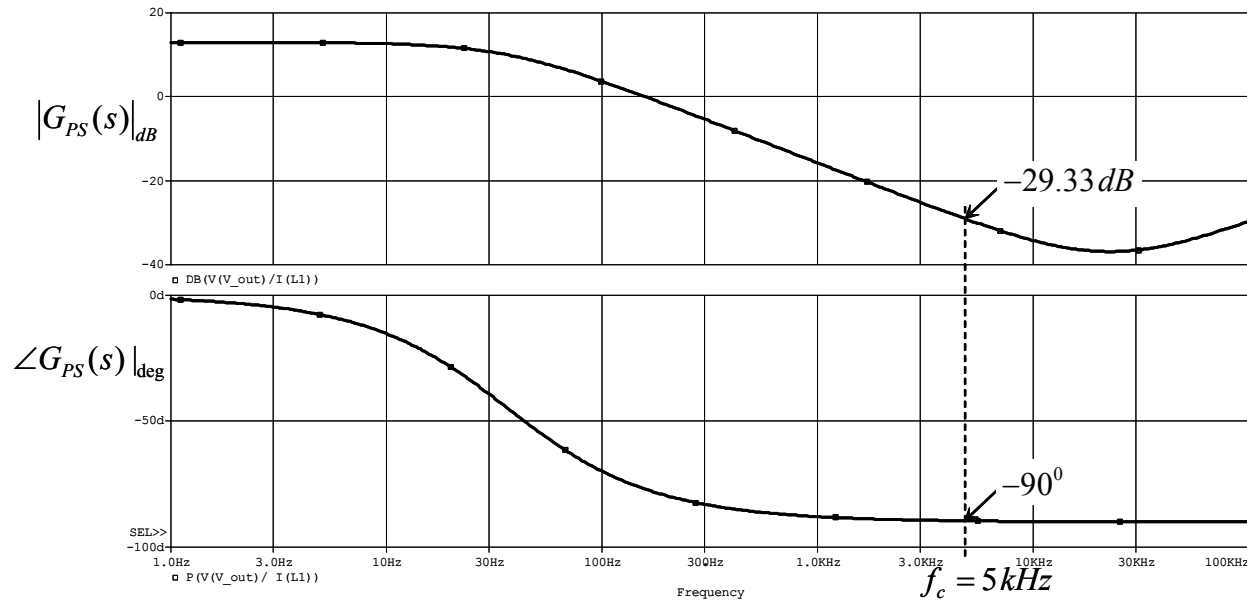



Figure 4-18 Bode plot of  $\tilde{v}_o / \tilde{i}_L$ .

As shown in Fig. 4-18, the phase angle of the power-stage transfer function levels off at approximately  $-90^\circ$  at  $\sim 1kHz$ . The crossover frequency is chosen to be  $f_c = 5kHz$ , at which in Fig. 4-18,  $\angle G_{PS}(s)|_{f_c} \approx -90^\circ$ . As explained in the Appendix on the accompanying CD, the power-stage transfer function  $\tilde{v}_o(s)/\tilde{i}_L(s)$  of Buck-Boost converters contains a right-half-plane zero in CCM. The crossover frequency is chosen well below the frequency of the right-half-plane zero for reasons discussed in the Appendix.
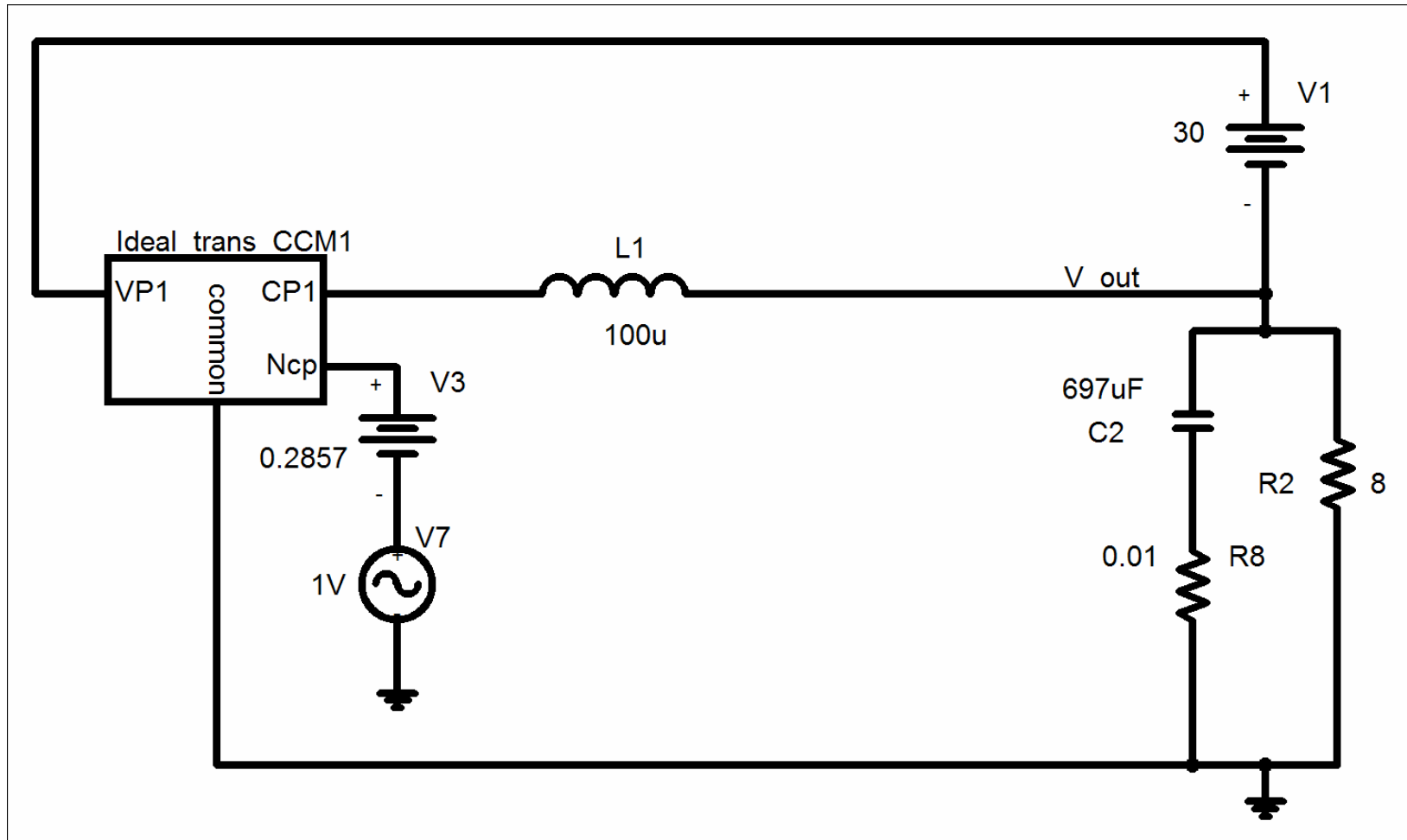
# PSpice Modeling: C:\FirstCourse\_PE\_Book03\Buck-Boost\_Freq\_Analysis.sch



# Simulation Results

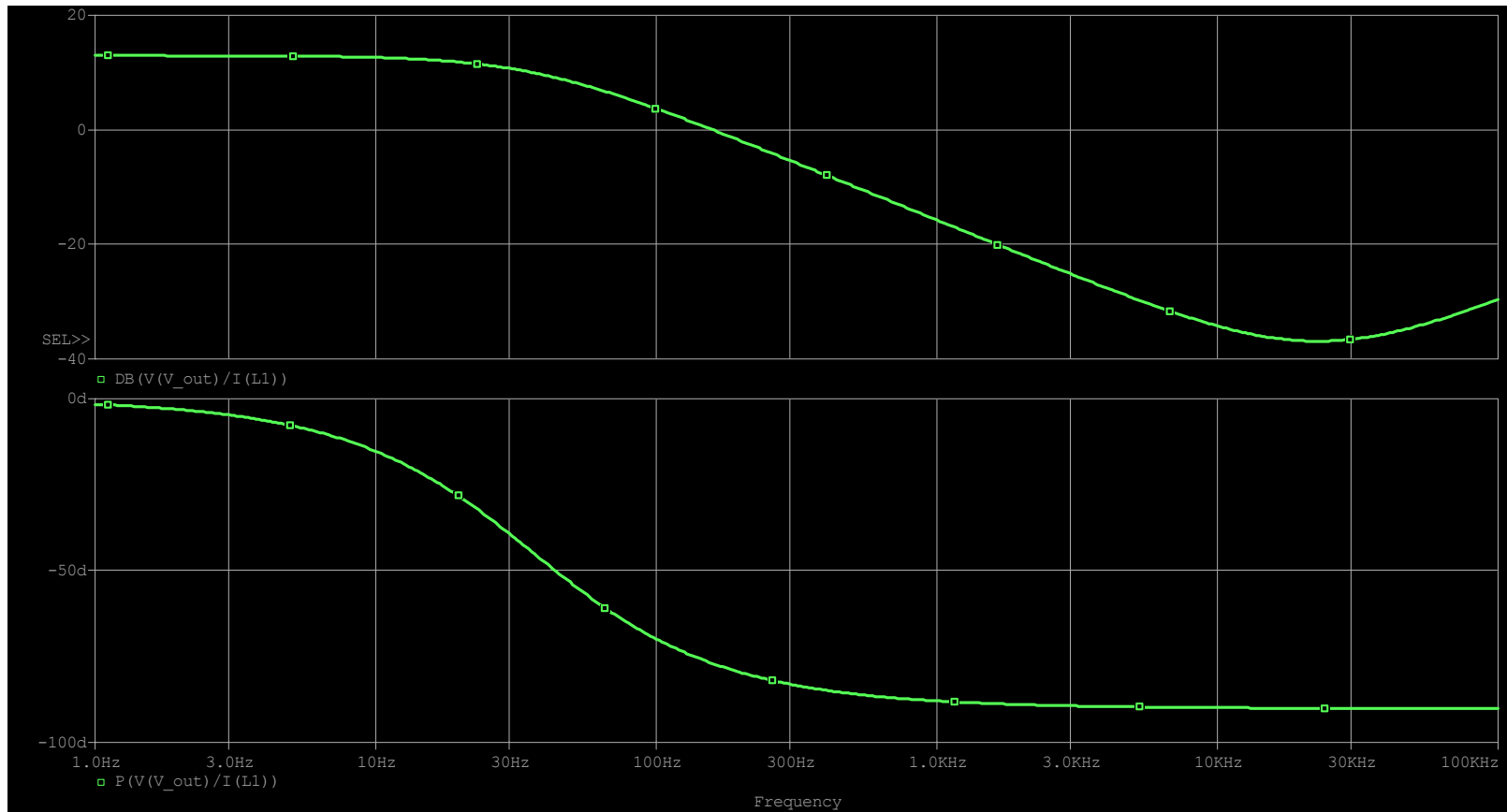

$$G_c(s) = \frac{k_c}{s} \underbrace{\frac{(1 + s/\omega_z)}{(1 + s/\omega_p)}}_{\text{phase-boost}}$$

$$K_{boost} = \tan\left(45^\circ + \frac{\phi_{boost}}{2}\right)$$

$$f_z = \frac{f_c}{K_{boost}} \qquad f_p = K_{boost} f_c$$

$$k_c = \omega_z |G_C(s)|_{f_c}$$

At the crossover frequency, as shown in Fig. 4-18, the power stage transfer function has a gain  $|G_{PS}(s)|_{f_c} = -29.33 \text{ dB}$ . Therefore, at the crossover frequency, by definition, in Fig. 4-16b

$$|G_C(s)|_{f_c} \times |G_{PS}(s)|_{f_c} = 1 \quad (4-37)$$

Hence,

$$|G_C(s)|_{f_c} = 29.33 \text{ dB} = 29.27 \quad (4-38)$$

Using the equations above for  $f_c = 5 \text{ kHz}$ ,  $\phi_{boost} \approx 60^\circ$ , and  $|G_C(s)|_{f_c} = 29.27$ ,  $K_{boost} = 3.732$  in Eq. 4-32. Therefore, the parameters in the controller transfer function of Eq. 4-31 are calculated as  $f_z = 1340 \text{ Hz}$ ,  $f_p = 18660 \text{ Hz}$ , and  $k_c = 246.4 \times 10^3$ .

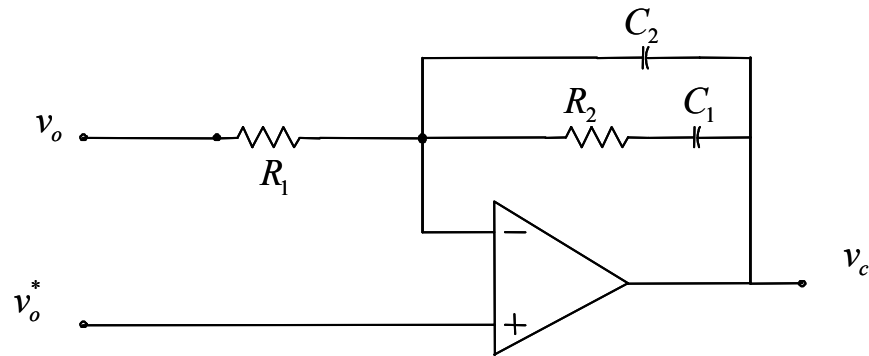


Figure 4-19 Implementation of controller in Eq. 4-32 by an op-amp circuit.

$$R_1 = 10k\Omega$$

$$C_2 = \frac{\omega_z}{\omega_p R_1 k_c} = 30 \text{ pF}$$

$$C_1 = C_2 (\omega_p / \omega_z - 1) = 380 \text{ pF}$$

$$R_2 = 1/(\omega_z C_1) = 315k\Omega$$



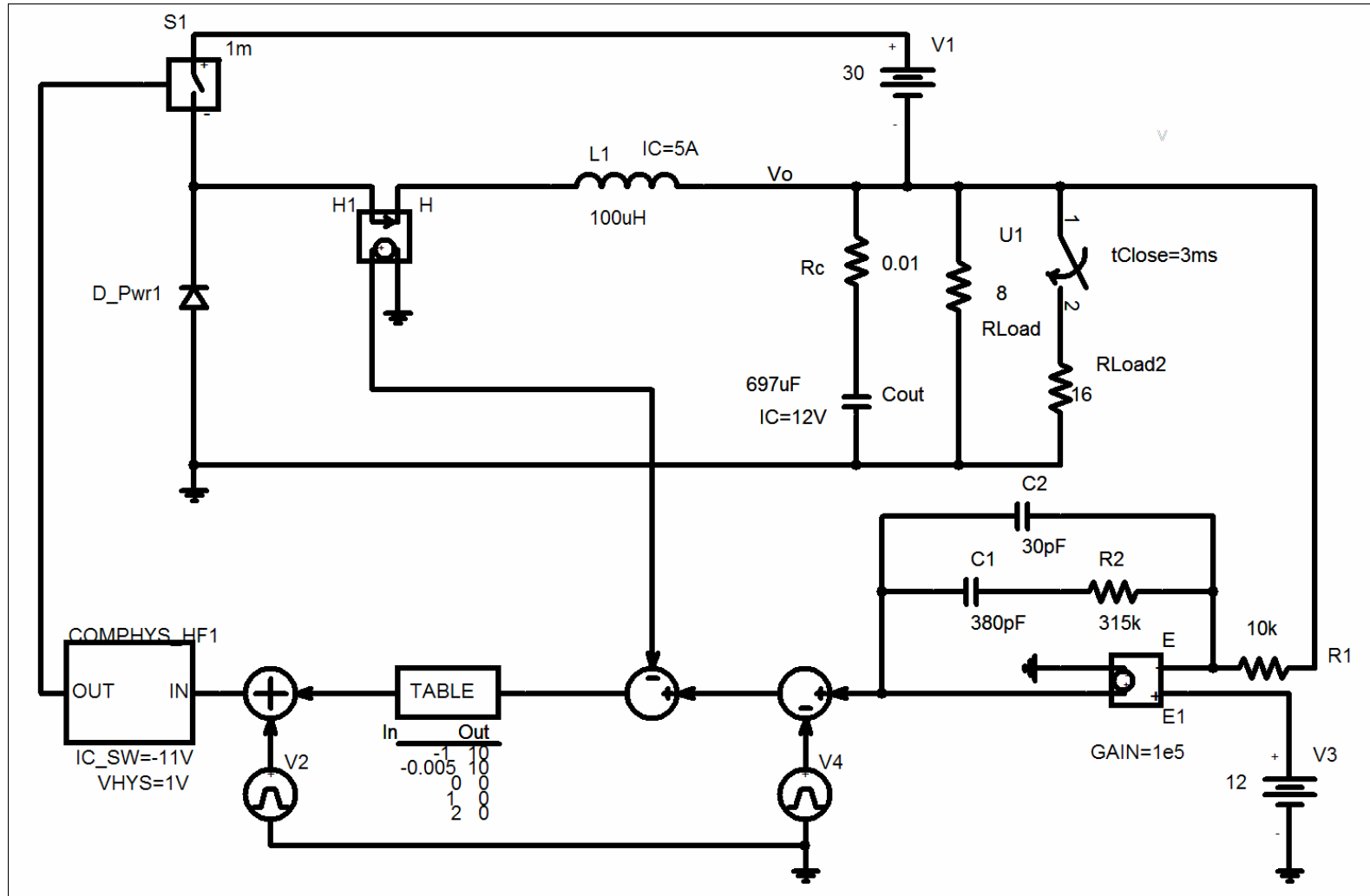


Figure 4-20 PSpice simulation diagram of the peak-current-mode control.



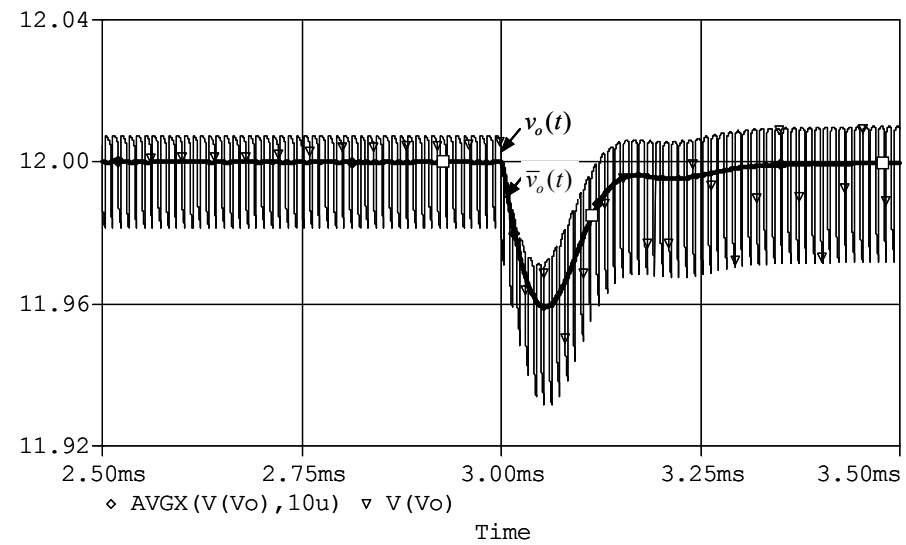


Figure 4-21 Peak current mode control: Output voltage waveform.

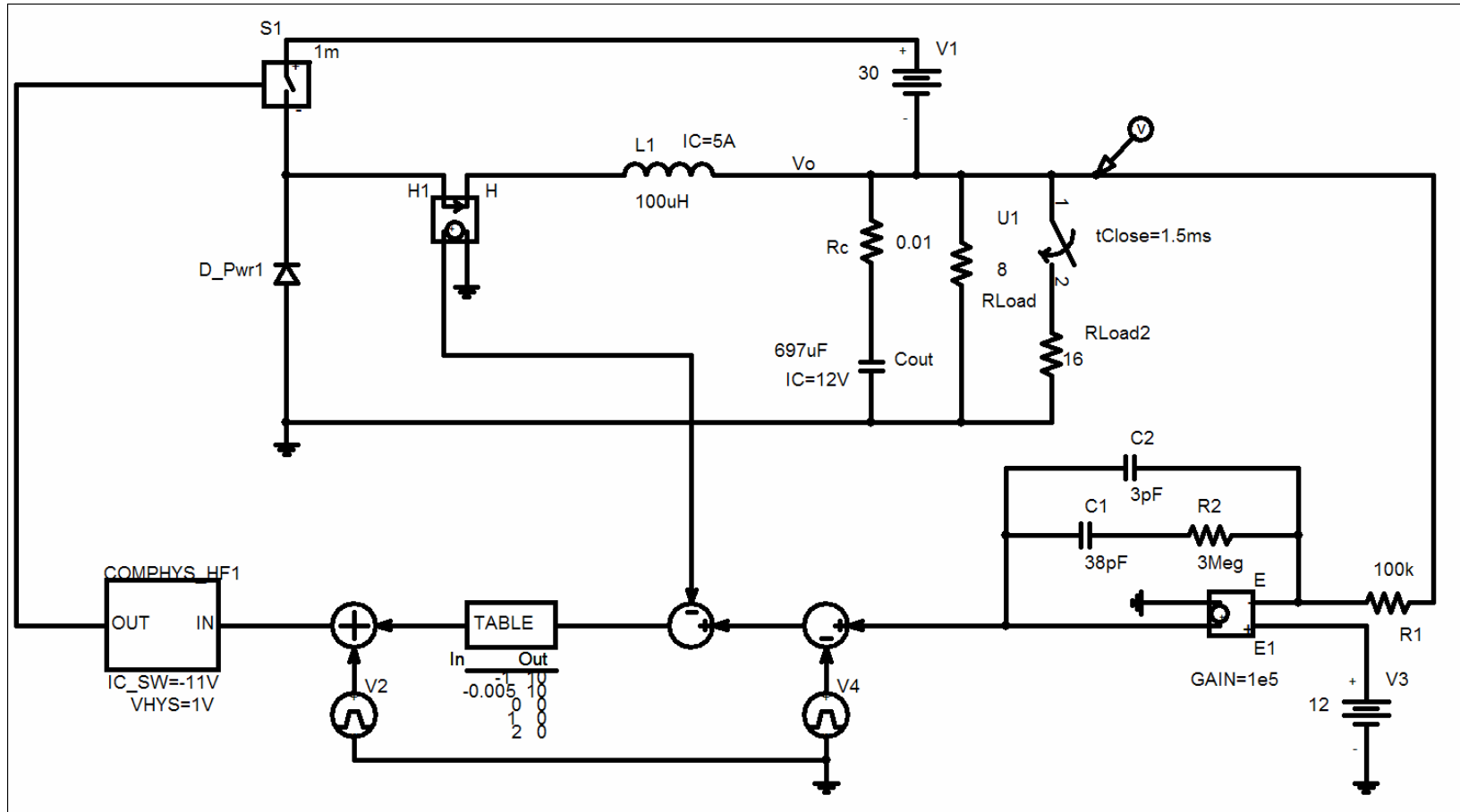
# PSpice Modeling: C:\FirstCourse\_PE\_Book03\bboost\_conv\_curr\_mode\_ctrl\_opamp.sch




## Simulation Results

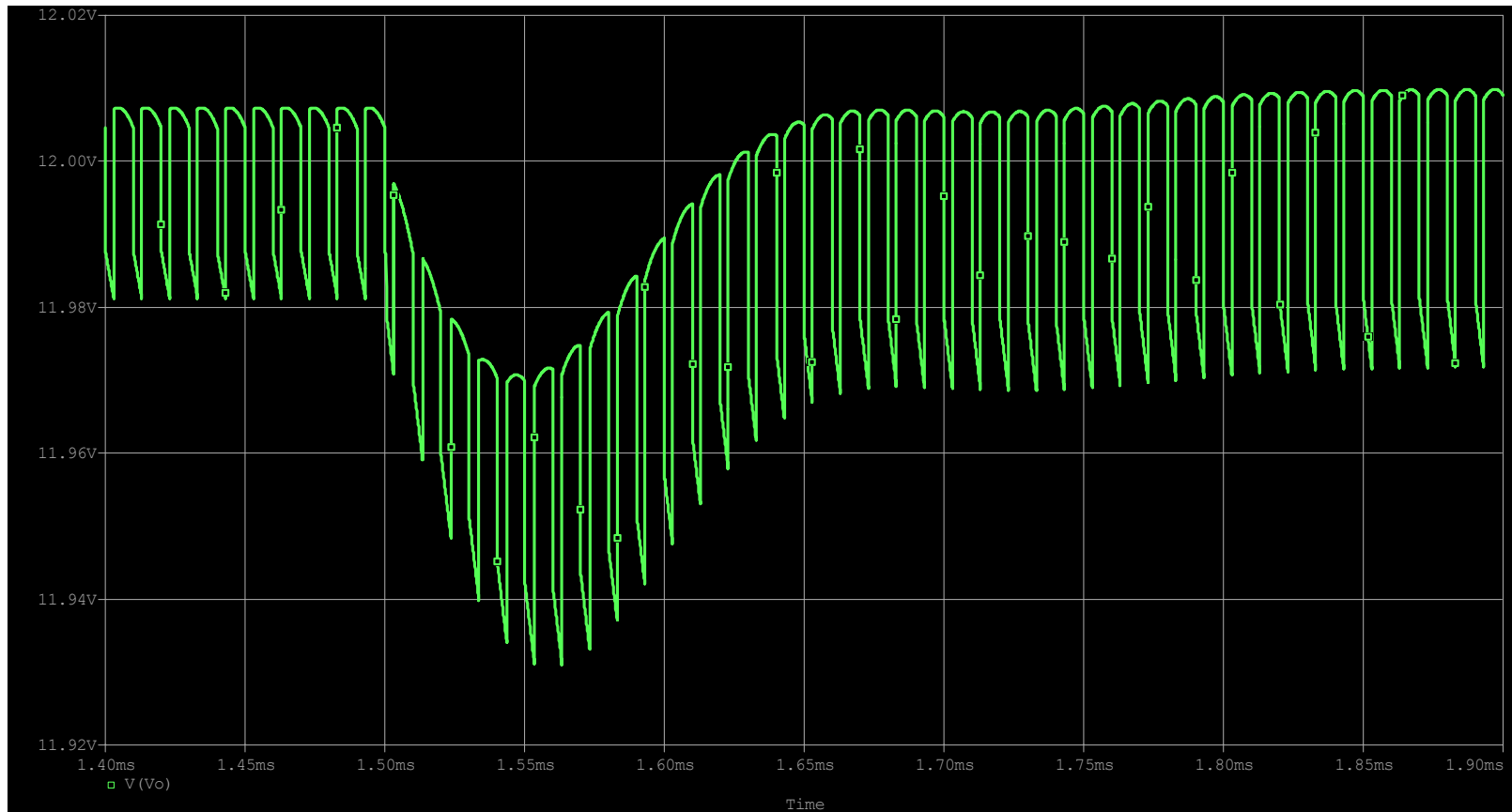

# FEEDBACK CONTROLLER DESIGN IN DCM

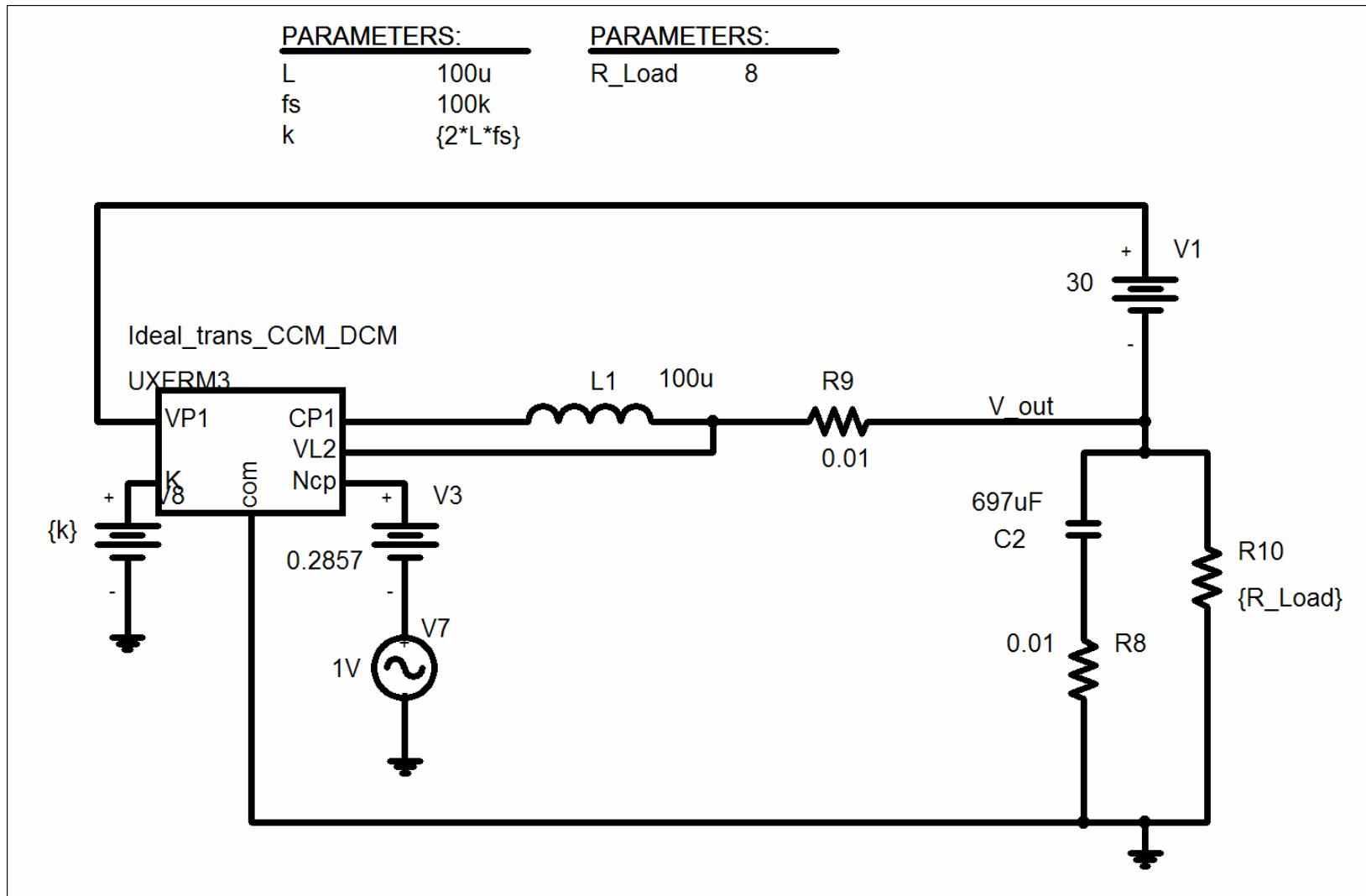
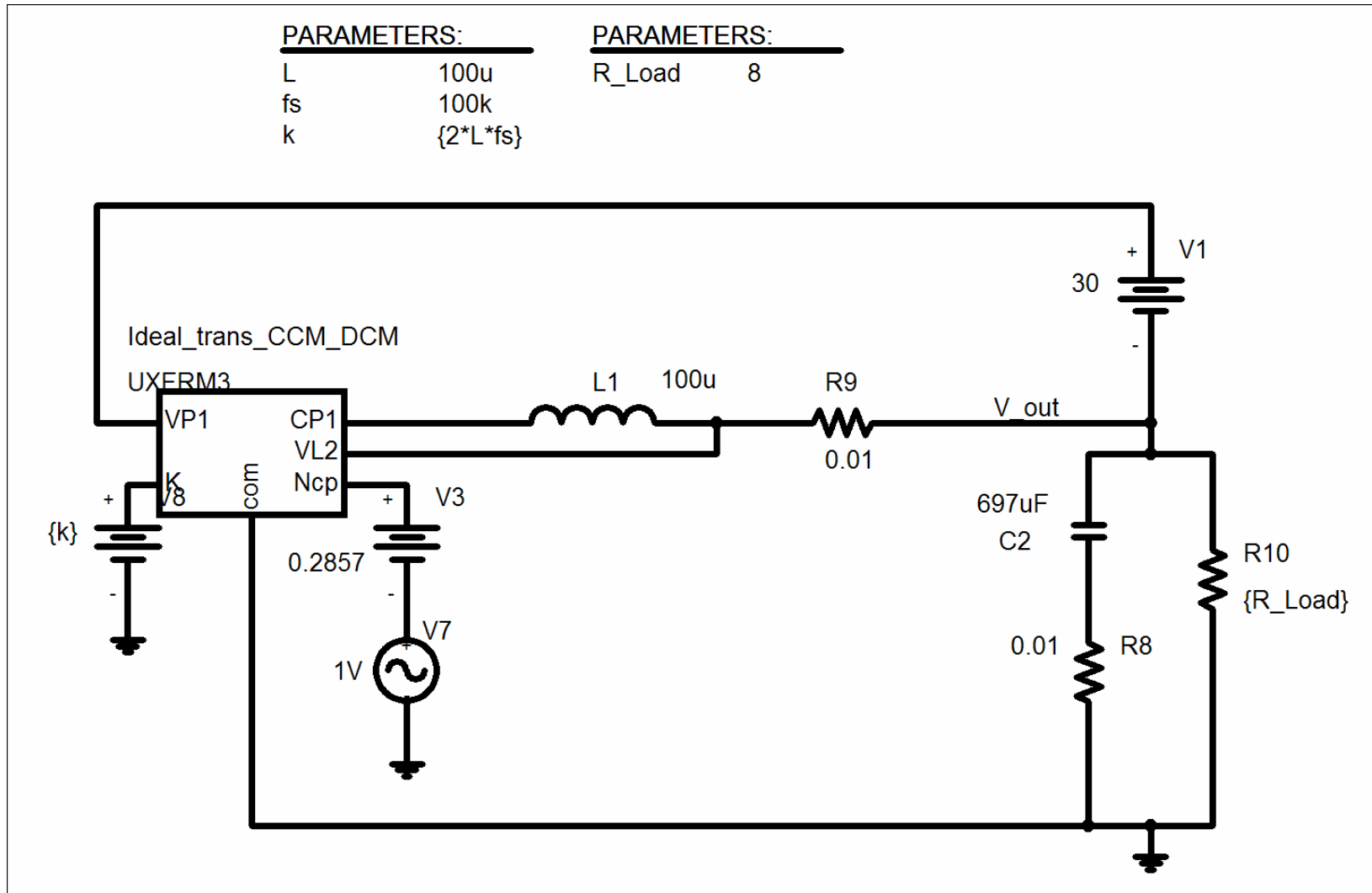
# PSpice Modeling: C:\FirstCourse\_PE\_Book03\Buck-Boost\_CCM\_DCM\_Freq\_Analysis.sch



# Simulation Results

