

Old Exam Questions on Amplifier Design – EE4011 – (this section from EE4005).

4. Discuss the theory and application of *stability circles* in small-signal microwave amplifier design.

A GaAs MESFET has the following noise-figure parameters measured at $V_{ds}=5V$, $I_{ds}=20$ mA with 50Ω resistance at 9 GHz.

$$F_0=1.6\text{dB}, \Gamma_0=0.45\angle 145^\circ, R_n=5\Omega.$$

Determine the centre point and radius of the noise-figure circle for $F_i=3\text{dB}$.

5. Outline the design procedure used when designing a microwave amplifier for maximum gain.

A microwave junction transistor has the following characteristics (at 5 GHz with 50 ohm reference);

$$S_{11} = 0.5 \angle -145^\circ$$

$$S_{12} = 0.05 \angle 25^\circ$$

$$S_{21} = 2.75 \angle 190^\circ$$

$$S_{22} = 0.5 \angle -40^\circ$$

Check the stability of the device and design input and output matching networks for maximum power gain.

(b) A GaAs MESFET has the following noise-figure parameters measured at $V_{ds}=5$ V, $I_{ds}=20$ mA with 50Ω resistance at 8 GHz.

$$F_0 = 1.6 \text{ dB}, \Gamma_0 = 0.45\angle 145^\circ, R_n = 5 \Omega.$$

Determine the centre point and radius of the noise-figure circle for $F_i = 2.5$ dB.

5. Outline the design procedure used when designing a microwave amplifier for maximum gain.

A microwave junction transistor has the following characteristics (at 2.5 GHz with 50 ohm reference);

$$S_{11} = 0.5 \angle -140^\circ$$

$$S_{12} = 0.15 \angle 48^\circ$$

$$S_{21} = 1.74 \angle 32^\circ$$

$$S_{22} = 0.41 \angle -92^\circ$$

Check the stability of the device and design input and output matching networks for maximum power gain.

- (b) A microwave transistor has the following *s*-parameters at 3GHz

$$S_{11} = 0.707 \angle -155^\circ \quad S_{12} = 0$$

$$S_{21} = 4 \angle 180^\circ \quad S_{22} = 0.51 \angle -20^\circ$$

Design a 3GHz amplifier with maximum possible gain.

[10 marks]