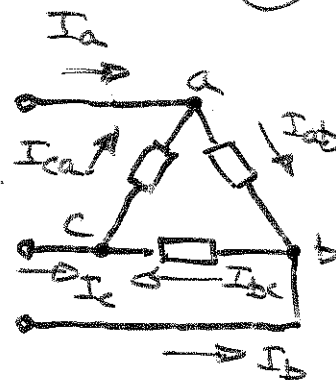


Q.5

PHASE CURRENTS :-

19

$$\begin{bmatrix} I_{ab} \\ I_{bc} \\ I_{ca} \end{bmatrix} = \begin{bmatrix} 10 \angle 0^\circ \\ 20 \angle -90^\circ \\ 15 \angle 90^\circ \end{bmatrix} \text{ A}$$



THE SEQUENCE COMPONENTS OF THE PHASE CURRENTS ARE

$$\begin{bmatrix} I_{ph0} \\ I_{ph1} \\ I_{ph2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} I_{ab} \\ I_{bc} \\ I_{ca} \end{bmatrix}$$

$$= \begin{bmatrix} 3.73 \angle -26.6^\circ \\ 13.46 \angle 3.5^\circ \\ 6.82 \angle 172.9^\circ \end{bmatrix} \text{ A} *$$

THE LINE CURRENTS ARE

$$I_a = I_{ab} - I_{ca} = 18.03 \angle -56.3^\circ \text{ A}$$

$$I_b = I_{bc} - I_{ab} = 22.36 \angle -116.5^\circ \text{ A}$$

$$I_c = I_{ca} - I_{bc} = 35.00 \angle 90.0^\circ \text{ A}$$

Q.6 (contd.)

(20)

THE SEQUENCE COMPONENTS OF THE LINE CURRENTS ARE

$$\begin{bmatrix} I_{L0} \\ I_{L1} \\ I_{L2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}$$

$$= \begin{bmatrix} 0 \\ 23.32 \angle -26.5^\circ \\ 11.82 \angle -157.0^\circ \end{bmatrix} \text{ A} \times$$

NOTE THAT


$$I_{L0} = 0 \quad I_{Ph0}$$

$$I_{L1} = \sqrt{3} e^{-j30^\circ} I_{Ph1}$$

$$I_{L2} = \sqrt{3} e^{j30^\circ} I_{Ph2}$$

SYMMETRICAL COMPONENTS II

①

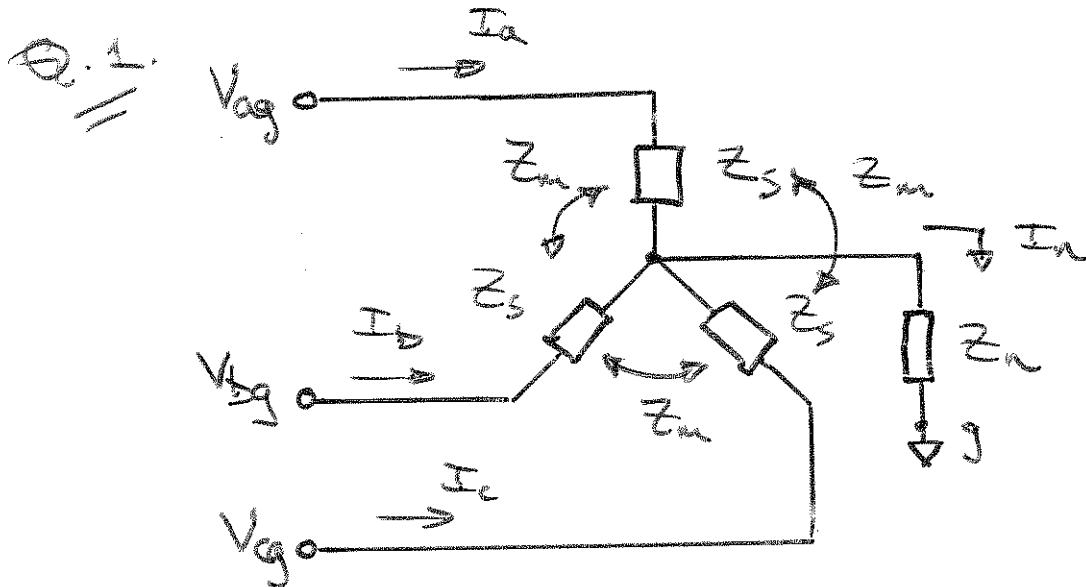

BY K.V.L. APPLIED TO THE THREE PHASES

$$V_{ag} = I_a Z_s + I_b Z_m + I_c Z_m + I_n Z_n$$

$$V_{bg} = I_a Z_m + I_b Z_s + I_c Z_m + I_n Z_n$$

$$V_{cg} = I_a Z_m + I_b Z_m + I_c Z_s + I_n Z_n$$

BUT SINCE $I_n = I_a + I_b + I_c$ BY K.C.L. APPLIED TO THE STAR POINT, WE GET

$$V_{ag} = I_a (Z_s + Z_n) + I_b (Z_m + Z_n) + I_c (Z_m + Z_n)$$

$$V_{bg} = I_a (Z_m + Z_n) + I_b (Z_s + Z_n) + I_c (Z_m + Z_n)$$

$$V_{cg} = I_a (Z_m + Z_n) + I_b (Z_m + Z_n) + I_c (Z_s + Z_n)$$

IN MATRIX FORM

$$\bar{V}_p = \bar{Z}_p \bar{I}_p$$

Q. 1. (contd.)
WHERE

(2)

$$\bar{V}_p = \begin{bmatrix} V_{ag} \\ V_{bg} \\ V_{cg} \end{bmatrix} \quad \bar{I}_p = \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}$$

AND

$$\bar{Z}_p = \begin{bmatrix} (Z_s + Z_n) & (Z_m + Z_n) & (Z_m + Z_n) \\ (Z_m + Z_n) & (Z_s + Z_n) & (Z_m + Z_n) \\ (Z_m + Z_n) & (Z_m + Z_n) & (Z_s + Z_n) \end{bmatrix}$$

TRANSFORMING TO THE SEQUENCE DOMAIN


$$\bar{A} \bar{V}_s = \bar{Z}_p \bar{A} \bar{I}_s$$

$$\Rightarrow \bar{V}_s = (\bar{A}^{-1} \bar{Z}_p \bar{A}) \bar{I}_s \\ = \bar{Z}_s \bar{I}_s$$

HENCE, SHOW THAT

$$\bar{Z}_s = \begin{bmatrix} (\bar{Z}_s + 2\bar{Z}_m + 3\bar{Z}_n) & 0 & 0 \\ 0 & (\bar{Z}_s - \bar{Z}_m) & 0 \\ 0 & 0 & (\bar{Z}_s - \bar{Z}_m) \end{bmatrix}$$

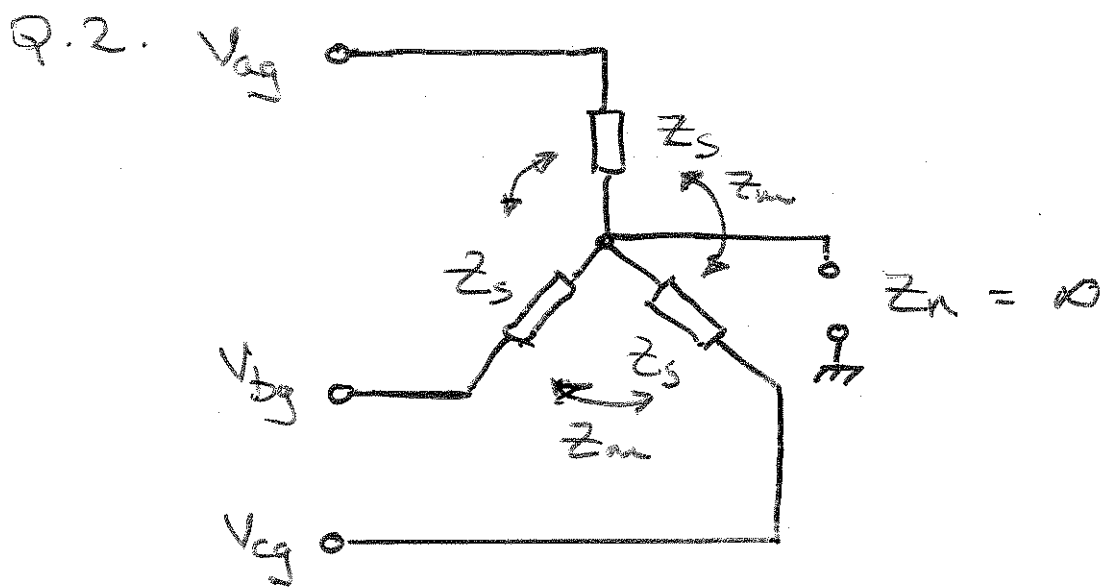NOTE THAT Z_n APPEARS ONLY IN THE ZERO SEQUENCE NETWORK.



$$\bar{Z}_s = j12\Omega$$


$$\bar{Z}_m = j4\Omega.$$

FOR BALANCED INPUT VOLTAGES,

$$V_{ag} = \frac{V_{LL}}{\sqrt{3}} = 230\angle 0^\circ$$

TAKING THE PHASE VOLTAGE AS REFERENCE.

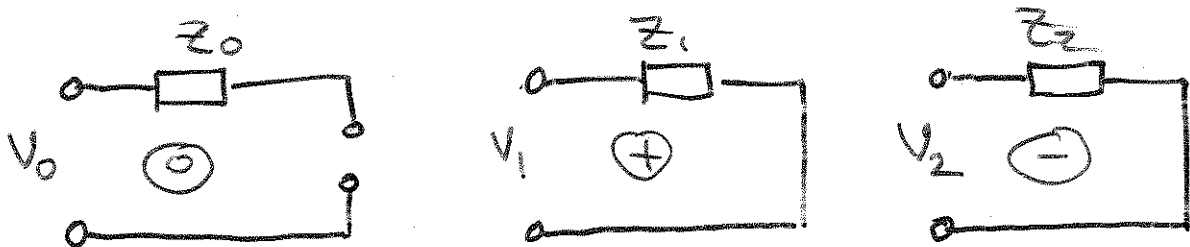FROM PROBLEM 1, THE SEQUENCE IMPEDANCE NETWORKS ARE AS FOLLOWS :-



$$Z_0 = Z_s + 2Z_m + 3Z_n$$

$$Z_1 = Z_s - Z_m$$

$$Z_2 = Z_s - Z_m$$

Q.2 (contd)

④

IN THIS CASE $Z_n \rightarrow \infty$ GIVING AN OPEN CIRCUIT IN THE ZERO SEQUENCE NETWORK.

SINCE THE INPUT SOURCE VOLTAGE IS BALANCED

$$V_1 = V_{ag} = 230 \angle 0^\circ \text{ V}$$

$$V_2 = 0 \text{ V}$$

$$V_0 = 0 \text{ V}$$

Now, $Z_s - Z_m = j12 - j4 = j8 \Omega$

HENCE, THE SEQUENCE CURRENTS ARE

$$I_0 = 0$$

$$I_1 = \frac{230}{j8} = -j28.75 \text{ A}$$


$$I_2 = 0$$

THUS, THE ACTUAL CURRENTS FORM A BALANCED THREE-PHASE SET

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 28.75 \angle -90^\circ \\ 28.75 \angle -210^\circ \\ 28.75 \angle 30^\circ \end{bmatrix} \text{ A}$$

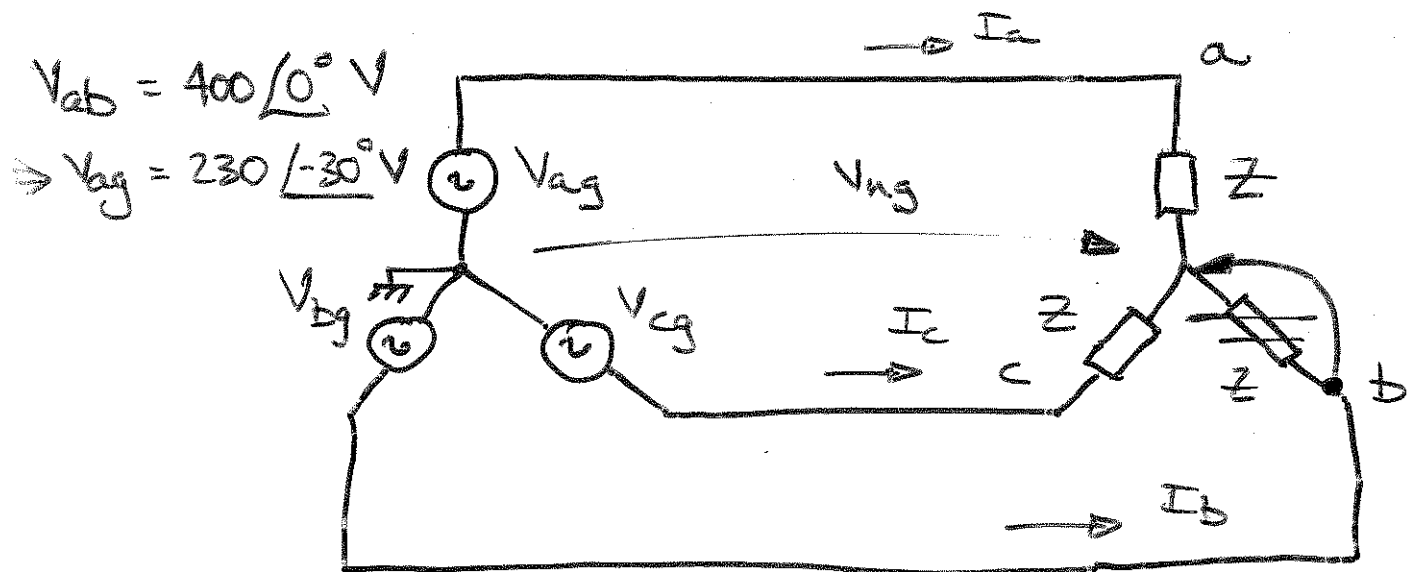Q. 3

THE THREE-PHASE SYSTEM IS AS SHOWN BELOW. (5)



USING KVL WE GET IN MATRIX FORM

$$\begin{bmatrix} V_{ag} \\ V_{bg} \\ V_{cg} \end{bmatrix} = \begin{bmatrix} Z & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & Z \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} + \begin{bmatrix} V_{ng} \\ V_{ng} \\ V_{ng} \end{bmatrix}$$

TRANSFORMING TO THE SEQUENCE DOMAIN

$$\begin{bmatrix} 0 \\ 230 \angle -30^\circ \\ 0 \end{bmatrix} = \begin{bmatrix} Z_{00} & Z_{01} & Z_{02} \\ Z_{10} & Z_{11} & Z_{12} \\ Z_{20} & Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_0 \\ I_1 \\ I_2 \end{bmatrix} + \begin{bmatrix} V_{ng} \\ 0 \\ 0 \end{bmatrix}$$

SINCE $I_n = 3I_0 = 0$ THEN $I_0 = 0$
 AND WE CAN SOLVE FOR I_1 AND I_2
 FROM THE 2×2 MATRIX EQUATION

$$\begin{bmatrix} 230 \angle -30^\circ \\ 0 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

SO THAT

$$\begin{aligned} 230 \angle -30^\circ &= z_{11} I_1 + z_{12} I_2 \\ 0 &= z_{21} I_1 + z_{22} I_2 \end{aligned}$$

$$\Rightarrow I_2 = - \frac{z_{21}}{z_{22}} I_1$$

AND SO

$$230 \angle -30^\circ = \left[z_{11} - z_{12} \left(\frac{z_{21}}{z_{22}} \right) \right] I_1$$

$$\Rightarrow I_1 = \frac{230 \angle -30^\circ}{z_{11} - \left(\frac{z_{21}}{z_{22}} \right) z_{12}}$$

THE SEQUENCE IMPEDANCE MATRIX IS GIVEN AS USUAL BY

$$\bar{Z}_S = \bar{A}^{-1} \bar{Z}_p \bar{A}$$

WHERE

$$\bar{Z}_p = \begin{bmatrix} z & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & z \end{bmatrix}$$

Q.3

(7)

HENCE

$$Z_S = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} Z & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & Z \end{bmatrix} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix}$$

$$= \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} Z & Z & Z \\ 0 & 0 & 0 \\ Z & aZ & a^2Z \end{bmatrix}$$

$$= \frac{1}{3} \begin{bmatrix} 2Z & Z+aZ & Z+a^2Z \\ Z+a^2Z & 2Z & Z+aZ \\ Z+aZ & Z+a^2Z & 2Z \end{bmatrix}$$

THUS, USING THE USUAL NOTATION

$$Z_S = \begin{bmatrix} Z_{00} & Z_{01} & Z_{02} \\ Z_{10} & Z_{11} & Z_{12} \\ Z_{20} & Z_{21} & Z_{22} \end{bmatrix}$$

WE GET

$$\begin{aligned} Z_{11} &= Z_{22} = 2Z = \frac{2}{3}(18 + j6) \\ &= (12 + j4) \Omega \end{aligned}$$

$$Z_{12} = \frac{Z}{3}(1+a) = (1.268 + j6.196) \Omega$$

$$Z_{21} = \frac{Z}{3}(1+a^2) = (4.732 - j4.196) \Omega$$

Q.3.

(8)

HENCE, FROM ABOVE

$$I_1 = \frac{230 \angle -30^\circ}{Z_{11} - Z_{12} \left(\frac{Z_{21}}{Z_{22}} \right)} = 24.3 \angle -48.4^\circ \text{ A}$$

$$I_2 = - \left(\frac{Z_{21}}{Z_{22}} \right) I_1 = 12.2 \angle 71.6^\circ \text{ A}$$

AND SO

$$\begin{aligned} I_a &= I_0 + I_1 + I_2 \\ &= 21.1 \angle -18.4^\circ \text{ A} \end{aligned}$$


ALTERNATIVE METHOD!

LINE VOLTAGE V_{ab} IS CONNECTED DIRECTLY ACROSS THE IMPEDANCE IN PHASE a SO THAT

$$\begin{aligned} I_a &= \frac{V_{ab}}{Z} \\ &= \frac{400 \angle 0}{18 + j6} \\ &= 21.1 \angle -18.4^\circ \text{ A} \end{aligned}$$

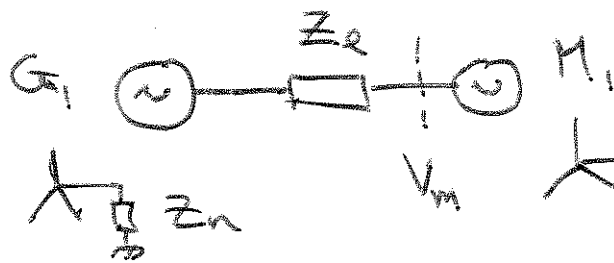Q.4.




$$\begin{aligned} Z_{0g} &= j5 \Omega \\ Z_{1g} &= j15 \Omega \\ Z_{2g} &= j10 \Omega \\ Z_{ng} &= j5 \Omega \end{aligned}$$



$$\begin{aligned} Z_{0m} &= j5 \Omega \\ Z_{1m} &= j15 \Omega \\ Z_{2m} &= j10 \Omega \\ Z_{nm} &= j5 \Omega \end{aligned}$$

$$Z_e = 0.5 \angle 80^\circ \Omega$$

THE SEQUENCE NETWORKS ARE AS FOLLOWS

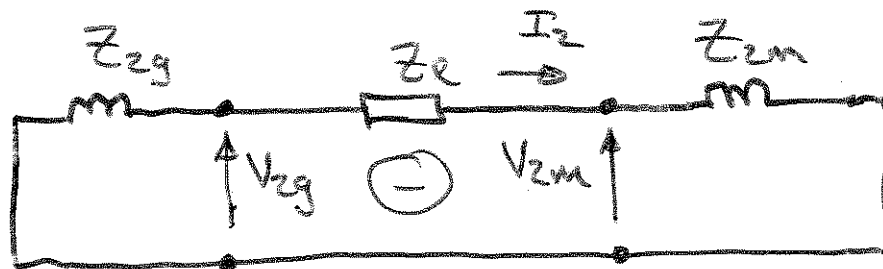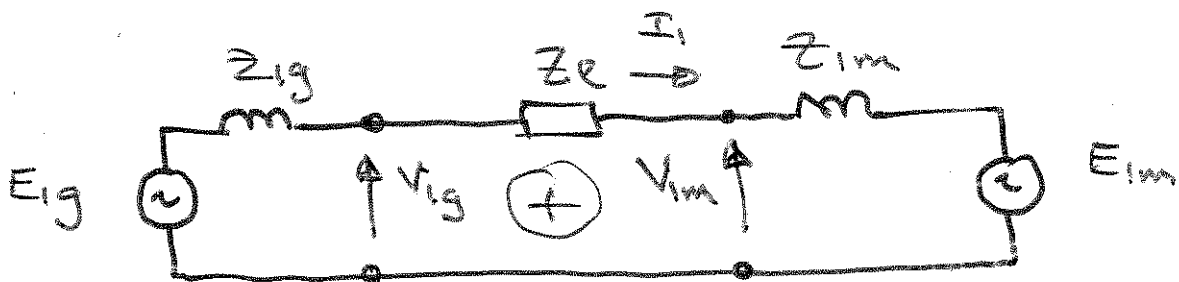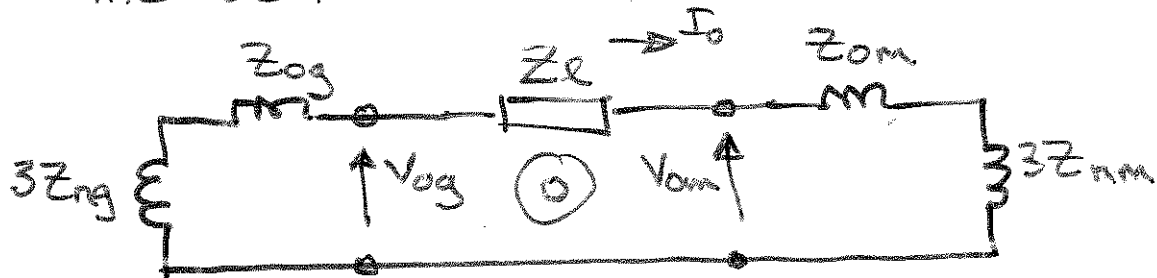

Now

$$P = 10 \text{ kW}$$

$$\text{Pf} = 0.8 \text{ leading}$$

$$\Rightarrow S = \frac{P}{\text{Pf}} = 12.5 \text{ kVA}$$

$$\Rightarrow Q = \sqrt{S^2 - P^2} = 7.5 \text{ kVAR}$$

Q.4. (contd) $V_{lm} = \frac{400}{\sqrt{3}} \angle 0^\circ$

$$= 230 \angle 0^\circ$$

$$S = P - jQ = 3VI^*$$

$$\Rightarrow I = \left(\frac{P - jQ}{3V} \right)^*$$

$$= 18.1 \angle +36.87^\circ \text{ A}$$

SINCE THE VOLTAGES ARE BALANCED AND THE MACHINES AND THE TRANSMISSION LINE ARE SYMMETRICAL LOADS,

$$I_0 = 0$$

$$I_1 = 18.1 \angle +36.87^\circ \text{ A}$$

$$I_2 = 0$$

SO THAT

$$V_{lg} = V_{lm} + Z_L I_1$$

$$\begin{aligned} \Rightarrow V_{lg} &= 230 \angle 0^\circ + (0.5 \angle 80^\circ)(18.1 \angle +36.87^\circ) \\ &= 224.9 \angle 1.89^\circ \text{ V.} \end{aligned}$$

$$\Rightarrow V_{lgLL} = 389.6 \text{ V.}$$