

$$y_{11} = \left. \frac{i_1}{v_1} \right|_{v_2=0} \quad y_{21} = \left. \frac{i_2}{v_1} \right|_{v_2=0} \quad y_{12} = \left. \frac{i_1}{v_2} \right|_{v_1=0} \quad y_{22} = \left. \frac{i_2}{v_2} \right|_{v_1=0}$$

Applying the y-parameter definitions to the above circuit and performing the circuit analysis under the appropriate conditions gives:

$$y_{11} = \frac{1}{r_\pi} + j\omega(c_\pi + c_\mu)$$

$$y_{12} = -j\omega c_\mu$$

$$y_{21} = g_m - j\omega c_\mu$$

$$y_{22} = \frac{1}{r_o} + j\omega(c_s + c_\mu)$$

Question 1(a) continued

The equations on the previous page have to be manipulated to give the small signal-element values as follows:

$$g_m = \mathbf{Re}(y_{21}) = 0.15S$$

$$r_\pi = \frac{1}{\mathbf{Re}(y_{11})} = 250\Omega$$

$$r_o = \frac{1}{\mathbf{Re}(y_{22})} = 1.5k\Omega$$

$$c_\mu = \frac{-\mathbf{Im}(y_{12})}{2\pi f} = 0.7pF$$

$$c_\pi = \frac{\mathbf{Im}(y_{11})}{2\pi f} - c_\mu = 4.5pF$$

$$c_s = \frac{\mathbf{Im}(y_{22})}{2\pi f} - c_\mu = 0.3pF$$

Question 1(b) 6 marks

$$V_T = \frac{kT}{q} = 25.9mV$$


$$(i) \quad I_C = g_m V_T = 3.9mA$$

$$(ii) \quad V_A = r_o I_C = 5.82V$$

$$(iii) \quad \beta = g_m r_\pi = 37.5$$

$$(iv) \quad f_T = \frac{g_m}{2\pi(c_\pi + c_\mu)} = 4.59GHz$$

Question 2(a) 8 marks

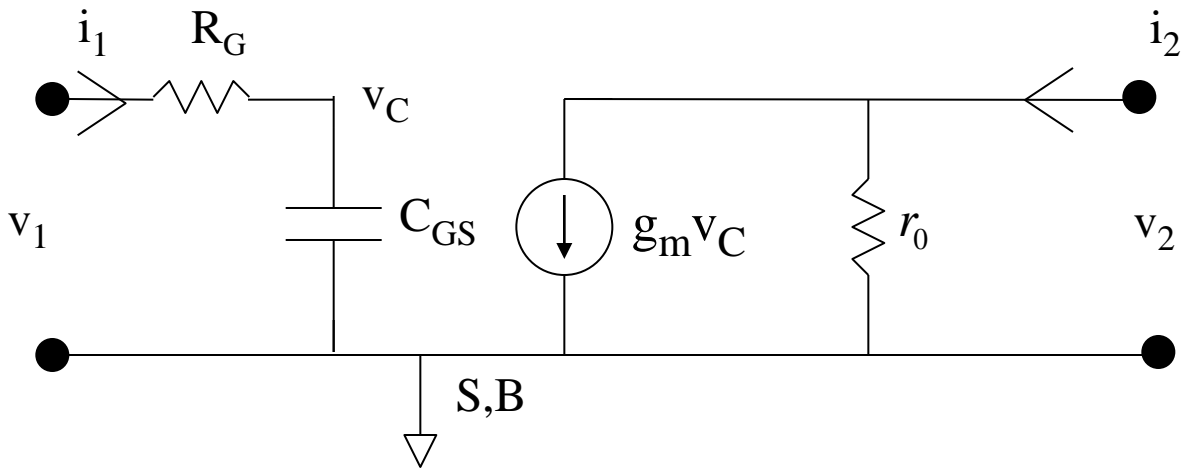

Applying the z-parameter definitions to the above circuit and performing the circuit analysis under the appropriate conditions gives:

$$z_{11} = \left. \frac{v_1}{i_1} \right|_{i_2=0} = R_G + \frac{1}{j\omega C_{GS}}$$

$$z_{21} = \left. \frac{v_2}{i_1} \right|_{i_2=0} = -\frac{g_m r_o}{j\omega C_{GS}}$$

$$z_{12} = \left. \frac{v_1}{i_2} \right|_{i_1=0} = 0$$

$$z_{22} = \left. \frac{v_2}{i_2} \right|_{i_1=0} = r_o$$

Question 2(b) 8 marks

$$C'_{ox} = \frac{\epsilon_{ox}}{T_{ox}} \quad V_{DS} > (V_{GS} - V_{TH}) \text{ so MOSFET in saturation}$$

For a MOSFET in saturation:

$$I_{DS} = \frac{1}{2} \frac{W}{L} \mu C'_{ox} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$g_m = \frac{W}{L} \mu C'_{ox} (V_{GS} - V_{TH}) = \sqrt{2 \frac{W}{L} \mu C'_{ox} I_{DS}}$$

$$g_{ds} = \frac{1}{r_o} = \frac{1}{2} \frac{W}{L} \mu C'_{ox} (V_{GS} - V_{TH})^2 \lambda$$

$$C_{GS} = \frac{2}{3} W L C'_{ox}$$

Doing the calculations and inserting these values into the previous formulas for the z-parameters at 1GHz gives:

$$z_{11} = 987.7 \angle -89.4^\circ \quad z_{12} = 0 \quad z_{21} = 13929 \angle 90^\circ \quad z_{22} = 100 \angle 0^\circ$$

(c) 4 marks

Gate resistance with parallel layout and gate contacted at both sides.

$$R_{Geff} = \frac{R_G}{4N^2} = \frac{10}{4 \times 25} = 0.1 \Omega$$

Question 3


3(a) 3 marks

$$\text{Noise Figure, } NF = 10 \log_{10} \left(\frac{SNR_{in}}{SNR_{out}} \right) \quad (\text{in dB, } \geq 0)$$

$$SNR_{in} = (\text{signal power in})/(\text{noise power in})$$


$$SNR_{out} = (\text{signal power out})/(\text{noise power out})$$

3(b) 7 marks

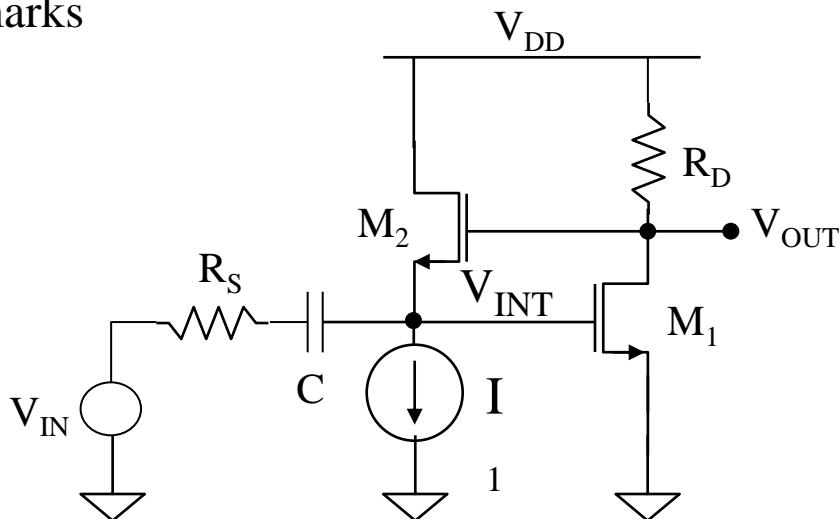

A small-signal analysis has to be performed to determine the voltage gain. For the small-signal analysis the DC power supply can be replaced by an ac ground. The current source is ideal so it can be replaced by an open circuit (i.e. just pretend it isn't there) for small-signal analysis. We are told that the impedance of the capacitor is negligible (for ac signals) so it can be "shorted-out" for the ac analysis. We are told that the MOSFETs can be represented by ideal transconductances so we'll only need to represent the MOSFETs by g_m elements in the small-signal analysis. For these g_m elements the current will flow from source to drain (which for M1 is from the V_{OUT} node to ground and for M2 it is from the V_{DD} node to the V_{INT} node). We also need to know what voltage to use to control each of the transconductances. From looking at the circuit we see that for M1 $V_{GS1} = V_{INT}$ and for M2 $V_{GS2} = V_{OUT} - V_{INT}$. Taking all these considerations together gives the small-signal circuit on the following page.

Question 3(b) continued

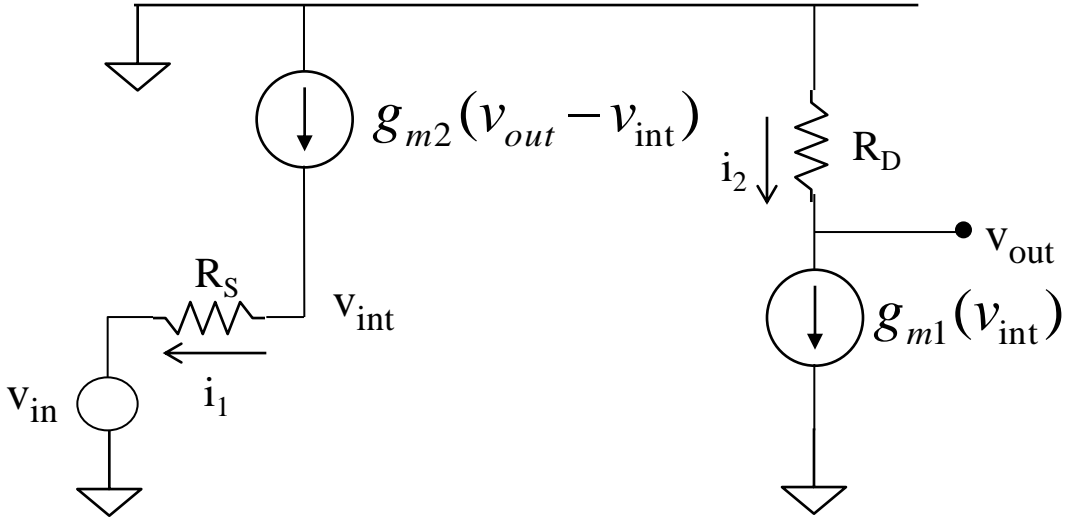

$$i_2 = g_{m1}v_{\text{int}}$$

$$v_{\text{out}} = -i_2 R_D = -g_{m1} R_D v_{\text{int}} \Rightarrow v_{\text{int}} = -\frac{v_{\text{out}}}{g_{m1} R_D} \quad (A)$$

$$i_1 = \frac{v_{\text{int}} - v_{\text{in}}}{R_S} \quad \text{also} \quad i_1 = g_{m2}(v_{\text{out}} - v_{\text{int}}) \Rightarrow \frac{v_{\text{int}} - v_{\text{in}}}{R_S} = g_{m2}(v_{\text{out}} - v_{\text{int}}) \quad (B)$$

rearrange (B) and substitute v_{int} from (A) :

$$v_{\text{int}} - v_{\text{in}} = g_{m2} R_S (v_{\text{out}} - v_{\text{int}}) \Rightarrow -\frac{v_{\text{out}}}{g_{m1} R_D} - v_{\text{in}} = g_{m2} R_S \left(v_{\text{out}} - \left(-\frac{v_{\text{out}}}{g_{m1} R_D} \right) \right)$$

multiply across by $g_{m1} R_D$ and rearrange to find voltage gain, A :

$$\begin{aligned} -v_{\text{out}} - v_{\text{in}} g_{m1} R_D &= g_{m2} R_S (g_{m1} R_D v_{\text{out}} + v_{\text{out}}) \\ \Rightarrow -v_{\text{in}} g_{m1} R_D &= g_{m2} R_S (g_{m1} R_D v_{\text{out}} + v_{\text{out}}) + v_{\text{out}} = [g_{m2} R_S (g_{m1} R_D + 1) + 1] v_{\text{out}} \\ \Rightarrow A = \frac{v_{\text{out}}}{v_{\text{in}}} &= -\frac{g_{m1} R_D}{1 + g_{m2} R_S (g_{m1} R_D + 1)} \end{aligned}$$

The output voltage and its square (related to power) can then be calculated:

$$v_{\text{out}} = A v_{\text{in}} \Rightarrow v_{\text{out}}^2 = A^2 v_{\text{in}}^2$$

3(c) 10 marks

The thermal noise contributed by is the source resistance R_S is

$$v_{n,in}^2 = 4kTR_S \quad v^2 / Hz$$

The signal to noise ratio at the input in then:


$$SNR_{in} = \frac{v_{in}^2}{v_{n,in}^2} = \frac{v_{in}^2}{4kTR_S}$$

To calculate the SNR at the output, the total noise at the output from both R_S and R_D have to be calculated. The noise from R_S occurs at the input of the amplifier and is gained up by the full gain, A , of the amplifier, just like any other input signal. Therefore, the square noise voltage at the output resulting from the R_S noise can be calculated using the amplifier gain i.e.

$$(v_{n,out}^2)_{RS} = A^2(v_{n,in}^2)_{RS} = A^2 4kTR_S \quad v^2 / Hz$$

To calculate the noise contributed at the output from R_D , a new circuit analysis has to be performed. This is a small-signal analysis where the only signal source will be thermal noise (current or voltage) coming from R_D . All other signal sources (including v_{in}) will be set to 0 for this analysis. For this analysis it is more convenient to represent the thermal noise coming from R_D as a current source instead of a voltage source. Taking all these considerations into account gives the small-signal circuit on the next page.

Question 3(c) continued

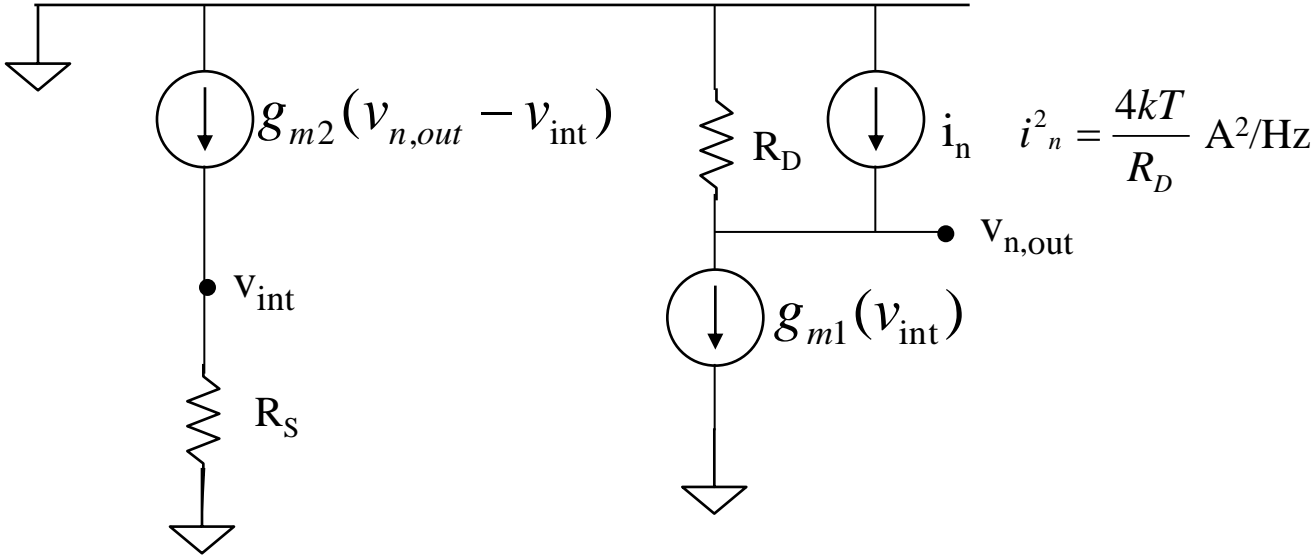

Working through the small-signal analysis of this circuit gives the output voltage noise caused by i_n as follows R_D as:

$$v_{n,out} = i_n \frac{R_D(1 + g_{m2}R_S)}{(1 + g_{m2}R_S + g_{m1}R_Dg_{m2}R_S)}$$

The square noise voltage is then:

$$(v_{n,out})_{RD}^2 = (i_n)_{RD}^2 \frac{R_D^2(1 + g_{m2}R_S)^2}{(1 + g_{m2}R_S + g_{m1}R_Dg_{m2}R_S)^2} = \frac{4kTR_D(1 + g_{m2}R_S)^2}{(1 + g_{m2}R_S + g_{m1}R_Dg_{m2}R_S)^2}$$

The total o/p noise is then

$$v_{n,out}^2 = (v_{n,out}^2)_{RS} + (v_{n,out}^2)_{RD}$$

The signal to noise ratio at the output can then be calculated and the noise factor:

$$SNR_{out} = \frac{v_{out}^2}{v_{n,out}^2} \quad F = \frac{SNR_{in}}{SNR_{out}}$$

The final expressions are cumbersome so the formulas determined up to this point are sufficient

Question 4

$$s_{11} = 0.46 \angle -143^\circ \quad s_{12} = 0.01 \angle 98^\circ \quad s_{21} = 1.70 \angle 59^\circ \quad s_{22} = 0.70 \angle -30^\circ$$

$$F_{\min} = 2.5 \text{ dB} \quad \Gamma_{opt} = 0.55 \angle -160^\circ \quad R_N = 5.5 \Omega$$

$$Z_0 = 50 \Omega \quad f = 14 \text{ GHz}$$

(a) (i) 3 marks

For unconditional stability the following conditions are necessary
(K is the Rollet Stability Factor):

$$K > 1 \quad \text{and} \quad |\Delta| < 1$$

$$K = \frac{1 - |s_{11}|^2 - |s_{22}|^2 + |\Delta|^2}{2|s_{12}s_{21}|} \quad \Delta = s_{11}s_{22} - s_{12}s_{21}$$

Putting in the s-parameters into the formulas gives:

$$K = 11.56 \quad \text{and} \quad |\Delta| = 0.31$$

Thus the amplifier will be unconditionally stable.

(a)(ii) 2 marks

$$F_{dB} = 10 \log_{10}(F_{ratio}) \Rightarrow F_{ratio} = 10^{\frac{F_{dB}}{10}}$$

The noise circle for $F_i = 3 \text{ dB}$

$$F_{\min, ratio} = 10^{\frac{2.5}{10}} = 1.778 \quad F_{i, ratio} = 10^{\frac{3}{10}} = 1.995$$

$$N_i = \frac{F_{i, ratio} - F_{\min, ratio}}{4R_N / Z_0} |1 + \Gamma_{opt}|^2 = \frac{1.995 - 1.778}{4 \times 5.5 / 50} |1 + 0.55 \angle -160^\circ|^2 = 0.133$$

$$C_{Fi} = \frac{\Gamma_{opt}}{N_i + 1} = \frac{0.55 \angle -160^\circ}{0.133 + 1} = 0.49 \angle -160^\circ$$

Note: Γ_{OPT} is a complex number in these calculations

$$R_{Fi} = \frac{\sqrt{N_i(N_i + 1 - |\Gamma_{opt}|^2)}}{(N_i + 1)} = \frac{\sqrt{0.133(0.133 + 1 - (0.55)^2)}}{(0.133 + 1)} = 0.29$$

The 3dB noise circle can now be drawn on the Smith Chart.

Question 4

(b) 15 marks

First calculate the maximum unilateral transducer gain:

$$G_{S,\max} \frac{1}{1 - |s_{11}|^2} = \frac{1}{1 - (0.46)^2} = 1.268(\text{ratio}) = 1.03\text{dB}$$

$$G_0 = |s_{21}|^2 = (1.70)^2 = 2.89(\text{ratio}) = 4.61\text{dB}$$

$$G_{L,\max} \frac{1}{1 - |s_{22}|^2} = \frac{1}{1 - (0.70)^2} = 1.961(\text{ratio}) = 2.92\text{dB}$$

$$G_{TU,\max,\text{dB}} = G_{S,\max,\text{dB}} + G_{0,\text{dB}} + G_{L,\max,\text{dB}} = 1.03\text{dB} + 4.61\text{dB} + 2.92\text{dB} = 8.56\text{dB}$$

If there was no constraint on noise, the source reflection coefficient could be set to s_{11}^* and the load reflection coefficient could be set to s_{22}^* and in that case the maximum unilateral transducer gain would be 8.56dB. But it is seen that s_{11}^* is outside the 3dB noise circle and so the noise in that case would be too much. Therefore the input reflection coefficient will have to be moved so that it sits on the 3dB noise circle but this will decrease the source gain term. Some source gain circles will have to be drawn to do the design.

$G_{S,\max} = 1.03\text{dB}$ so draw a source gain circle for $G_S = 0.95\text{dB}$ to start

$$G_{S,\text{dB}} = 10\log_{10}(G_S) \Rightarrow G_S = 10^{\frac{G_{S,\text{dB}}}{10}} = 10^{\frac{0.95}{10}} = 1.245$$

$$g_s = \frac{G_S}{G_{S,\max}} = \frac{1.245}{1.268} = 0.981$$

$$|C_S| = \frac{g_s |s_{11}|}{1 - |s_{11}|^2 (1 - g_s)} = \frac{0.981 \times |0.46|}{1 - |0.46|^2 (1 - 0.981)} = 0.45$$

$$R_S = \frac{\sqrt{1 - g_s} (1 - |s_{11}|^2)}{1 - |s_{11}|^2 (1 - g_s)} = \frac{\sqrt{1 - 0.981} (1 - |0.46|^2)}{1 - |0.46|^2 (1 - 0.981)} = 0.11$$

The centre of this circle is a distance 0.45 along the line joining the centre of the Smith Chart to s_{11}^* and the radius is 0.11 and this can be drawn on the Smith Chart.

Question 4(b) continued

It is seen that the source gain circle for 0.95dB doesn't touch the 3dB noise circle so the noise would still be more than 3dB if the source reflection coefficient was placed on the 0.95dB source gain circle. Therefore the gain has to be reduced again – try a source gain of 0.85dB and draw the circle for this.

$$G_{S,dB} = 10\log_{10}(G_S) \Rightarrow G_S = 10^{\frac{G_{S,dB}}{10}} = 10^{\frac{0.85}{10}} = 1.216$$

$$g_s = \frac{G_S}{G_{S,\max}} = \frac{1.216}{1.268} = 0.959$$

$$|C_S| = \frac{g_s |s_{11}|}{1 - |s_{11}|^2 (1 - g_s)} = \frac{0.959 \times |0.46|}{1 - |0.46|^2 (1 - 0.959)} = 0.44$$

$$R_S = \frac{\sqrt{1 - g_s} (1 - |s_{11}|^2)}{1 - |s_{11}|^2 (1 - g_s)} = \frac{\sqrt{1 - 0.959} (1 - |0.46|^2)}{1 - |0.46|^2 (1 - 0.959)} = 0.16$$

When the source gain circle for 0.85dB is drawn it is seen to touch the 3dB noise circle. Therefore, the source reflection coefficient can be set to the point where the two circles touch – then the source gain will be 0.85dB and the noise figure will be 3dB. Because noise is not influenced by the output reflection coefficient, the load reflection coefficient can be set to s_{22}^* . Therefore, the maximum unilateral transducer gain that can be achieved is:

$$G_{TU,dB} = G_{S,dB} + G_{0,dB} + G_{L,\max,dB} = 0.85dB + 4.61dB + 2.92dB = 8.38dB \approx 8.4dB$$

Now the matching networks can be designed – see the Smith Chart on the next page.

EXAMINATION NUMBER


QUESTION NUMBER

DATE

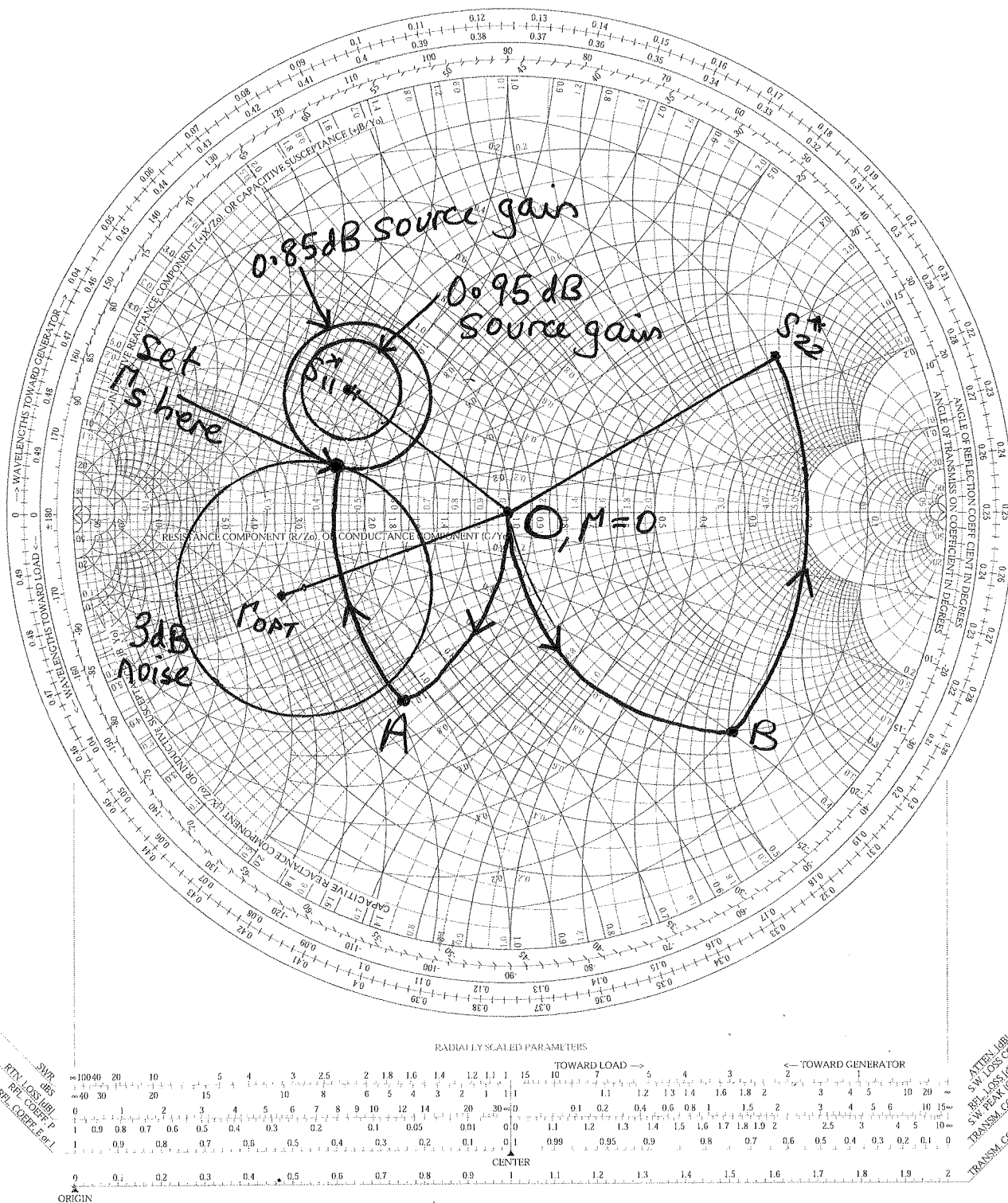Q4 Summer 2010 EE4011

EE4011 RF IC Design

NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES



At the origin of the Smith Chart, O : $x = 0, b = 0$

At point A : $x = -0.5, b = 1.18$

At point B : $x = -2.1, b = 0.4$

At M_s : $x = 0.11, b = -0.6$

At S_{22}^* : $x = +2.55, b = -0.27$

Question 4(b) continued

Input Matching Element Values

Moving from Z_0 ($\Gamma=0$) to point A:

Clockwise on conductance circle – shunt capacitor

$$\begin{array}{l} \text{susceptance at } Z_0: b = 0 \\ \text{susceptance at A: } b = 1.18 \end{array} \quad C = \frac{|\Delta b|}{2\pi f Z_0} = \frac{|1.18|}{2\pi \times 14 \times 10^9 \times 50} = 0.27 \text{ pF}$$

Moving from A to Γ_S :

Clockwise on resistance circle – series inductor

$$\begin{array}{l} \text{reactance at A: } x = -0.5 \\ \text{reactance at } \Gamma_S: x = 0.11 \end{array} \quad L = \frac{Z_0 |\Delta x|}{2\pi f} = \frac{50 \times |0.61|}{2\pi \times 14 \times 10^9} = 0.35 \text{ nH}$$

Output Matching Element Values

Moving from Z_0 ($\Gamma=0$) to point B:

Anti-clockwise on resistance circle – series capacitor

$$\begin{array}{l} \text{reactance at } Z_0: x = 0 \\ \text{reactance at B: } x = -2.1 \end{array} \quad C = \frac{1}{2\pi f |\Delta x| Z_0} = \frac{1}{2\pi \times 14 \times 10^9 \times |-2.1| \times 50} = 0.11 \text{ pF}$$


Moving from B to s_{22}^* :

Anti-clockwise on conductance circle – shunt inductor

$$\begin{array}{l} \text{susceptance at B: } b = 0.4 \\ \text{susceptance at } s_{22}^*: b = -0.27 \end{array} \quad L = \frac{Z_0}{2\pi f |\Delta b|} = \frac{50}{2\pi \times 14 \times 10^9 \times |-0.67|} = 0.85 \text{ nH}$$

The matching circuit is shown on the next page.

Question 4(b) continued

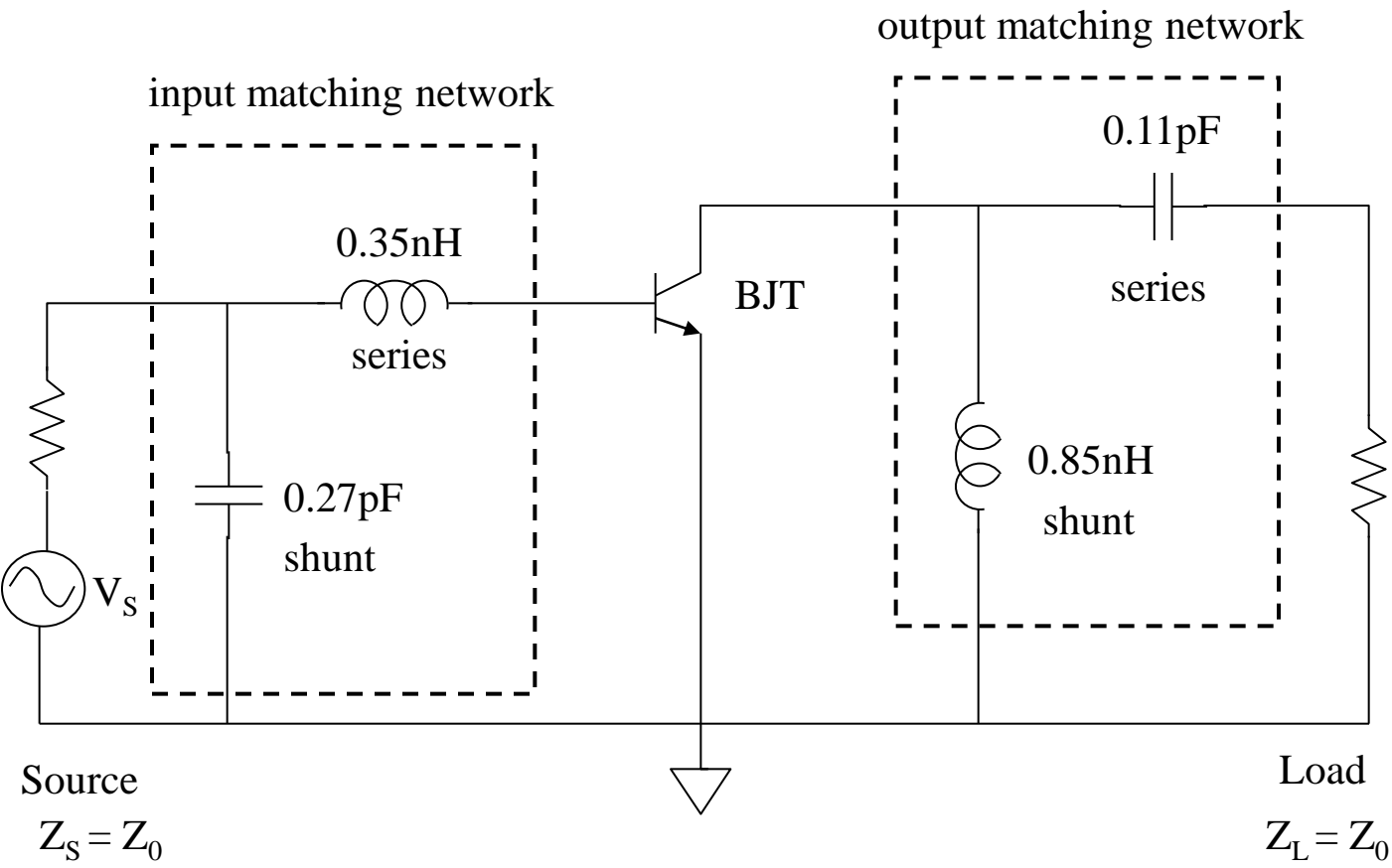


Question 5 concerns derivations from the notes

Question 6

6(a) 5 marks

Suitable PD with transfer function

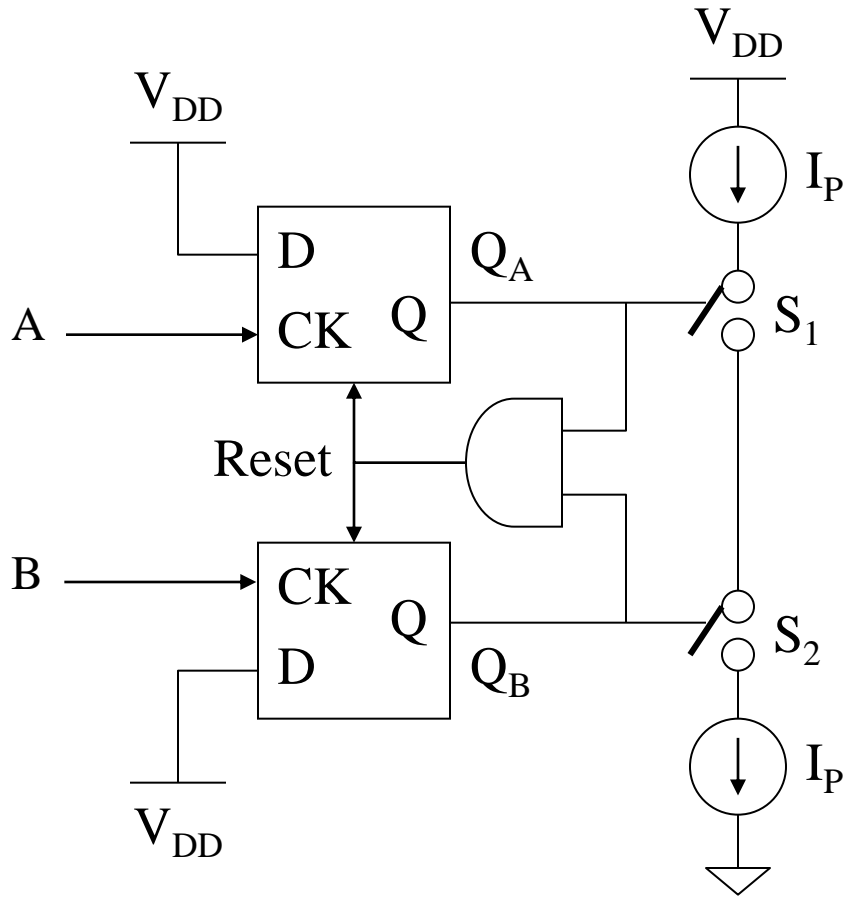

$$I(s) = \frac{I_P}{2\pi} \Delta \phi(s)$$

(b) The control voltage is given by:

$$V_C(s) = \frac{I_P}{2\pi} \left(\frac{R_P C_P s + 1}{(R_P C_P C_2 s + C_P + C_2)s} \right) \Delta \phi(s)$$

The transfer function is found from this through a closed loop analysis.

Q6(c) concerns production of clock phases from the notes

Q7 This is an essay type question based on a continuous assessment assignment.