

Chapter 12

SYNTHESIS OF DC AND LOW-FREQUENCY SINUSOIDAL AC VOLTAGES FOR MOTOR DRIVES AND UPS

- 12-1 Introduction
- 12-2 Switching Power-Pole as the Building Block
- 12-3 DC-Motor Drives
- 12-4 AC-Motor Drives
- 12-5 Voltage-Link Structure with Bi-Directional Power Flow
- 12-6 Uninterruptible Power Supplies (UPS)
- References
- Problems

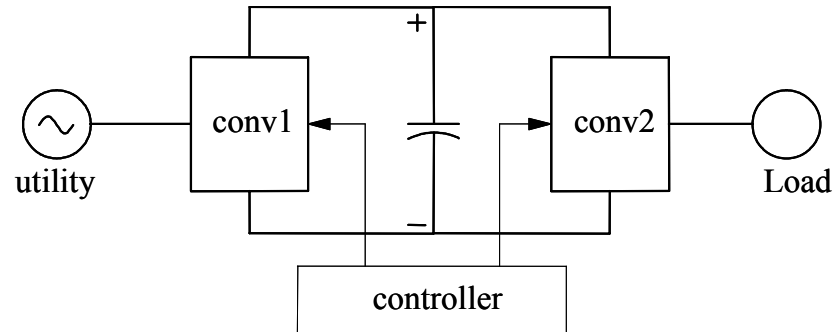


Figure 12-1 Voltage-link system.

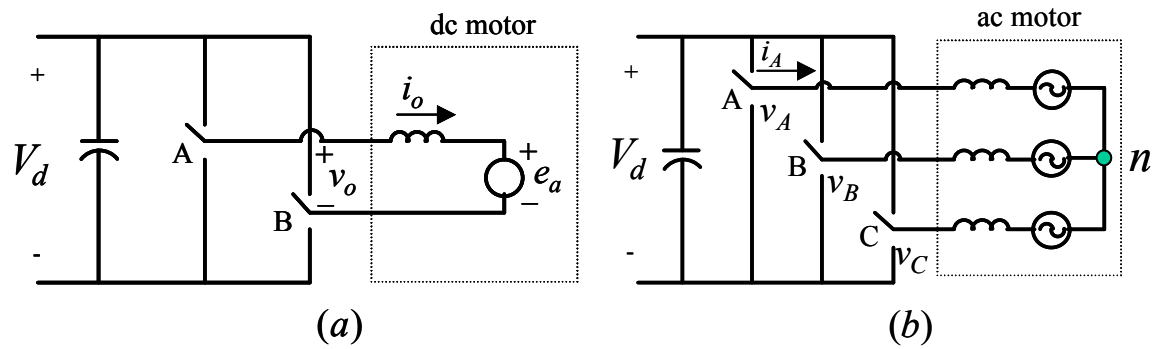


Figure 12-2 Converters for dc and ac motor drives.

SWITCHING POWER-POLE AS THE BUILDING BLOCK

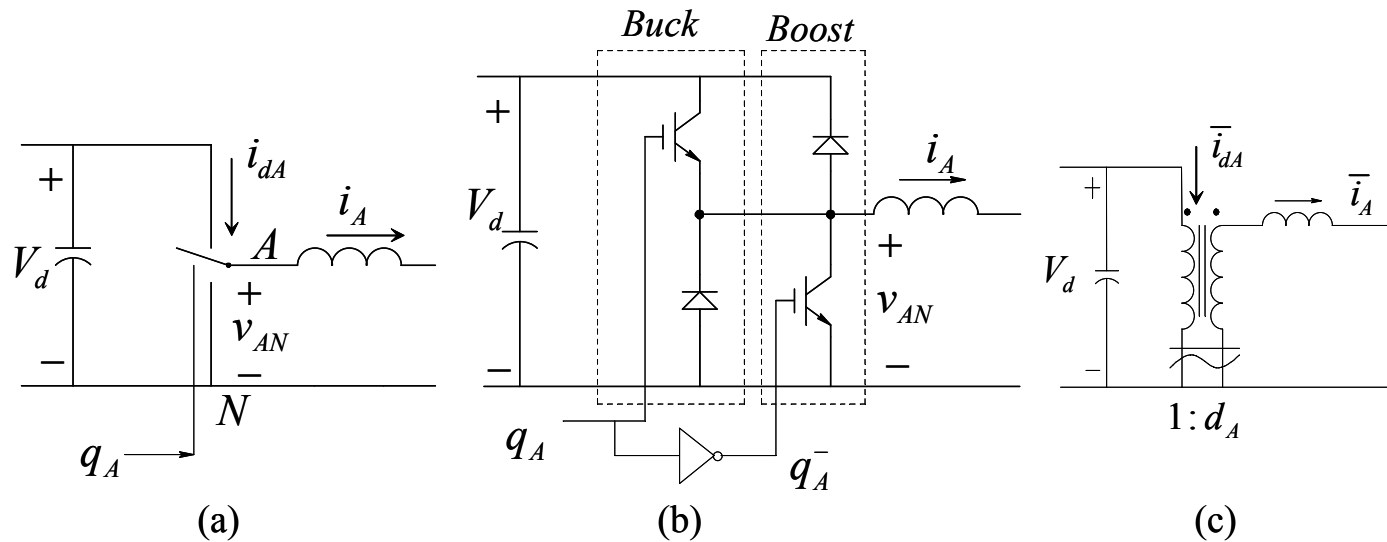


Figure 12-3 Bi-directional switching power-pole.

Pulse-Width-Modulation (PWM) of the Bi-Directional Switching Power-Pole

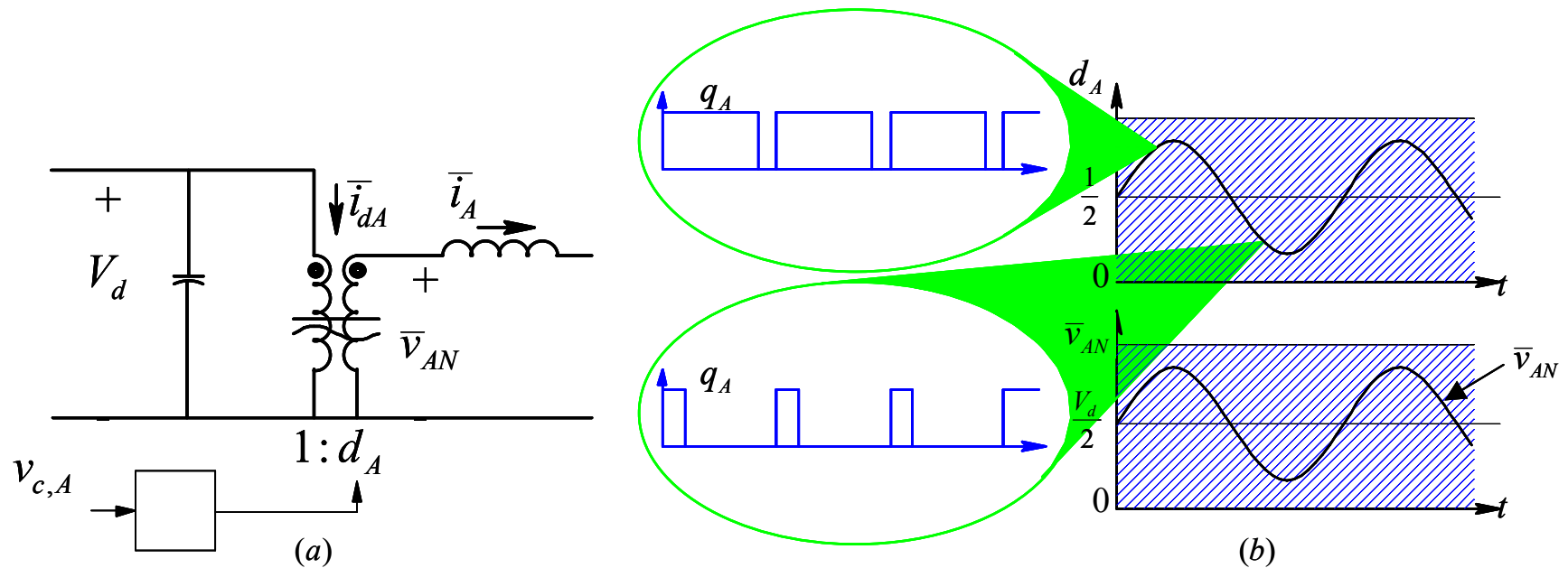


Figure 12-4 Varying the duty-ratio around 0.5 varies \bar{v}_{AN} around $V_d/2$.

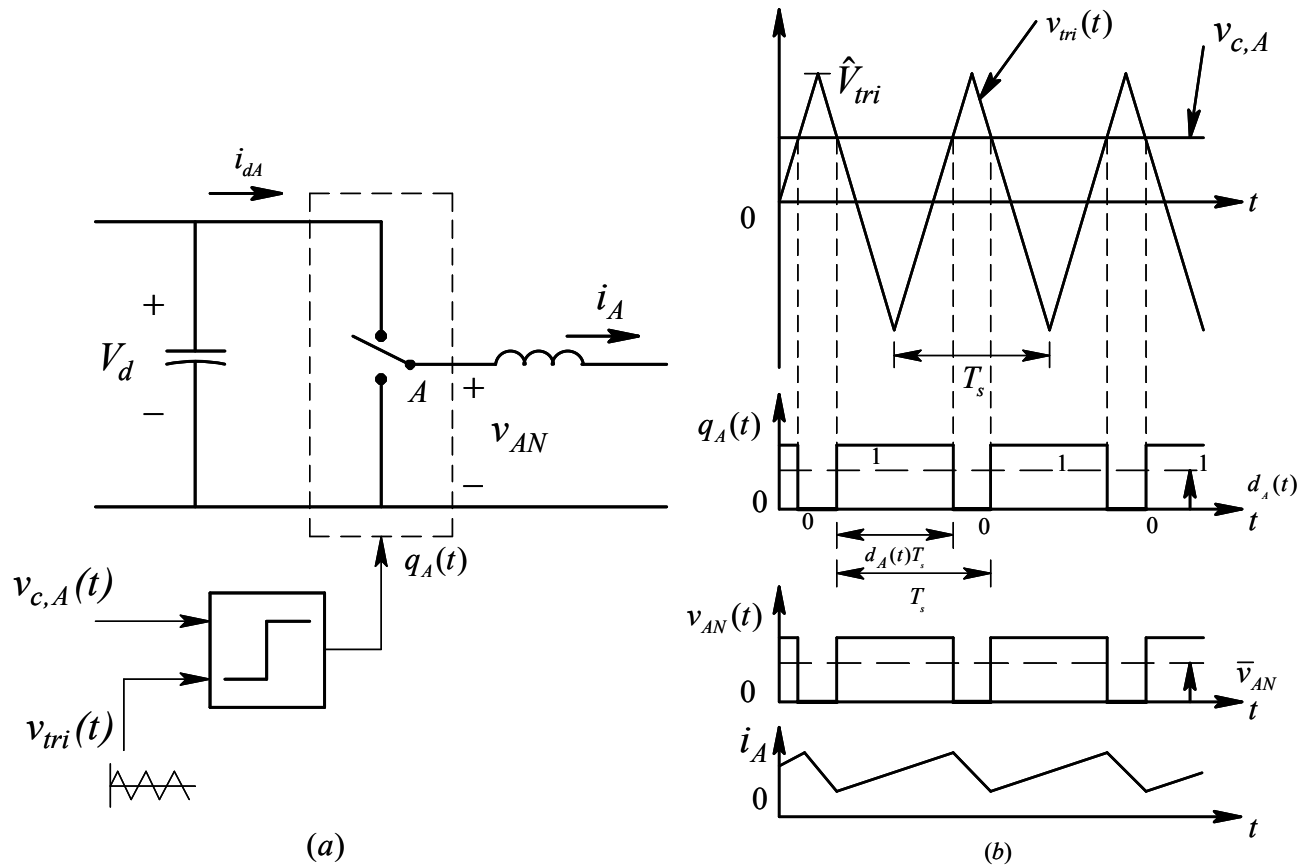


Figure 12-5 Switching power-pole and its voltage and current waveforms.

$$d_A(t) = 0.5 + 0.5 \frac{v_{c,A}(t)}{\hat{V}_{tri}}$$

$$\bar{v}_{AN}(t) = d_A(t)V_d = \underbrace{0.5V_d}_{dc\ offset} + 0.5 \underbrace{\frac{V_d}{\hat{V}_{tri}}}_{k_{pole}} v_{c,A}(t)$$

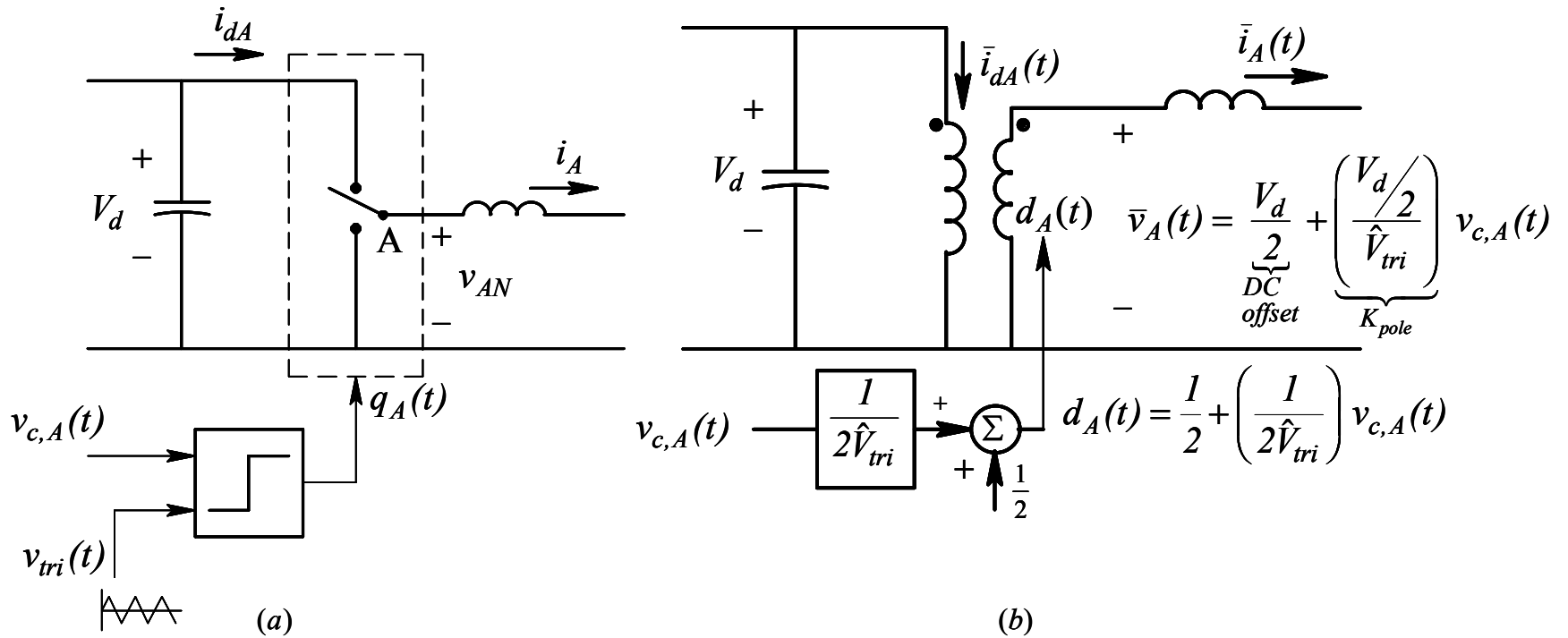


Figure 12-6 Average representation of the pulse-width-modulated power-pole.

Harmonics in the PWM Waveforms v_A and i_{dA}

$$f_h = k_1 f_s \pm \underbrace{k_2 f_1}_{\text{sidebands}}$$

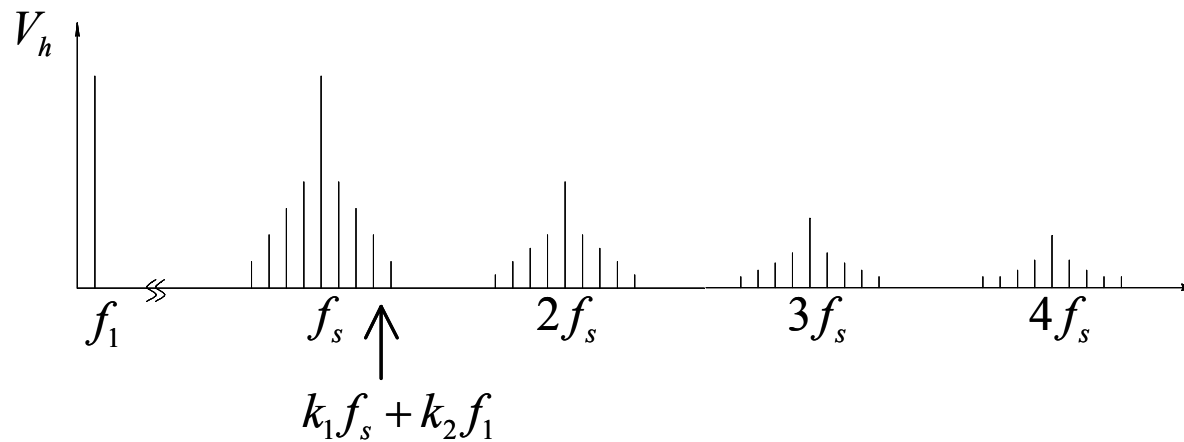


Figure 12-7 Harmonics in the switching power-pole.

DC-MOTOR DRIVES

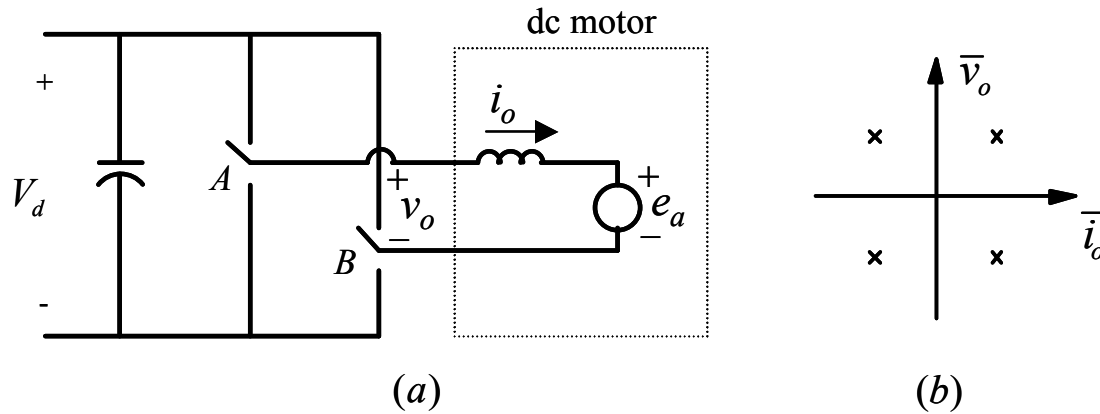


Figure 12-8 DC-motor four-quadrant operation.

$$\bar{v}_{AN}(t) = d_A(t)V_d = 0.5V_d + 0.5\frac{V_d}{\hat{V}_{tri}}v_c(t)$$

$$\bar{v}_{BN}(t) = d_B(t)V_d = 0.5V_d - 0.5\frac{V_d}{\hat{V}_{tri}}v_c(t)$$

$$\bar{v}_o(t) = \bar{v}_{AN}(t) - \bar{v}_{BN}(t) = \underbrace{\frac{V_d}{\hat{V}_{tri}}}_{k_{pwm}}v_c(t)$$

$$\bar{i}_d(t) = \bar{i}_{dA} + \bar{i}_{dB} = d_A(t)\bar{i}_A(t) + d_B(t)\bar{i}_B(t)$$

$$i_A(t) = -i_B(t) = i_o(t)$$

$$\bar{i}_d(t) = \frac{v_c(t)}{\hat{V}_{tri}}\bar{i}_o(t)$$

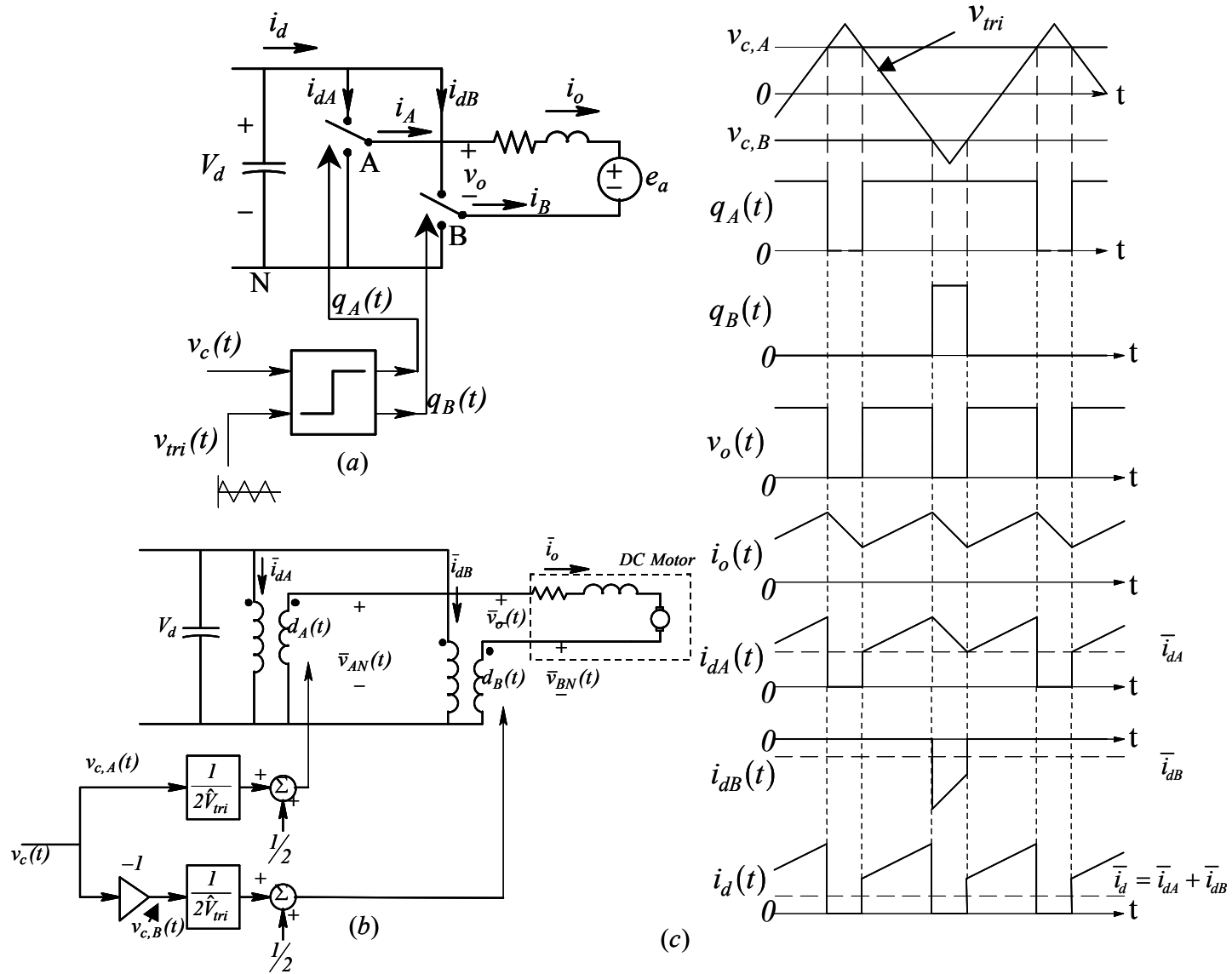


Figure 12-9 Converter for dc-motor drives.

AC-MOTOR DRIVES

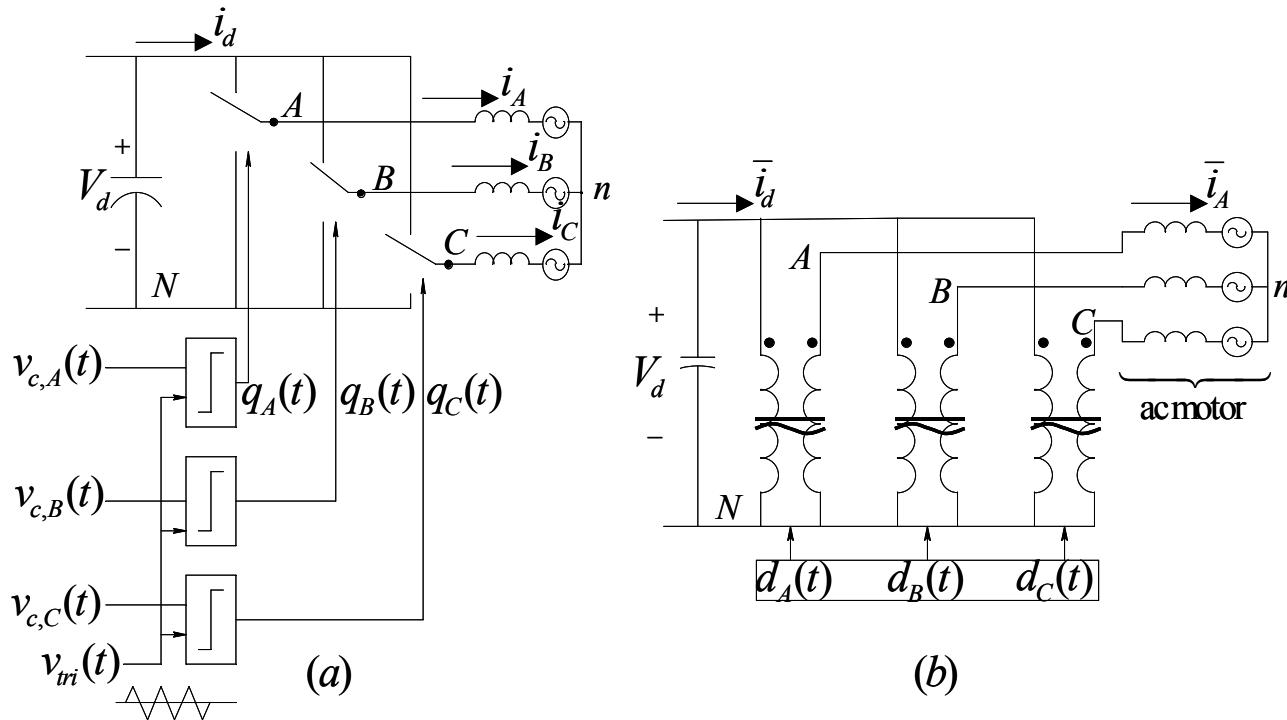


Figure 12-10 Converter for three-phase motor drive and UPS.

$$v_{c,A}(t) = \hat{V}_c \sin \omega_1 t$$

$$v_{c,B}(t) = \hat{V}_c \sin(\omega_1 t - 120^\circ)$$

$$v_{c,C}(t) = \hat{V}_c \sin(\omega_1 t - 240^\circ)$$

$$d_A(t) = 0.5 + \frac{\hat{V}_c}{\hat{V}_{tri}} \sin \omega_1 t$$

$$d_B(t) = 0.5 + \frac{\hat{V}_c}{\hat{V}_{tri}} \sin(\omega_1 t - 120^\circ)$$

$$d_C(t) = 0.5 + \frac{\hat{V}_c}{\hat{V}_{tri}} \sin(\omega_1 t - 240^\circ)$$

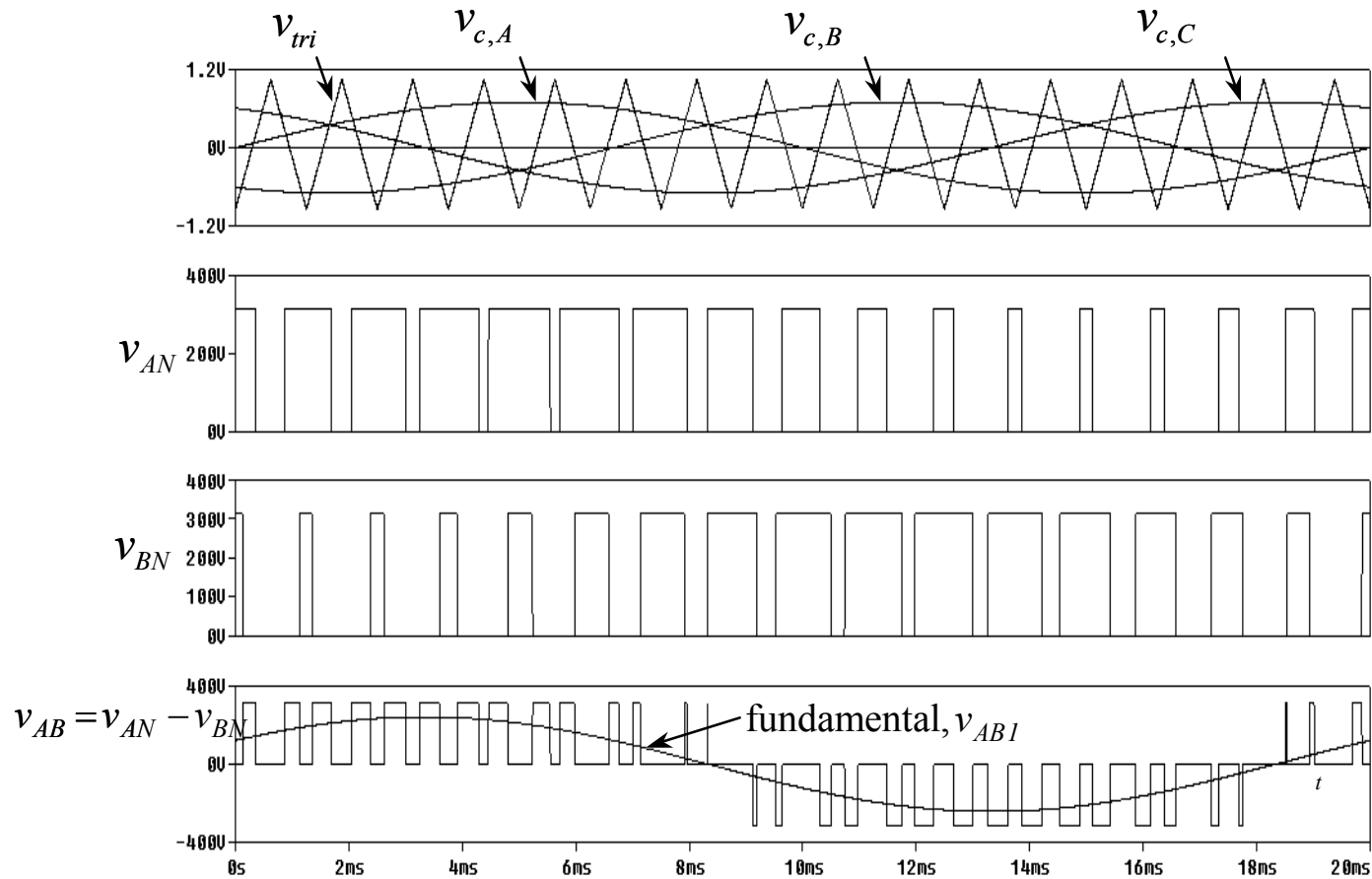


Figure 12-11 Switching waveforms in three-phase converter.

$$\bar{v}_{AN}(t) = 0.5V_d + \underbrace{0.5\frac{V_d}{\hat{V}_{tri}}}_{k_{pole}} \underbrace{\hat{V}_c \sin \omega_1 t}_{v_{c,A}}$$

$$\bar{v}_{BN}(t) = 0.5V_d + \underbrace{0.5\frac{V_d}{\hat{V}_{tri}}}_{k_{pole}} \underbrace{\hat{V}_c \sin(\omega_1 t - 120^\circ)}_{v_{c,B}}$$

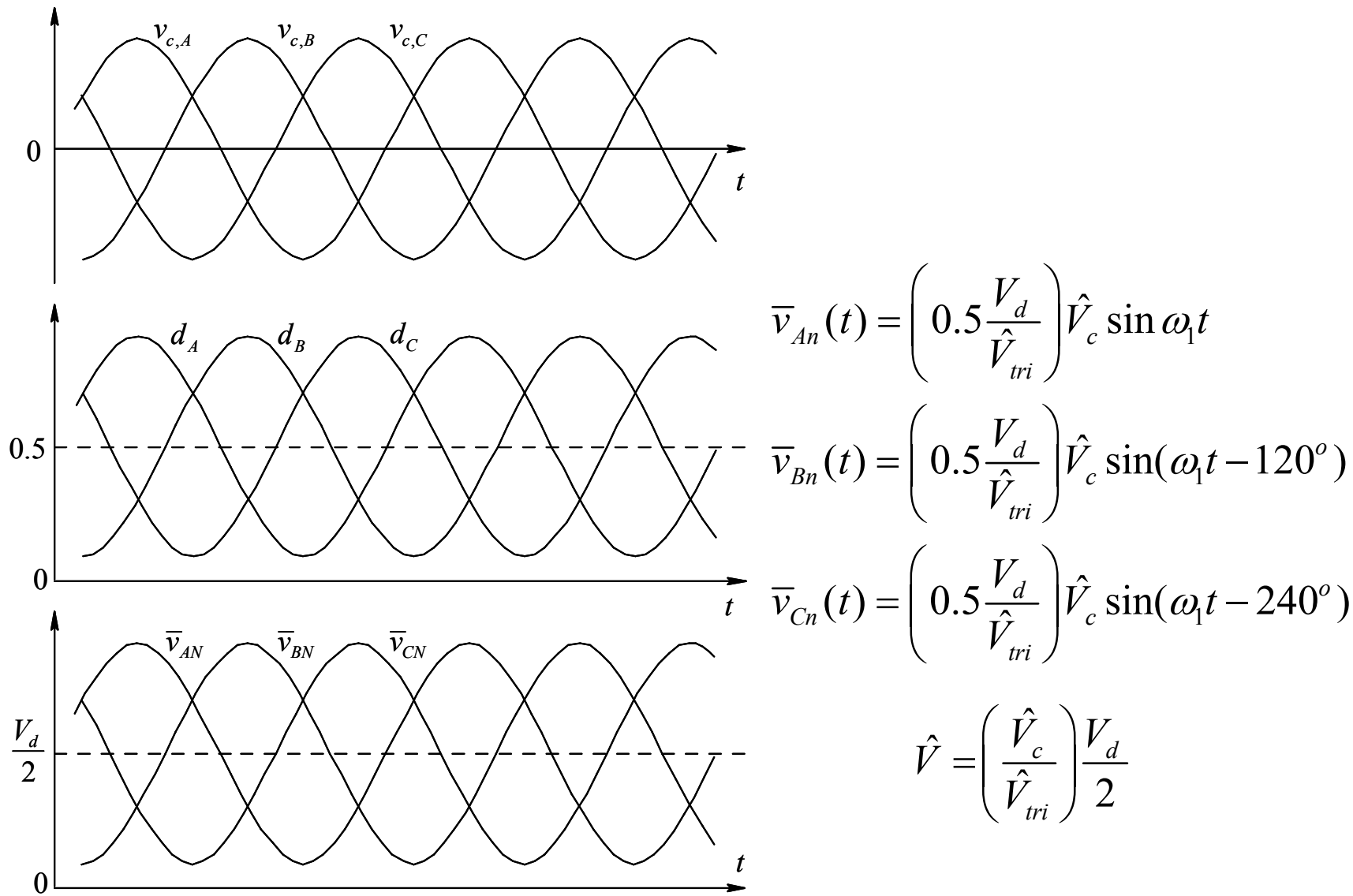


Figure 12-12 Duty-ratios and the average output voltages of the power-pole.

$$\bar{i}_A(t) = \hat{I} \sin(\omega_1 t - \phi_1)$$

$$\bar{i}_B(t) = \hat{I} \sin(\omega_1 t - \phi_1 - 120^\circ)$$

$$\bar{i}_C(t) = \hat{I} \sin(\omega_1 t - \phi_1 - 240^\circ)$$

$$\bar{i}_{dA}(t) = d_A(t) \bar{i}_A(t) = 0.5 \bar{i}_A(t) + 0.5 \frac{v_{c,A}(t)}{\hat{V}_{tri}} \bar{i}_A(t)$$

$$\bar{i}_{dB}(t) = d_B(t) \bar{i}_B(t) = 0.5 \bar{i}_B(t) + 0.5 \frac{v_{c,B}(t)}{\hat{V}_{tri}} \bar{i}_B(t)$$

$$\bar{i}_{dC}(t) = d_C(t) \bar{i}_C(t) = 0.5 \bar{i}_C(t) + 0.5 \frac{v_{c,C}(t)}{\hat{V}_{tri}} \bar{i}_C(t)$$

$$\bar{i}_d(t) = \bar{i}_{dA}(t) + \bar{i}_{dB}(t) + \bar{i}_{dC}(t)$$

$$\bar{i}_A(t) + \bar{i}_B(t) + \bar{i}_C(t) = 0$$


$$\bar{i}_d(t) = \frac{0.5}{\hat{V}_{tri}} \left[v_{c,A}(t) \bar{i}_A(t) + v_{c,B}(t) \bar{i}_B(t) + v_{c,C}(t) \bar{i}_C(t) \right]$$

$$\bar{i}_d(t) = 0.5 \frac{\hat{V}_c}{\hat{V}_{tri}} \hat{I} \left[\sin(\omega_1 t) \sin(\omega_1 t - \phi_1) + \sin(\omega_1 t - 120^\circ) \sin(\omega_1 t - \phi_1 - 120^\circ) \right. \\ \left. + \sin(\omega_1 t - 240^\circ) \sin(\omega_1 t - \phi_1 - 240^\circ) \right]$$


$$\bar{i}_d(t) = I_d = \frac{3}{4} \frac{\hat{V}_c}{\hat{V}_{tri}} \hat{I} \cos \phi_1$$

$$V_d \bar{i}_d(t) = \frac{3}{2} \hat{V} \hat{I} \cos \phi_1$$

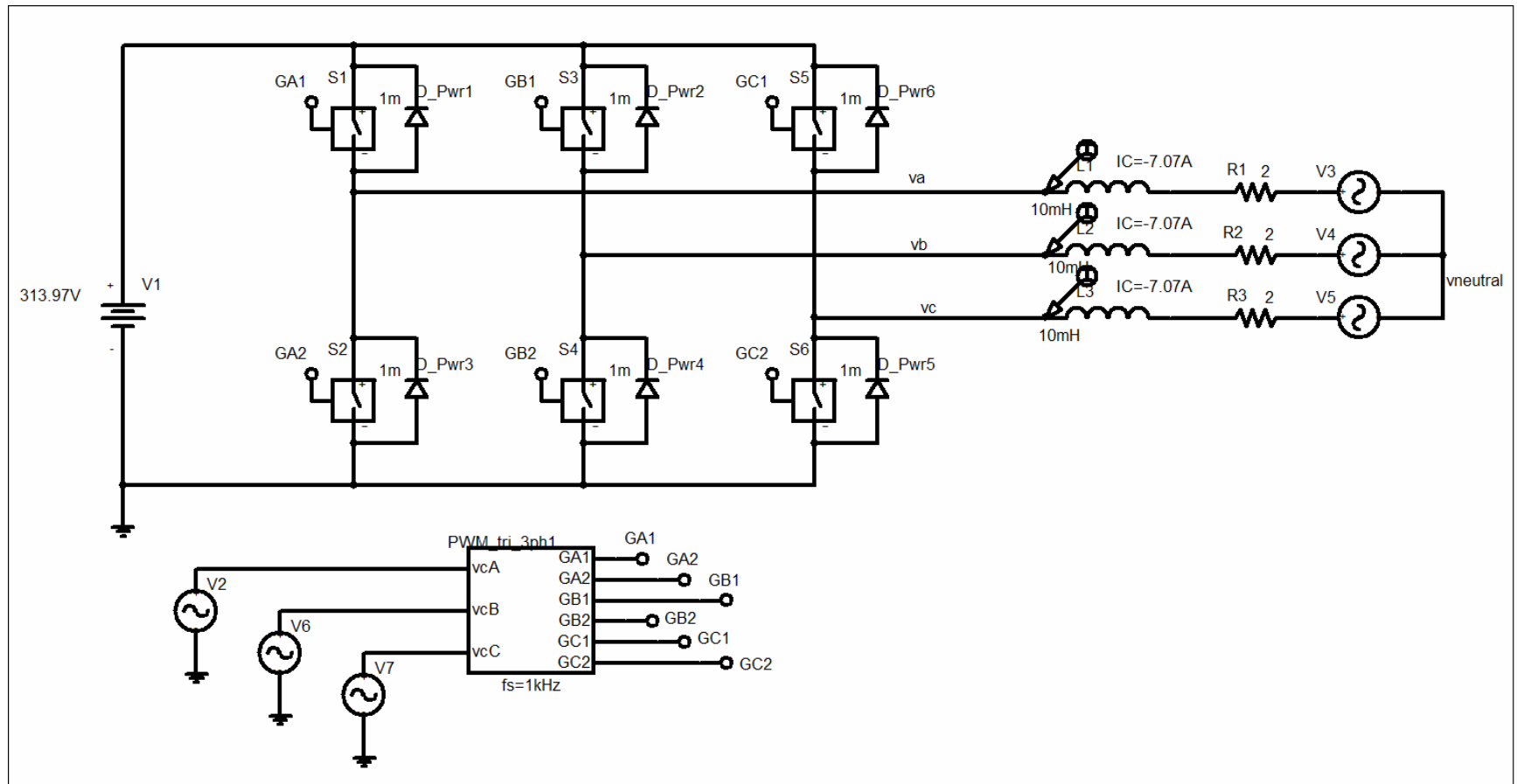
PSpice Modeling: C:\FirstCourse_PE_Book03\PWMinv3.sch



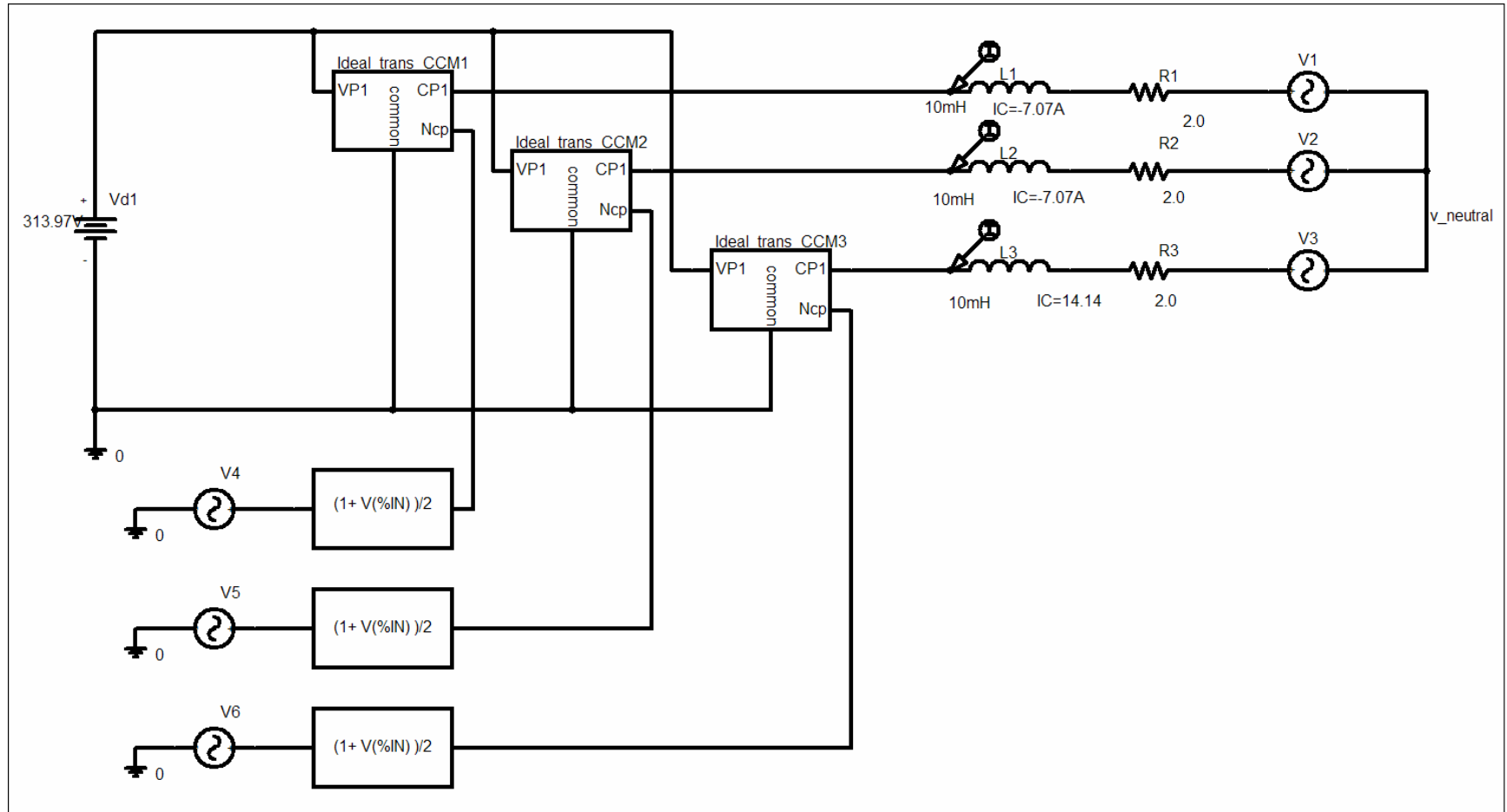PSpice Modeling: C:\FirstCourse_PE_Book03\pwninv3ph_avg.sch



Simulation Results

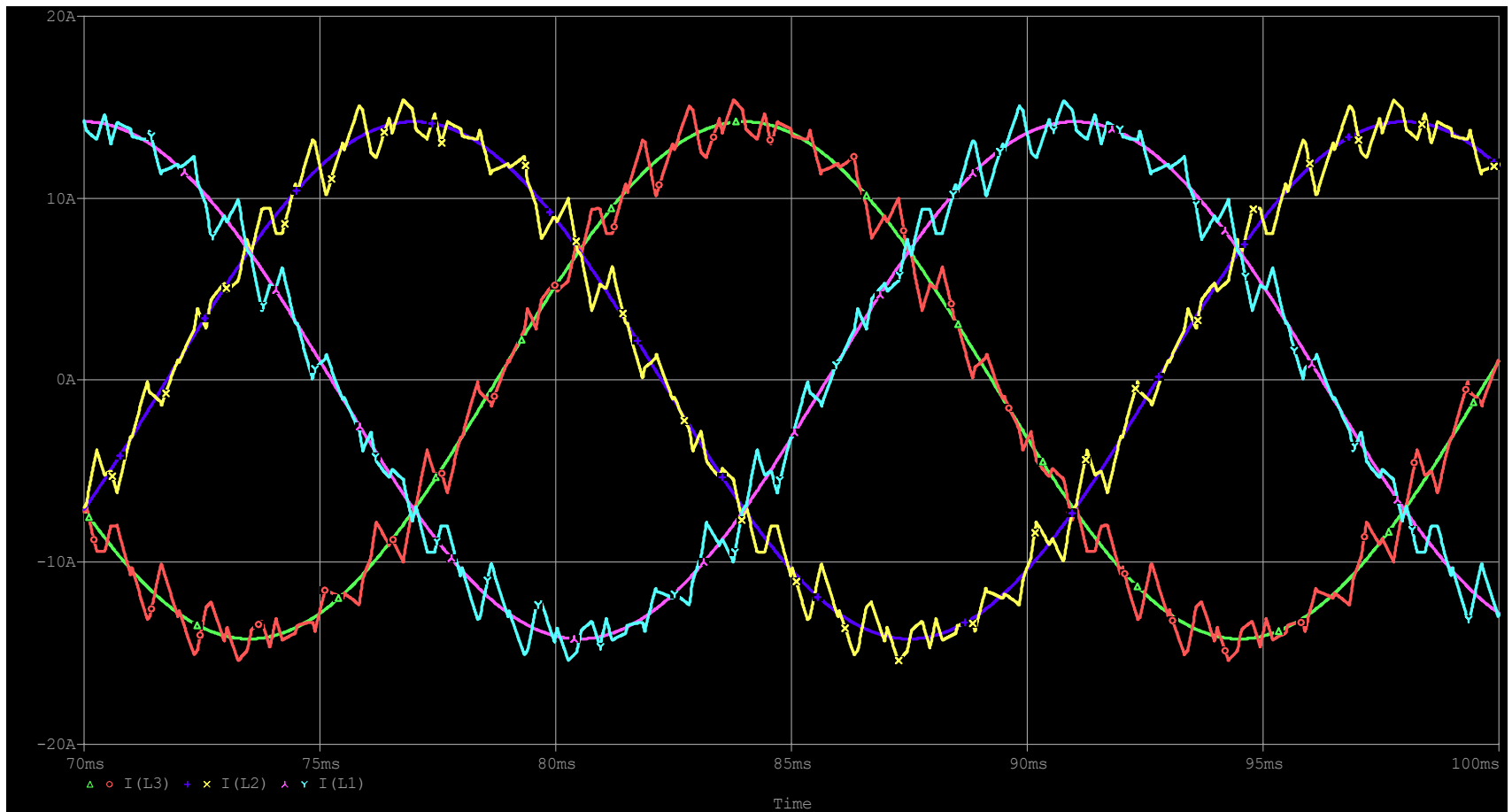

VOLTAGE-LINK STRUCTURE WITH BI-DIRECTIONAL POWER FLOW

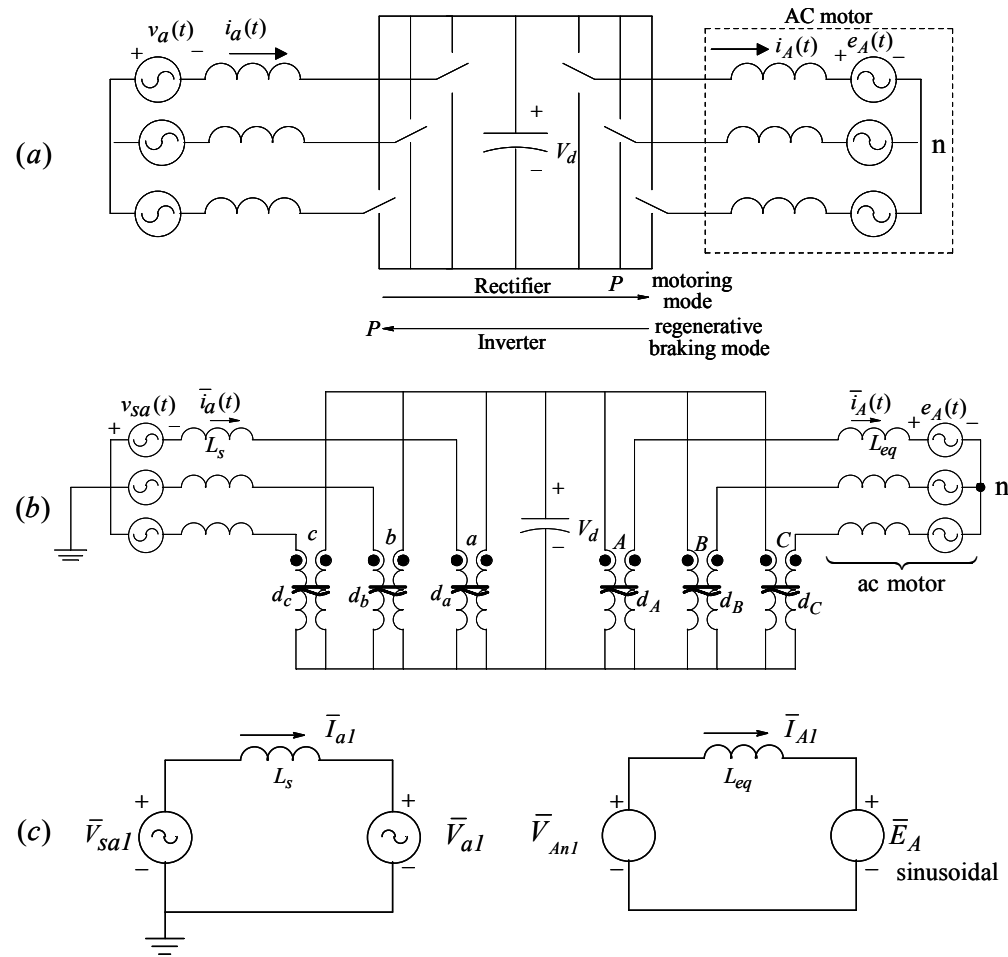


Figure 12-13 Voltage-link structure for bi-directional power flow.

UNINTERRUPTIBLE POWER SUPPLIES (UPS)

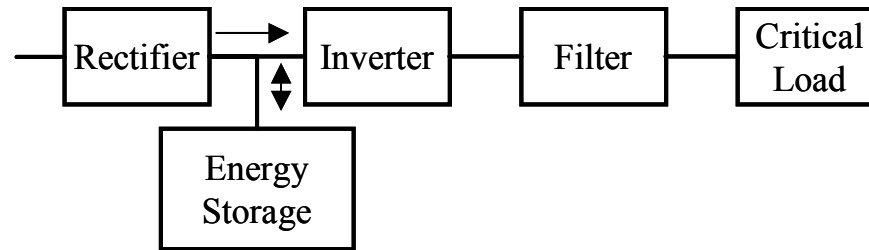


Figure 12-14 Block diagram of UPS.

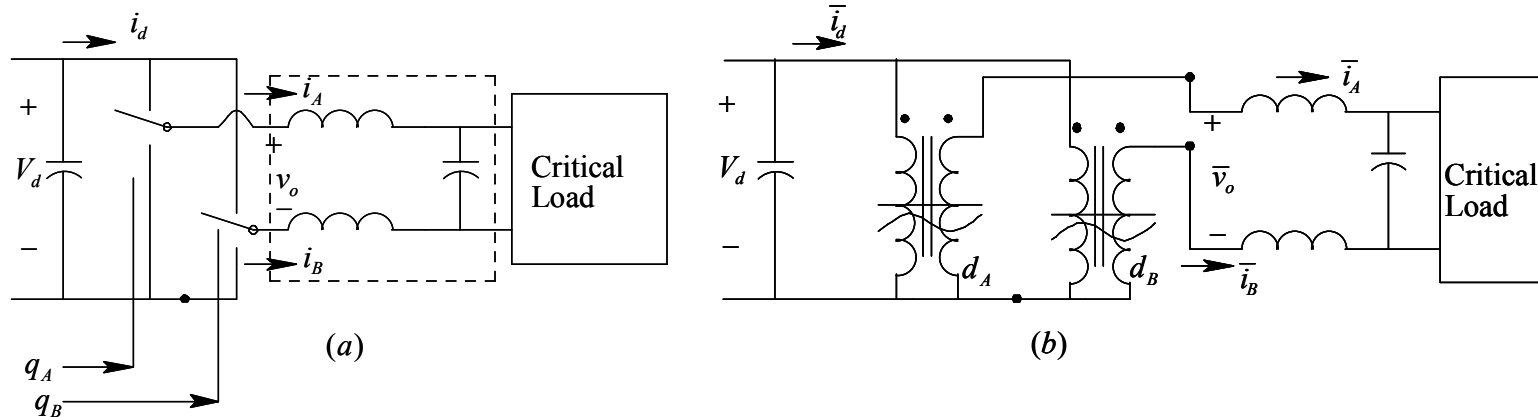


Figure 12-15 Single-phase UPS.

$$v_c(t) = \hat{V}_c \sin \omega_1 t$$

$$v_{c,B}(t) = \hat{V}_c \sin(\omega_1 t - 180^\circ) = -\hat{V}_c \sin \omega_1 t$$

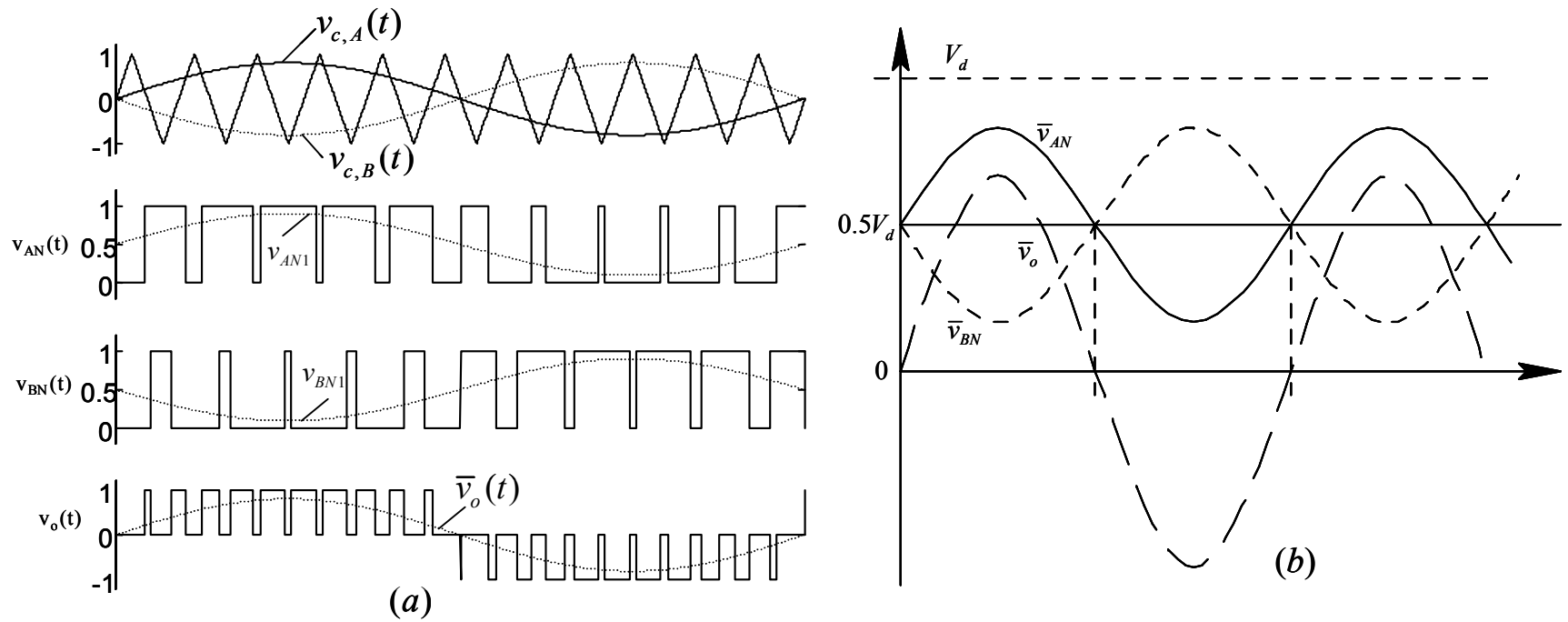


Figure 12-16 UPS waveforms.

$$d_A(t) = 0.5 + 0.5 \frac{\hat{V}_c}{\hat{V}_{tri}} \sin \omega_1 t$$

$$d_B(t) = 0.5 - 0.5 \frac{\hat{V}_c}{\hat{V}_{tri}} \sin \omega_1 t$$

$$\bar{v}_{AN}(t) = 0.5V_d + 0.5 \frac{\hat{V}_c}{\hat{V}_{tri}} V_d \sin \omega_1 t$$

$$\bar{v}_{BN}(t) = 0.5V_d - 0.5 \frac{\hat{V}_c}{\hat{V}_{tri}} V_d \sin \omega_1 t$$

$$\hat{V}_o = \frac{\hat{V}_c}{\hat{V}_{tri}} V_d$$

$$\bar{v}_o(t) = \bar{v}_{AN}(t) - \bar{v}_{BN}(t) = \frac{\hat{V}_c}{\hat{V}_{tri}} V_d \sin \omega_1 t$$

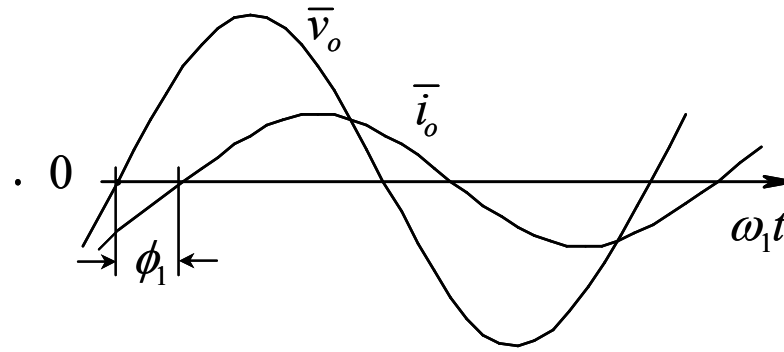


Figure 12-17 Output voltage and current.

$$\bar{i}_o(t) = \hat{I}_o \sin(\omega_1 t - \phi_1)$$

$$\begin{aligned} \bar{i}_d &= \frac{\bar{v}_o \bar{i}_o}{V_d} = \frac{\hat{V}_c}{\hat{V}_{tri}} \hat{I}_o \sin \omega_1 t \times \sin(\omega_1 t - \phi_1) \\ &= \underbrace{0.5 \frac{\hat{V}_c}{\hat{V}_{tri}} \hat{I}_o}_{I_d} - \underbrace{0.5 \frac{\hat{V}_c}{\hat{V}_{tri}} \hat{I}_o \sin(2\omega_1 t - \phi_1)}_{i_{d2}(t)} \end{aligned}$$