

Name:

Student Number:

1. What are the disadvantages of switch-mode power electronics amplifiers compared to linear amplifiers?

Harmonics  $\rightarrow$  noise  $\rightarrow$  EMI  
Lower bandwidth

2. Express the Pulse A duty ratio,  $d_A$ , in terms of the control voltage,  $v_{c,A}$  and the peak of the triangular voltage,  $V_{tri}$ .

$$d_A = \frac{1}{2} + \frac{1}{2} \cdot \frac{v_{c,A}}{V_{tri}}$$


3. In a two-quadrant single-pole converter of dc bus voltage  $V_d = 100V$ , fed by a generator of back emf  $E_g = 45V$  and armature resistance  $R_a = 0.25 \Omega$ , calculate the output pole voltage  $V_{AN}$  and the duty ratio  $d_A$  when pulling an armature current  $I_a = 20A$ .



$$\begin{aligned} V_{AN} &= E - I_a R_a \\ &= (45 - 5) V \\ &= 40 V \end{aligned}$$

$$\begin{aligned} d &= \frac{40}{100} \\ &= 0.4 \end{aligned}$$

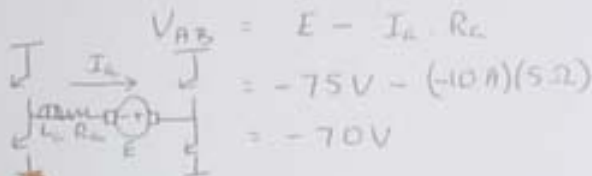4. In a first-quadrant two-pole converter of dc bus voltage  $V_d = 100V$ , supplied by a generator of back emf  $E_g = 75V$  (spinning in reverse) and armature resistance  $R_a = 0.5 \Omega$ , calculate the output pole voltage  $V_{AB}$  and the duty ratio  $d$  when pulling an armature current  $I_a = 10A$ .




$$\begin{aligned} V_{AB} &= E - I_a R_a \\ &= -75V - (-10A)(0.5\Omega) \\ &= -70V \end{aligned}$$

$$\begin{aligned} d &= \left| \frac{70}{100} \right| \\ &= 0.7 \end{aligned}$$

5. Calculate the peak-peak armature current ripple in the above generating question when armature inductance  $L_a = 1mH$  and the triangular frequency  $f_{tri} = 10kHz$ .

$$\begin{aligned} \Delta I_{p-p} &= \frac{V_d - \cancel{(-E)}}{L} \cdot d \cdot \frac{T_s}{2} \\ &= \frac{(100 - 75)V}{1mH} \cdot 0.7 \cdot \frac{1 \times 10^{-4}s}{2} = 1.05 A_{p-p} \end{aligned}$$

6. Sketch a synchronous buck converter.

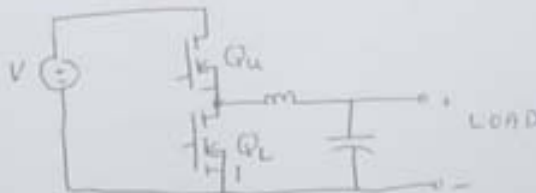


7. A buck converter, switching at 1 MHz, powers a 1.5 V, 100 mA microprocessor from 3.0 V. Calculate the inductance required to limit the current ripple to  $\pm 10\%$ .

$$d = \frac{V_o}{V_{in}} = 0.5$$

$$V_L = L \frac{\Delta I_L}{\Delta t}$$

$$L = \frac{V_L \Delta t}{\Delta I_L}$$
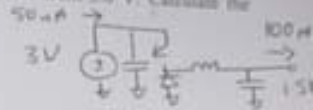
$$= \frac{(3-1.5) \cdot 0.5 \cdot 1 \times 10^{-6}}{0.2 \cdot 100 \times 10^{-3}} = 37.5 \mu\text{H}$$



8. Calculate the capacitance required in the above converter to reduce the output voltage ripple to  $\pm 20\text{ mV}$ .

$$C = \frac{1}{2} \cdot \frac{T_s}{2} \cdot \frac{\Delta I}{2} \cdot \frac{1}{\Delta V}$$

$$= \frac{1}{2} \cdot \frac{1 \times 10^{-6}}{2} \cdot \frac{0.2 \cdot 100 \times 10^{-3}}{2} \cdot \frac{1}{40 \times 10^{-3}} = 62.5 \text{ nF}$$

9. What are the peak and rms currents in the above inductor?

$$\Delta I_{p-p} = 20 \text{ mA}$$

$$I_{pk} = I_o + \frac{\Delta I_{p-p}}{2} = 110 \text{ mA (pk)}$$

$$I_{L,rms} = \sqrt{I_o^2 + \left(\frac{\Delta I_{p-p}}{\sqrt{12}}\right)^2} = \sqrt{0.1^2 + \left(\frac{0.02}{\sqrt{12}}\right)^2} \approx 100 \text{ mA (rms)}$$

10. What are the rms currents in the controlled switch and the input capacitor on the 3V dc bus?

$$I_{Q_{u,rms}} = \sqrt{d} \cdot I_{L,rms} = \sqrt{0.5} \cdot 100 \text{ mA} = 70.7 \text{ mA (rms)}$$

$$I_{C_I} = \sqrt{I_{Q_{u,rms}}^2 - (I_{I,d})^2} = \sqrt{(70.7 \text{ mA})^2 - (50 \text{ mA})^2} = 50 \text{ mA (rms)}$$

11. A three-phase sinusoidal PWM inverter is required to output 400 V line-line. What is the minimum dc bus voltage required?

$$V_{LL} = 400 \text{ V}_{rms}$$

$$V_{ph} = \frac{V_{LL}}{\sqrt{3}} = 231 \text{ V}_{rms}$$

$$V_{dc} = \sqrt{2} \cdot V_{ph} \cdot 2 = 653 \text{ V}_{dc}$$

12. A sinusoidal PWM full bridge inverter is required to output single phase 100 V in Japan. What is the minimum dc bus voltage required?

$$V_{ph} = 100 \text{ V}_{rms}$$

$$V_{dc} = \sqrt{2} \cdot V_{ph} = 141 \text{ V}_{dc}$$