

APPENDIX 4A BODE PLOTS OF TRANSFER FUNCTIONS WITH POLES AND ZEROS

In this section, Bode plots of various transfer functions are presented as a review.

4A-1 A Pole in a Transfer Function

A transfer function with a pole at ω_p is expressed below

$$T(s) = \frac{1}{1 + \frac{s}{\omega_p}} \quad (4A-1)$$

whose gain and phase plots in Fig. 4A-1 show that the gain beyond the pole frequency of ω_p starts to fall at a rate of -20 dB/decade and the phase angle falls to -90° approximately a decade later.

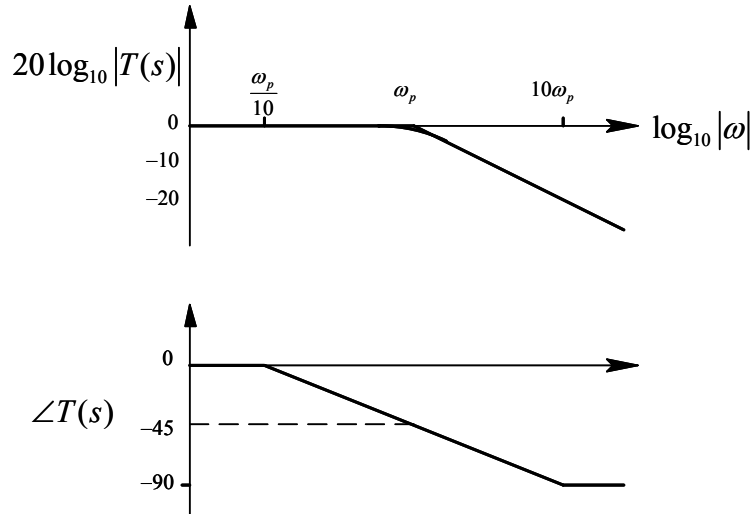


Fig. 4A-1 Gain and phase plots of a pole.

4A-2 A Zero in a Transfer Function

The transfer function with a zero at a frequency of ω_z is expressed below

$$T(s) = 1 + \frac{s}{\omega_z} \quad (4A-2)$$

whose gain and phase plots in Fig. 4A-2 show that the gain beyond the frequency of ω_z starts to rise at a rate of 20 dB/decade and the phase angle rises to $+90^\circ$ approximately a decade later.

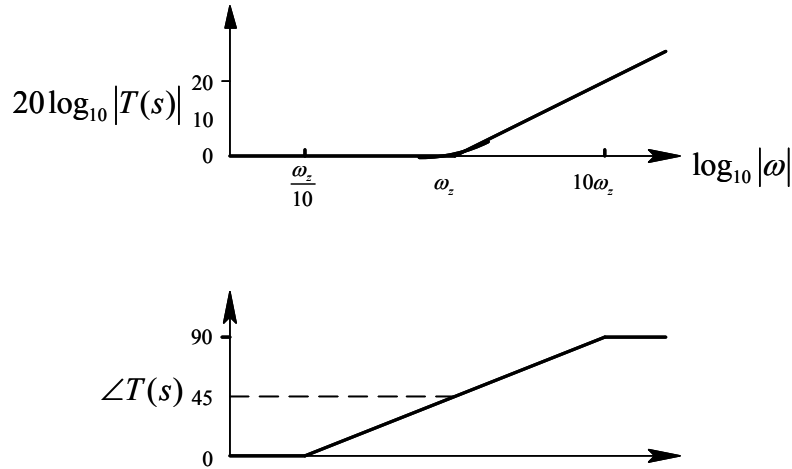


Fig. 4A-2 Gain and phase plots of a zero.

4A-3 A Right-Hand-Plane (RHP) Zero in a Transfer Function

In boost and buck-boost dc-dc converters, transfer functions contain a so called right-hand plane (RHP) zero, with a transfer function expressed below

$$T(s) = 1 - \frac{s}{\omega_z} \quad (4A-3)$$

whose gain and phase plots in Fig. 4A-3 show that the gain beyond the frequency of ω_z starts to rise at a rate of 20 dB/decade while the phase angle drops to -90° approximately a decade later. This RHP zero presents special challenges in designing feedback controllers in boost and buck-boost converters, as is discussed in this chapter.

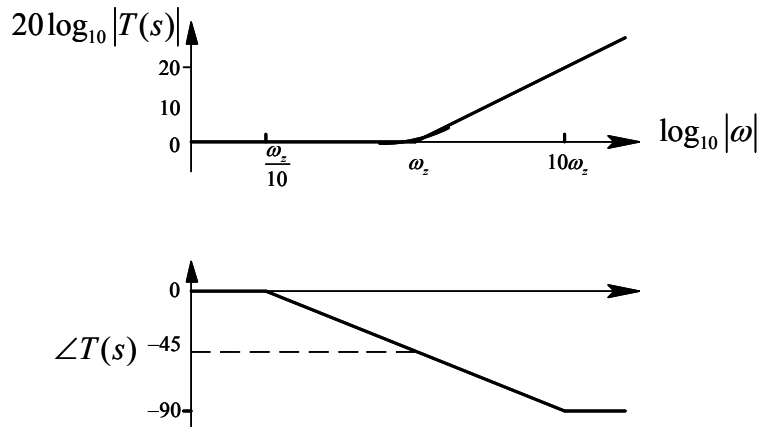


Fig. 4A-3 Gain and phase plots of a right-hand side zero.

4A-4 A Double Pole in a Transfer Function

In dc-dc converter transfer functions, presence of L-C filters introduces a double pole, that can be expressed as below

$$T(s) = \frac{1}{1 + \alpha s + \left(\frac{s}{\omega_o}\right)^2} \quad (4A-4)$$

whose gain and plots in Fig. 4A-4 show that the gain beyond the frequency ω_o starts to fall at a rate of -40 dB/decade and the phase angle falls towards -180° . These plots depend on the damping coefficient $\xi = (\alpha/2)\omega_o$.

APPENDIX 4B TRANSFER FUNCTIONS IN CONTINUOUS CONDUCTION MODE (CCM)

In this section, we will derive the transfer function \tilde{v}_o/\tilde{d} for the three converters operating in CCM

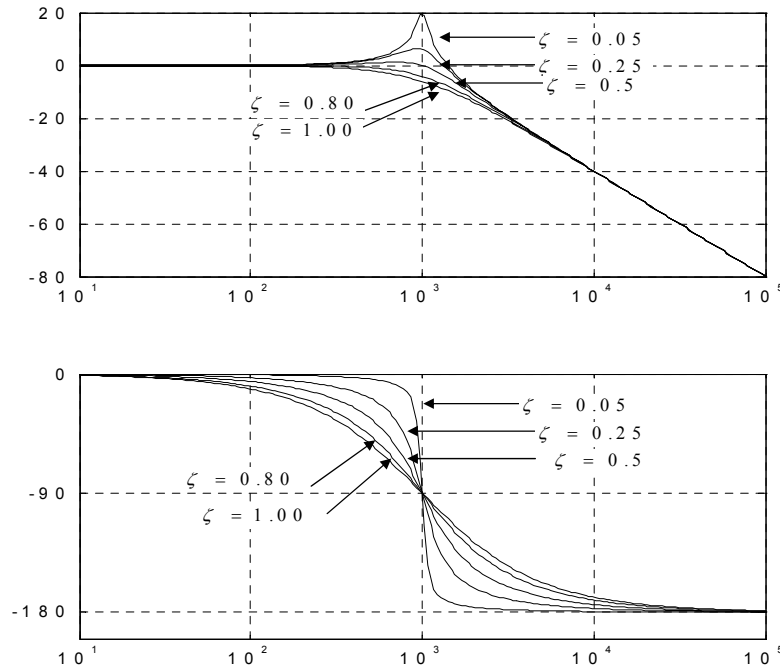


Fig.4A-4 Gain and phase plots of a double-pole.

4B-1 Buck Converters

From Fig. 4-7, the small signal diagram for a Buck converter is shown in Fig. 4B-1.

Defining the output stage impedance Z_{os} as the parallel combination of the filter capacitor and the load resistance,

$$Z_{os} = \frac{R(r + \frac{1}{sC})}{R + (r + \frac{1}{sC})} = R \frac{1 + srC}{1 + s(R+r)C} \quad (4B-1)$$

In any practical converter, $r \ll R$, and therefore, $R + r \simeq R$. Making use of this assumption in Eq. 4B-1,

$$Z_{os} \simeq R \frac{1 + srC}{1 + sRC} \quad (4B-2)$$

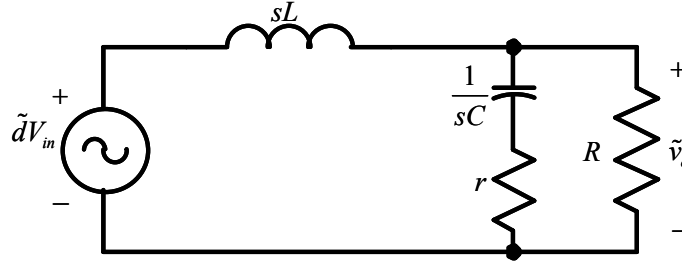


Fig. 4B-1 Equivalent circuit of average buck converter.

Defining Z_{eff} as the sum of the filter inductor and the output stage impedance,

$$Z_{eff} = sL + Z_{os} = \frac{1 + srC}{LC \left[s^2 + s \left(\frac{1}{RC} + \frac{r}{L} \right) + \frac{1}{LC} \right]} \quad (4B-3)$$


Therefore, in the Fig. 4B-1 by voltage division

$$\frac{\tilde{v}_o}{\tilde{d}} = V_{in} \frac{Z_{os}}{Z_{eff}} = V_{in} \frac{1 + srC}{LC \left[s^2 + s \left(\frac{1}{RC} + \frac{r}{L} \right) + \frac{1}{LC} \right]} \quad (4B-4)$$


4B-2 Boost Converter

From Fig. 4-7, the small signal diagram of a Boost converter is shown in Fig. 4B-2a. In this circuit, the dc steady state operating point values can be calculated as follows:


Appendix 4-4

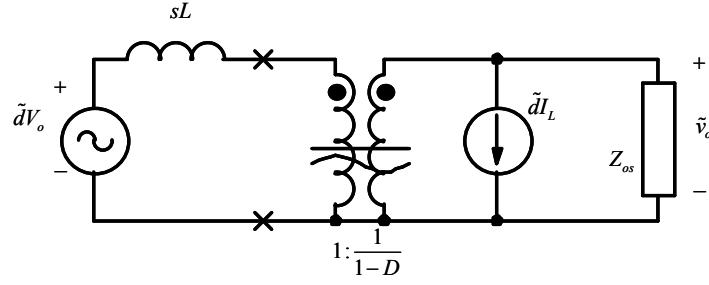


(a)

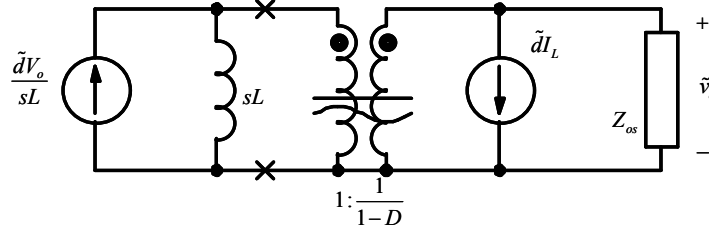

(b)

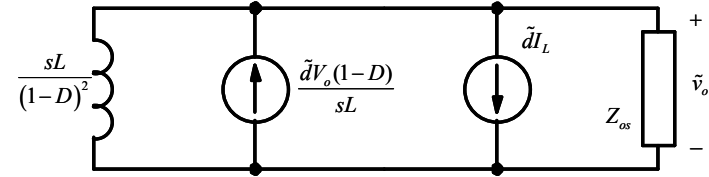

(c)

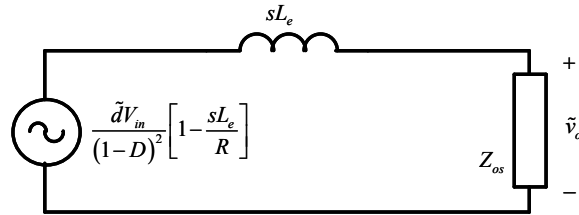

(d)

Fig. 4B-2 Equivalent circuit of average boost converter.

$$I_o = \frac{V_o}{R} \quad (4B-5)$$

Equating the input and the output power,

$$V_o I_o = V_{in} I_{in} \quad (4B-6)$$

Substituting Eq. 4B-5 into Eq. 4B-6,

$$I_L = I_{in} = \frac{V_o I_o}{V_{in}} = \frac{V_o^2}{R V_{in}} \quad (4B-7)$$

In Fig. 4B-2a, the sub-circuit left of the marked terminals can be replaced by its Norton equivalent, as shown in Fig. 4B-2b. The sub-circuit left of the transformer in Fig. 4B-2b can be transformed to the right, as shown in Fig. 4B-2c, where

$$L_e = \frac{L}{(1-D)^2} \quad (4B-8)$$

The two current sources in Fig. 4B-2c can be combined and using the Thevenin's equivalent, the equivalent voltage in Fig. 4B-2d is

$$v_{eq} = \tilde{d} \frac{V_{in}}{(1-D)^2} \left(1 - \frac{sL_e}{R} \right) \quad (4B-9)$$

Using the equivalent voltage in Eq. 4B-9 and applying the voltage division in the circuit of Fig. 4B-2d,

$$\frac{\tilde{v}_o}{\tilde{d}} = \frac{V_{in}}{(1-D)^2} \left(1 - \frac{sL_e}{R} \right) \frac{1 + srC}{L_e C \left[s^2 + s \left(\frac{1}{RC} + \frac{r}{L_e} \right) + \frac{1}{L_e C} \right]} \quad (4B-10)$$

4B-3 Buck-Boost Converter

From Fig. 4-7, the small signal diagram of a Buck-Boost converter is shown in Fig. 4B-3a. First, we will calculate the values of the needed quantities at the dc steady state operating point.

In a Buck-Boost converter,

$$I_o = \frac{V_o}{R} \quad (4B-11)$$

$$V_o = \frac{D}{1-D} V_{in} \quad (4B-12)$$

Equating the input and the output power,

$$I_{in} V_{in} = V_o I_o \quad (4B-13)$$

and hence,

$$I_{in} = \frac{V_o^2}{R V_{in}} \quad (4B-14)$$

Appendix 4-6

Since, $I_L = I_o + I_{in}$,

$$I_L = \frac{V_{in}}{R} \frac{D}{(1-D)^2} \quad (4B-15)$$

Considering the sub-circuit to the left of the marked terminals in Fig. 4B-3a and drawn in Fig. 4B-3b,

$$i_1 = i_2 \quad (4B-16)$$

where,

$$i_1 = Di_2 \quad (4B-17)$$

Eqs. 4B-16 and 4B-17 are valid in general only if $i_1 = i_2 = 0$. Therefore in Fig. 4B-3b,

$$v_{oc} = \tilde{d} \frac{V_{in}}{(1-D)^2} \quad (4B-18)$$

Shorting the terminals as shown in Fig. 4B-3c,

$$i_{sc} = i_1 - Di_1 = (1-D)i_1 \quad (4B-19)$$

In Fig. 4B-3c,

$$i_1 = \tilde{d} \frac{V_{in}}{(1-D)sL} \quad (4B-20)$$

Substituting Eq. 4B-20 into Eq. 4B-19,


$$i_{sc} = \tilde{d} \frac{V_{in}}{sL} \quad (4B-21)$$

From Figs. 4B-3b and 4B-3c, and Eqs. 4B-18 and 4B-21, the Thevenin impedance to the left of the marked terminals in Fig. 4B-3a is


$$Z_{Th} = \frac{v_{oc}}{i_{sc}} = sL_e \quad (4B-22)$$

where

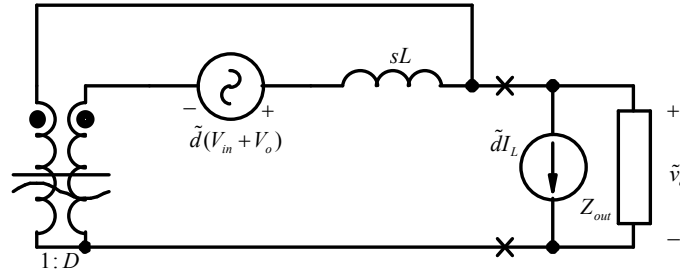
$$L_e = \frac{L}{(1-D)^2} \quad (4B-23)$$



(a)

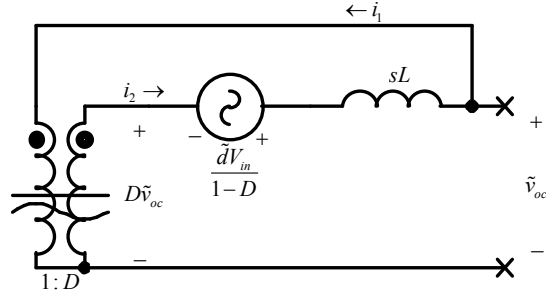

(b)

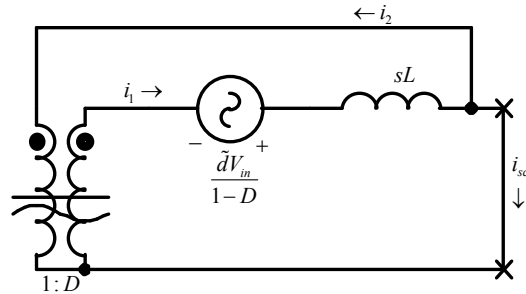

(c)


Fig. 4B-3 Equivalent circuit of average buck-boost converter.

and,


$$v_{Th} = \tilde{d} \frac{V_{in}}{(1-D)^2} \quad (4B-24)$$

With this Thevenin equivalent, the circuit of Fig. 4B-3a, can be drawn as shown in Fig. 4B-4a. The sub-circuit to the left of the marked terminals can be represented by its Norton equivalent, as shown in Fig. 4B-4b. Combining the current sources and representing the sub-circuit in Fig. 4B-4b by its Thevenin equivalent as shown in Fig. 4B-4c,


Appendix 4-8

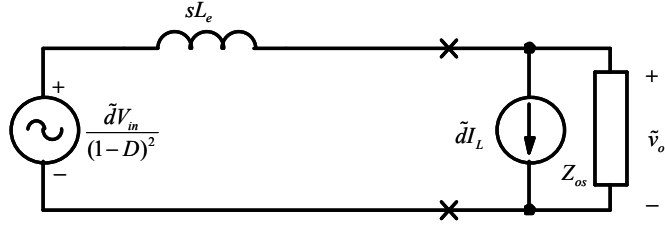

(a)

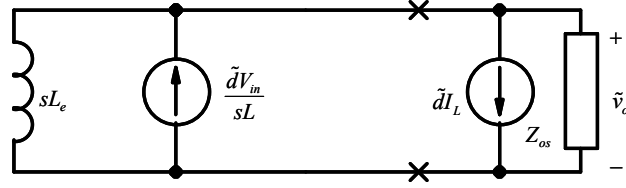

(b)

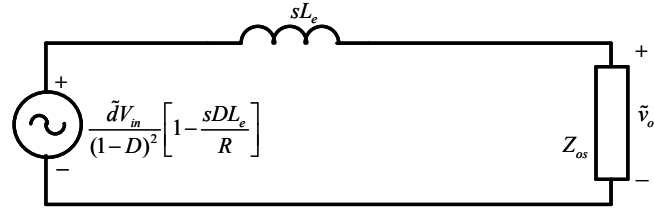

(c)

Fig. 4B-4 Equivalent circuit of average buck-boost converter (contd.)

$$v_{eq} = \tilde{d} \frac{V_{in}}{(1-D)^2} \left(1 - sD \frac{L_e}{R} \right) \quad (4B-25)$$

Hence,

$$\frac{\tilde{v}_o}{\tilde{d}} = \frac{V_{in}}{(1-D)^2} \left(1 - sD \frac{L_e}{R} \right) \frac{1 + srC}{L_e C \left[s^2 + s \left(\frac{1}{RC} + \frac{r}{L_e} \right) + \frac{1}{L_e C} \right]} \quad (4B-26)$$

APPENDIX 4C DERIVATION OF PARAMETERS OF THE CONTROLLER TRANSFER FUNCTIONS

4C-1 CONTROLLER TRANSFER FUNCTION WITH ONE POLE-ZERO PAIR

$$G_c(s) = k_c \frac{1 + s / \omega_z}{1 + s / \omega_p} \quad (4C-1)$$

$$\phi = \angle G_c(s) = \tan^{-1} \frac{\omega}{\omega_z} - \tan^{-1} \frac{\omega}{\omega_p} \quad (4C-2)$$

4C-1-1 Frequency at which ϕ_{boost} Occurs

The maximum angle ϕ_{boost} provided by the controller occurs at the geometric mean of the zero and pole frequencies, as shown below. (This geometric mean frequency is made to coincide with $\omega = \omega_c$ where ω_c is the cross over frequency.) To find the frequency at which ϕ_{boost} occurs, we will set the derivative of the phase angle to zero:

$$\frac{d}{d\omega} \phi = \frac{1}{\omega_z} \frac{1}{\left(1 + \frac{\omega^2}{\omega_z^2}\right)} - \frac{1}{\omega_p} \frac{1}{\left(1 + \frac{\omega^2}{\omega_p^2}\right)} = 0 \quad (4C-3)$$

Therefore,

$$\frac{\omega_z}{\left(\omega^2 + \omega_z^2\right)} - \frac{\omega_p}{\left(\omega^2 + \omega_p^2\right)} = 0 \quad (4C-4)$$

or,

$$\left(\omega^2 - \omega_z \omega_p\right) \left(\omega_z - \omega_p\right) = 0 \quad (4C-5)$$

From Eq. 4C-5,

$$\omega = \sqrt{\omega_z \omega_p} \quad (4C-6)$$

which shows that the phase angle of the controller transfer function reaches its maximum at the geometric-mean frequency.

4C-1-2 Deriving the Zero and Pole Frequencies

Substituting Eq. 4C-4 into Eq. 4C-2,

$$\phi_{boost} = \tan^{-1} \frac{\sqrt{\omega_z \omega_p}}{\omega_z} - \tan^{-1} \frac{\sqrt{\omega_z \omega_p}}{\omega_p} \quad (4C-7)$$

or,

$$\phi_{boost} = \tan^{-1} \sqrt{\frac{\omega_p}{\omega_z}} - \tan^{-1} \sqrt{\frac{\omega_z}{\omega_p}} \quad (4C-8)$$

Note that $\tan^{-1} x = \cot^{-1} \left(\frac{1}{x} \right)$ and $\tan^{-1} y + \cot^{-1} y = \frac{\pi}{2}$. Therefore, in Eq. 4C-8

$$\phi_{boost} = \tan^{-1} \sqrt{\frac{\omega_p}{\omega_z}} - \left(\frac{\pi}{2} - \tan^{-1} \sqrt{\frac{\omega_p}{\omega_z}} \right) = 2 \tan^{-1} \sqrt{\frac{\omega_p}{\omega_z}} - \frac{\pi}{2} \quad (4C-9)$$

We will define an intermediate variable, called the K-factor, as

$$K_{boost} = \sqrt{\frac{\omega_p}{\omega_z}} \quad (4C-10)$$

Solving Eqs. 4C-9 and 4C-10

$$K_{boost} = \tan \left(\frac{\phi_{boost}}{2} + \frac{\pi}{2} \right) \quad (4C-11)$$

or,

$$K_{boost} = \tan \left(\frac{\phi_{boost}}{2} + 45^\circ \right) \quad (4C-12)$$

4C-1-2 Realizing the Controller Transfer Function with a Single Op-Amp

The controller transfer function in Eq. 4C-1 can be realized by a single op-amp, as derived below.

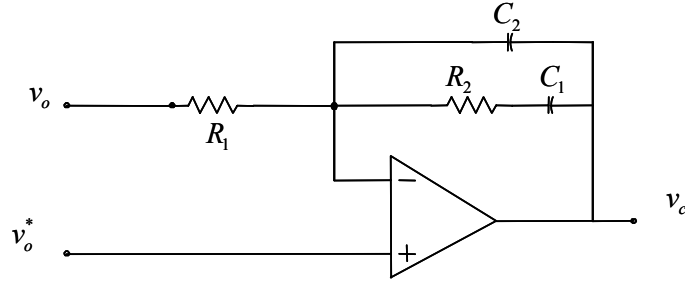


Figure 4C-1 Implementation of the controller transfer function in Eq. 4C-1.

In Fig. 4C-1, we can derive that

$$\begin{aligned}
 k_c &= \frac{1}{R_1(C_1 + C_2)} \\
 \omega_z &= \frac{1}{C_1 R_2} \\
 \omega_p &= \frac{C_1 + C_2}{R_2 C_1 C_2}
 \end{aligned} \tag{4C-13}$$

From Eq. 4C-13, in terms of R_1

$$\begin{aligned}
 C_2 &= \frac{\omega_z}{\omega_p R_1 k_c} \\
 C_1 &= C_2 (\omega_p / \omega_z - 1) \\
 R_2 &= 1/(\omega_z C_1)
 \end{aligned} \tag{4C-14}$$

4C-2 CONTROLLER TRANSFER FUNCTION WITH TWO POLE-ZERO PAIRS

A similar derivation can be carried out where,

$$G_c(s) = k_c \frac{(1 + s/\omega_z)^2}{(1 + s/\omega_p)^2} \tag{4C-15}$$