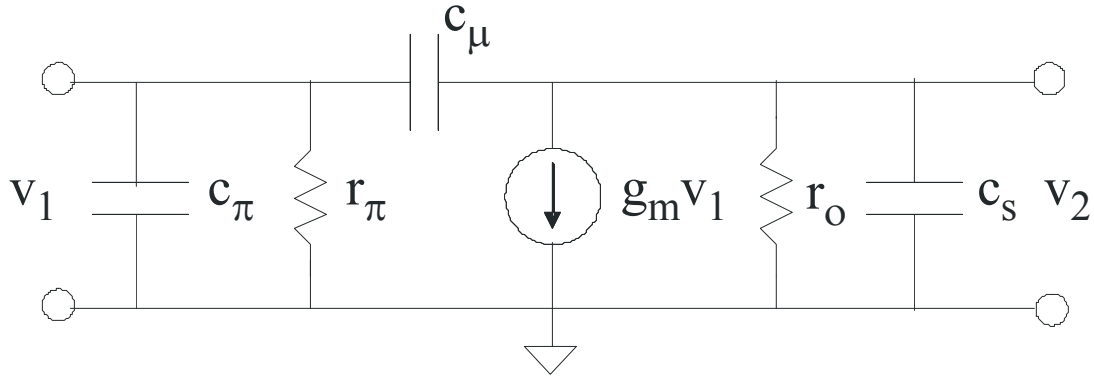


Question 1(a) 14 marks



$$y_{11} = \left. \frac{i_1}{v_1} \right|_{v_2=0} \quad y_{21} = \left. \frac{i_2}{v_1} \right|_{v_2=0} \quad y_{12} = \left. \frac{i_1}{v_2} \right|_{v_1=0} \quad y_{22} = \left. \frac{i_2}{v_2} \right|_{v_1=0}$$

Applying the y-parameter definitions to the above circuit and performing the circuit analysis under the appropriate conditions gives:

$$y_{11} = \frac{1}{r_\pi} + j\omega(c_\pi + c_\mu)$$

$$y_{12} = -j\omega c_\mu$$

$$y_{21} = g_m - j\omega c_\mu$$

$$y_{22} = \frac{1}{r_o} + j\omega(c_s + c_\mu)$$

Question 1(a) continued

The equations on the previous page have to be manipulated to give the small signal-element values as follows:

$$g_m = \mathbf{Re}(y_{21}) = 0.15S$$

$$r_\pi = \frac{1}{\mathbf{Re}(y_{11})} = 250\Omega$$

$$r_o = \frac{1}{\mathbf{Re}(y_{22})} = 1.5k\Omega$$

$$c_\mu = \frac{-\mathbf{Im}(y_{12})}{2\pi f} = 0.7pF$$

$$c_\pi = \frac{\mathbf{Im}(y_{11})}{2\pi f} - c_\mu = 4.5pF$$

$$c_s = \frac{\mathbf{Im}(y_{22})}{2\pi f} - c_\mu = 0.3pF$$

Question 1(b) 6 marks

$$V_T = \frac{kT}{q} = 25.9mV$$


$$(i) \quad I_C = g_m V_T = 3.9mA$$

$$(ii) \quad V_A = r_o I_C = 5.82V$$

$$(iii) \quad \beta = g_m r_\pi = 37.5$$

$$(iv) \quad f_T = \frac{g_m}{2\pi(c_\pi + c_\mu)} = 4.59GHz$$

Question 2(a) 8 marks

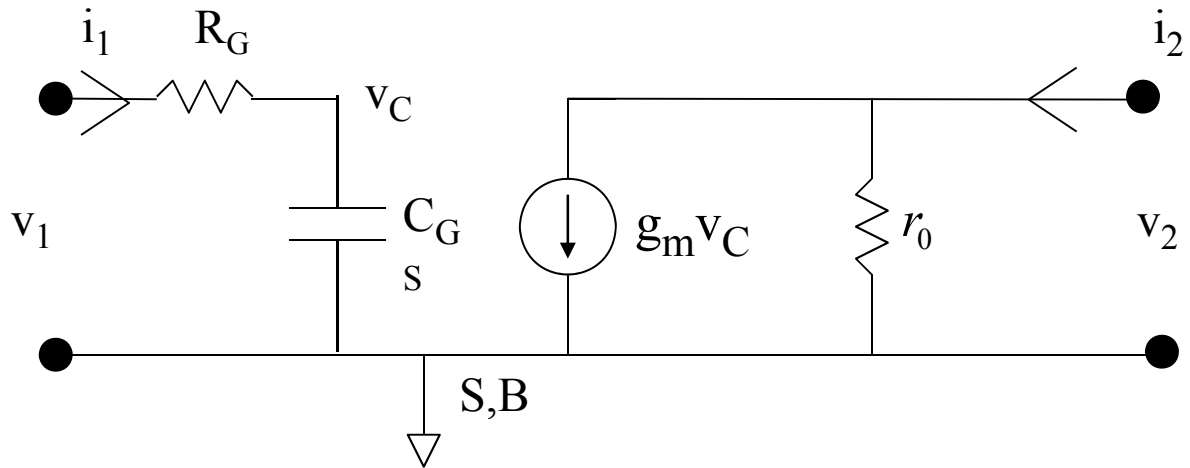

Applying the z-parameter definitions to the above circuit and performing the circuit analysis under the appropriate conditions gives:

$$z_{11} = \left. \frac{v_1}{i_1} \right|_{i_2=0} = R_G + \frac{1}{j\omega C_{GS}}$$

$$z_{21} = \left. \frac{v_2}{i_1} \right|_{i_2=0} = -\frac{g_m r_o}{j\omega C_{GS}}$$

$$z_{12} = \left. \frac{v_1}{i_2} \right|_{i_1=0} = 0$$

$$z_{22} = \left. \frac{v_2}{i_2} \right|_{i_1=0} = r_o$$

Question 2(b) 8 marks

$$C'_{OX} = \frac{\epsilon_{OX}}{T_{OX}} \quad V_{DS} > (V_{GS} - V_{TH}) \text{ so MOSFET in saturation}$$

For a MOSFET in saturation:

$$I_{DS} = \frac{1}{2} \frac{W}{L} \mu C'_{OX} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$g_m = \frac{W}{L} \mu C'_{OX} (V_{GS} - V_{TH}) = \sqrt{2 \frac{W}{L} \mu C'_{OX} I_{DS}}$$

$$g_{ds} = \frac{1}{r_o} \frac{1}{2} \frac{W}{L} \mu C'_{OX} (V_{GS} - V_{TH})^2 \lambda$$

$$C_{GS} = \frac{2}{3} W L C'_{OX}$$

Doing the calculations and inserting these values into the previous formulas for the z-parameters at 1GHz gives:

$$z_{11} = 987.7 \angle -89.4^\circ \quad z_{12} = 0 \quad z_{21} = 13929 \angle 90^\circ \quad z_{22} = 100 \angle 0^\circ$$

(c) 4 marks

Gate resistance with parallel layout and gate contacted at both sides.

$$R_{Geff} = \frac{R_G}{4N^2} = \frac{10}{4 \times 25} = 0.1 \Omega$$

Question 3


3(a) 3 marks

$$\text{Noise Figure, NF} = 10 \log_{10} \left(\frac{SNR_{in}}{SNR_{out}} \right) \quad (\text{in dB, } \geq 0)$$


$$SNR_{in} = (\text{signal power in})/(\text{noise power in})$$

$$SNR_{out} = (\text{signal power out})/(\text{noise power out})$$

3(b) 7 marks

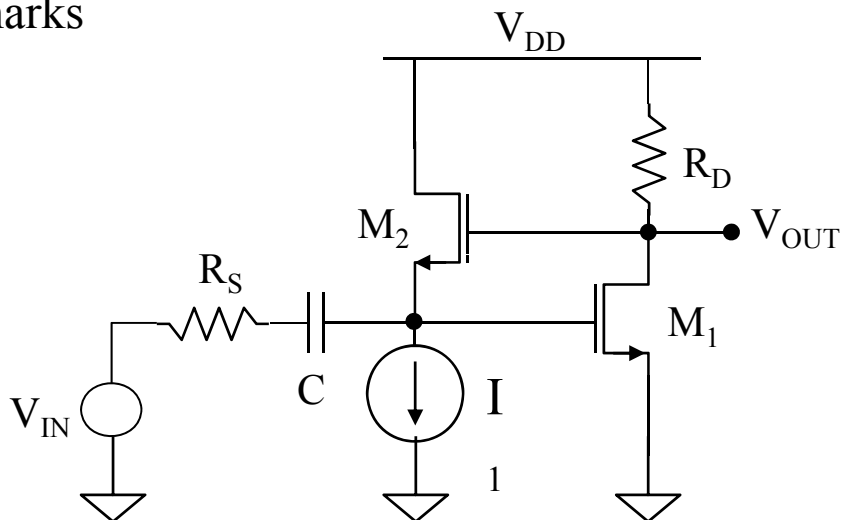

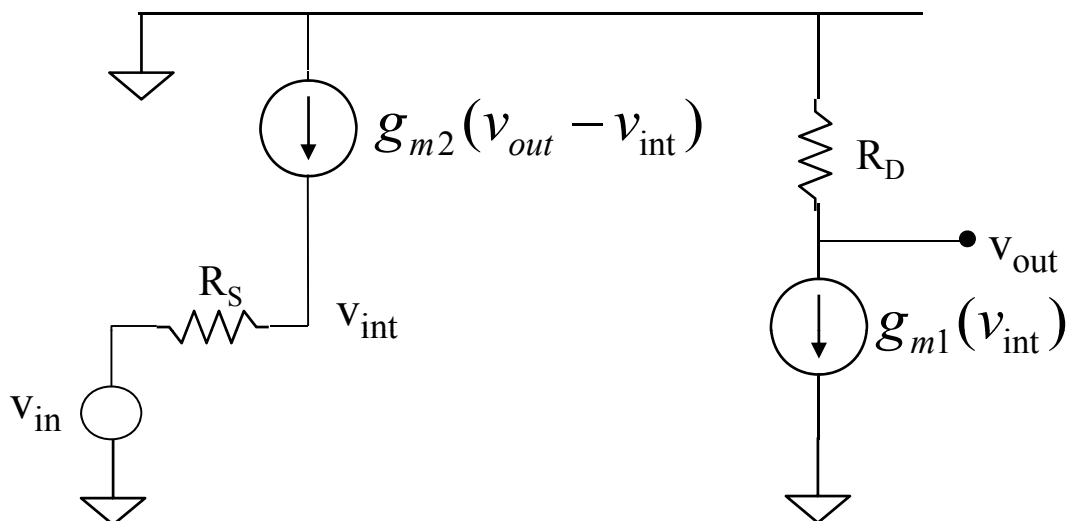Using all the assumptions stated in the question, the circuit to calculate the small-signal gain is as follows:



Question 3(b) continued

Going through the small-signal analysis of the circuit on the previous page will produce the formulas for output voltage and circuit gain:

$$v_{out} = -R_D g_{m1} \frac{v_{in}}{1 + R_S g_{m2} (1 + R_D g_{m1})}$$

$$v_{out} = -R_D g_{m1} \frac{v_{in}}{1 + R_S g_{m2} (1 + R_D g_{m1})}$$

$$A = \frac{v_{out}}{v_{in}} = -\frac{R_D g_{m1}}{1 + R_S g_{m2} (1 + R_D g_{m1})}$$

3(c)

The noise contributed by is the source resistance R_S is

$$v_{n,in}^2 = 4kTR_S \quad v^2 / Hz$$

The signal to noise ratio at the input in then:

$$SNR_{in} \frac{v_{in}^2}{v_{n,in}^2} = \frac{v_{in}^2}{4kTR_S}$$

To calculate the SNR at the output, the total noise at the output from both R_S and R_D have to be calculated. The output noise from the source resistance can be calculated just assuming the source resistance is a normal input voltage source i.e.


$$(v_{n,out}^2)_{RS} = A^2 4kTR_S$$

Similarly the signal power at the output can be calculated from the gain of the circuit:

$$v_{out}^2 = A^2 v_{in}^2$$

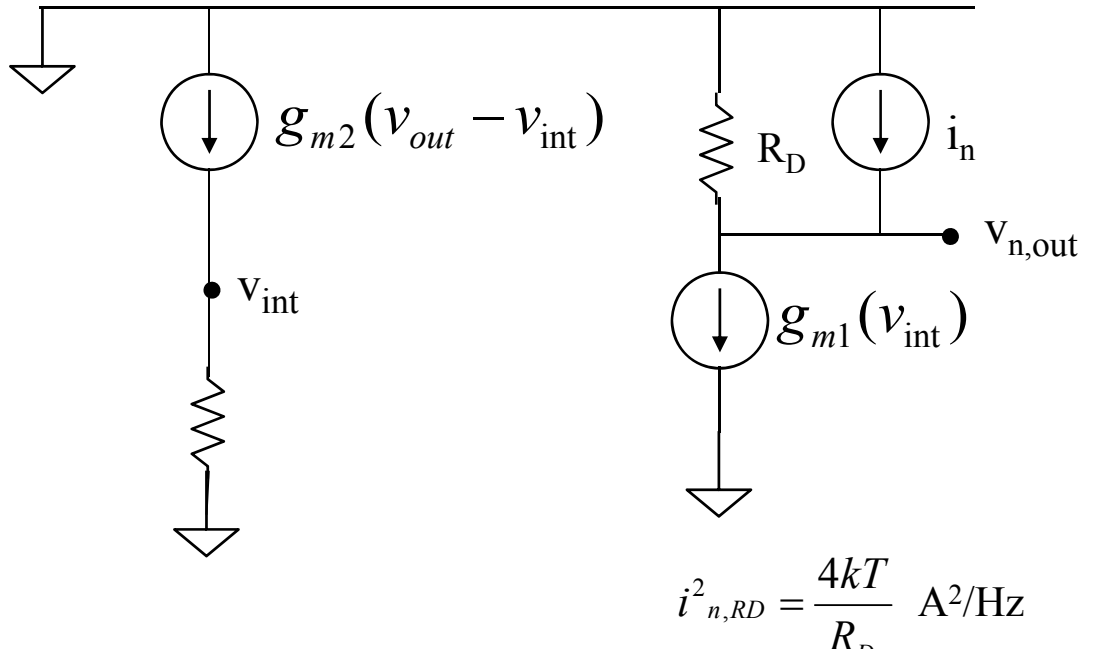Question 3(c) continued

To calculate the noise contributed at the output from R_D , a new circuit analysis has to be performed assuming the noise current from R_D is the only signal supplied in the circuit.



Working through the small-signal analysis of this circuit gives the Output voltage noise caused by R_D as:

$$\left(v_{n,out}^2\right)_{RD} = \frac{4kT / R_D}{\left(\frac{1}{R_D} + \frac{g_{m1}R_S g_{m2}}{1 + R_S g_{m2}}\right)}$$

The total o/p noise is then

$$v_{n,out}^2 = \left(v_{n,out}^2\right)_{RS} + \left(v_{n,out}^2\right)_{RD} = A^2 4kTR_S + \frac{4kT / R_D}{\left(\frac{1}{R_D} + \frac{g_{m1}R_S g_{m2}}{1 + R_S g_{m2}}\right)}$$


$$SNR_{out} = \frac{v_{out}^2}{v_{n,out}^2} \quad F = \frac{SNR_{in}}{SNR_{out}}$$

As the expressions which include output noise are cumbersome the final three expressions with those on the previous page will be accepted as the answer.

Question 4

The matching transformations and calculations give the matching network shown on the next page (15 marks)

Question 4(b) continued

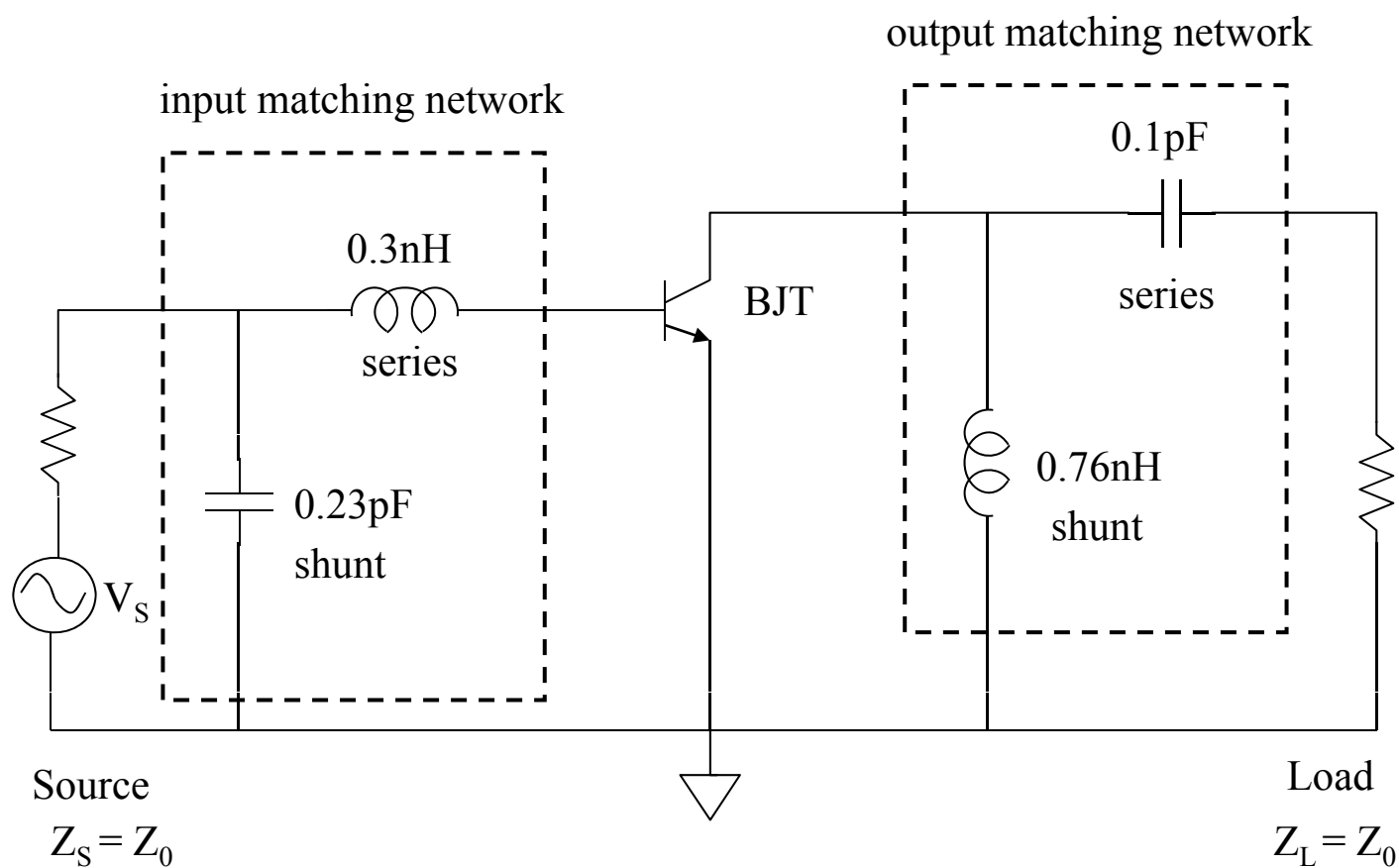


Question 5 concerns derivations from the notes

Question 6

6(a) 5 marks

Suitable PD with transfer function

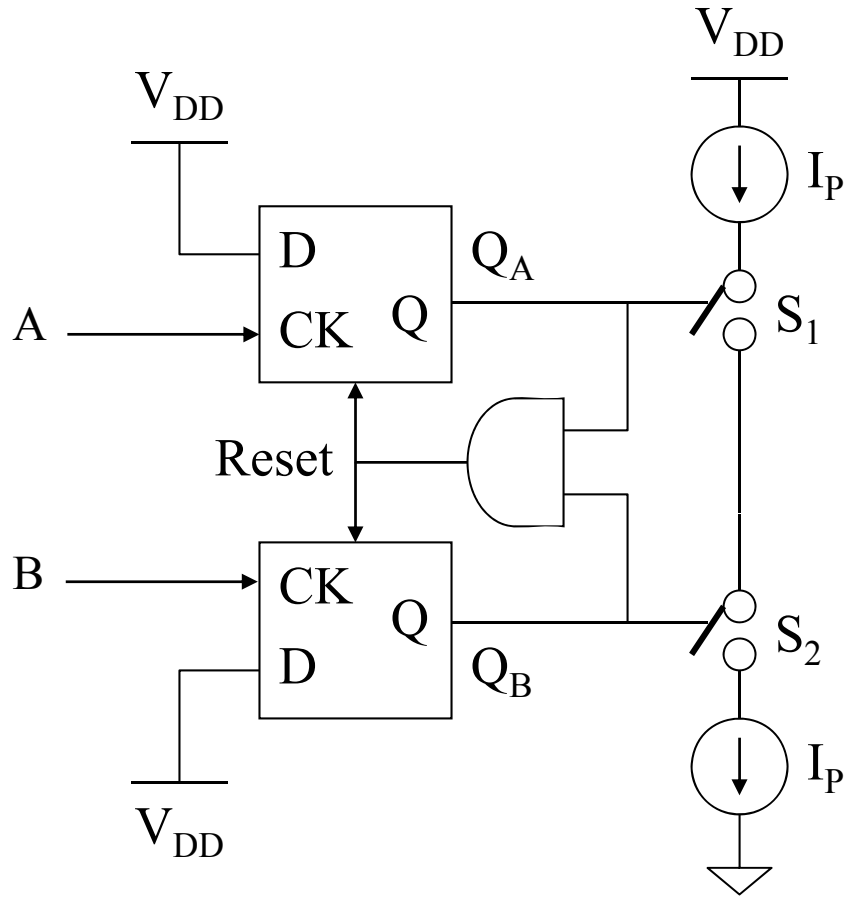

$$I(s) = \frac{I_P}{2\pi} \Delta \phi(s)$$

(b) The control voltage is given by:

$$V_C(s) = \frac{I_P}{2\pi} \left(\frac{R_P C_P s + 1}{(R_P C_P C_2 s + C_P + C_2)s} \right) \Delta \phi(s)$$

The transfer function is found from this through a closed loop analysis.

Q6(c) concerns production of clock phases from the notes

Q7 This is an essay type question based on a continuous assessment assignment.