

Name:

Student Number:

1. What are the *disadvantages* of switch-mode power electronics amplifiers compared to linear amplifiers?

2. Express the Pole A duty ratio, d_A , in terms of the control voltage, $v_{c,A}$ and the peak of the triangular voltage, $V_{tri, pk}$.

3. In a two-quadrant single-pole converter of dc bus voltage $V_d=100\text{V}$, fed by a **generator** of back emf $E_a=45\text{V}$ and armature resistance $R_a=0.25\ \Omega$, calculate the output pole voltage V_{AN} and the duty ratio d_A when pulling an armature current $I_a=20\text{A}$.

4. In a four-quadrant two-pole converter of dc bus voltage $V_d=100\text{V}$, supplied by a **generator** of back emf $E_a=-75\text{V}$ (spinning in reverse) and armature resistance $R_a=0.5\ \Omega$, calculate the output pole voltage V_{AB} and the duty ratio d when pulling an armature current $I_a=10\text{A}$.

5. Calculate the peak-peak armature current ripple in the above generating question when armature inductance $L_a=1\text{mH}$ and the triangular frequency $f_{tri}=10\text{ kHz}$?

6. Sketch a synchronous buck converter.

7. A buck converter, switching at 1 MHz, powers a 1.5 V, 100 mA microprocessor from 3.0 V. Calculate the inductance required to limit the current ripple to $\pm 10\%$.
8. Calculate the capacitance required in the above converter to reduce the output voltage ripple to ± 20 mV.
9. What are the peak and rms currents in the above inductor?
10. What are the rms currents in the controlled switch and the input capacitor on the 3V dc bus?
11. A three-phase sinusoidal PWM inverter is required to output 400 V line-line. What is the minimum dc bus voltage required?
12. A sinusoidal PWM full bridge inverter is required to output single phase 100 V in Japan. What is the minimum dc bus voltage required?