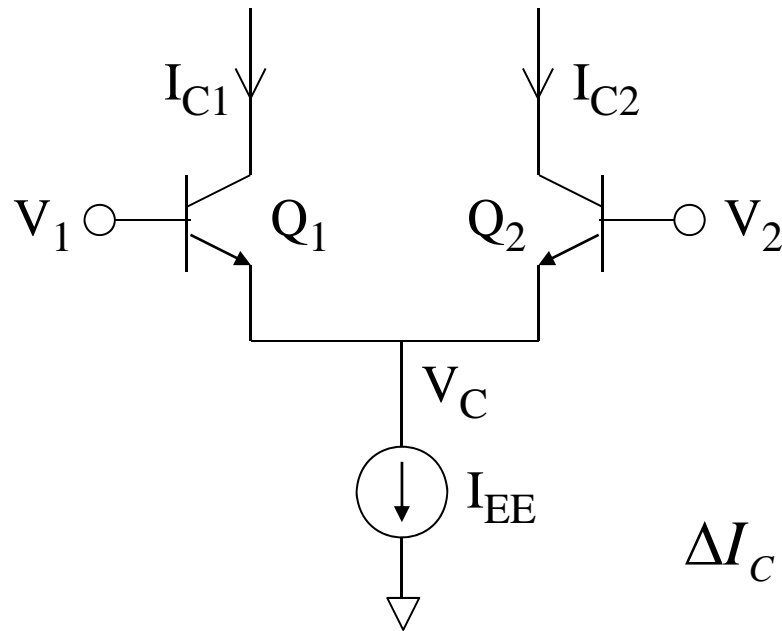


EE4011 RFIC

Common-Emitter Pairs and Dynamic Range

Another Look at the Emitter Coupled Pair



$$V_d = V_1 - V_2$$

$$\Delta I_C = I_{EE} \tanh\left(\frac{V_d}{2V_T}\right)$$


If V_d is small then because of the behaviour of $\tanh(x)$ for small x :

$$\Delta I_C = I_{EE} \tanh\left(\frac{V_d}{2V_T}\right) \approx I_{EE} \frac{V_d}{2V_T} = \frac{I_{EE}}{2V_T} V_d$$

i.e. the differential output current is linearly proportional to the differential input voltage

Common Emitter Pair – Small Signal (1)

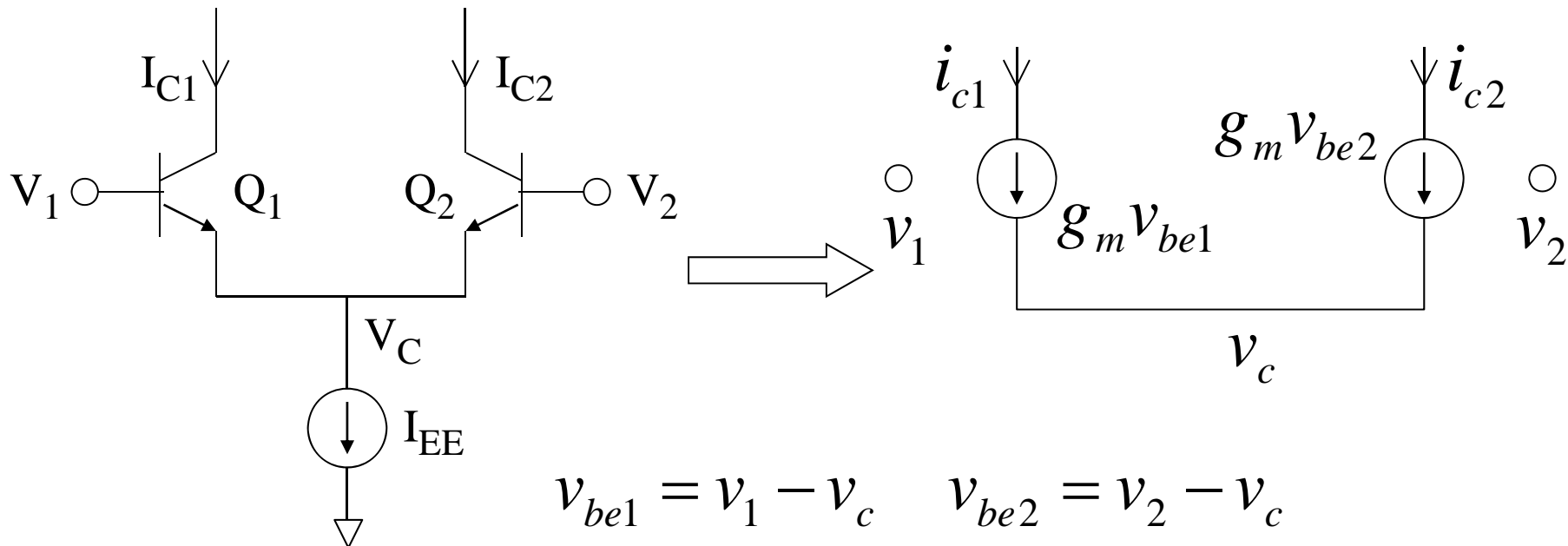Small-signal: Q1/Q2 replaced by transconductances. Ignoring i/p resistance and output conductance for simplicity. Current source is a small-signal “open”:




$$v_{be1} = v_1 - v_c \quad v_{be2} = v_2 - v_c$$

$$v_{be1} - v_{be2} = v_1 - v_2 = \delta v$$


$$i_{c1} - i_{c2} = g_m v_{be1} - g_m v_{be2} = g_m \delta v$$

Common Emitter Pair – Small Signal (2)

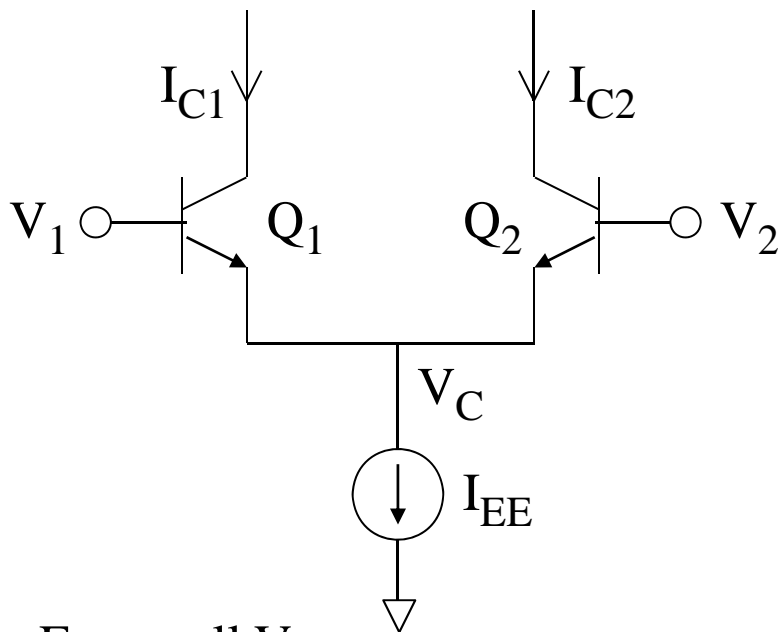

For small V_d :

$$\Delta I_C = \frac{I_{EE}}{2V_T} V_d$$

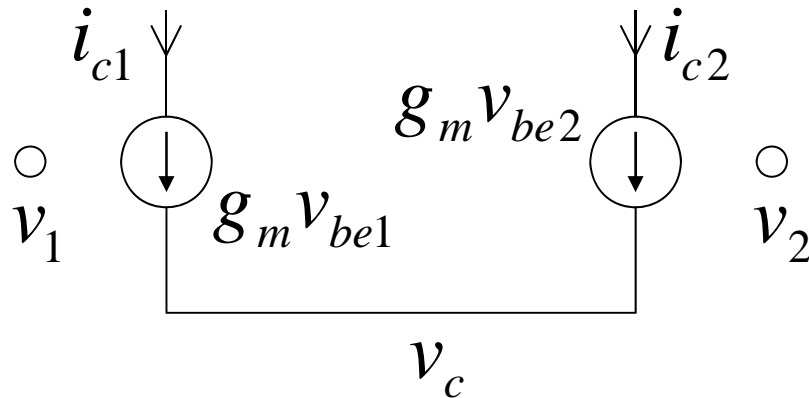


$$\delta i_c = i_{c1} - i_{c2} = g_m \delta v$$

$$g_m = \frac{I_C}{V_T} = \frac{I_{EE}}{2V_T} \Rightarrow \delta i_c = \frac{I_{EE}}{2V_T} \delta v$$


(assuming the DC biases V_1 and V_2 are the same, I_{EE} is shared equally by Q_1 and Q_2)

The large-signal analysis gives the same results as the small-signal analysis if the input differential voltage is made small in the large-signal analysis – this is a reassuring consistency check.

Common Emitter Pair – Symmetry Property

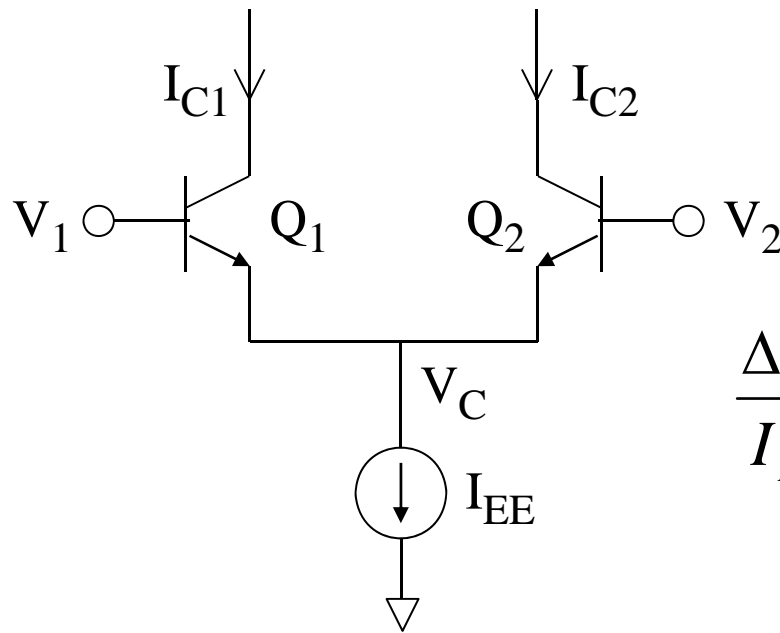
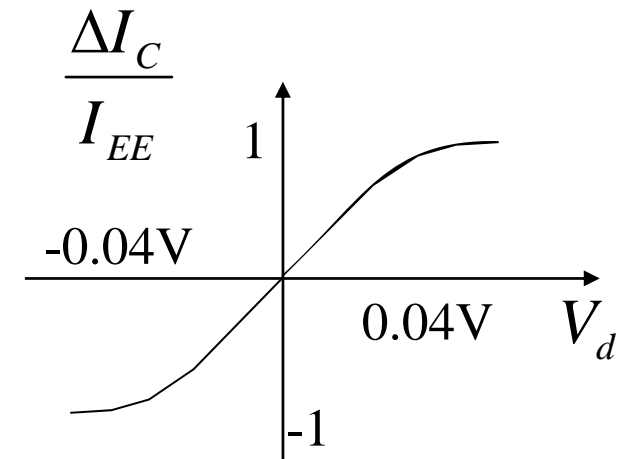
$$\frac{\Delta I_C}{I_{EE}} = \tanh\left(\frac{V_d}{2V_T}\right)$$



$$\tanh(x) = x - \frac{x^3}{3} + \frac{2x^5}{15} - \frac{17x^7}{315} + \dots = \sum_{n=1}^{\infty} \frac{(-1)^{n-1} 2^{2n} (2^{2n} - 1) B_n x^{2n-1}}{(2n)!}, |x| < \frac{\pi}{2}$$

B_n is the Bernoulli number n .


This is a typical balanced or differential system encountered in RF systems. All the even order terms in the transfer function are zero. Also, the system is compressive i.e. the coefficient of x^3 has the opposite sign to the coefficient of x . These could be used to find the 1dB compression point of the system.

Common Emitter Pair – Transconductance



$$\frac{d}{dx} \tanh(x) = \text{sech}^2(x)$$

$$\Delta I_C = I_{EE} \tanh\left(\frac{V_d}{2V_T}\right) \Rightarrow g_m = \frac{d\Delta I_C}{dV_d} = \frac{I_{EE}}{2V_T} \text{sech}^2\left(\frac{V_d}{2V_T}\right)$$

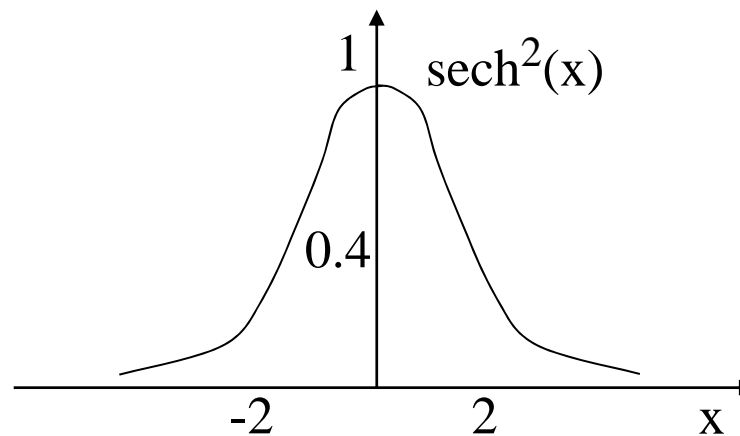When $V_d=0$: $g_m = \frac{I_{EE}}{2V_T} \text{sech}^2(0) = \frac{I_{EE}}{2V_T}$ as expected




Common Emitter Pair – Dynamic Range

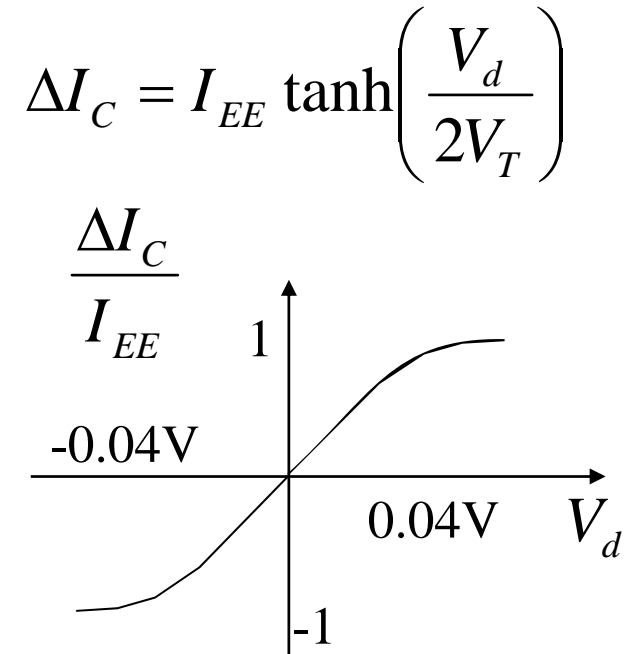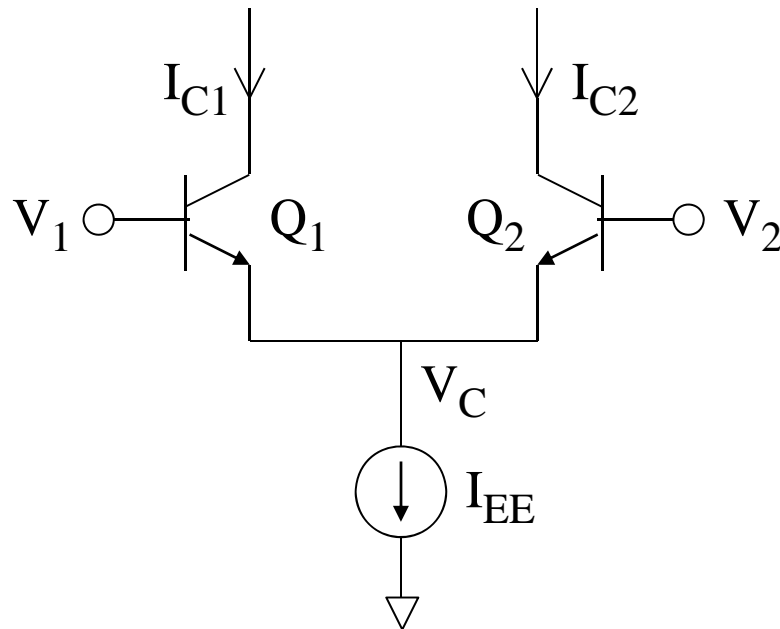

The linear range of the standard common emitter pair is not very large – when the differential input voltage exceeds about 40mV (at 300K) the output characteristic deviates strongly from a linear response. Various techniques are used to increase the dynamic range of common emitter pairs for both amplifiers and mixers – these are mainly based on the use of emitter degeneration resistors or cross coupled pairs (Schmoock's method) or both.

Emitter-Coupled Pair: Different Emitter Areas (1)

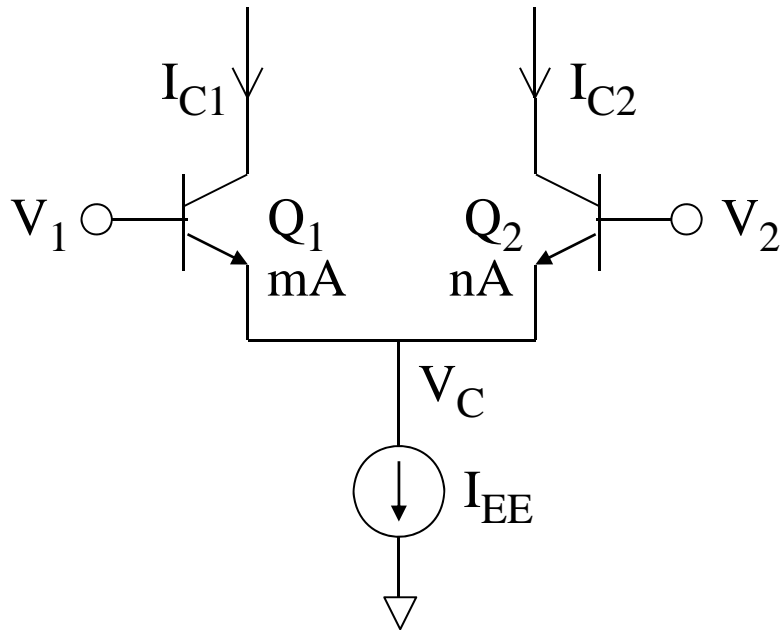The transistors emitter areas are multiples of a unit size A.



$$I_{C1} = mI_s e^{\frac{V_1 - V_C}{V_T}}, \quad I_{C2} = nI_s e^{\frac{V_2 - V_C}{V_T}}$$

$$\frac{I_{C1}}{I_{C2}} = \frac{mI_s e^{\frac{V_1 - V_C}{V_T}}}{nI_s e^{\frac{V_2 - V_C}{V_T}}} = \frac{m}{n} e^{\frac{V_1 - V_2}{V_T}} = r e^{\frac{V_d}{V_T}}$$

$$V_d = V_1 - V_2, \quad r = \frac{m}{n}$$

$$\Rightarrow \frac{I_{C2}}{I_{C1}} = \frac{1}{r} e^{-\frac{V_d}{V_T}}$$

Emitter-Coupled Pair: Different Emitter Areas (2)

$$I_{C1} + I_{C2} = I_{EE} \Rightarrow I_{C1} \left(1 + \frac{I_{C2}}{I_{C1}} \right) = I_{EE} \Rightarrow I_{C1} = \frac{I_{EE}}{1 + \frac{I_{C2}}{I_{C1}}} = \frac{I_{EE}}{1 + \frac{1}{r} e^{-\frac{V_d}{V_T}}}$$

$$I_{C1} + I_{C2} = I_{EE} \Rightarrow I_{C2} \left(1 + \frac{I_{C1}}{I_{C2}} \right) = I_{EE} \Rightarrow I_{C2} = \frac{I_{EE}}{1 + \frac{I_{C1}}{I_{C2}}} = \frac{I_{EE}}{1 + r e^{\frac{V_d}{V_T}}}$$

$$\Delta I = I_{C1} - I_{C2} = I_{EE} \left(\frac{1}{1 + \frac{1}{r} e^{-\frac{V_d}{V_T}}} - \frac{1}{1 + r e^{\frac{V_d}{V_T}}} \right) = I_{EE} \left(\frac{r e^{\frac{V_d}{V_T}}}{r e^{\frac{V_d}{V_T}} + 1} - \frac{1}{1 + r e^{\frac{V_d}{V_T}}} \right)$$

$$\Delta I = I_{EE} \left(\frac{r e^{\frac{V_d}{V_T}} - 1}{r e^{\frac{V_d}{V_T}} + 1} \right) \quad (\text{ignoring base current as before})$$


Emitter-Coupled Pair: Different Emitter Areas (3)

$$\Delta I = I_{EE} \left(\frac{re^{\frac{V_d}{V_T}} - 1}{re^{\frac{V_d}{V_T}} + 1} \right)$$

The current in the two transistors is the same when $\Delta I = 0$ i.e.

$$\Delta I = 0 \Rightarrow re^{\frac{V_d}{V_T}} - 1 = 0 \Rightarrow e^{\frac{V_d}{V_T}} = \frac{1}{r} \Rightarrow V_d = -V_T \ln(r)$$

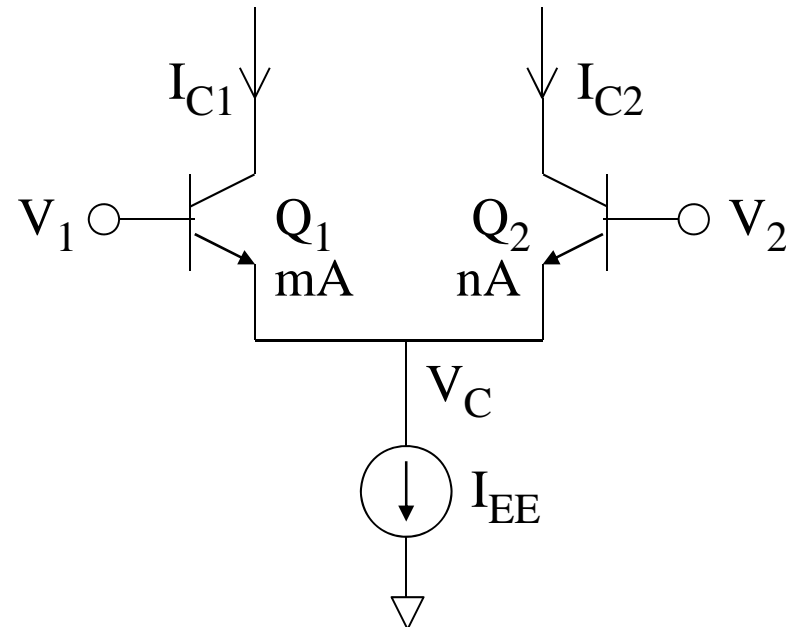So the transfer characteristic can be moved left or right by choosing r . If $r > 1$ (i.e. $m > n$) V_d is negative, if $r < 1$ (i.e. $n > m$) V_d is positive and if $r = 1$ ($m = n$) V_d is zero.



Emitter-Coupled Pair: Different Emitter Areas (4)

$$\Delta I = I_{EE} \left(\frac{re^{\frac{V_d}{V_T}} - 1}{re^{\frac{V_d}{V_T}} + 1} \right) \quad \tanh\left(\frac{x}{2}\right) = \frac{e^x - 1}{e^x + 1}$$


$$\text{define } s = \ln(r) = \ln\left(\frac{m}{n}\right) \Rightarrow r = e^s$$

$$\Delta I = I_{EE} \left(\frac{re^{\frac{V_d}{V_T}} - 1}{re^{\frac{V_d}{V_T}} + 1} \right) = I_{EE} \left(\frac{e^s e^{\frac{V_d}{V_T}} - 1}{e^s e^{\frac{V_d}{V_T}} + 1} \right) = I_{EE} \left(\frac{e^{\left(\frac{V_d}{V_T} + s\right)} - 1}{e^{\left(\frac{V_d}{V_T} + s\right)} + 1} \right)$$


$$\Rightarrow \Delta I = I_{EE} \tanh\left(\frac{1}{2}\left(\frac{V_d}{V_T} + s\right)\right)$$

So the characteristic is a tanh function offset on the x-axis by an amount s
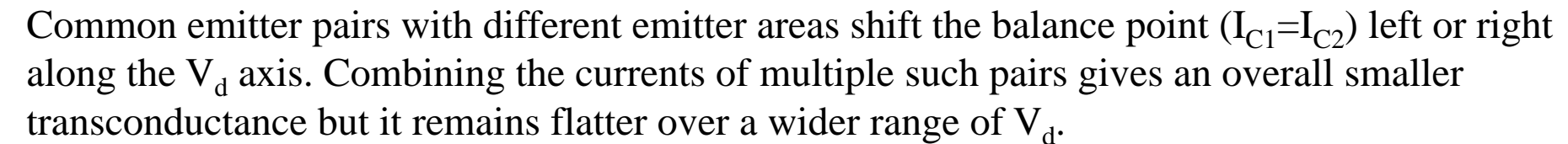
$$g_m = \frac{d\Delta I}{dV_d} = \frac{I_{EE}}{2V_T} \operatorname{sech}^2\left(\frac{1}{2}\left(\frac{V_d}{V_T} + s\right)\right)$$



A Version of Schmook's Circuit

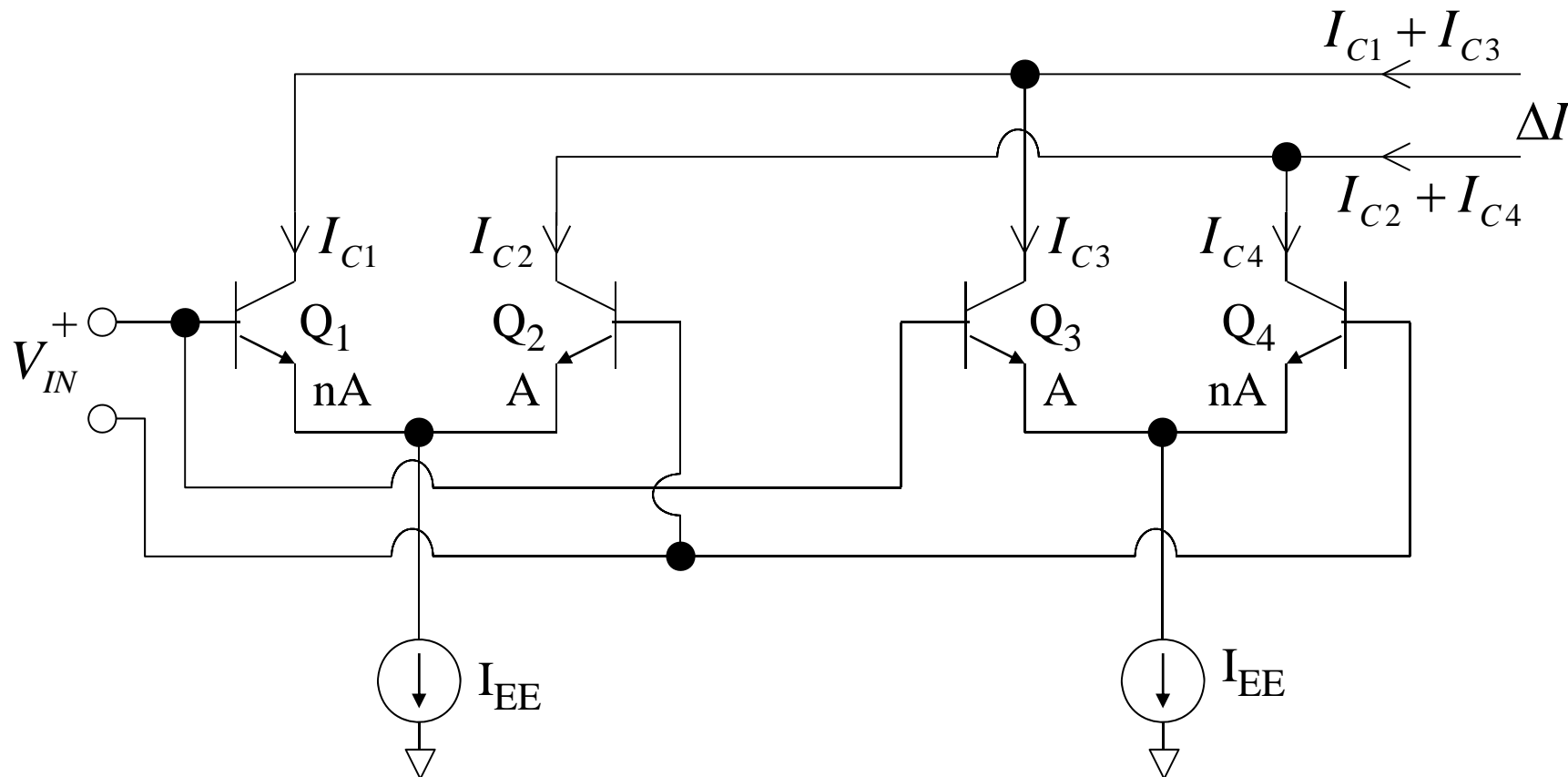


$$\Delta I = I_{C1} + I_{C3} - (I_{C2} + I_{C4}) = (I_{C1} - I_{C2}) + (I_{C3} - I_{C4})$$


$$g_m = \frac{d\Delta I}{dV_{IN}} = \frac{d(I_{C1} - I_{C2})}{dV_{IN}} + \frac{d(I_{C3} - I_{C4})}{dV_{IN}} = g_m|_{Q1, Q2} + g_m|_{Q3, Q4}$$

Schmook Circuit: Currents and g_m

$$I_{EE}=1\text{A}, n=4$$

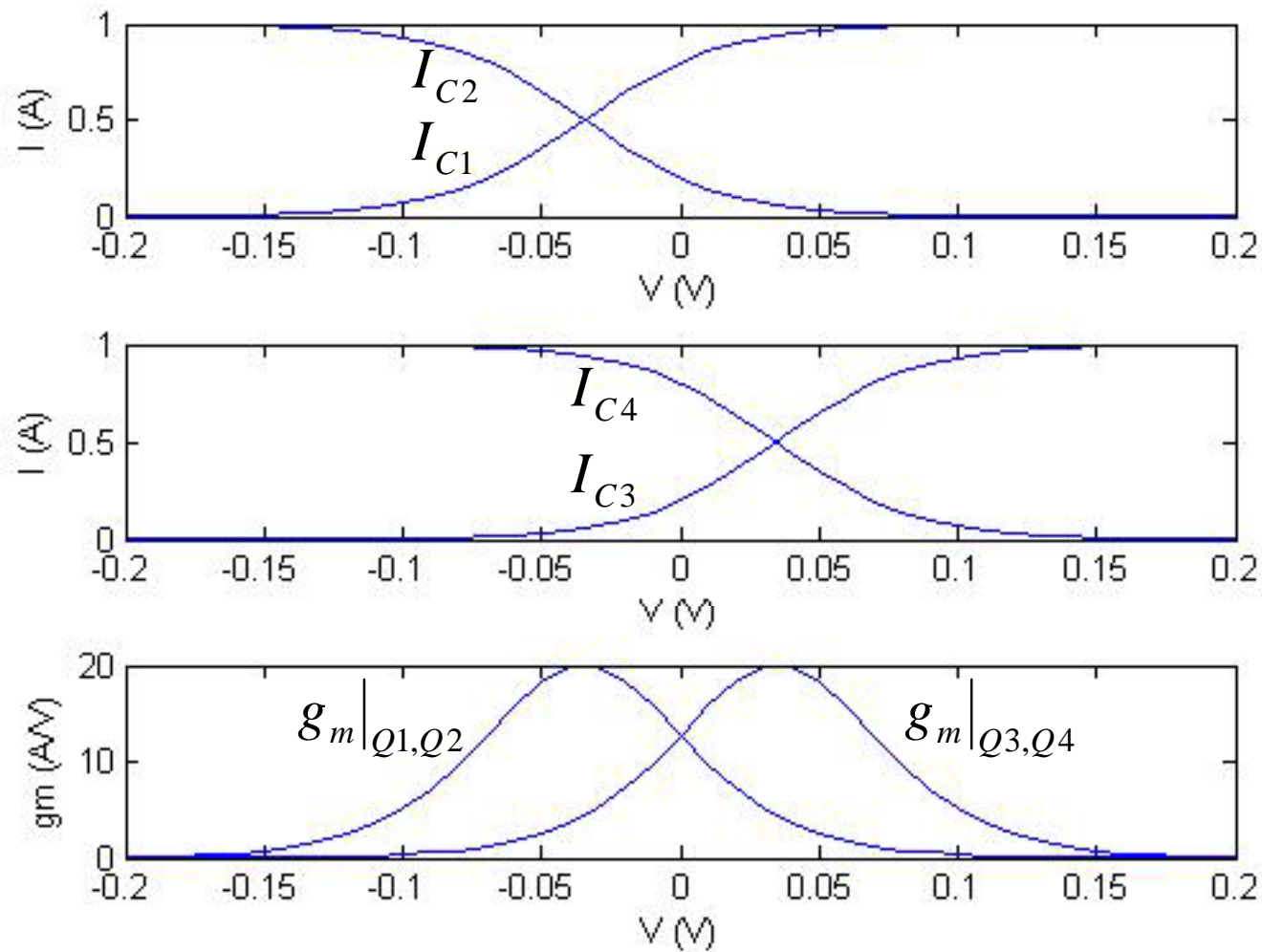


Total g_m from Schmook Circuit

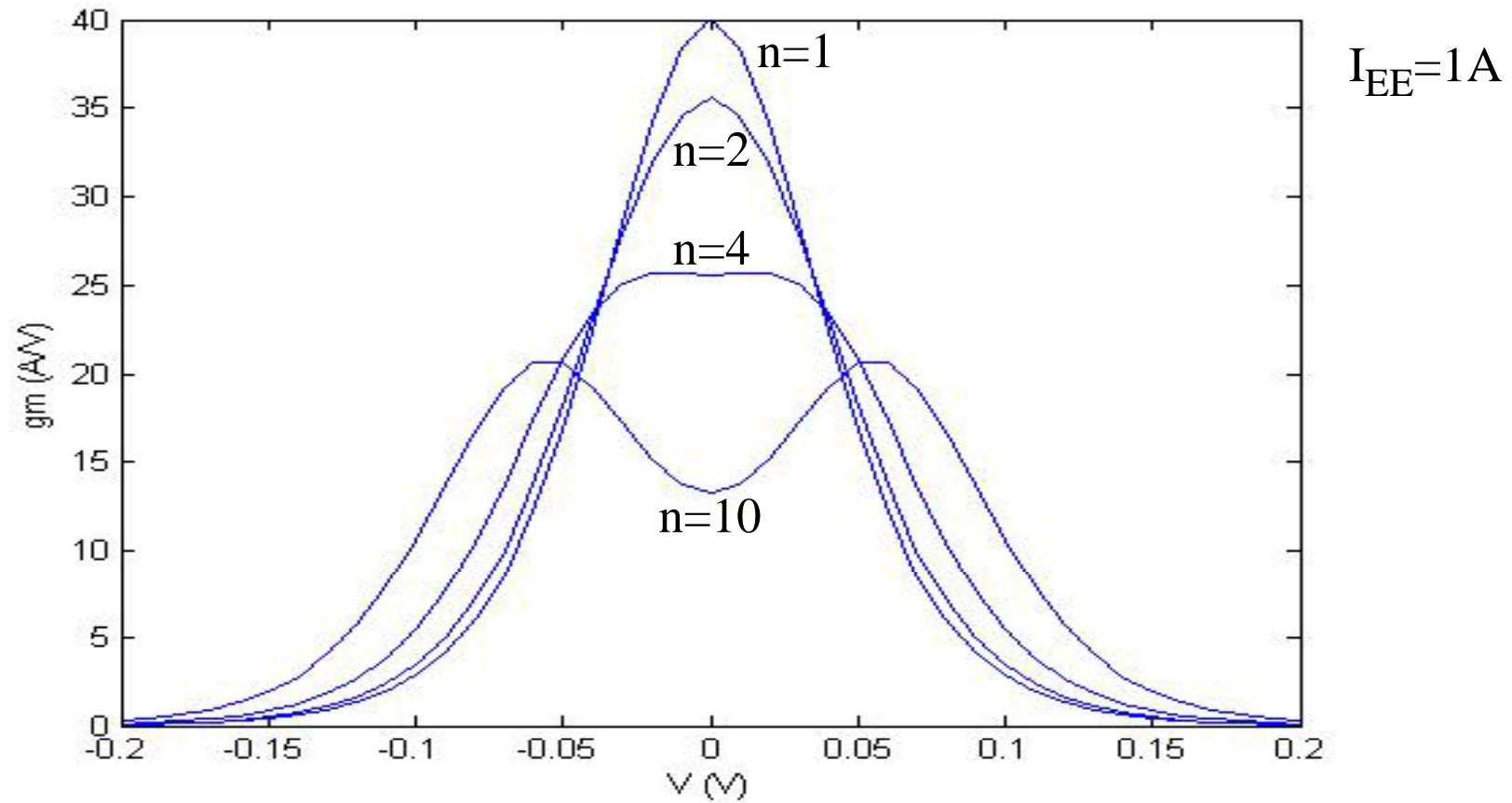

For $n=4$, the transconductance is flat over a “wide” range of V_{IN} (± 30 mV)

CE Pair with Emitter Degeneration Resistors

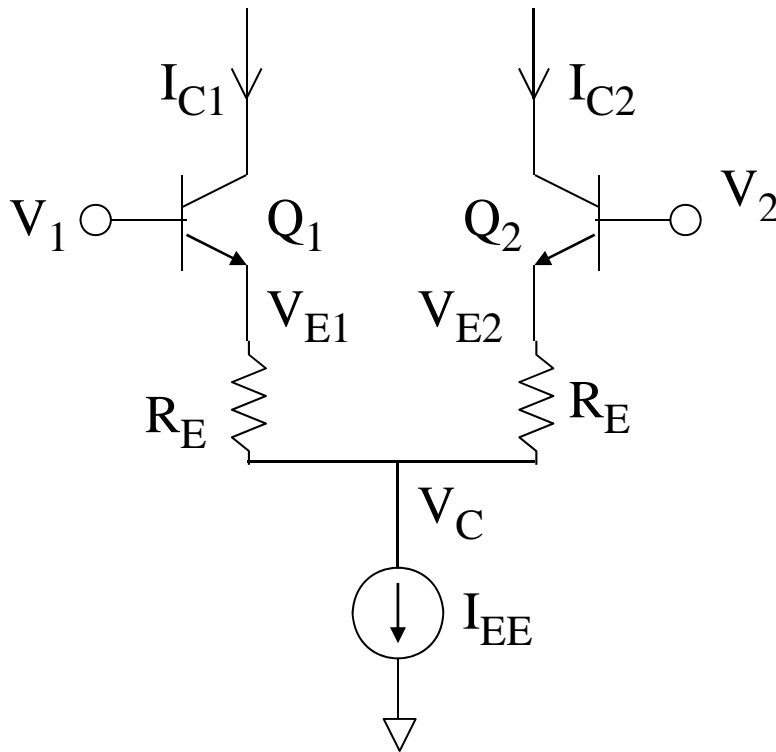same transistor areas
same emitter resistors



$$I_{C1} = I_S e^{\frac{V_1 - V_{E1}}{V_T}}, I_{C2} = I_S e^{\frac{V_2 - V_{E2}}{V_T}}$$

$$\Rightarrow \frac{I_{C1}}{I_{C2}} = e^{[(V_1 - V_2) - (V_{E1} - V_{E2})]/V_T}$$

$$V_{E1} = V_C + R_E I_{C1}, V_{E2} = V_C + R_E I_{C2}$$

$$\Rightarrow V_{E1} - V_{E2} = R_E \Delta I_C$$

$$\Rightarrow \frac{I_{C1}}{I_{C2}} = e^{(V_d - R_E \Delta I_C)/V_T}$$

This leads eventually to:


$$\Delta I_C = I_{EE} \tanh\left(\frac{V_d - R_E \Delta I_C}{2V_T}\right)$$

This is a non-linear equation in ΔI_C requiring a non-linear solution or circuit simulator. The general trend is to flatten out the transfer characteristic.

Effect of Degeneration Resistors

$$I_{EE}=1\text{mA}$$

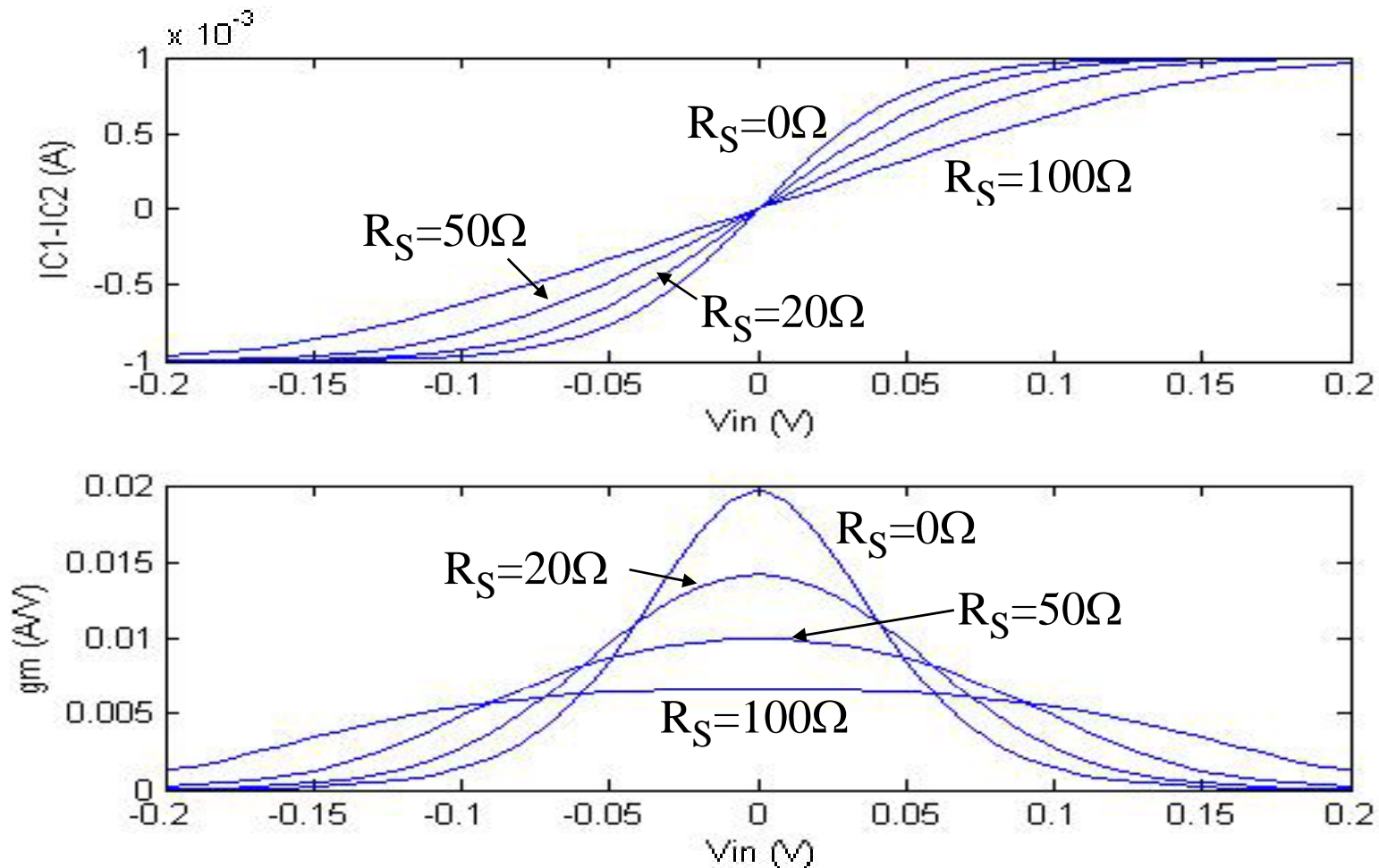Degeneration resistors give a wider and flatter dynamic range at the expense of overall transconductance (and gain).



If you're fascinated by common emitter pairs, see...

“An Input Stage Transconductance Reduction Technique for High-Slew Rate Operational Amplifiers”,

James. C. Schmoock,

IEEE Journal of Solid-State Circuits, Vol. SC-10, No. 6, Dec. 1975.

“The Multi-tanh Principle: A Tutorial Overview”,

Barrie Gilbert,

IEEE Journal of Solid-State Circuits, Vol. 33, No. 1, Jan. 1998.

Both are available from www.ieeeexplore.ieee.org