

Question 1

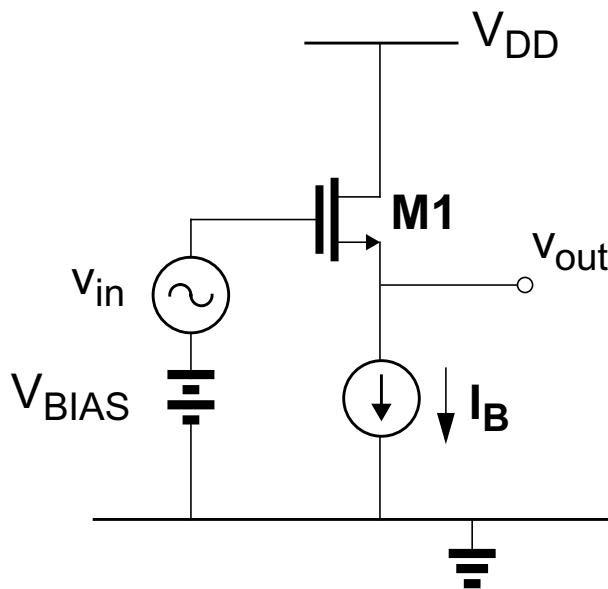


Figure 1

Assume M1 is operating in saturation and that $g_{m1} \gg g_{ds1}$.

I_B is an ideal current source

The body effect may be ignored in the analysis.

- (i) Draw the small signal model for the circuit shown in Figure 1. Ignore all capacitances.
- (ii) Derive an expression for the impedance at the output node.
- (iii) What is the low-frequency small signal voltage gain (v_{out}/v_{in})?
- (iv) The circuit shown in Figure 1 is required to drive a resistive load of $1k\Omega$. What is the requirement on g_{m1} if the small-signal attenuation of the stage is not to be greater than 6dB?

Question 2

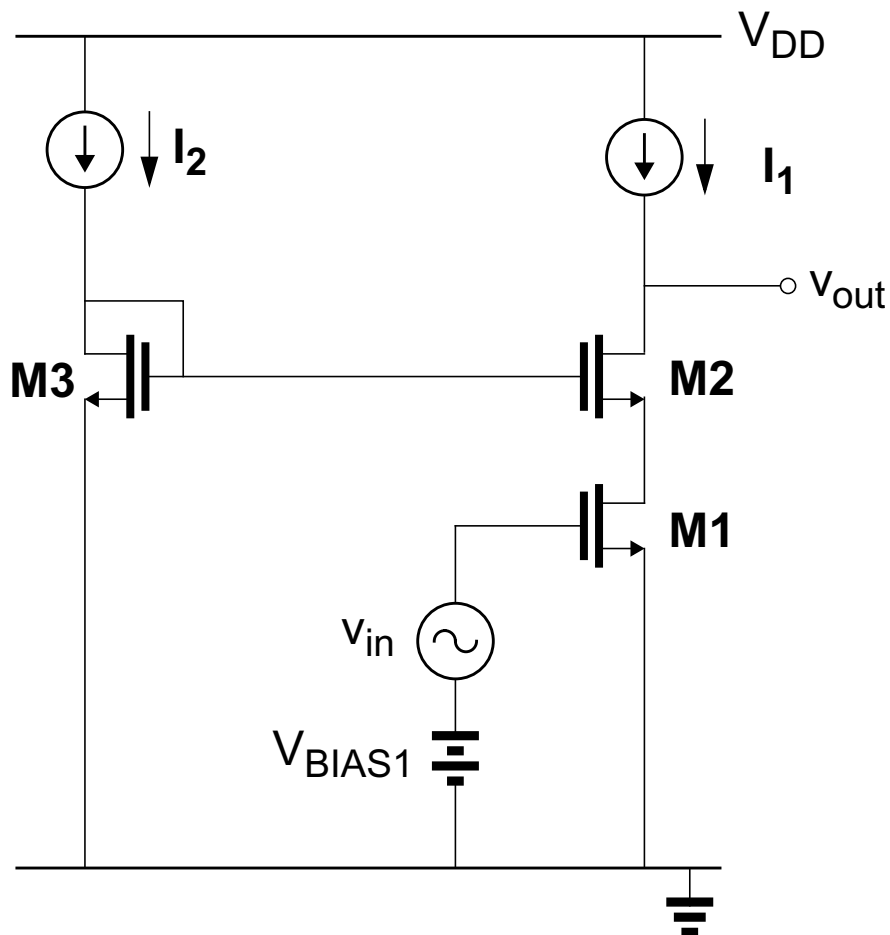



Figure 2

Figure 2 shows a cascode gain stage. I_1 and I_2 are ideal current sources.

For the questions below ignore the body effect.

- (i) Draw the small signal model for the circuit shown in Figure 2. Ignore all capacitances.
- (ii) The voltage gain of this stage can be approximated by $v_{out}/v_{in} = g_{m1}r_{out}$ where r_{out} is the impedance at the output node. Derive an expression for v_{out}/v_{in} in terms of the small signal transistor parameters. Reduce the expression to its simplest form assuming $g_{m1} = g_{m2} = g_{m3} = g_m$, $g_{ds1} = g_{ds2} = g_{ds3} = g_{ds}$, $g_m \gg g_{ds}$.
- (iii) The circuit is to be biased for optimal low-voltage operation. If $V_{BIAS1} = 1.25V$, $V_T = 1V$, $I_1 = 100\mu A$, $(W/L)_{M1} = (W/L)_{M2} = (W/L)_{M3} = 16\mu m/1\mu m$ calculate the minimum value of the voltage at the output node (i.e. at the drain of M2) for both M1 and M2 to be in saturation and the value of I_2 necessary to achieve this. Neglect λ for this calculation.
- (iv) For low power I_2 is changed to $40\mu A$. What value of $(W/L)_{M3}$ is required to preserve the bias conditions of M1 and M2.

Question 3

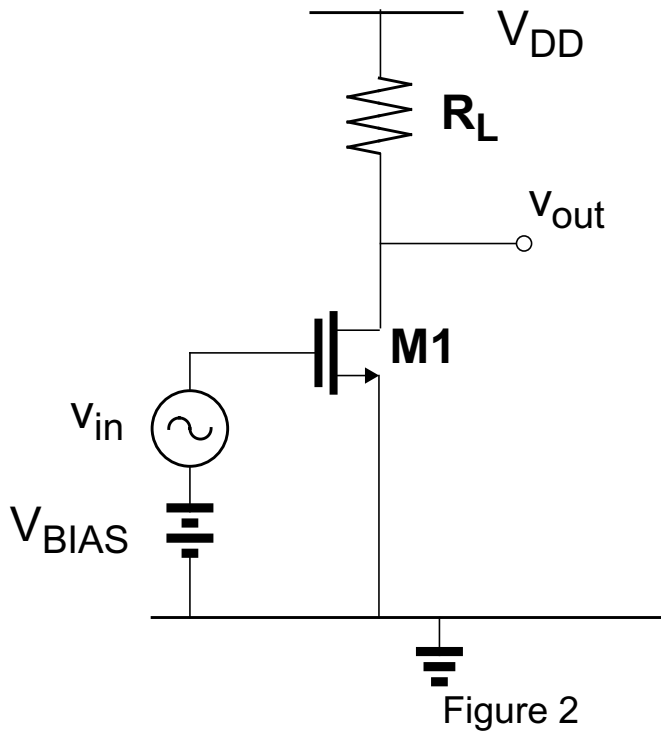


Assume M1 and M2 are operating in saturation and ignore the body effect.

Assume that $g_{m1} \gg g_{ds1}$

- (i) Draw the small signal model for the circuit shown in Figure 2. Ignore all capacitances. What is the low-frequency small signal voltage gain (v_{out}/v_{in})?
- (ii) What is the input-referred thermal noise in terms of R_L , the small signal parameters of M1 and M2, Boltzmann's constant k and temperature T ?
- (iii) If a capacitor C_L is connected between the output node and ground what is the total integrated thermal noise at the output node?

You may assume the following:

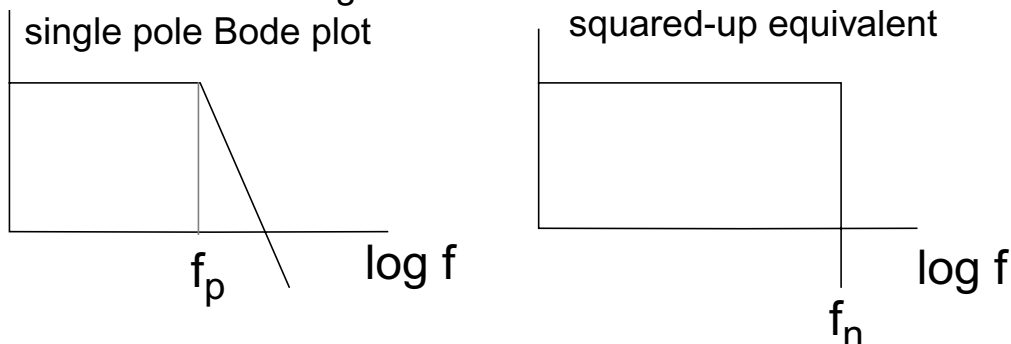

For the area underneath the curves to be the same then $f_n = (\pi/2) \cdot f_p$

- (iv) Using the result of (iii) calculate the signal-to noise ratio at the output if the input signal v_{in} is a 20mV_{rms} sine wave with a frequency much lower than the frequency of the pole at the output node.

For this calculation take $V_{GS1} = 1\text{V}$, $|V_T| = 0.75\text{V}$, $R_L = 5\text{k}\Omega$, $C_L = 1\text{pF}$.

The drain current of M1 is $100\mu\text{A}$.

Boltzmann's constant $k = 1.38 \times 10^{-23} \text{J/K}$, temperature $T = 300^\circ\text{K}$.