

## Question 1

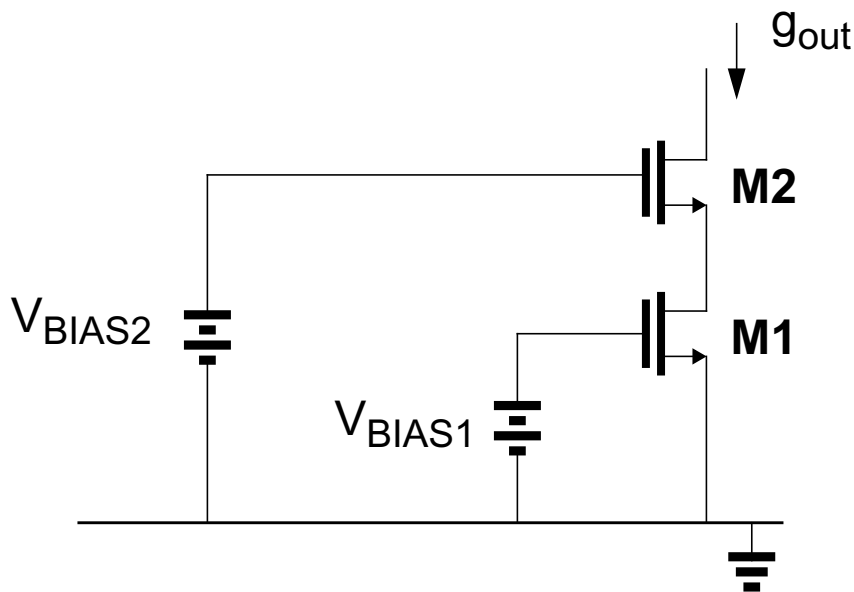



Figure 1

Ignore the body effect.

- (i) Draw the small signal model for the circuit shown in Figure 1. Ignore all capacitances.
- (ii) Derive an expression for the output conductance  $g_{out}$  in terms of the small signal parameters of M1 and M2. Reduce the expression to its simplest form assuming  $g_{m1}=g_{m2}=g_m$ ,  $g_{ds1}=g_{ds2}=g_{ds}$ ,  $g_m \gg g_{ds}$
- (iii) The circuit is to be biased for optimal low-voltage operation. If  $V_{BIAS1}=1.2V$   
 $V_T = 0.8V$   
 $(W/L)_{M2}=(W/L)_{M1}$   
 calculate the minimum value of the voltage at the output node (i.e. at the drain of M2) for both M1 and M2 to be in saturation and the value of  $V_{BIAS2}$  necessary to achieve this.  
 Neglect  $\lambda$  for this calculation.
- (iv) Repeat the calculations in (iii) if the aspect ratio of M2 is four times that of M1 i.e  $(W/L)_{M2}=4*(W/L)_{M1}$

## Solution

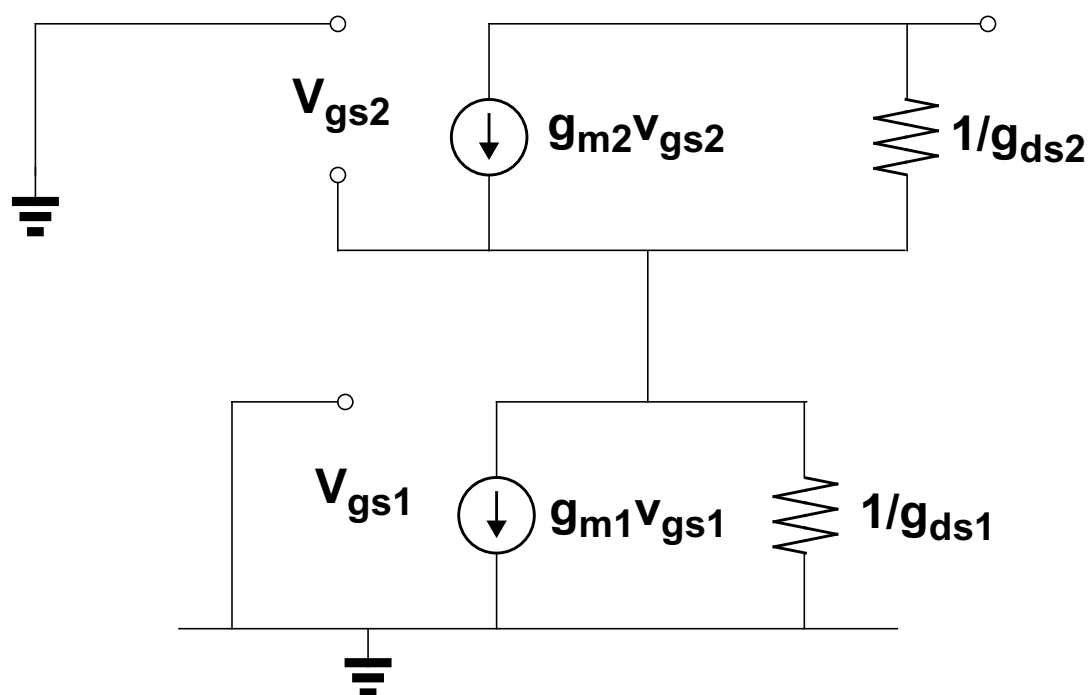- (i) Draw the small signal model for the circuit shown in Figure 1.  
Ignore all capacitances.



---


(ii) Derive an expression for the output conductance  $g_{out}$  in terms of the small signal parameters of M1 and M2.

Reduce the expression to its simplest form assuming

$$g_{m1}=g_{m2}=g_m, g_{ds1}=g_{ds2}=g_{ds}, g_m \gg g_{ds}$$

To derive the output conductance put a test voltage at the output node and calculate the

small-signal current into the circuit.

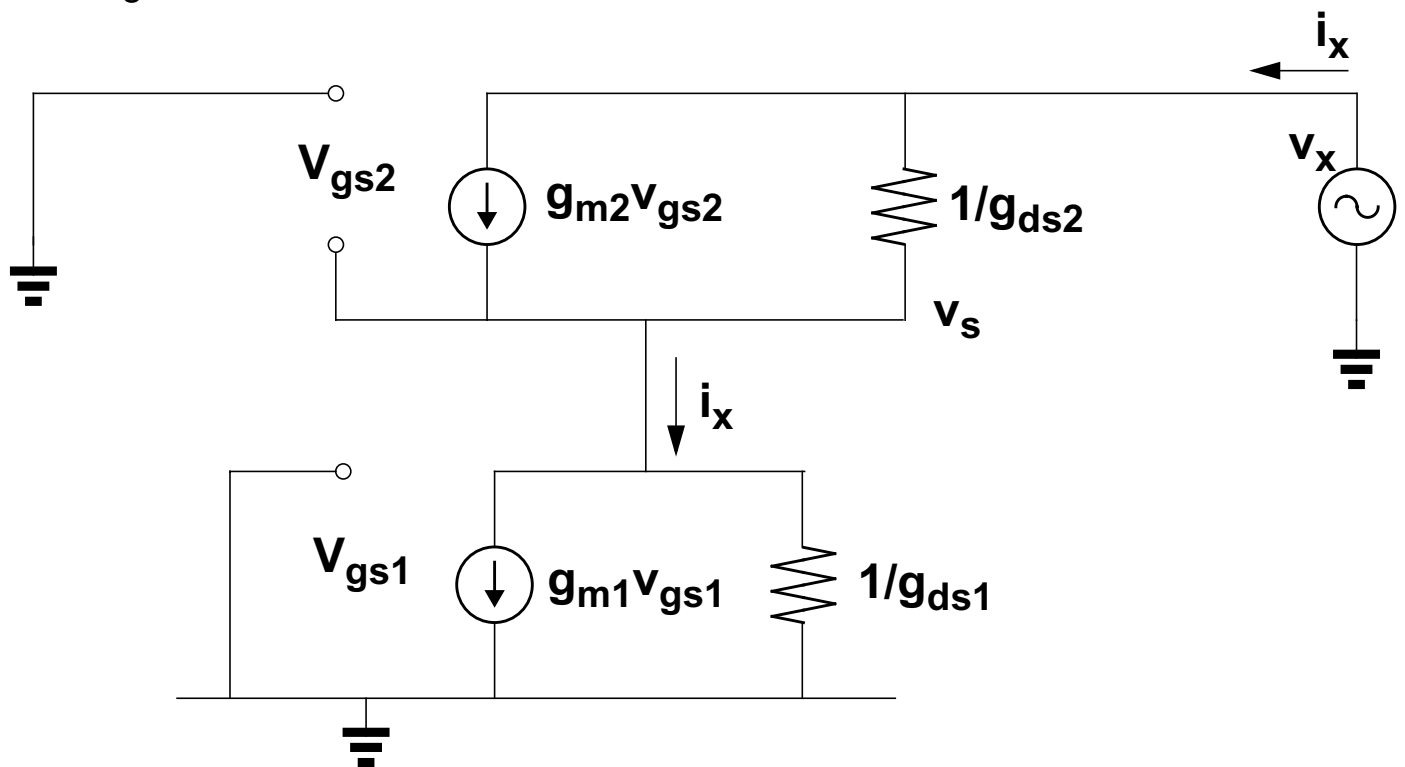

Note:  $v_{gs1} = 0 \Rightarrow g_{m1}v_{gs1} = 0$

$$i_x = g_{m2}v_{gs2} + (v_x - v_s)g_{ds2}$$

Since  $v_{gs2} = -v_s$  and  $v_s = \frac{i_x}{g_{ds1}}$

$$i_x = -(g_{m2})\frac{i_x}{g_{ds1}} + \left(v_x - \frac{i_x}{g_{ds1}}\right)g_{ds2}$$

$$g_{out} = \frac{i_x}{v_x} = \frac{g_{ds2}}{1 + \frac{g_{m2}}{g_{ds1}} + \frac{g_{ds2}}{g_{ds1}}}$$

Since  $g_{m1}=g_{m2}=g_m$ ,  $g_{ds1}=g_{ds2}=g_{ds}$ ,  $g_m \gg g_{ds}$  this can be reduced to any of

$$g_{out} \cong \frac{g_{ds2}}{g_{m2}/g_{ds1}} = \frac{g_{ds1}}{g_{m2}/g_{ds2}} = \frac{g_{ds}}{g_m/g_{ds}}$$

(iii) The circuit is to be biased for optimal low-voltage operation. If

$$V_{BIAS1} = 1.2V$$

$$V_T = 0.8V$$

$$(W/L)_{M2} = (W/L)_{M1}$$

calculate the minimum value of the voltage at the output node (i.e. at the drain of M2) for both M1 and M2 to be in saturation and the value of  $V_{BIAS2}$  necessary to achieve this.

Neglect  $\lambda$  for this calculation.

For M1 to be in saturation then

$$V_{DS1} \geq V_{GS1} - V_T$$

$$(V_{DS1})_{min} = V_{GS1} - V_T = 1.2V - 0.8V = 0.4V$$

If M2 is in saturation its drain current is given by

$$I_{D2} = \frac{K'_n W}{2L} (V_{GS2} - V_T)^2$$

Since M2 has same drain current, W/L and  $V_T$  as M1 it will also have the same  $V_{GS}$

$$(V_{DS2})_{min} = V_{GS2} - V_T = 0.4V$$

so minimum voltage at the output for both transistors to be in saturation is given by

$$V_{out} = (V_{DS1})_{min} + (V_{DS2})_{min} = 0.8V$$

The bias voltage  $V_{BIAS2}$  necessary to achieve this is given by

$$V_{BIAS2} = V_{GS2} + (V_{DS1})_{min} = 1.2V + 0.4V = 1.6V$$

(iv) Repeat the calculations in (iii) if the aspect ratio of M2 is four times that of M1  
i.e  $(W/L)_{M2} = 4 \cdot (W/L)_{M1}$

Since  $I_{D1} = I_{D2}$  then

$$\frac{K'_n}{2} \left( \frac{W}{L} \right) (V_{GS1} - V_T)^2 = \frac{K'_n}{2} 4 \left( \frac{W}{L} \right) (V_{GS2} - V_T)^2$$

$$V_{GS2} - V_T = \frac{V_{GS1} - V_T}{2} = 0.2V$$

$$V_{GS2} = 1V$$

$$(V_{DS2})_{min} = 0.2V$$

so minimum voltage at the output for both transistors to be in saturation is given by

$$V_{out} = (V_{DS1})_{min} + (V_{DS2})_{min} = 0.6V$$

The bias voltage  $V_{BIAS2}$  necessary to achieve this is given by

$$V_{BIAS2} = V_{GS2} + (V_{DS1})_{min} = 1.0V + 0.4V = 1.4V$$

## Question 2


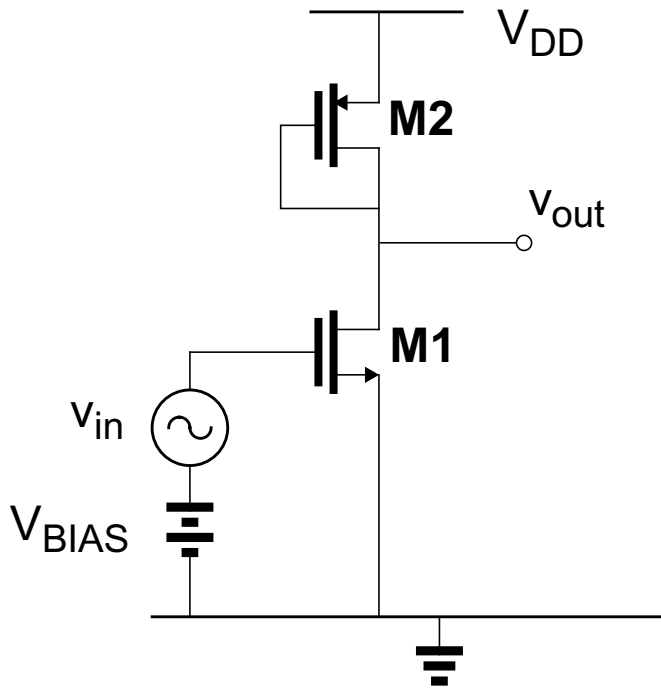


Figure 2

Assume M1 and M2 are operating in saturation and ignore the body effect.

- Draw the small signal model for the circuit shown in Figure 2. Ignore all capacitances.
- What is the low-frequency small signal voltage gain ( $v_{out}/v_{in}$ )? Assume that  $g_{m1} \gg g_{ds1}, g_{ds2}$  and that  $g_{m2} \gg g_{ds1}, g_{ds2}$
- What is the input-referred thermal noise in terms of the small signal parameters of M1 and M2, Boltzmann's constant  $k$  and temperature  $T$ ?
- If a capacitor  $C_L$  is connected between the output node and ground what is the total integrated thermal noise at the output node?

You may assume the following:

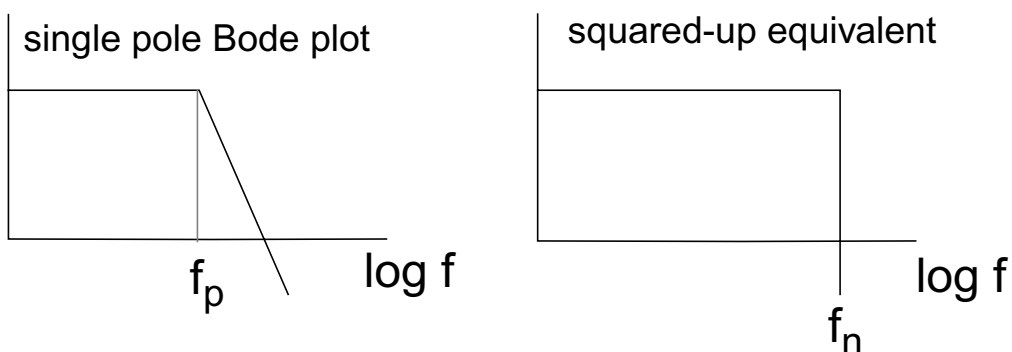


For the area underneath the curves to be the same then  $f_n = (\pi/2) * f_p$

- Using the result of (iv) calculate the signal-to noise ratio at the output if the input signal  $v_{in}$  is a  $10\text{mV}_{\text{rms}}$  sine wave. For this calculation take  $V_{GS1} = 1\text{V}$ ,  $|V_{GS2}| = 2.8\text{V}$ ,  $|V_T| = 0.8\text{V}$  for M1, M2.  $C_L = 10\text{pF}$ . The drain current of M1 is  $100\mu\text{A}$ .

Assume Boltzmann's constant  $k=1.38 \times 10^{-23} \text{ J/}^\circ\text{K}$ , temperature  $T=300^\circ\text{K}$ .

Solution

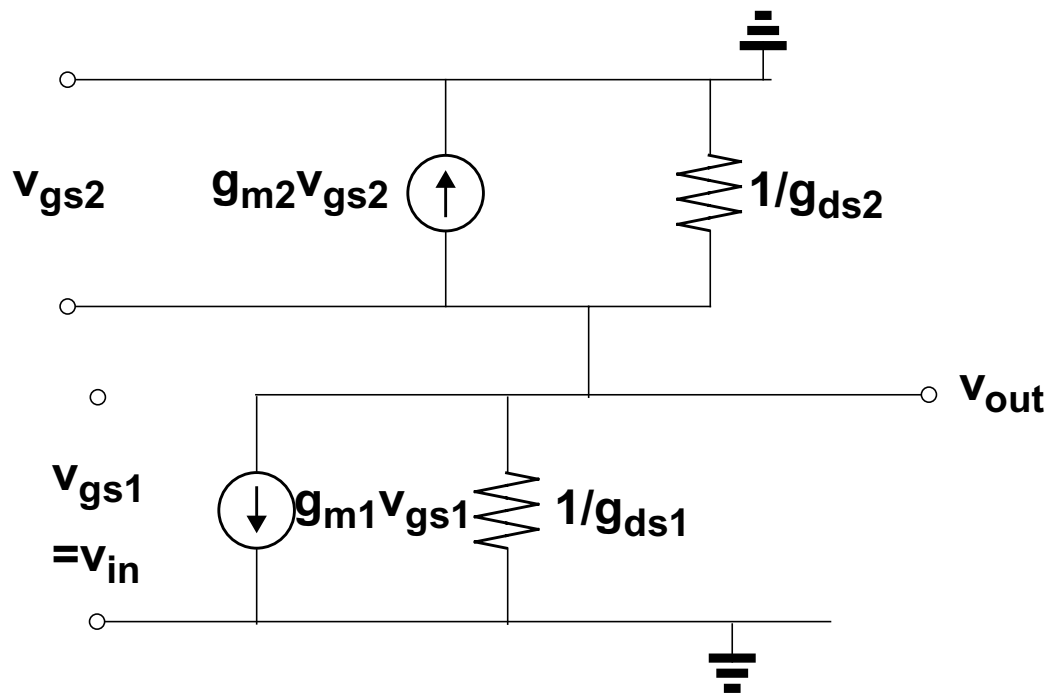- (i) Draw the small signal model for the circuit shown in Figure 2.  
Ignore all capacitances.





---

(ii) What is the low-frequency small signal voltage gain ( $v_{out}/v_{in}$ )?

Assume that  $g_{m1} \gg g_{ds1}, g_{ds2}$  and that  $g_{m2} \gg g_{ds1}, g_{ds2}$

Current at outout node

$$g_{m1}v_{gs1} + g_{m2}v_{gs2} + v_{out}g_{ds1} + v_{out}g_{ds2} = 0$$

$$g_{m1}v_{in} + g_{m2}v_{out} + v_{out}g_{ds1} + v_{out}g_{ds2} = 0$$

$$\frac{v_{out}}{v_{in}} = -\frac{g_{m1}}{g_{m2} + g_{ds1} + g_{ds2}} \cong -\frac{g_{m1}}{g_{m2}}$$


Alternatively recognise that the current of the current-source  $g_{m2}v_{gs2}$  is determined by voltage across its terminals i.e. is equivalent to a resistance  $1/g_{m2}$ .

Since  $1/g_{m2} \ll 1/g_{ds2}$ ,  $1/g_{m2} \ll 1/g_{ds1}$ , can write directly

$$\frac{v_{out}}{v_{in}} = -\frac{g_{m1}}{g_{m2}}$$

---

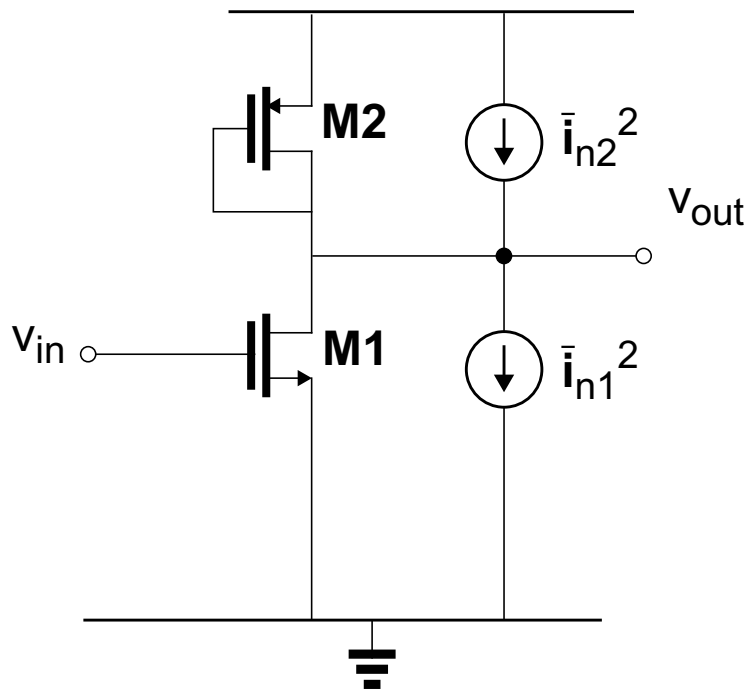(iii) What is the input-referred thermal noise voltage in terms of the small signal parameters of M1 and M2, Boltzmann's constant  $k$  and temperature  $T$ ?



Total noise current at output is square root of the individual noise currents

$$\overline{i_{nt}} = \sqrt{i_{n1}^2 + i_{n2}^2} = \sqrt{4kT\left(\frac{2}{3}g_{m1}\right) + 4kT\left(\frac{2}{3}g_{m2}\right)}$$

Input-referred noise voltage given by

$$\overline{v_{ni}} = \frac{\overline{i_{nt}}}{g_m} = \frac{\sqrt{4kT\left(\frac{2}{3}g_{m1}\right) + 4kT\left(\frac{2}{3}g_{m2}\right)}}{g_{m1}} \quad V/\sqrt{Hz}$$

(iv) If a capacitor  $C_L$  is connected between the output node and ground what is the total integrated thermal noise at the output node?

Noise voltage at output given by input referred noise multiplied by gain

$$\begin{aligned}\overline{v_{no}^2} &= \overline{v_{ni}^2} \frac{g_{m1}}{g_{m2}} = \frac{\sqrt{4kT\left(\frac{2}{3}g_{m1}\right) + 4kT\left(\frac{2}{3}g_{m2}\right)} g_{m1}}{g_{m1}} \frac{g_{m1}}{g_{m2}} \\ &= \frac{\sqrt{4kT\left(\frac{2}{3}g_{m1}\right) + 4kT\left(\frac{2}{3}g_{m2}\right)}}{g_{m2}}\end{aligned}$$

Capacitor  $C_L$  connected between the output node and ground  
=> pole at output node given by

$$|f_p| = \frac{g_{m2}}{2\pi C_L}$$

Total integrated thermal noise power at the output node is given by the product of the thermal noise power and the squared-up equivalent of the first order filter function

$$\overline{v_{nototal}^2} = \overline{v_{no}^2} \frac{\pi}{2} f_p$$

$$\overline{v_{nototal}^2} = \frac{4kT\left(\frac{2}{3}g_{m1}\right) + 4kT\left(\frac{2}{3}g_{m2}\right)}{g_{m2}} \cdot \frac{\pi}{2} \cdot \frac{g_{m2}}{2\pi C_L}$$

$$\overline{v_{nototal}^2} = \frac{\frac{2}{3}(g_{m1} + g_{m2})}{g_{m2}} \cdot \frac{kT}{C_L}$$

- (v) Using the result of (iv) calculate the signal-to noise ratio at the output if the input signal  $v_{in}$  is a  $10mV_{rms}$  sine wave.

For this calculation take  $V_{GS1}=1V$ ,  $|V_{GS2}|=2.8V$ ,  $|V_T| = 0.8V$  for M1,M2.  $C_L=10pF$ . The drain current of M1 is  $100\mu A$ .

Assume Boltzmann's constant  $k=1.38 \times 10^{-23} J/^{\circ}K$ , temperature  $T=300^{\circ}K$ .

$g_m$  given by

$$g_m = \frac{2I_D}{(V_{GS} - V_T)}$$

$$g_{m1} = \frac{2 \cdot 100\mu A}{1V - 0.8V} = 1mA/V$$

$$g_{m2} = \frac{2 \cdot 100\mu A}{2.8V - 0.8V} = 100\mu A/V$$

Output signal

$$v_{out} = -\frac{g_{m1}}{g_{m2}} v_{in} = -10 \cdot 10mV_{rms} = 100mV_{rms}$$

Total output noise:

$$\overline{v_{nototal}} = \sqrt{\frac{\frac{2}{3}(g_{m1} + g_{m2})}{g_{m2}} \cdot \frac{kT}{C_L}}$$

$$\overline{v_{nototal}} = \sqrt{\frac{\frac{2}{3}(1mA/V + 100\mu A/V)}{100\mu A/V} \cdot \frac{1.38 \times 10^{-23} 300}{10pF}} = 55.1\mu V_{rms}$$

Signal-to-Noise ratio given by

$$\frac{S}{N} = \frac{100mV}{55.1\mu V} = 1815 \quad \text{or } 65dB$$

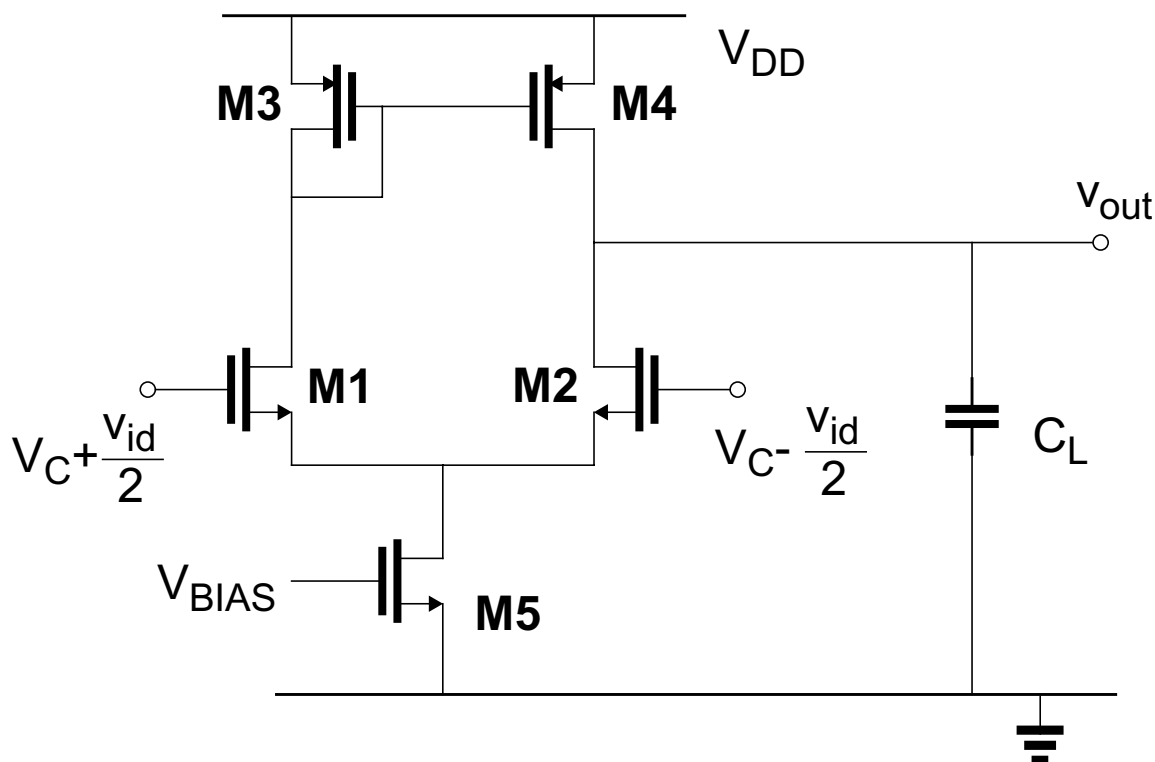


Figure 3.

Assume all devices are operating in saturation. Ignore the body effect.

Use  $M_1=M_2$ ,  $g_{m1}=g_{m2}=g_{mn}$ ,  $g_{ds1}=g_{ds2}=g_{dsn}$

Use  $M_3=M_4$ ,  $g_{m3}=g_{m4}=g_{mp}$ ,  $g_{ds3}=g_{ds4}=g_{dsp}$

$V_C$  is the fixed common mode voltage.

A small differential voltage  $v_{id}$  is applied to the amplifier.

- (i) Derive an expression for the small signal transfer function ( $V_{out}/v_{id}$ ) of the amplifier in Figure 3 in terms of  $g_m$ ,  $g_{ds}$  and  $C_L$ . Consider only capacitance  $C_L$ .
- (ii) Give expressions for the following: low frequency gain, pole frequency, unity gain frequency.
- (iii) Draw a Bode plot identifying the low-frequency gain, pole frequency, and unity gain frequency.
- (iv) What is the effect on each of the parameters in (ii) if the bias current is doubled? Assume all devices remain in saturation.
- (v) If the signal at the output node is a sine wave given by  $V_{out}=A\sin\omega t$ , calculate the maximum frequency such that no slewing occurs. Take  $A=0.5V$ ,  $C_L=10pF$ . The drain current through M5 is  $100\mu A$ .

- (i) Derive an expression for the small signal transfer function ( $v_{out}/v_{id}$ ) of the amplifier in Figure 3 in terms of  $g_m$ ,  $g_{ds}$  and  $C_L$ . Consider only capacitance  $C_L$ .

Source of M1, M2 is at ac ground.

Half signal  $v_{id}/2$  and  $-v_{id}/2$  are amplified separately to output so that

$$v_{out}(s) = -\frac{g_{m1}}{g_{m3}} \cdot -\frac{g_{m4}}{g_{ds2} + g_{ds4} + sC_L} \left( \frac{v_{id}(s)}{2} \right) - \frac{g_{m2}}{g_{ds2} + g_{ds4} + sC_L} \left( -\frac{v_{id}(s)}{2} \right)$$

Using,  $g_{m1}=g_{m2}=g_{mn}$ ,  $g_{ds1}=g_{ds2}=g_{dsn}$  and  $g_{m3}=g_{m4}=g_{mp}$ ,  $g_{ds3}=g_{ds4}=g_{dsp}$

$$v_{out}(s) = -\frac{g_{mn}}{g_{mp}} \cdot -\frac{g_{mp}}{g_{dsn} + g_{dsp} + sC_L} \left( \frac{v_{id}}{2} \right) - \frac{g_{mn}}{g_{dsn} + g_{dsp} + sC_L} \left( -\frac{v_{id}}{2} \right)$$

$$\frac{v_{out}}{v_{id}}(s) = \frac{g_{mn}}{g_{dsn} + g_{dsp} + sC_L}$$

(ii) Give expressions for the following: low frequency gain, pole frequency, unity gain frequency

$$\frac{v_{out}}{v_{id}}(s) = \frac{g_{mn}}{g_{dsn} + g_{dsp} + sC_L}$$

Re-write to get

$$\frac{v_{out}}{v_{id}}(s) = \frac{g_{mn}}{g_{dsn} + g_{dsp}} \cdot \frac{g_{mn}}{1 + \frac{sC_L}{g_{dsn} + g_{dsp}}}$$

Low-frequency gain  $A_o$  given by

$$A_o = \frac{g_{mn}}{g_{dsn} + g_{dsp}}$$

Pole  $\omega_p$  given by


$$|\omega_p| = \frac{g_{dsn} + g_{dsp}}{C_L}$$

Unity gain frequency  $\omega_u$  given by

$$\omega_u = \frac{g_{mn}}{g_{dsn} + g_{dsp}} \frac{g_{dsn} + g_{dsp}}{C_L} = \frac{g_{mn}}{C_L}$$



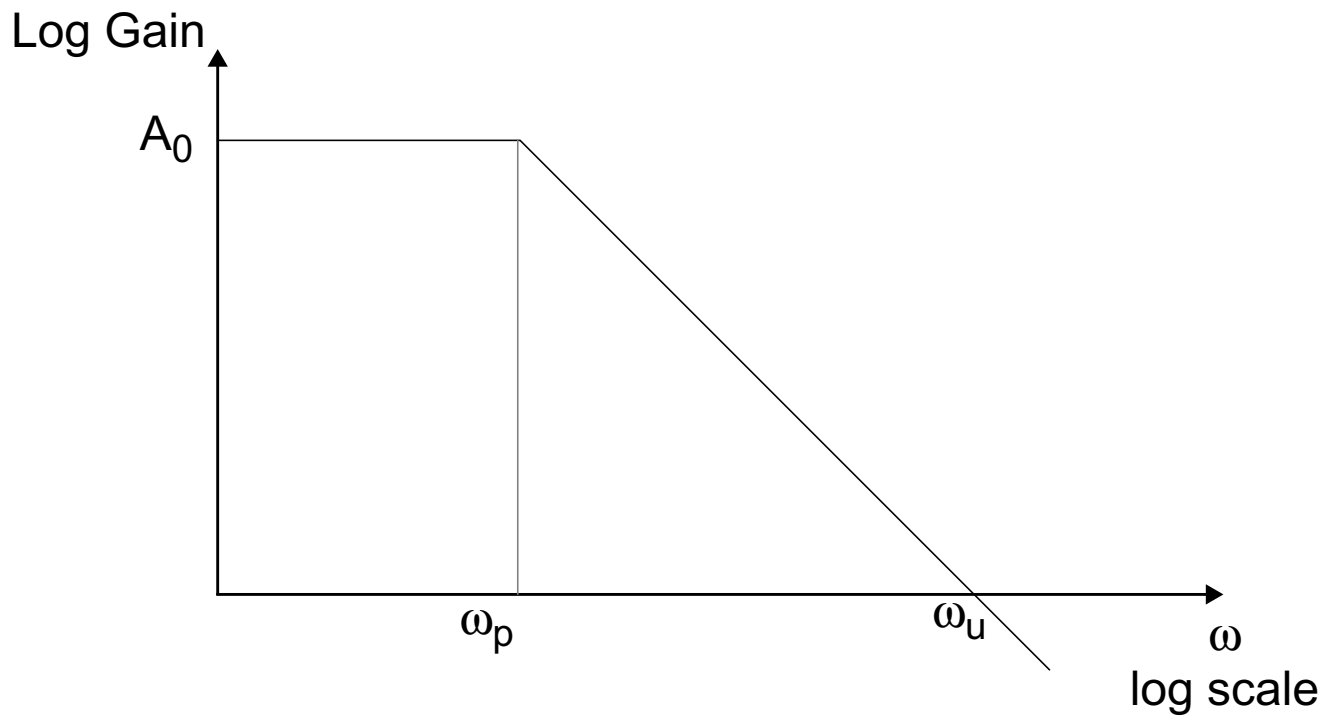- (iii) Draw a Bode plot identifying the low-frequency gain, pole frequency, and unity gain frequency.



- (iv) What is the effect on each of the parameters in (ii) if the bias current is doubled? Assume all devices remain in saturation.

$$g_m = \sqrt{2K'_n \frac{W}{L} I_D}$$

If the bias current is doubled  $g_m$  will increase by factor square root 2

$$g_{ds} = \lambda I_D$$

If the bias current is doubled  $g_{ds}$  will increase by factor 2

Low-frequency gain  $A_o$

$$A_o = \frac{g_{mn}}{g_{dsn} + g_{dsp}} \quad \Rightarrow A_o \text{ will decrease by factor square root 2}$$

Pole  $\omega_p$

$$\omega_p = \frac{g_{dsn} + g_{dsp}}{C_L} \quad \Rightarrow \omega_p \text{ will increase by factor 2}$$

Unity gain frequency  $\omega_u$

$$\omega_u = \frac{g_{mn}}{C_L} \quad \Rightarrow \omega_u \text{ will increase by factor square root. 2}$$

- (v) If the signal at the output node is a sine wave given by  $V_{out} = A \sin \omega t$ , calculate the maximum frequency such that no slewing occurs. Take  $A = 0.5V$ ,  $C_L = 10pF$ . The drain current through M5 is  $100\mu A$ .

$$\text{Slew Rate} = \left( \frac{dv_{out}}{dt} \right)_{max} = \frac{I_B}{C_L} \quad \text{where } I_B = I_{DM5}$$

$$v_{out} = A \sin \omega t$$

$$\left( \frac{dv_{out}}{dt} \right)_{max} = A \omega$$

For no slewing

$$\left( \frac{dv_{out}}{dt} \right)_{max} = A \omega \leq \frac{I_B}{C_L} \Rightarrow \omega \leq \frac{I_B}{AC_L}$$

$$\omega_{max} = \frac{I_B}{AC_L} = \frac{100\mu A}{0.5V \cdot 10pF} = 20 \times 10^6 \text{ rad/s}$$

or  $f_{max} = 3.18 \text{ MHz}$