

APPENDIX 6A Proving that $\frac{\hat{I}_{s,3}}{\hat{I}_{L,2}} = \frac{1}{2}$

The output of the voltage regulator G_v in Fig. 6-6 in steady state is

$$\text{output of } G_v = \hat{I}_L - \hat{I}_{L,2} \cos 2\omega t \quad (6A-1)$$

in which $\hat{I}_{L,2}$, by a proper controller design is much smaller than \hat{I}_L , for example less than 1.5 percent. The above expression is multiplied by $|\sin \omega t|$ to establish the reference for the inductor current. The second-harmonic distortion in Eq. 6A-1 results in a third-harmonic distortion in the input ac current. This can be proven by multiplying the second-harmonic component in Eq. 6A-1 with $\sin \omega t$, in order to see the distortion in the input ac current, as follows:

$$(-\hat{I}_{L,2} \cos 2\omega t) \sin \omega t = \frac{1}{2} \hat{I}_{L,2} \sin \omega t - \underbrace{\frac{1}{2} \hat{I}_{L,2} \sin 3\omega t}_{\hat{I}_{s,3}} \quad (6A-2)$$

In Eq. 6A-2, the fundamental-frequency component, due to the second-harmonic distortion, is compensated by the voltage-loop controller. However, the second-harmonic distortion with a peak $\hat{I}_{L,2}$ results in a third-harmonic distortion with one-half the amplitude. Therefore,

$$\frac{\hat{I}_{s,3}}{\hat{I}_{L,2}} = \frac{1}{2} \quad (6A-3)$$

APPENDIX 6B Proving that $\frac{\tilde{v}_d(s)}{\hat{I}_{L,\sim}(s)} = \frac{1}{2} \frac{\hat{V}_s}{V_d} \frac{R}{1+sRC}$

In designing the controller, the output of $G_v(s)$ in Fig. 6-6 under dynamic conditions has a strong dc component plus a low-frequency (less than 15 Hz) perturbation term:

$$\text{Output of the voltage regulator} = \hat{I}_L + i_{L,\sim}(t) \quad (6B-1)$$

The perturbation term can be expressed as

$$\tilde{i}_{L,\sim}(t) = \hat{i}_{L,\sim} \sin(\omega_{\sim} t + \phi) \quad (6B-2)$$

where, ω_{\sim} is the perturbation frequency below 15 Hz (assumed upper limit on the bandwidth of the voltage loop). It has an arbitrary phase angle ϕ . Substituting Eq. 6B-2 into Eq. 6B-1 and multiplying with $|\sin \omega t|$, the inductor current is

$$\bar{i}_L(t) = [\hat{I}_L + \hat{i}_{L,\sim} \sin(\omega_{\sim} t + \phi)] |\sin \omega t| \quad (6B-3)$$

In the circuit of Fig. 6-2, assuming that the voltage drop across L_d is negligible,

$$|v_s(t)| \bar{i}_L(t) = V_d \bar{i}_d \quad (6B-4)$$

Substituting into Eq. 6B-4 $|v_s(t)| = \hat{V}_s |\sin \omega t|$ and the inductor current from Eq. 6B-3,

$$\hat{V}_s |\sin \omega t| [\hat{I}_L + \hat{i}_{L,\sim} \sin(\omega_{\sim} t + \phi)] |\sin \omega t| = V_d \bar{i}_d(t) \quad (6B-5)$$

Noting that $|\sin \omega t|^2 = \sin^2 \omega t$,

$$\bar{i}_d(t) = \frac{\hat{V}_s \hat{I}_L}{V_d} \sin^2 \omega t + \frac{\hat{V}_s}{V_d} \underbrace{\hat{i}_{L,\sim} \sin(\omega_{\sim} t + \phi)}_{=i_{L,\sim}(t)} \sin^2 \omega t \quad (6B-6)$$

Substituting $\sin^2 \omega t = \frac{1}{2} - \frac{1}{2} \cos 2\omega t$ in Eq. 6B-6,

$$\bar{i}_d(t) = \frac{\hat{V}_s \hat{I}_L}{2V_d} (1 - \cos 2\omega t) + \underbrace{\frac{\hat{V}_s}{2V_d} i_{L,\sim}(t)}_{\text{only pert. freq. term}} - \frac{\hat{V}_s}{2V_d} i_{L,\sim}(t) \cos 2\omega t \quad (6B-7)$$

Appendix 6-2

Equating the perturbation-frequency term on the right-side of Eq. 6B-7 to the low-frequency perturbation in the output current,

$$\frac{\tilde{\tilde{i}}_d(s)}{\tilde{i}_{L,\sim}(s)} = \frac{1}{2} \frac{\hat{V}_s}{V_d} \quad (6B-8)$$

The transfer function of the power stage in Fig. 6-6b at these low perturbation frequencies (ignoring the capacitor ESR) is:

$$\frac{\tilde{v}_d(s)}{\hat{\tilde{i}}_{L,\sim}(s)} = \frac{\tilde{\tilde{i}}_d(s)}{\tilde{i}_{L,\sim}(s)} \frac{\tilde{v}_d(s)}{\tilde{\tilde{i}}_d(s)} = \frac{1}{2} \frac{\hat{V}_s}{V_d} \frac{R}{1 + sRC} \quad (6B-9)$$