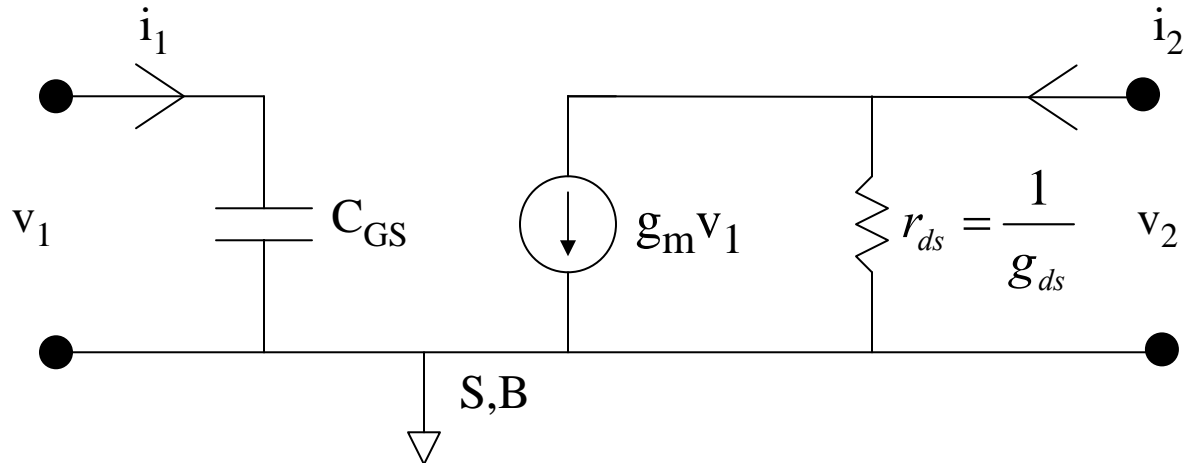


Question 1(a)

Small-signal model of MOSFET ignoring gate resistance and considering C_{GS} as the only important capacitance.



$$h_{21} = \left. \frac{i_2}{i_1} \right|_{v_2=0} = \frac{g_m v_1}{j\omega C_{GS} v_1} = \frac{g_m}{j\omega C_{GS}} \Rightarrow |h_{21}| = \frac{g_m}{2\pi f C_{GS}}$$

The cut-off frequency is when $|h_{21}|$ drops to 1:

$$|h_{21}| = 1 \Rightarrow f = f_T = \frac{g_m}{2\pi C_{GS}}$$

The elements of the model are:

$$I_{DS} = \frac{1}{2} \frac{W}{L} \mu C_{OX} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$g_m = \frac{dI_{DS}}{dV_{GS}} = \frac{W}{L} \mu C_{OX} (V_{GS} - V_{TH}) (1 + \lambda V_{DS})$$

$$g_{ds} = \frac{dI_{DS}}{dV_{DS}} = \frac{1}{2} \frac{W}{L} \mu C_{OX} (V_{GS} - V_{TH})^2 (\lambda)$$

$$C_{GS} \approx \frac{2}{3} W L C_{OX}$$

Question 1(b)

$$C_{OX} = \frac{\epsilon_0 \epsilon_r}{T_{OX}} = \frac{8.854 \times 10^{-12} \times 3.9}{4 \times 10^{-9}} = 0.0086 \text{ F/m}^2$$

$$k = \frac{W}{L} \mu C_{OX} = \frac{20}{0.25} \times 350 \times 10^{-4} \times 0.0086 = 0.0242 \text{ A/V}^2$$

$$g_m = k(V_{GS} - V_{TH})(1 + \lambda V_{DS}) = 0.0242 \times (2.5 - 0.6) \times (1 + 0.15 \times 2) = 0.0597 \text{ A/V}$$

$$g_{ds} = \frac{1}{2} k(V_{GS} - V_{TH})^2 (\lambda) = \frac{1}{2} \times 0.0242 \times (2.5 - 0.6)^2 \times 0.15 = 0.0065 \text{ A/V}$$

$$C_{GS} \approx \frac{2}{3} W L C_{OX} = \frac{2}{3} \times 20 \times 10^{-6} \times 0.25 \times 10^{-6} \times 0.0086 = 28.8 \times 10^{-15} \text{ F}$$

(i)
$$f_T = \frac{g_m}{2\pi C_{GS}} = 330 \text{ GHz} \quad 2 \text{ marks}$$

(This is unrealistic in practice for this geometry transistor but the model here is very simplistic)

(ii) Using the definitions of the y-parameters and setting $f=1 \text{ GHz}$:

$$y_{11} = \left. \frac{i_1}{v_1} \right|_{v_2=0} \quad y_{21} = \left. \frac{i_2}{v_1} \right|_{v_2=0} \quad y_{12} = \left. \frac{i_1}{v_2} \right|_{v_1=0} \quad y_{22} = \left. \frac{i_2}{v_2} \right|_{v_1=0}$$

$$y_{11} = j\omega C_{GS} = 1.8 \times 10^{-4} \angle 90^\circ$$


$$y_{12} = 0$$

$$y_{21} = g_m = 0.0597 \angle 0^\circ$$

$$y_{22} = g_{DS} = 0.0065 \angle 0^\circ$$

8 marks

Question 2(a)

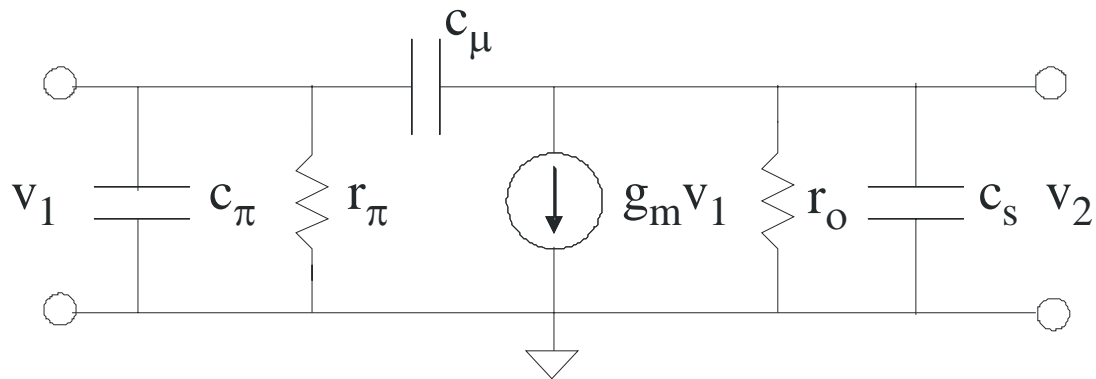

$$y_{11} = \left. \frac{i_1}{v_1} \right|_{v_2=0} \quad y_{21} = \left. \frac{i_2}{v_1} \right|_{v_2=0} \quad y_{12} = \left. \frac{i_1}{v_2} \right|_{v_1=0} \quad y_{22} = \left. \frac{i_2}{v_2} \right|_{v_1=0}$$

Applying the y-parameter definitions to the above circuit and performing the circuit analysis under the appropriate conditions gives:

$$y_{11} = \frac{1}{r_\pi} + j\omega(c_\pi + c_\mu)$$

$$y_{12} = -j\omega c_\mu$$

$$y_{21} = g_m - j\omega c_\mu$$

$$y_{22} = \frac{1}{r_o} + j\omega(c_s + c_\mu)$$

Question 2(a) continued

The expressions on the previous page have to be manipulated to express the circuit element values in terms of the y-parameters.

The final result of this manipulation is as follows:

$$g_m = \mathbf{Re}(y_{21}) = 0.1S$$

$$r_\pi = \frac{1}{\mathbf{Re}(y_{11})} = 400\Omega$$

$$r_o = \frac{1}{\mathbf{Re}(y_{22})} = 2k\Omega$$

$$c_\mu = \frac{-\mathbf{Im}(y_{12})}{2\pi f} = 1pF$$

$$c_\pi = \frac{\mathbf{Im}(y_{11})}{2\pi f} - c_\mu = 5pF$$

$$c_s = \frac{\mathbf{Im}(y_{22})}{2\pi f} - c_\mu = 2pF$$

16 marks

Question 2(b)

$$f_T = \frac{g_m}{2\pi(c_\pi + c_\mu)} = 2.65GHz$$

4 marks

Question 3(a)

$$\begin{aligned}
y(t) = & \left[\alpha_1 A_1 + \frac{3}{4} \alpha_3 A_1^3 + \frac{3}{2} \alpha_3 A_1 A_2^2 \right] \cos(\varpi_1 t) \\
& + \left[\alpha_1 A_2 + \frac{3}{4} \alpha_3 A_2^3 + \frac{3}{2} \alpha_3 A_1^2 A_2 \right] \cos(\varpi_2 t) \\
& + \frac{1}{4} \alpha_3 A_1^3 \cos 3\varpi_1 t + \frac{1}{4} \alpha_3 A_2^3 \cos 3\varpi_2 t \\
& + \frac{3}{4} \alpha_3 A_1^2 A_2 \cos(2\varpi_1 + \varpi_2)t + \frac{3}{4} \alpha_3 A_1^2 A_2 \cos(2\varpi_1 - \varpi_2)t \\
& + \frac{3}{4} \alpha_3 A_1 A_2^2 \cos(2\varpi_2 + \varpi_1)t + \frac{3}{4} \alpha_3 A_1 A_2^2 \cos(2\varpi_2 - \varpi_1)t
\end{aligned}$$

(i) P1dB

P1dB is defined for a single frequency input so A_2 can be set to 0 in the above formula and then just looking at the o/p component at the fundamental frequency:

$$y_1(t) = \left(\alpha_1 A + \frac{3\alpha_3 A^3}{4} \right) \cos(\varpi t) = A_{OUT} \cos(\varpi t)$$

The voltage gain of the circuit considering the fundamental is:

$$G_V = \frac{y_1(t)}{x(t)} = \frac{A_{OUT} \cos(\varpi t)}{A \cos(\varpi t)} = \frac{\alpha_1 A + \frac{3\alpha_3 A^3}{4}}{A} = \alpha_1 + \frac{3\alpha_3 A^2}{4}$$

Converting to dB:

$$G_{dB} = 20 \log_{10}(G_V) = 20 \log_{10} \left(\alpha_1 + \frac{3\alpha_3 A^2}{4} \right)$$

For small A (amplitude) the A^2 term is very small and the gain is the “ideal gain” for small input amplitudes:

$$G_{dB,small} = 20 \log_{10}(\alpha_1)$$

Question 3(a)(i) continued

The power gain in dB is:

$$G_{dB} = 20 \log_{10}(G_V) = 20 \log_{10} \left(\alpha_1 + \frac{3\alpha_3 A^2}{4} \right)$$

For a compressive gain stage α_3 has the opposite sign to α_1 i.e.
if $\alpha_1 > 0$ then $\alpha_3 < 0$

For small input signals (small A) the power gain is approximately:

$$G_{dB,small} = 20 \log_{10}(\alpha_1)$$

At the 1dB point the gain is 1dB smaller than this ideal value i.e.

$$G_{dB,P1dB} = G_{dB,small} - 1 = 20 \log_{10}(\alpha_1) - 1$$

The amplitude A corresponding to P1dB can be found by equating the last expression to the first expression:

$$G_{dB} = G_{dB,P1dB} \Rightarrow 20 \log_{10} \left(\alpha_1 + \frac{3\alpha_3 A^2}{4} \right) = 20 \log_{10}(\alpha_1) - 1$$

$$20 \log_{10} \left(\alpha_1 + \frac{3\alpha_3 A^2}{4} \right) = 20 \log_{10}(\alpha_1) - 1$$

$$\Rightarrow 20 \log_{10} \left(\alpha_1 + \frac{3\alpha_3 A^2}{4} \right) - 20 \log_{10}(\alpha_1) = -1$$

$$\Rightarrow \log_{10} \left(\left(\alpha_1 + \frac{3\alpha_3 A^2}{4} \right) / \alpha_1 \right) = -0.05$$

$$\Rightarrow 1 + \frac{3\alpha_3 A^2}{4\alpha_1} = 10^{-0.05}$$

$$\Rightarrow A^2 = \left(10^{-0.05} - 1 \right) \frac{4}{3} \frac{\alpha_1}{\alpha_3} = -0.145 \frac{\alpha_1}{\alpha_3} = 0.145 \left| \frac{\alpha_1}{\alpha_3} \right|$$

$$\Rightarrow A = \sqrt{0.145 \left| \frac{\alpha_1}{\alpha_3} \right|}$$

Note α_1 and α_3 have opposite signs so:

$$\frac{\alpha_1}{\alpha_3} = - \left| \frac{\alpha_1}{\alpha_3} \right|$$

5 marks

Question 3(a) continued

(ii) IIP3

Again, taking the case of $A_1=A_2=A$, and considering the outputs at the fundamental frequencies to be the desired outputs, the amplitudes of the desired signals are:

$$A_{SIG} = \left| \alpha_1 A + \frac{3}{4} \alpha_3 A^3 + \frac{3}{2} \alpha_3 A^3 \right| = \left| \alpha_1 A + \frac{9}{4} \alpha_3 A^3 \right|$$

$$\approx |\alpha_1| A \quad \text{if} \quad \alpha_1 \gg \frac{9}{4} \alpha_3 A^2$$

In this case the unwanted 3rd-order inter-modulation (IM) signals are given by:

$$A_{IM3} = \frac{3}{4} |\alpha_3| A^3$$

As A increases the IM3 outputs will eventually reach the same level as the desired signal output. This condition is called the “third-order IM intercept point”, IP3. The input amplitude corresponding to this condition is $A=A_{IP3}$ and at this amplitude:

$$A_{SIG} = A_{IM3} \Rightarrow |\alpha_1| A_{IP3} = \frac{3}{4} |\alpha_3| A_{IP3}^3 \Rightarrow A_{IP3} = \sqrt{\frac{4 |\alpha_1|}{3 |\alpha_3|}}$$


5 marks

(b)

$$|\alpha_1| = \frac{300}{2} = 150 \quad |\alpha_3| = \frac{4 \times 2 \times 10^{-9}}{(2 \times 10^{-3})^3} = 1 \Rightarrow A_{IP3} = \sqrt{\frac{3 |\alpha_1|}{4 |\alpha_3|}} = \sqrt{\frac{3 \times 150}{4 \times 1}} = 10.6V$$

5 marks

Question 3(c)

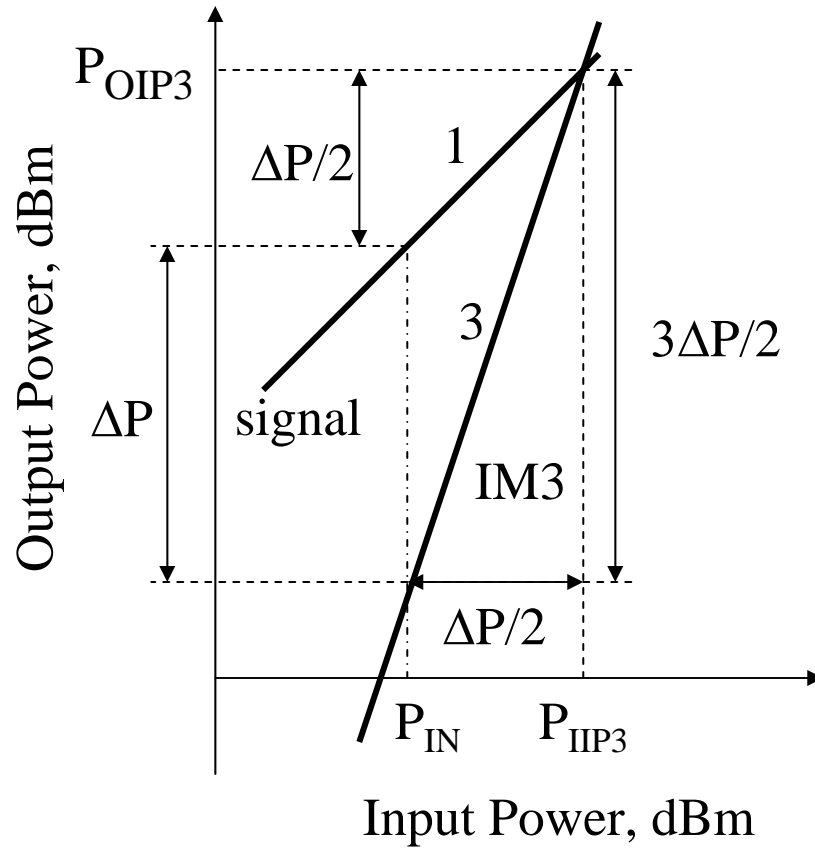

By applying two signals with input power (P_{in}) and measuring the associated output power at the signal frequency ($P_{sig,out}$) and at the IM3 frequencies ($P_{IM3,out}$) it is apparent from the graph that:

$$P_{IIP3} = P_{in} + \frac{P_{sig,out} - P_{IM3,out}}{2}$$

5 marks


Question 4

(a)

- (i) The operating power gain (also just called the power gain) is the ratio of the power delivered to the load to the power delivered to the network by the source.
- (ii) The transducer power gain is the ratio of the power delivered to the load to the power *available* from the source.
- (iii) The available power gain is the ratio of the power *available* from the network to the power *available* from the source.

3 marks

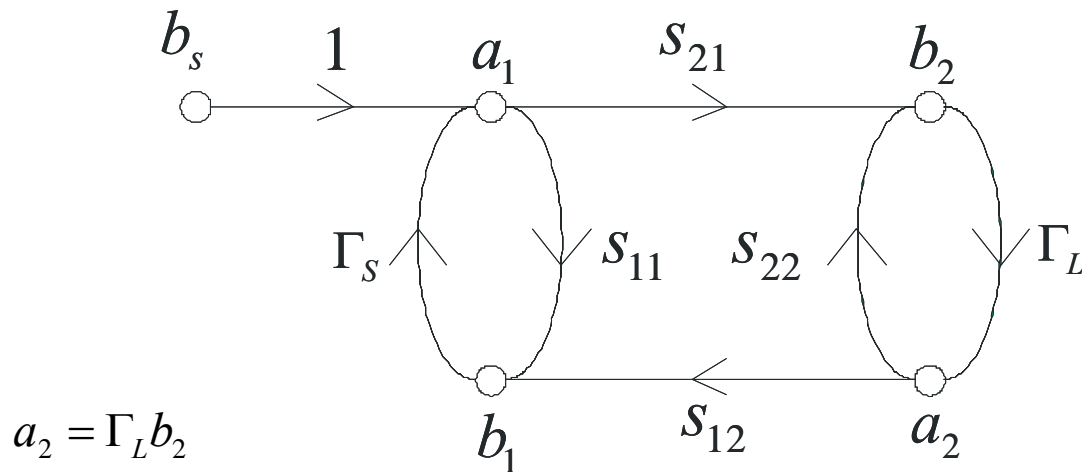(b) Operating power gain of the amplifier



$$a_2 = \Gamma_L b_2$$

$$b_2 = s_{21}a_1 + s_{22}a_2 = s_{21}a_1 + s_{22}\Gamma_L b_2 \Rightarrow b_2 = \frac{s_{21}a_1}{1 - s_{22}\Gamma_L} \Rightarrow a_2 = \frac{s_{21}\Gamma_L a_1}{1 - s_{22}\Gamma_L}$$

$$b_1 = s_{11}a_1 + s_{12}a_2 = s_{11}a_1 + \frac{s_{12}s_{21}\Gamma_L a_1}{1 - s_{22}\Gamma_L} = \frac{(s_{11} - s_{11}s_{22}\Gamma_L + s_{12}s_{21}\Gamma_L)a_1}{1 - s_{22}\Gamma_L}$$

$$a_1 = b_s + \Gamma_s b_1 = b_s + \frac{(s_{11} - s_{11}s_{22}\Gamma_L + s_{12}s_{21}\Gamma_L)\Gamma_s a_1}{1 - s_{22}\Gamma_L}$$

$$\Rightarrow a_1 = \frac{(1 - s_{22}\Gamma_L)b_s}{1 - s_{11}\Gamma_s - s_{22}\Gamma_L + s_{11}s_{22}\Gamma_s\Gamma_L - s_{12}s_{21}\Gamma_s\Gamma_L}$$

$$= \frac{(1 - s_{22}\Gamma_L)b_s}{1 - s_{11}\Gamma_s - s_{22}\Gamma_L + s_{11}s_{22}\Gamma_s\Gamma_L - s_{12}s_{21}\Gamma_s\Gamma_L}$$

Question 4(b) continued

$$\begin{aligned}
a_1 &= \frac{(1 - s_{22}\Gamma_L)b_s}{1 - s_{11}\Gamma_S - s_{22}\Gamma_L + s_{11}s_{22}\Gamma_S\Gamma_L - s_{12}s_{21}\Gamma_S\Gamma_L} \\
b_1 &= \frac{(s_{11} - s_{11}s_{22}\Gamma_L + s_{12}s_{21}\Gamma_L)a_1}{1 - s_{22}\Gamma_L} \\
&= \frac{(s_{11} - s_{11}s_{22}\Gamma_L + s_{12}s_{21}\Gamma_L)b_s}{1 - s_{11}\Gamma_S - s_{22}\Gamma_L + s_{11}s_{22}\Gamma_S\Gamma_L - s_{12}s_{21}\Gamma_S\Gamma_L} \\
a_2 &= \frac{s_{21}\Gamma_L a_1}{1 - s_{22}\Gamma_L} = \frac{s_{21}\Gamma_L b_s}{1 - s_{11}\Gamma_S - s_{22}\Gamma_L + s_{11}s_{22}\Gamma_S\Gamma_L - s_{12}s_{21}\Gamma_S\Gamma_L} \\
b_2 &= \frac{s_{21}a_1}{1 - s_{22}\Gamma_L} = \frac{s_{21}b_s}{1 - s_{11}\Gamma_S - s_{22}\Gamma_L + s_{11}s_{22}\Gamma_S\Gamma_L - s_{12}s_{21}\Gamma_S\Gamma_L} \\
G_P &= \frac{P_{OUT}}{P_{IN}} = \frac{\frac{1}{2}|b_2|^2 - \frac{1}{2}|a_2|^2}{\frac{1}{2}|a_1|^2 - \frac{1}{2}|b_1|^2} = \frac{|b_2|^2 - |a_2|^2}{|a_1|^2 - |b_1|^2} \\
&= \frac{|s_{21}|^2 - |s_{21}\Gamma_L|^2}{|1 - s_{22}\Gamma_L|^2 - |s_{11} - s_{11}s_{22}\Gamma_L + s_{12}s_{21}\Gamma_L|^2} \\
&= \frac{|s_{21}|^2(1 - |\Gamma_L|^2)}{|1 - s_{22}\Gamma_L|^2 - |s_{11}(1 - s_{22}\Gamma_L) + s_{12}s_{21}\Gamma_L|^2} \\
&= \frac{|s_{21}|^2(1 - |\Gamma_L|^2)}{|1 - s_{22}\Gamma_L|^2 - |s_{11} - \Delta\Gamma_L|^2} \quad \text{where } \Delta = s_{11}s_{22} - s_{12}s_{21}
\end{aligned}$$

14 marks

(c) If $\Gamma_L = 0$

$$G_P = \frac{P_{OUT}}{P_{IN}} = \frac{|s_{21}|^2}{1 - |s_{11}|^2} = \frac{|3.434|^2}{1 - |0.836|^2} = 46.2$$

3 marks

Question 5

(a) Design Procedure for Low Noise Amplifier (LNA)

1. Select transistor based on s-parameters, noise figure, power level, process technology, etc
2. Check the stability – stability factor K, input/output stability circles
3. Check gain – gain circles
4. Check noise – noise circles
5. Design input and output matching networks (and DC biasing)
6. Re-iterate if necessary

5 marks

(b) Transistor with the following s-parameters at 3GHz.

$$s_{11} = 0.38 \angle -169^\circ \quad s_{12} = 0 \quad s_{21} = 1.33 \angle -39^\circ \quad s_{22} = 0.95 \angle -66^\circ$$

$$\begin{aligned} G_{TU, \max} &= \frac{1}{1 - |s_{11}|^2} |s_{21}|^2 \frac{1}{1 - |s_{22}|^2} \\ &= \frac{1}{1 - |0.38|^2} |1.33|^2 \frac{1}{1 - |0.95|^2} \\ &= 1.169 \times 1.769 \times 10.256 = 21.2 \quad \text{ratio} \\ &= 0.68 \text{ dB} + 2.48 \text{ dB} + 10.11 \text{ dB} = 13.27 \text{ dB} \end{aligned}$$

3 marks

Question 5 continued

(c) Design for source gain = 0.3dB, load gain = 4dB

Identifying the gain circle to give a source gain of 0.3dB

$$G_{S,dB} = 10 \log_{10}(G_S) \Rightarrow G_S = 10^{\frac{G_{S,dB}}{10}} = 10^{\frac{0.3}{10}} = 1.0715$$

$$\Rightarrow g_s = \frac{G_S}{G_{S,\max}} = \frac{1.0715}{1.169} = 0.92$$

$$|C_S| = \frac{g_s |s_{11}|}{1 - |s_{11}|^2 (1 - g_s)} = \frac{0.92 \times |0.38|}{1 - |0.38|^2 (1 - 0.92)} = 0.35$$

$$R_S = \frac{\sqrt{1 - g_s} (1 - |s_{11}|^2)}{1 - |s_{11}|^2 (1 - g_s)} = \frac{\sqrt{1 - 0.92} (1 - |0.38|^2)}{1 - |0.38|^2 (1 - 0.92)} = 0.25$$

The centre of the 0.3dB source gain circle is a distance 0.35 along the line joining the origin and the point s_{11}^* and its radius is 0.25

Identifying the gain circle to give a load gain of 4dB

$$G_{L,dB} = 10 \log_{10}(G_L) \Rightarrow G_L = 10^{\frac{G_{L,dB}}{10}} = 10^{\frac{4}{10}} = 2.512$$


$$\Rightarrow g_L = \frac{G_L}{G_{L,\max}} = \frac{2.512}{10.256} = 0.245$$

$$|C_L| = \frac{g_L |s_{22}|}{1 - |s_{22}|^2 (1 - g_L)} = \frac{0.245 \times |0.95|}{1 - |0.95|^2 (1 - 0.245)} = 0.73$$

$$R_L = \frac{\sqrt{1 - g_L} (1 - |s_{22}|^2)}{1 - |s_{22}|^2 (1 - g_L)} = \frac{\sqrt{1 - 0.245} (1 - |0.95|^2)}{1 - |0.95|^2 (1 - 0.245)} = 0.27$$

The centre of the 4dB load gain circle is a distance 0.73 along the line joining the origin and the point s_{22}^* and its radius is 0.27

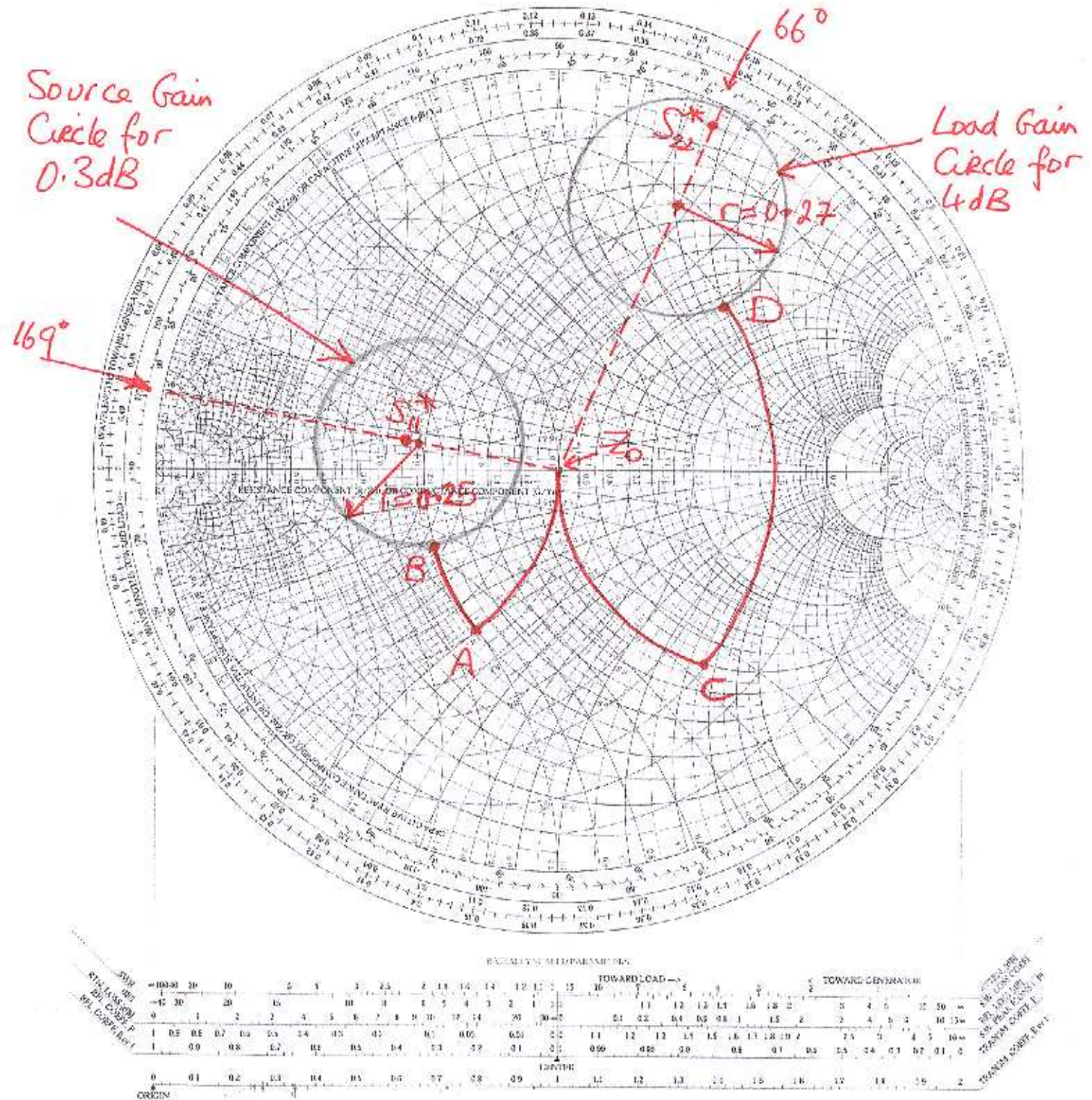NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES



EE4011 Summer 2008 Q5 (c)

Question 5(c) continued

Input Matching Element Values – need to get from origin to source gain circle

Moving from Z_0 ($\Gamma=0$) to point A:

Clockwise on conductance circle – shunt capacitor

$$\begin{array}{l} \text{susceptance at } Z_0: b = 0 \\ \text{susceptance at A: } b = 1.0 \end{array} \quad C = \frac{|\Delta b|}{2\pi f Z_0} = \frac{|1.0|}{2\pi \times 3 \times 10^9 \times 50} = 1.06 pF$$

Moving from A to B:

Clockwise on resistance circle – series inductor

$$\begin{array}{l} \text{reactance at A: } x = -0.5 \\ \text{reactance at B: } x = -0.22 \end{array} \quad L = \frac{Z_0 |\Delta x|}{2\pi f} = \frac{50 \times |0.28|}{2\pi \times 3 \times 10^9} = 0.74 nH$$

Output Matching Element Values – need to get from origin to load gain circle

Moving from Z_0 ($\Gamma=0$) to point C:

Anti-clockwise on resistance circle – series capacitor

reactance at Z_0 : $x = 0$ reactance at C: $x = -1.5$

$$C = \frac{1}{2\pi f |\Delta x| Z_0} = \frac{1}{2\pi \times 3 \times 10^9 \times |-1.5| \times 50} = 0.71 pF$$


Moving from C to D:

Anti-clockwise on conductance circle – shunt inductor

susceptance at C: $b = 0.46$


susceptance at D: $b = -0.38$

$$L = \frac{Z_0}{2\pi f |\Delta b|} = \frac{50}{2\pi \times 3 \times 10^9 \times |-0.84|} = 3.16 nH$$

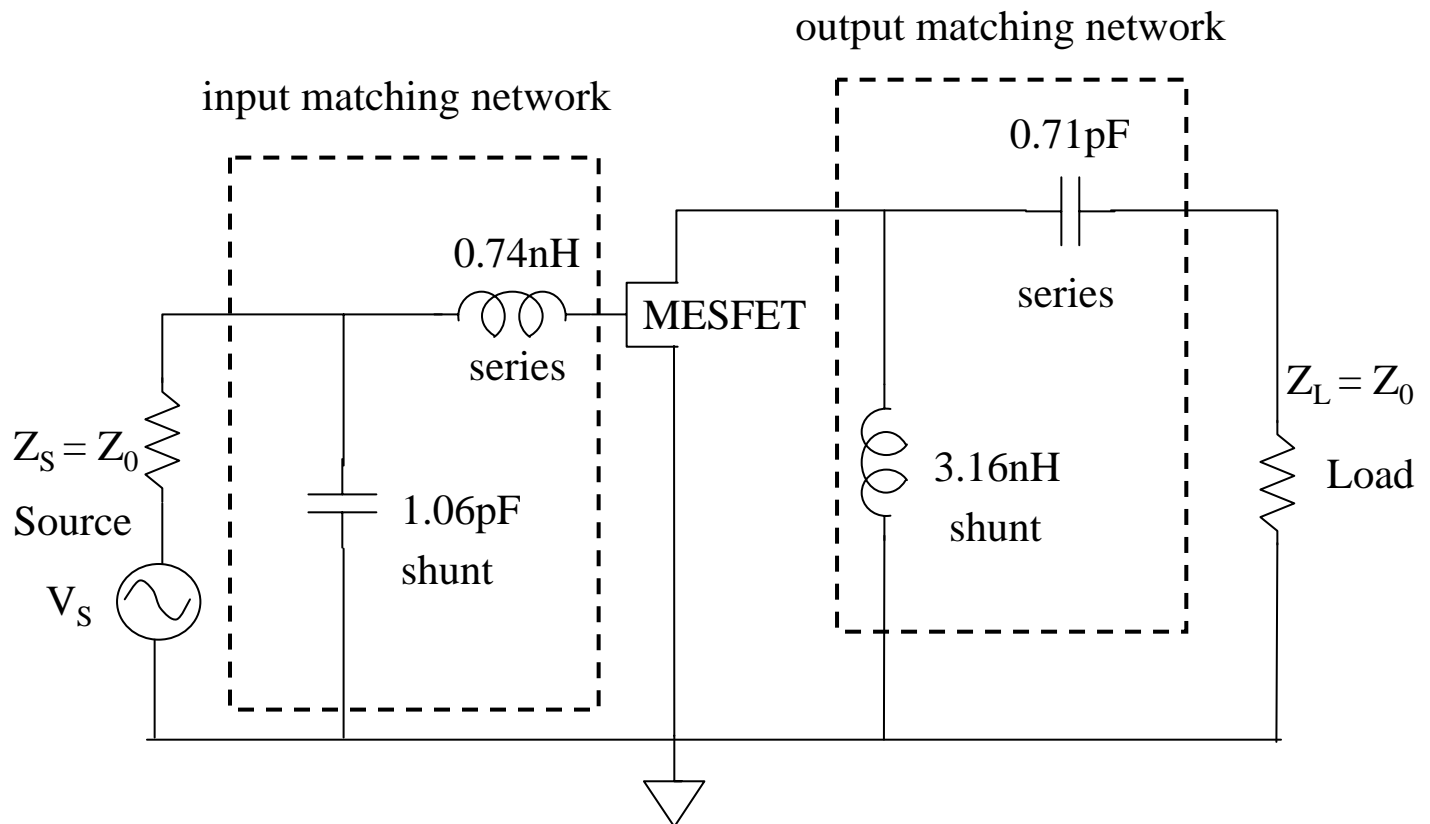

12 marks

Question 6(a) Switch-based mixer

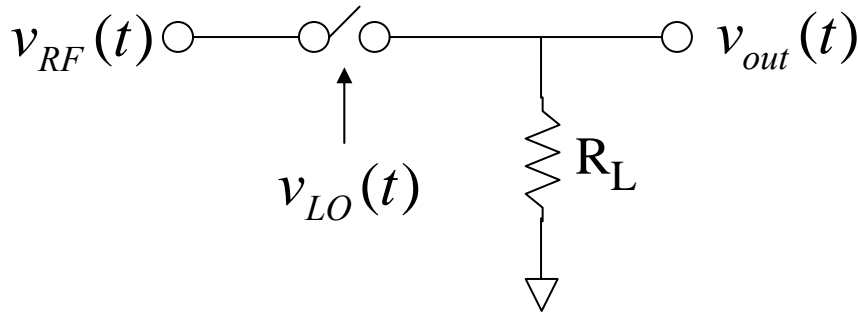

The LO signal controls the switch. For alternate half-cycles the switch is on so connecting the RF signal to the o/p or off so grounding the output. This is equivalent to multiplying the RF signal by a square wave at the LO frequency.

$$\begin{aligned}
 v_{out}(t) &= v_{RF}(t) \left[\frac{1}{2} + \frac{2}{\pi} \sin(\omega_{LO}t) + \frac{2}{3\pi} \sin(3\omega_{LO}t) + \frac{2}{5\pi} \sin(5\omega_{LO}t) + \dots \right] \\
 &= V_{RF} \cos(\omega_{RF}t) \left[\frac{1}{2} + \frac{2}{\pi} \sin(\omega_{LO}t) + \frac{2}{3\pi} \sin(3\omega_{LO}t) + \frac{2}{5\pi} \sin(5\omega_{LO}t) + \dots \right] \\
 &= \frac{1}{2} V_{RF} \cos(\omega_{RF}t) + \frac{2}{\pi} V_{RF} \cos(\omega_{RF}t) \sin(\omega_{LO}t) + \frac{2}{3\pi} V_{RF} \cos(\omega_{RF}t) \sin(3\omega_{LO}t) \\
 &\quad + \frac{2}{5\pi} V_{RF} \cos(\omega_{RF}t) \sin(5\omega_{LO}t) + \dots
 \end{aligned}$$

Using $\cos A \sin B = \frac{1}{2} (\sin(A+B) - \sin(A-B))$ gives


$$\begin{aligned}
 v_{out}(t) &= \frac{1}{2} V_{RF} \cos(\omega_{RF}t) + \frac{V_{RF}}{\pi} [\sin((\omega_{RF} + \omega_{LO})t) - \sin((\omega_{RF} - \omega_{LO})t)] \\
 &\quad + \frac{V_{RF}}{3\pi} [\sin((\omega_{RF} + 3\omega_{LO})t) - \sin((\omega_{RF} - 3\omega_{LO})t)] \\
 &\quad + \frac{V_{RF}}{5\pi} [\sin((\omega_{RF} + 5\omega_{LO})t) - \sin((\omega_{RF} - 5\omega_{LO})t)] + \dots
 \end{aligned}$$

Question 6(a) continued

The formula just derived indicates spectral components at:

$$\omega_{RF}, \omega_{RF} \pm \omega_{LO}, \omega_{RF} \pm 3\omega_{LO}, \omega_{RF} \pm 5\omega_{LO}, etc$$

Voltage conversion gain of mixer:

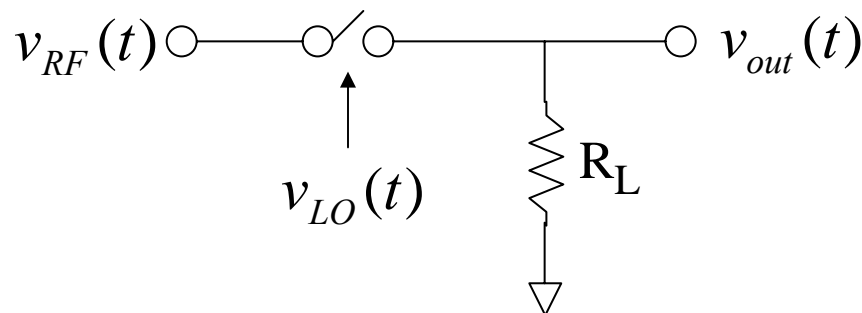

$$v_{out}(t) = \frac{1}{2} V_{RF} \cos(\omega_{RF} t) + \frac{V_{RF}}{\pi} [\sin((\omega_{RF} + \omega_{LO})t) - \sin((\omega_{RF} - \omega_{LO})t)] + \dots$$

↖ amplitude of desired IF signal


The voltage conversion gain (CG) is the ratio of the amplitudes of output IF signal and the input RF signal i.e.

$$A_{CG} = \frac{V_{IF}}{V_{RF}} = \frac{V_{RF}}{\pi} \frac{1}{V_{RF}} = \frac{1}{\pi} \quad A_{CG,dB} = 20 \log_{10} \left(\frac{1}{\pi} \right) \approx -10dB$$

10 marks

Question 6(b)

A Gilbert Cell Double Balanced Mixer

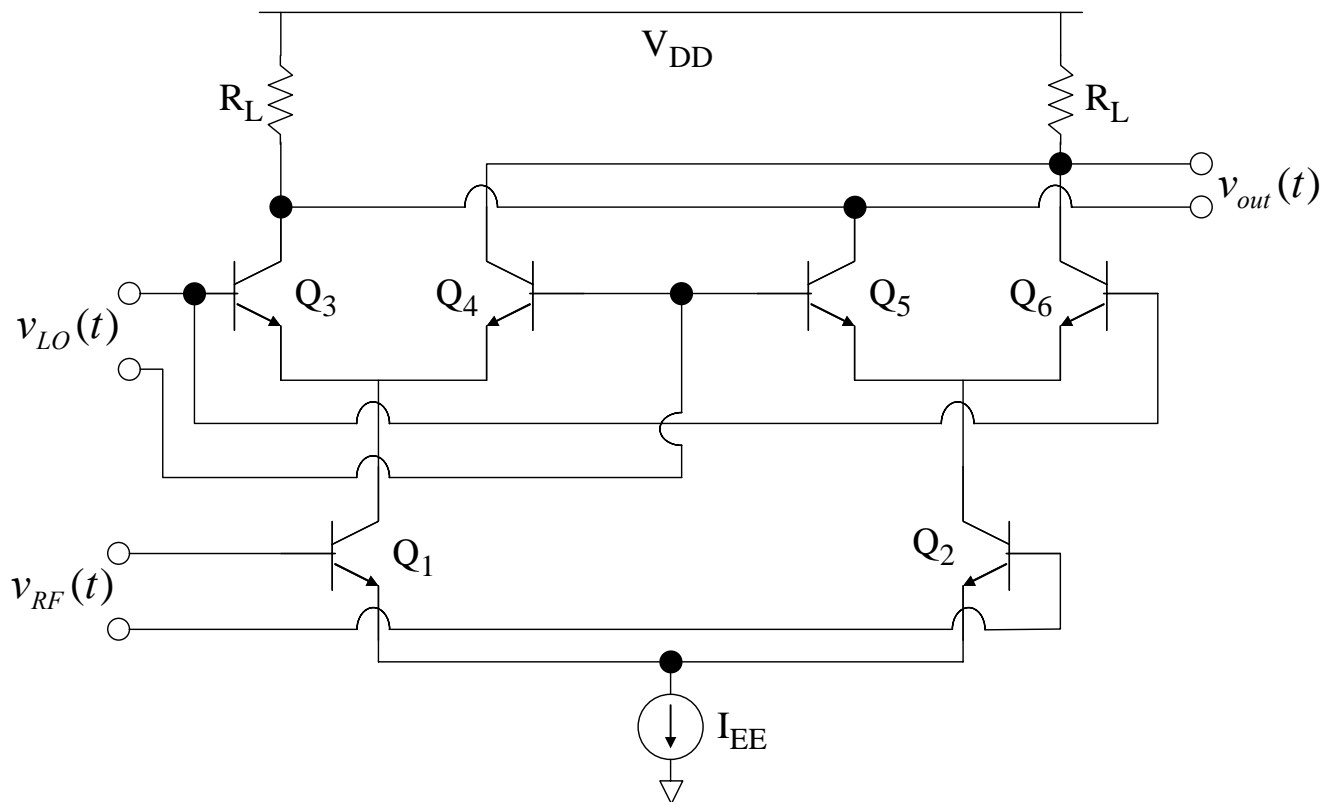

4 marks


Question 6(c) – 3 possible operating modes

- (i) If both V_{RF} and V_{LO} are low-amplitude signals, then the circuit performs as a true analogue multiplier.
- (ii) If V_{RF} is a low-amplitude signal and V_{LO} has a large amplitude, then the circuit operated as a frequency mixer.
- (iii) If both V_{RF} and V_{LO} are large-amplitude signals, then the circuit acts as a phase detector.

6 marks

Question 7

7(a) Type 1 PLL with integer feedback

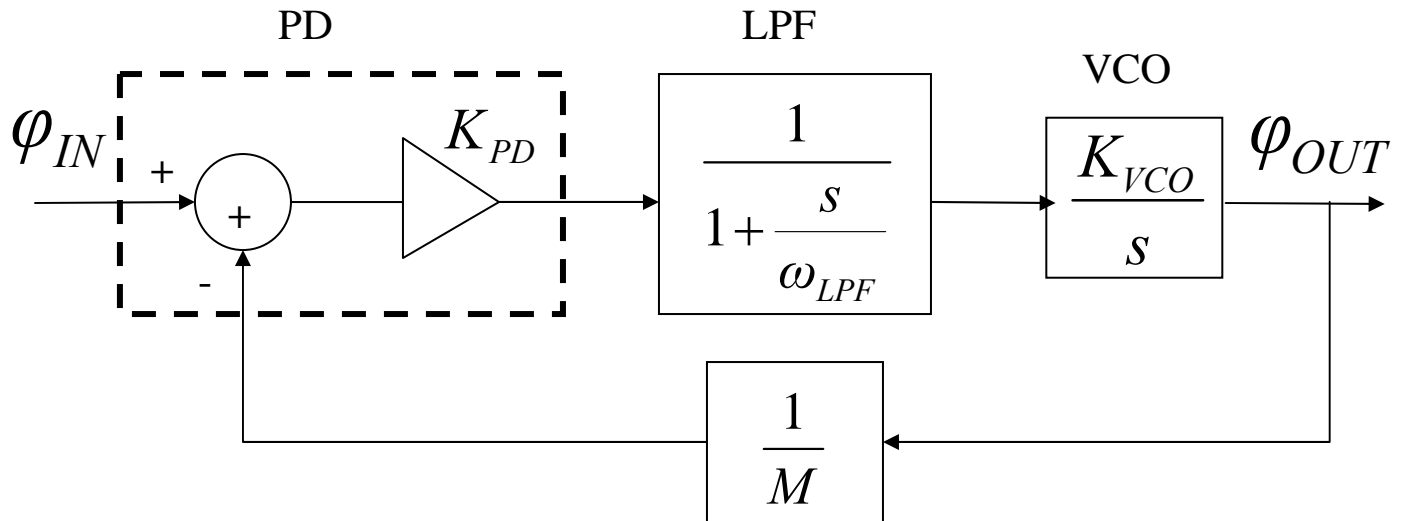

4 marks

7(b) Closed loop transfer function

$$H(s)\Big|_{OPEN} = \frac{\phi_{OUT}(s)}{\phi_{IN}(s)}\Big|_{OPEN} = K_{PD} \cdot \frac{1}{1 + \frac{s}{\omega_{LPF}}} \cdot \frac{K_{VCO}}{s} = \frac{K_{PD}K_{VCO}}{s + \frac{s^2}{\omega_{LPF}}}$$

$$\phi_{OUT}(s) = H(s) \left(\phi_{IN}(s) - \frac{\phi_{OUT}(s)}{M} \right)$$

$$\Rightarrow \phi_{OUT}(s) \left(1 + \frac{H(s)}{M} \right) = H(s) \phi_{IN}(s)$$

$$\Rightarrow \frac{\phi_{OUT}(s)}{\phi_{IN}(s)} = \frac{H(s)}{1 + \frac{H(s)}{M}} = \frac{1}{\frac{1}{H(s)} + \frac{1}{M}}$$

$$\frac{\varphi_{OUT}(s)}{\varphi_{IN}(s)} = \frac{1}{\frac{1}{H(s)} + \frac{1}{M}} = \frac{1}{s + \frac{s^2}{\omega_{LPF}} + \frac{1}{K_{PD}K_{VCO}M}}$$

$$= \frac{K_{PD}K_{VCO}}{s + \frac{s^2}{\omega_{LPF}} + \frac{K_{PD}K_{VCO}}{M}}$$

$$= \frac{K_{PD}K_{VCO}\omega_{LPF}}{s^2 + \omega_{LPF}s + \frac{K_{PD}K_{VCO}\omega_{LPF}}{M}}$$

$$\frac{K_{PD}K_{VCO}\omega_{LPF}}{s^2 + \omega_{LPF}s + \frac{K_{PD}K_{VCO}\omega_{LPF}}{M}} \equiv \frac{K_{PD}K_{VCO}\omega_{LPF}}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

$$\Rightarrow \omega_n = \sqrt{\frac{K_{PD}K_{VCO}\omega_{LPF}}{M}}$$

$$\Rightarrow 2\zeta\omega_n = \omega_{LPF} \Rightarrow \zeta = \frac{1}{2} \frac{\omega_{LPF}}{\omega_n} = \frac{1}{2} \sqrt{\frac{M\omega_{LPF}}{K_{PD}K_{VCO}}}$$

Question 7(c)

- (i) For an integer feedback the reference frequency must be equal to the desired step size i.e. 200kHz in this case

2 marks

- (ii) Range of divider values

$$M = \frac{935}{0.2} = 4675 \quad \text{to} \quad M = \frac{960}{0.2} = 4800$$

2 marks

- (iii) Cut-off frequency of LPF

A rule of thumb to ensure good stability is to set the low-pass filter cut-off frequency to 10% of the reference frequency i.e. 20kHz.

2 marks

- (iv) PLL gain constant (use average M value)

$$\zeta = \frac{1}{2} \sqrt{\frac{M\omega_{LPF}}{K_{PD}K_{VCO}}} \Rightarrow K_{PD}K_{VCO} = \frac{M\omega_{LPF}}{4\zeta^2}$$

$$K_{PD}K_{VCO} = \frac{M\omega_{LPF}}{4\zeta^2} = \frac{4737.5 \times 2\pi \times 20000}{4 \times 0.707^2} = 2.98 \times 10^8$$

2 marks